

Nuts & Volts

Exploring Electronics And Technology For The Hobbyist And Professional

February 1999 Vol. 20 No. 2

Lightning Observing

*Turn your oscilloscope into a
"Storm Scope" and detect lightning
at distances up to 100 miles!*

U.S. \$3.50 CANADA \$5.00



**BOTH SINGLE AND DUAL
DRIVE MODELS AVAILABLE.**

**MAKE CUSTOM DISKS WITH
JUST THE MUSIC YOU LIKE**

**EXTERNAL SCSI-II PORT WORKS
LIKE A STANDARD CD WRITER
FOR CREATING CUSTOM DISKS.**

**INTERNAL A/V HARD DRIVE
STORES DISK IMAGES FOR MULTIPLE
COPIES, AND CUSTOM AUDIO DISKS.**

**TOTALLY SELF CONTAINED,
NO ADDITIONAL HARDWARE
IS REQUIRED**

**ADVANCED FORMAT DETECTION
PRODUCES PERFECT DUPLICATES
ON STANDARD CD-R MEDIA.**



COPY ANY CD NOW. NO PC REQUIRED.

DUPE-IT!

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce compact discs quickly and economically. No mastering or multimedia experience is required.

Insert your original CD and press "start." The multimedia processor quickly copies any disc to the internal A/V hard drive. Insert blank CDs and make as many copies as you like. You'll produce perfect duplicates. The system is totally self contained — no additional hardware is required.

BUY DIRECT: FROM \$795! 408 330-5524

Just plug in the power cord and press "start"—it's that easy.

You can even make your own custom music CD without a PC! Insert your original CD's, select the tracks you want, and Dupe-It will copy them to the internal hard drive. Then insert a blank CD, and you'll have a custom music CD with just the songs you want.

With the included CD mastering software, Dupe-It will work over-time as your personal CD design system. Just attach a SCSI cable to your PC or Mac, and you're

ready to design and create your own original CD's. Similar systems used in duplication houses cost over \$5,000. Now you can easily copy CDs yourself for a fraction of the price.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DUPE-IT.COM

Musicians—ask about our pro-audio CD recorders. Software publishers—ask about our high-volume multi-drive duplication systems. Dupe-It is sold and intended for backup and in-house design purposes only. Copyright laws must be observed.

HSC Electronic Supply

Serving
Silicon Valley
since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer!
For thirty years we have been your source for Silicon Valley exotica!

Tiny Color CCD Camera!

- One of the world's smallest color cameras!
- Camera-on-a-board measures 1.87" x 1.3", 1" thick!
- Has glass micro-lens element, not pinhole lens
- DSP on board for auto white-balance, shutter
- Standard NTSC composite video output
- 350 lines horiz. resolution, 7 lux sensitivity
- Uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
- New in OEM pkg (no box), 90-day HSC warranty



HSC#17736 \$89.95

Drive-bay Amp & Equalizer

- Made by NEC, fits into standard 5.25" drive bay
- 5-Band equalizer has 4 channels
- 6 watts RMS/channel, 25 watts RMS total power output
- Connects to drive power connector
- No special software or drivers req'd!
- Compatible with any sound card
- NEC Speakers are 11" tall, 4.5" wide
- Speakers have 4" 40-watt woofer, 1" dome tweeter
- Includes all cables, hookup accessories
- New in plain brown box, 90-day warranty



HSC#80462 \$39.95

Workhorse Hard Drives!

- Seagate with SCSI interface full-height drives
- Good, Reliable drives for many applications
- Choose from 670 or 330 MB size
- With 90-day warranty!



HSC#17556 ST4766N \$35.00
HSC#17557 ST4385N \$29.00

Video-hacker Dream!

- Logitech Videoman Video-conference camera & interface
- These units were sold with Hewlett Packard S-700 workstations for videoconference capability
- We do not have technical data, software or manuals
- All we have is cameras with stand, and SCSI-II interface
- The camera is on a weighted stand that extends from 13" tall to over 20" tall, and has a stereo microphone
- Color camera is digital output only (not NTSC) as far as we can tell -- but who knows?
- Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic. out jack, composite video out (BNC), and the connector for the camera cable.
- Note: HP and Logitech will provide no information on these



HSC#17503 \$39.95

RAID Server Chassis

- Trimm H420 Super Server rack-mount chassis will accommodate a high-end multiprocessor system board with a PCI RAID controller.
- Slots for eight RAID drives on removable slides
- Space for two CD-ROM or tape drives
- Three hot-swappable power supplies (300W) included
- Environmental processor and LCD display
- Can accommodate Alpha or SPARC system boards
- Three 95 CFM fans and one 17 CFM blower
- Measures 17.75" high, 19" wide, 17" deep
- New in box, with rack slides, 90-day warranty



HSC#80463 \$395.00

Fujitsu 1 GB Drives

- Model #s M1606S, M2694E \$ M2932SA
- SCSI Interface - 3.5" size, includes 5.25" brackets
- Tested good and DOS formatted
- Used - w/90-day warranty!



HSC#17555 New Price!! \$69.00

External SCSI Drive Cases

- Bargain case for 5.25" drives, brand new!
- 7" x 4.5" x 10.5" overall size
- 50-pin SCSI connectors
- SCSI ID switch
- 65W Power supply (lots of power for hard drives, etc.)
- Fan-cooled, uses standard IEC Power cord (not included)



HSC# 17130 \$39.95

- High quality low profile case for 5.25" drives, brand new!
- 7" x 2.25" x 11" overall size
- 50-pin SCSI connectors, RCA Audio connectors
- SCSI ID switch, termination switch
- Tiny 12W Power Supply (5VDC @ 1.4A, 12VDC @ .4A, probably only good for CD-ROM's)
- Fan-cooled, uses standard IEC Power cord (not included)



HSC# 17357 \$29.95

Corel Office Professional 7

- Great Software Bundle -- Amazing Value!
- Includes Corel Wordperfect 7, Corel Quattro Pro 7, Paradox 7, Corel Presentations 7, CorelDRAW 6, CorelFLOW 3, Sidekick 95, Netscape Navigator, Dash board 95, 1000 fonts, 10000 clip-art images, more!
- For Windows 95, Windows NT 3.51 and Windows NT 4.0
- Distributed on CD-ROMs, with hefty manual pack
- New, shrink-wrapped in box, 90-day warranty

HSC#80436 \$47.50

ATX Pentium Motherboard

- Support for Intel Pentium 90-200, 166-200 MMX CPU's
- Also supports Cyrix/IBM 6x86 P, PR 150 & 166 CPU's
- Also supports AMD K5, and, with special VRM, K6 CPU's
- 4 PCI slots, 4 ISA slots (one shared), 16-bit stereo sound
- 4 DIMM RAM sockets, parity or non-parity, ECC, EDO, FP
- On-board 2 x IDE, 2 x 16550 Serial ports, 1 parallel port
- New, 90-day warranty (CPU not included)

HSC# 80437 New Price! \$39.95

Compaq Docking Bay

- Compaq docking "Smartstation" for laptop computer (we don't know which!)
- Has two internal ISA slots
- SCSI port, network ports, serial, parallel, video, keyboard & mouse ports on back.
- Used, 90-day warranty



HSC#17713 \$39.00

PCI-Bus 56K Modem!

- Genica PCI-Bus 56K Modem at unheard-of price!
- Data, FAX, voice, full V.90 compatibility
- Voice from handset
- Windows 95/98 or NT only (Not Win 3.1 compatible)
- Uses latest Lucent chipset, comes with Lucent drivers
- New retail box, with Trio application software on CD
- 90-Day Warranty



HSC#17532 \$39.95

Laptop Carrying Cases

- Two sizes, 12" x 9.5" x 1.5" and 12.5" x 10" x 2" inside dim.
- Both have velcro-sealed outer pouch, padded shoulder strap with heavy-duty swivel hooks, zipper closure.
- Handsome black vinyl "leather-grain" exterior
- Cushiony plush interior protects your laptop's case

HSC#17662 Large size case \$22.50
HSC#17663 Small size case \$17.50

Off-Brand Alarm Stuff!

These items are dealer-returned inventory (shelf worn packaging but unused) of home security components that were made by Telco Inc. Mix and match to create your own bargain security system! All items have mounting screws or adhesive pads, instructions, and alarm units have window warning stickers. All parts have 30-day warranty.

- ST911 Automatic Phone dialer has screw terminals for sensor input, power adapter, and very long phone cord.
- Instantly contacts up to four pre-selected phone numbers with your own digitally recorded 16 second message.

HSC#17718 Phone Message Dialer \$27.50

- S100M Magnetic entry sensors (mag-switch) have a reed-switch and magnet pair for door or window mounting, and approx. 50 feet of white hook-up wire.
- Use with PIR units or Entry Guard below for additional protection. Switches may be used in series for multiple door/window protection.

HSC#17723 Magnetic Entry Sensor \$1.95

- S002M Digital Control Motion Alarm has wall-mount keypad, PIR infrared motion detector with 110° coverage to 60 feet, programmable security code, 10 - 15 second entry delay, extremely loud alarm.
- Uses 9V battery or AC Adapter (neither included)

HSC#17720 Digital Control Motion Alarm \$15.00

- S008B Digital Control Motion Alarm with Safety Chime has wall-mount keypad, PIR infrared motion detector (same as S002M above) with very loud alarm OR safety chime alert.
- Uses 9V battery or AC Adapter (neither included)

HSC#17721 Digital Motion Alarm/Chime \$17.50

- S082X Entry Guard Alarm has wall-mount keypad, mag-switch activation (one switch included), programmable security code, 10 - 15 second entry delay, extremely loud alarm or pleasant door chime.
- Uses 3 AAA batteries (not included)

HSC#17722 Digital Entry Guard Alarm \$12.50

Lead-Acid Rechargeables!

These are all new batteries by Tempest with tab terminals. Perfect for hobbies, security systems, battery back-up, etc.

- TR1.2-6, 6VDC at 1.2 AH, measures 3.75 x 1 x 2" HSC#17589 \$3.95
- TR1.2-12, 12VDC at 1.2 AH, measures 3.75 x 1.875 x 2" HSC#17197 \$4.95
- TR4-6, 6VDC at 4 AH, measures 2.75 x 1.75 x 4" HSC#17588 \$4.95

Take Your Pick of Floppies!

- Teac 1.44MB 3.5" Floppy Drive
- Industry standard floppy drive, beige face plate
- New OEM Pack, 90-day warranty



HSC#17654 \$19.95

- Citizen W1D 1.44 MB floppy measures only .43" thick!
- Interface is 26 conductor 1mm pitch printed ribbon cable
- Short (1.25") ribbon cable included
- Black bezel -- New OEM Pack, 90-day warranty
- Sorry, we do not know which laptops will accept this drive!



HSC#17587 \$25.00

- Teac FD-05 HF 230-U 1.44 MB Laptop floppy - same specs as Citizen



HSC#17694 \$29.00

CD-ROM Writer/Readers!

- Ricoh RS-10600 CD Recorder/Player System
- SCSI Interface, 2x4 (2-speed write, 4-speed read)
- External type, case is 9.75" x 2" x 11" deep
- Caddy type, includes caddy, power cord, driver disk
- New in OEM box with manual, 90-day warranty

HSC#17567 New Price! \$159.00
Also available (only a few!) internal IDE type 2 x 6 speed
Sony CDU298E (factory refurb), caddy type, \$139.00

Used Mac Keyboards

- Two styles available, for Macintosh II and Performa
- Both are used, with 30-day warranty
- Replacement keyboards are hard to find!



HSC#17394 Mac II keyboard \$24.95
HSC#17386 Performa keyboard \$32.50

Briefcase of Goodies!



- These handsome hardshell cases were used to carry a laptop-computer estimating system (laptop not included)
- They were used with a Compaq LTE laptop, and provided a SCSI port for a CD-ROM drive with battery back-up
- Large Nicad pack has 10 Sanyo Cadnica cells.
- Built-in 19VDC power supply for battery charging
- Tiny piggy-back PC board seems to be a SCSI interface
- Case measures 18" x 14" x 7", with several compartments
- SCSI II to CEN50 SCSI cable, many great parts inside!
- Buy either the whole assembly, or just the parts you want!
- Not guaranteed to function with laptops -- for parts only!

HSC#17180 Complete Laptop Case \$29.95
HSC#17182 Empty Hardshell Case \$15.00
HSC#17181 Nicad Pack, 12.5VDC, 5AH \$17.50
HSC#17179 SCSI II Cable, 1 ft. long \$12.50

HALTED
specialties co.

HSC

Electronic
Supply

Toll Free (Orders Only) 1-800-4 HALTED
Internet World Wide Web:
3500 Ryder St., Santa Clara, CA 95051
4837 Amber Ln., Sacramento, CA 95841
5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)
http://www.halted.com
(408) 732-1573
(916) 338-2545
(707) 585-7344

FAX your orders to:
(408) 732-6428



Visit HSC's Website!


- Pay us a virtual visit on the World Wide Web!
- Simply point your browser to <http://www.halted.com>
- Site is constantly being revised, please visit often!
- Check out the amazing "Gizmo of the Week" feature!

HSC Catalog online!

- That's right, get HSC's catalog on the World-Wide Web!
- Simply go to www.halted.com and follow the big red link.
- Adobe .PDF files are available for download and viewing.
- Or drop on by and pick one up...we'd love to see you!

Terms: Some quantities limited, all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight!) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.

More than just a magazine ...

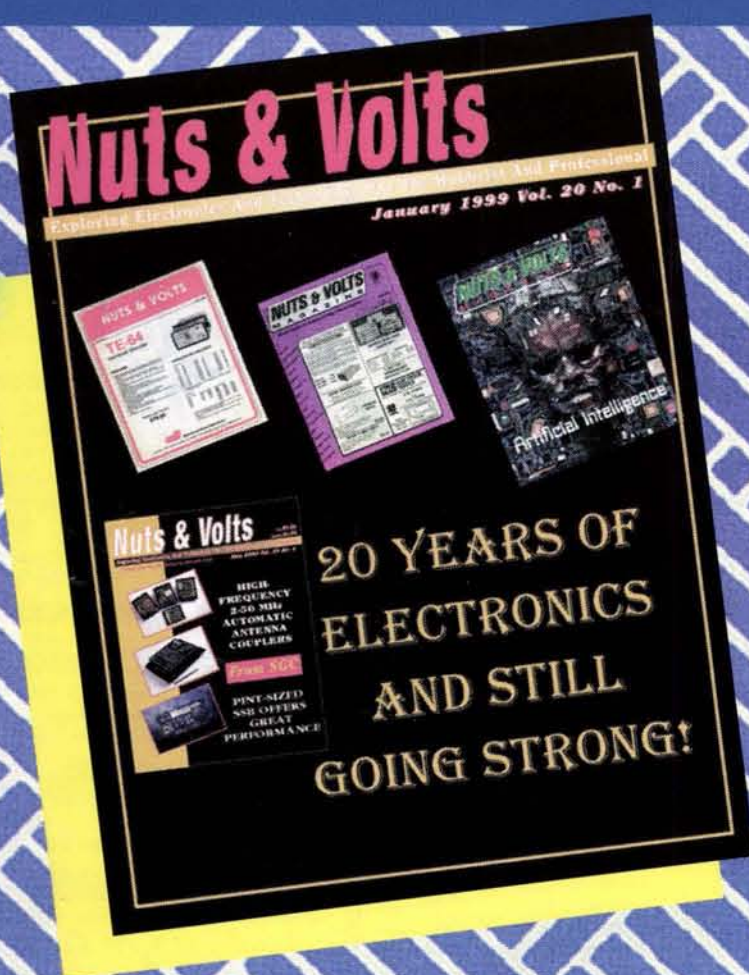

We want to be the place you go to for *all* your electronic needs!!!

Stay tuned ... we've got lots of exciting things planned for 1999!

New additions to our website, our monthly prize drawing, new features in the magazine, writing opportunities, special "giveaways" with your paid subscriptions, plus more!

Check us out on the web!
<http://www.nutsvolts.com>



You Win with Nuts & Volts

February Drawing hosted by
RESOURCES UNLIMITED (see page 14)

**A SUPER UNDERWATER "LIPSTICK" CAMERA
with INTEGRAL INFRARED ILLUMINATOR
valued at over \$200.00!!**

Our growing list of contributors includes ...

Parallax (back cover)
Corporate Systems Center (pages 2, 95)
HSC (page 3)
Timeline, Inc. (page 47)
Alltronics (page 23)
Electro Mavin (page 8)
All Electronics (page 60)
Roger's Systems Specialist (page 73)
Electronic Goldmine (page 49)
MCM Electronics (page 9)

OUR DECEMBER WINNER:

LARRY GUNSEOR
of New Glarus, WI

As a special bonus,
NETCOM (page 85)
will be furnishing
goodies monthly,
including the IC
MASTER and more!

**Subscribe today and be
automatically entered in our *new*
MONTHLY PRIZE DRAWING!!!**

As a current, paid subscriber, you
will be automatically entered each
month in our drawing.

To Subscribe — Just fill in and mail
the enclosed subscription card or
call our toll free order line at
(800) 783-4624 with a Visa or
MasterCard.

If you do not wish to order a subscription, but
would like to be entered in our drawing, simply
send or E-Mail your name, address, and
telephone number, to NUTS & VOLTS,
430 Princeland Court, Corona, CA 91719,
drawing@nutsvolts.com. *No phone entries
accepted.* All orders/entries must be received
by the last day of the month to be included in
that particular month's drawing.

Nuts & Volts

Expecting Electronics And Hardware For The Hobbyist And Professional
February 1999 Vol. 20 No. 2

Lightning Observing

Turn your oscilloscope into a "Storm Scope" and detect lightning at distances up to 100 miles!



**In this
issue ...**

Published Monthly By
T & L Publications, Inc.
430 Princeland Court
Corona, CA 91719
(909) 371-8497
FAX (909) 371-3052

E-Mail
editor@nutsvolts.com
URL
http://www.nutsvolts.com

Subscription
Order ONLY Line
1-800-783-4624

PUBLISHER
Jack Lemieux N6ZTD
EDITOR
Larry Lemieux KD6UWV
MANAGING EDITOR
Robin Lemieux KD6UWS
ON-THE-ROAD EXHIBIT
COORDINATOR
Audrey Lemieux N6VXW

SUBSCRIPTIONS
Abby Madain

CLASSIFIED ADS
Natalie Sigafus

Copyright 1999
by T & L Publications, Inc.
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, CA 91719.

Nuts & Volts Magazine is published monthly for \$19.00 per year by T&L Publications, Inc., 430 Princeland Court, Corona, CA. POSTMASTER: Send address changes to Nuts & Volts Magazine, 430 Princeland Court, Corona, CA 91719.

BOATERS AND ROVERS UPSET WITH HF SSB PHONE SERVICE SHUTDOWN

February 28th is the final day that AT&T will handle telephone calls over high-frequency single sideband. But there will still be ways to communicate effectively ...

Gordon West ... Page 6

LOOKING INSIDE A POWER SPLITTER

Ever wonder what's inside a TV power splitter? Read on ...

Gerald Roylance ... Page 10

AUTOMOTIVE NAVIGATION: WHERE IT'S AT AND WHERE IT'S GOING

This article explains the inner workings of automotive navigation systems.

Jeff Stefan ... Page 19

BUILD AN INEXPENSIVE WHOLE-HOUSE TEMPERATURE/HUMIDITY MONITORING SYSTEM — PART 1

With the THX10 remote monitoring system described in this article, you will be able to transmit data from up to eight monitoring stations on your house's power line, and receive the information on your PC, without any calibration or wiring between rooms.

Mike Keryan ... Page 33

MAGNIFIERS 1X TO 1000X

Magnifiers come in many sizes, shapes, and prices. Find out which one is the best for your applications.

John C. Little ... Page 76

DOING ELECTRONIC CALCULATIONS WITH ELCAD

Learn to use this simple software program that allows you to do some fairly complex electronic calculations quickly, and print out the results.

Fred Blechman ... Page 89

Columns ...

AMATEUR ROBOTICS NOTEBOOK

Even though you will be starting with a very simple hardware/software combination, this month's project will put your skills to the test.

Robert Nansel ... Page 82

ELECTRONICS Q & A

TJ Byers ... Page 66

OPEN CHANNEL

Lightning observing: some lightning detection history, types of lightning, and constructing a storm scope.

Cover Story

Joe Carr ... Page 15

RESOURCE BIN

Another look at some favorite websites.

Don Lancaster ... Page 79

STAMP APPLICATIONS

If you ever wanted to store a text file and parse the data out to some serial device, or have a string of serial data stored automatically, then the RAMPack B may be just what you're looking for.

Lon Glazner ... Page 62

THE COMPUTER-CONTROLLED WORLD

Will return next month ...

DEPARTMENTS

Advertiser's Index ... 74
Classified Ad Info ... 74
Dealer Directory ... 88
Events Calendar ... 41
New Product News ... 93
News Bytes ... 32
NV AdMart ... 86-87
Reader Feedback ... 13
Tech Forum ... 69

CLASSIFIED AD INDEX

10. Ham Gear for Sale	44	90. Satellite Equipment	50	145. Robotics	54
20. Ham Gear Wanted	0	95. Military Surplus Electronics	50	150. Plans/Kits/Schematics	54
30. CB/Scanners	44	100. Audio/Video/Laser	50	155. Manuals/Schematics	
40. Music & Accessories	0	110. Cable TV	51	Wanted	55
50. Computer Hardware	45	115. Telephone/Fax	52	160. Misc. Electronics For Sale	55
60. Computer Software	46	120. Components	52	170. Misc. Electronics Wanted	56
70. Computer Equip. Wanted	46	125. Microcontrollers	53	175. BBS & Online Services	57
80. Test Equipment	46	130. Antique Electronics	53	180. Education	57
85. Security	48	135. Aviation Electronics	54	190. Business Opportunities	57
		140. Publications	54	200. Repairs/Services	58

BOATERS AND ROVERS UPSET WITH HF SSB PHONE SERVICE SHUTDOWN


by Gordon West

Sometime in the late afternoon on February 28th, AT&T station KMI in San Francisco, AT&T station WOO in New Jersey, and AT&T station WOM in Miami go off the air. Thousands of boaters, missionary stations, RVers, backpackers, and isolated stations depending on them for powerful high-frequency telephone coverage won't even get a friendly operator to tell them there is no more service. All they will hear on the 50 channels on high frequency between 2 MHz to 26 MHz is white noise.

For decades, the AT&T high seas radiotelephone service has provided powerful global high-frequency connections to the AT&T land-line system in the United States. Their three stations each ran thousands of watts of power into phased-array towers, giving mariners out on the high seas almost global coverage to their stations manned by helpful technical and telephone operators. Ship station equipment could be a simple 10-watt marine single sideband, or an elaborate full-duplex commercial kilowatt origi-

is sometimes a problem. For satellite calls to the geostationary relay space stations, the delay is due to the 22,500-mile radio path. On local digital cellular networks, the delay is the analog-to-digital-to-analog conversion. The delay will sometimes cause an echo, but will usually make a fast-paced conversation almost impossible when both parties are trying to speak at the same time.

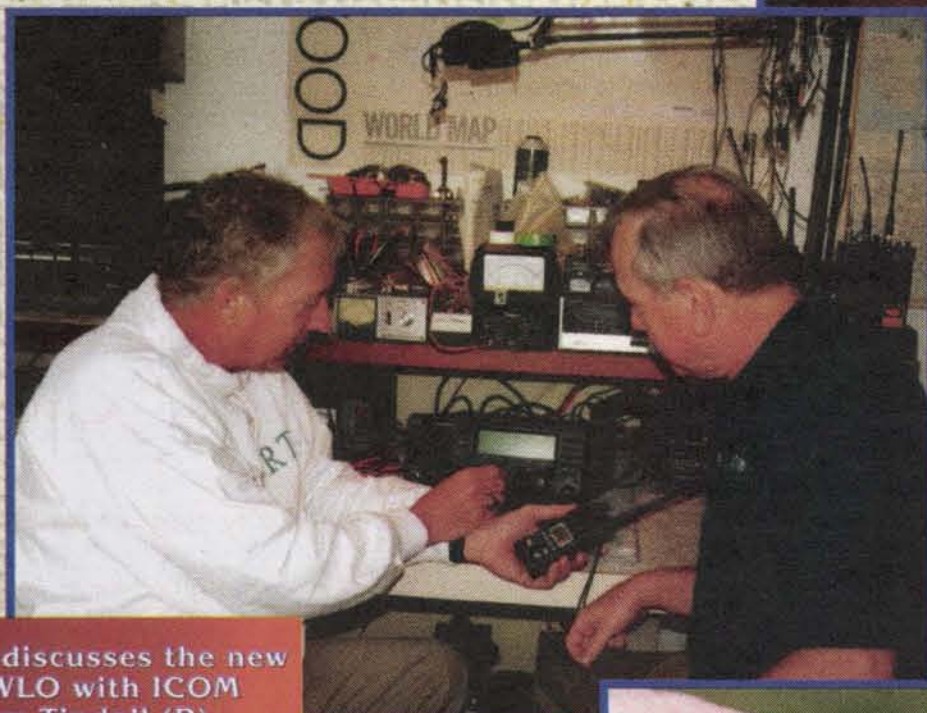But on marine single sideband over high frequency, there was no delay — and this made HF




Gordon West (L) discusses the new channels for WLO with ICOM America's Jim Tindall (R).

nally found aboard cruise ships. The AT&T channels were duplex, so bigger equipment could allow full duplex — talk and listen — so either party could interrupt each other during the phone call.

Full duplex on marine single sideband high frequencies is actually more desirable for a phone call than the new satellite systems. The satellite systems, including new digital cellular systems, have a delay in a full-duplex conversation, so interrupting a fast-paced phone call

February 28, 1999, is the final day that AT&T will handle telephone calls over high-frequency single sideband.

phone calls from a relatively simple piece of high-frequency equipment a great way to go. Prices were also cheap through the AT&T high seas service, who charged no monthly fee to be registered, and the only time you paid \$5.00 a minute was when you were actually speaking with a party you were calling or the party that had called you in the remote area. You would not be charged for a busy number, nor would you be charged for radio checks, calls to the Coast Guard, or calls to the operator just to double-check for messages holding.

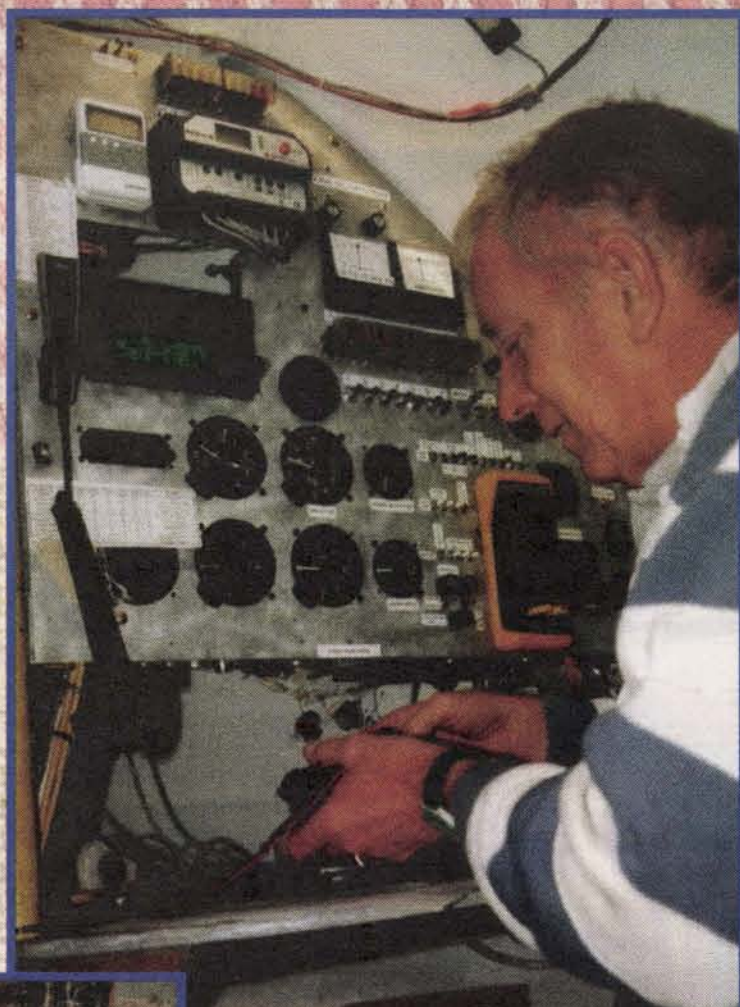

Electronic techs will have good business programming old SSB with new WLO channels.

"AT&T's high seas radiotelephone service has played an integral role in the development of maritime communications. However significant the accomplishment, time and technology have steadily advanced commercial mobile satellite communications. So much, in fact, that demand from seafarers for more sophisticated and cost-effective methods of communications has outpaced the needs for terrestrial radio services. As a result, AT&T will close its three radio coast stations as of February 28, 1999," comments Vince Zuza, Mobile Satellite Service Manager of AT&T.

This SGC direct entry SSB will easily tune in the new telephone channels.



Not only will boaters be off the air with single sideband phone calls to AT&T, but also the thousands of users who use the AT&T station to their SSB equipment SOMEWHERE out there in radio land. Although the high seas ser-



Kenwood marine and ham SSB will tune all the new WLO telephone channels.

vice is specifically for boats, there are thousands of users who may be sailing in jungles, mountain peaks, remote deserts, remote campsites in Alaska, remote valleys in Canada, remote villages in Mexico, and just about anywhere else that is not presently served by cellular telephone service. The AT&T operators were only concerned about your signal strength, not the fact that you were necessarily beside the ocean, on the ocean, or under the ocean. As long as you appeared as a registered ship station, that was fine with them.

"To help insure that customers migrate to substitute services in a smooth manner, we are introducing an INMARSAT satellite service for

AT&T radiotelephone customers with a special rate of \$2.50 per minute," comments Zuza. He is expecting that mariners will chuck their SSB equipment overboard and buy a "discount priced" \$5,000.00 INMARSAT marine mini-M terminal through Mackay Communications. I see no mention about the steep monthly service fees for INMARSAT, so for the mariner that doesn't make many phone calls, this might NOT be a viable way to go.

Does this shutdown of AT&T high-frequency service mean the demise of high-frequency single sideband? Absolutely not! Ham operators can run phone calls, called phone patch, through state-side ham stations. And the ham license for General class worldwide operation will be easier than ever to obtain next

fall when the code requirements drop from 13 wpm to 5 wpm. The only thing that ham radio cannot do is handle business traffic.

SSB equipment can also contact "private coast stations" that may offer phone patch capabilities to their member stations. There is a fine line here before that private coast station becomes a public coast station, so we'll have to wait and see what happens.

There is also single sideband E-Mail. E-Mail could be run on ham frequencies if the operator was a ham, and may also be run on public coast E-Mail stations if out on the water or roaming in a water region. There is also Sail Mail where a single sideband set can work through private coast stations to access E-Mail services on line. It takes an additional radio

modem to go along with the SSB, plus the computer, but nonetheless, E-Mail over high frequency is another good way to get the very last drop of signal out of your SSB radio investment. (Next month, high-frequency SSB E-Mail will be explained.)

GOOD NEWS FROM STATION WLO

AT&T is not the only FCC-licensed, public coast, single sideband radiotelephone station. Down in Mobile, AL, a company called Mobile Marine Radio offers 24-hour-a-day voice single sideband radiotelephone service, and they have a powerful antenna system that can reach out up to 10,000 miles away. They have been licensed to operate on specific ITU channels between 2 MHz to 25 MHz, and this allows 15 channels of half-duplex or full-duplex SSB communications to registered stations anywhere in the world. You could even register a dingy, using temporary FCC call signs made up of the dingy bow state registration number and the letter "K" preceding the two-letter, four-number combination.

The call sign of the high seas radio service is WLO — Whiskey, Lima, Oscar — and their signals come in loud and clear on the following frequencies:

ITU Channel	Receive Frequency	Transmit Frequency
2XX	2672 KHz	2430 KHz
405	4369 KHz	4077 KHz
414	4396 KHz	4104 KHz
419	4411 KHz	4119 KHz
607	6519 KHz	6218 KHz
824	8788 KHz	8264 KHz
829	8803 KHz	8279 KHz

Davileyn
CORP.

13406 Saticoy Street
North Hollywood, CA 91605
800-235-6222
818-787-3334 • F-818-787-4732
HTTP://WWW.Davileyn.com/Electronics
CALL FOR FREE CATALOG



THE BEST PRICE EVER
ON THIS INDUSTRY FAVORITE
\$1.095 + SHIPPING

HP 8640B SIGNAL GENERATOR OPT 003



CONDITION CODE "A"

Frequency: 500KHz to 512MHz. Indicates to 1024MHz. Requires external frequency doubler for 1024MHz (supplied with unit). Readout can be used as a frequency counter. Accuracy: 6.5 digits expandable to X10 and X100. Output: -145dBm to +19dBm (0.5 to 512MHz). Modulation: AM, FM, pulse, 400 and 1KHz, 1mV to 1V internal. Has input and output of modulation sources. PRICE: \$1,095

EXCEPTIONAL
CONDITION

LIMITED SUPPLY
DUE TO OVER-
WHELMING
DEMAND

- HP 200CD Oscillator\$95
- HP 312B Selective Voltmeter ..\$695
- HP 331 Distortion Analyzer ...\$249
- HP 400E Voltmeter\$325
- HP 412A Voltmeter\$95
- HP 415E Voltmeter\$125
- HP 3435A Multimeter\$295
- HP 8160A Generator\$2,800
- Krohn-Hite Model 4300A Oscillator\$395
- PRD Type 2020 Vector Voltmeter w/sampling heads\$250
- Syston Donner Spectrum Analyzer Consists of tuning unit Model 809-1, display unit Model 712-1\$1,995
- Watkins Johnson WJ-8628-4 Receiver\$8,500



AN/URM-120 50 OHM THRU-LINE RF WATTMETER

Frequency range: 2MHz to 1000MHz. Power range: 10 watts to 1000 watts. USWR: 1.08 to 1. Uses three plug-in coupler elements (included). CU-753 2 to 30MHz 50 to 100 watts CU-754 25 to 250MHz 10 to 500 watts CU-755 200 to 1000MHz 10 to 500 watts. Connector: Type N. Case included. Size: 7"Wx6-5/8"Hx7-1/5"D. Weight: 6.5 lbs. Price: \$395


TEKTRONIX 2336YA DUAL TRACE 100MHz PORTABLE OSCILLOSCOPE



Vertical: DC to 100MHz band with 5 mV per div. to 5V per div. maximum sensitivity of 2mV/div. Horizontal: Time Base A: 0.05 uS/div. 0.5 sec/div. X10 to 5 ns/div. Time Base B: 0.05 uS/div. to 50 mS/div. X10 to 5 ns/div. Has digital readout of delta time, delayed sweep, and XY input div.

Price: \$795

LAMBDA LK344A-FM POWER SUPPLY

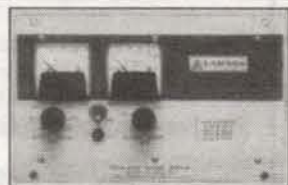

Front panel voltage and current meters. Con-vection-cooled, no blower. Voltage adjustable from 0 to 60 VDC at a maximum current of 4A. Regulation 0.015% or 1mV. Line or load. Series/parallel operation. Remotely programmable by voltage or resistance. Less than 500uV RMS ripple. Constant current/constant current. NEW Price: \$395

HP 180A SCOPE (MIL SPEC AN/USM-281A)



Includes vertical plug-in 1801A (PL1186), horizontal plug-in 1821A (PL1187). Tested. Manual Reproduction: 15

GREAT PRICE

\$195

TELEGRAPH KEYS

Unique item for military collectors. J37 telegraph key, new in original government package. \$49.95



JONES MODEL 1600-1 TACHOMETER

Instrument tachometer centrifugal mechanical tach measures RPM scale 0-500 RPM, coupling shaft 1/8" accessories, various size rubber tipped drive couplings, case new. Also Jones Model 1600-7 RPM scale 0-11,000 RPM w/accessories new. \$35/ea. or 2 for \$50

STACO TYPE 3PN1020

50/60 cycle, input 240 volts, output 0-240/280 volts, 3.5 amp. \$145 NEW



SINGER CSM-1 COMMUNICATIONS SERVICE MONITOR



RF signal source: 0 to 600MHz in 100MHz steps plus 100Hz vernier. RF output: 110 to 0 dBm, built-in oscilloscope monitor. Inputs: RF, detected, vertical, horizontal, AM/FM. Outputs: audio, tone, RF. Functions: generate 2mV to 2mV. AGC: manual or auto. \$395



CT SYSTEMS 3000B SERVICE MONITOR

\$2,500

MORGAN DATA SYSTEMS MODEL 8609



Constant voltage or current power supply voltage range: 0 to 50 volts. Current range: 0 to 1.5A. Readout: 3 digit with 0.1 volt and 1mA current resolution. Regulation: linear; input voltage: 115V/220V. Adjustments: voltage and current has remote control adjustment capability. NEW. Price: \$95

POWERSTAT TYPE 216CU

50/60 cycle, single phase, output voltage 0-280 3.5 amp

\$85 NEW



EXTENSION CORD ROYAL ELECTRIC

15 ft. long (5 yards), general purpose 16-3-SJT, 13A/125V, 0-7215, UL approved. PRICE: \$3.95 NEW

NICKEL CADMIUM BATTERY



G.E. Catalog No. 42B004KA01. Nominal volts 12 rated capacity 4.0Ah, wt. 5 lbs. NEW \$55



RT-202 RECTIFIER TRANSFORMER MFG. STANCOR Primaries 117 volts, 50/60Hz solder lug termination, secondary multiple voltages and currents. Spec sheet available.

\$15

830	8806 KHz	8282 KHz
836	8713 KHz	8113 KHz
1212	13110 KHz	12263 KHz
1225	13149 KHz	12302 KHz
1226	13152 KHz	12305 KHz
1607	17260 KHz	16378 KHz
1641	17362 KHz	16480 KHz
1647	17380 KHz	16498 KHz
2237	22804 KHz	22108 KHz

Both transmit and receive are all operated upper sideband. Equipment as small as the portable SGC-2020 at 20 watts output is capable of reaching this station thousands of miles away. Just be sure to give your receive and transmit frequencies correctly — the received frequency is always higher in kilohertz than the transmit frequency.

If you plan to use their radiotelephone service for both sending phone calls, as well as receiving them from shore, you need to register ahead of time. While you could do it on the radio, it's best NOT to give out a credit card number on transmit. Even though other stations may be listening duplex, you don't want a shortwave listener tuning into the transmit side of your duplex conversation and grabbing your credit card number.

Rates are similar to what AT&T had before they signed off — \$4.99 a minute anywhere in the USA with no land line charges. Three-minute minimum. If you can get through on 2 and 4 MHz frequencies, you can save money and make phone calls for \$2.99 a minute without land line charges. Pay a buck more and you can place phone calls through WLO to anywhere in the world, and they again pick up the land line charges.

The ICOM SSB (below VHF) will dial in all new telephone channels from ITD memory.


Here's how to register:

TELEPHONE: 334-666-5110
FAX: 334-666-8339
E-MAIL: wloemail@aol.com
(-@- in place of ASCII "atsign")
E-MAIL DIRECT: rene@shipcom.com

"Oh yeah, you can hear our signal just about anywhere in the world," comments K.C. Robinson, the lead radio technician at WLO, holding ham call sign KQ4ZL. "We are loud, and we have a very low-noise floor to sniff out weak signals coming in, too," adds Robinson.

"And we are looking for customers," comments Rene Stiegler of WLO. "We are capable of handling the registration of those mariners who may be leaving any other turned-off service," adds Stiegler.

But we will miss the friendly sounds of the AT&T high seas operators. These men and women were there to handle Mayday emergency calls, rescue calls to the Coast Guard Rescue Coordination Center, and just radio checks and "I'm lonely, anyone there?" calls in the middle of the night. We are disappointed that these operators won't be heard on the airwaves anymore — they have done a fabulous job over the years past for AT&T.

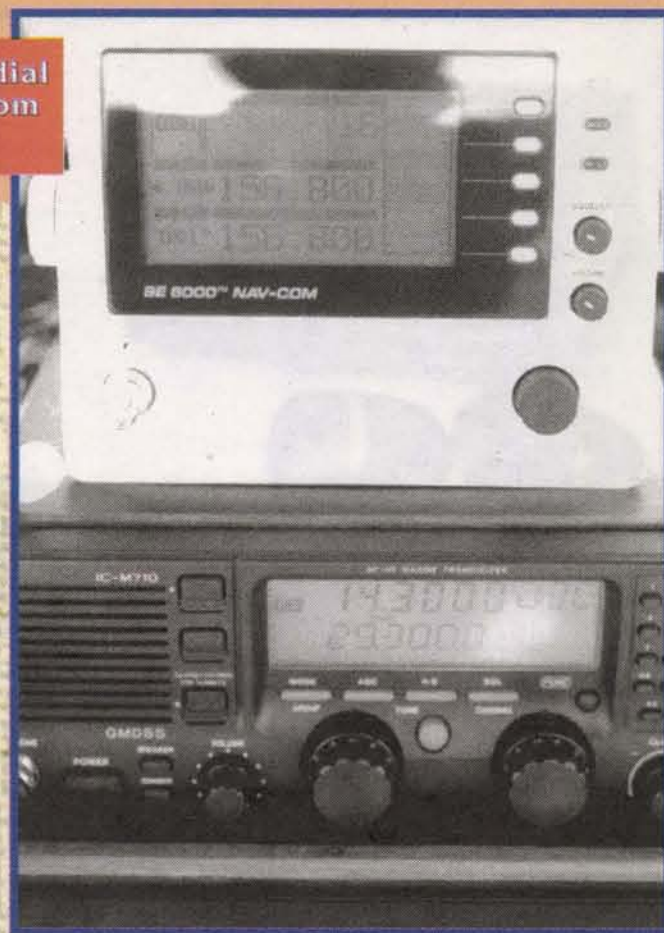

So don't throw out your marine SSB yet — and if you're looking for an inexpensive way of making phone calls from an SSB, contact WLO and get registered with no monthly registration charge.

Remember, next month — all about high-frequency SSB E-Mail. **NV**



Used HP Duplex Laser Printers Blowout Price \$300.00

Hewlett Packard IIID - Empty MIO Slot to Install a Jet Direct Card
300 DPI - Can Print Double or Single Sided - Dual Letter Trays
Can Take Letter or Legal Size - 3 Meg of Ram (Expandable to 8)
Lease Returns, but were well maintained Under Service Contract
No Hassle 30 Day Warranty - Uses 95A Cartridges

Quality Computer Towers AT Style (Not ATX)

Full (260 Watt)(11 bays) \$35.00

Mid Size (230 Watt)(7 bays) \$22.00

Mini Size (230 Watt)(6 bays) \$17.00



Hard Drives

New 2.1 Gig Seagate SCSI
\$80.00

New Micropolis 1.53 gig SCSI
\$50.00

New 760 Meg ESDI XT8760EH
\$40.00



Lots of MicroWave Goodies In Stock

Brand New Wavetek 907AF Frequency Generators

Range 7-12.4 GHz \$1000.00

HP Direct Reading Frequency Meter

#R532A 26.5-40 GHz New \$500.00

SMA Attenuators - Stepper Motors



Electro Mavin

800-421-2442 or FAX 310-632-9867

E-Mail john@mavin.com


Visit Our Web Site for More Info and Specials

<http://www.mavin.com/mavin.html>

Scott Edwards Electronics



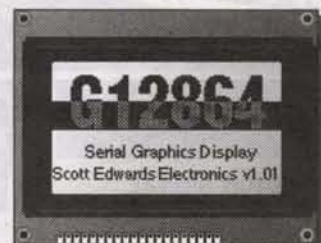Graphics LCD Module with Serial Interface



3.66" by
2.76"

The new G12864 makes it easy to display text and graphics on a 128-by-64-pixel LCD. It interfaces with a computer through a 2400 or 9600-baud RS-232 serial hookup.

Text Features

The G12864 works like a serial-receive terminal. It displays text in a 4-line by 16-character format. Text is displayed in a large 8- by 16-pixel font, which can be edited to include custom symbols.

Graphics Features

The display lets you plot points, draw lines, and display full-screen graphics using easy instructions. Its flash memory stores the text font plus 14 screens. You can create fonts and graphics on your PC, then download them to the G12864 using the included software.

Convenience Features

A power supply and DB9 serial-port connector are built in. Connect the display to the (included) AC adapter; plug the (included) serial cable into your PC or other computer, and you're ready to go. Current draw ranges from 15mA (typical, backlight off) to 100mA (max, backlight on). For complete specifications, see our web site: www.seetron.com.

Display, with starter pack: \$199 Display alone (OEM qty 1): \$179

Scott Edwards Electronics • PO Box 160 • Sierra Vista • AZ • 85636-0160

ph: 520-459-4802 • fax: 520-459-0623 • e-mail: info@seetron.com

Internet: www.seetron.com

We've Got It!

MCM Electronics®

Prices effective
January 15 through
February 26, 1999.

MCM is the leading supplier to the consumer electronics service industry. Additionally, hobbyists, educators and even manufacturers have looked to MCM for all of their component needs. Call today for your free catalog!

Multi-Voltage Power Supply

Fully regulated supply provides up to two amps, at the following selectable voltages: •3. •4½ •6V •7½V •9V •12V. Regular price 16.95.



Order #
#28-2200
\$9.95

Nickel-Metal Hydride Cells

Get NiMH performance in a standard "AA" or "AAA" cell. Performance is 50% over that of Ni-Cad batteries of the same size. Sold individually.

Order #	Size	(1-9)	(10-49)	(50-up)
29-2615	"AA"	\$3.59	\$3.29	\$2.99
29-2620	"AAA"	4.19	3.89	3.59



AS LOW AS
\$2.99

Micro PC Board Camera

DEFENDER SECURITY

B/W CCD camera measures only 1½" x 1¼" x 1". Provides NTSC composite video output. Built-in 3.6mm lens provides viewing angle of 92°. Requires 12VDC, 300mA. (#58-3330 AC adaptor). Regular price \$64.95



Order #
#82-2980
\$49.00

Color PC Board Camera

DEFENDER SECURITY

Ideal for any observation, multimedia or security application. Provides NTSC composite video output. Features automatic white balance, 330 lines of horizontal resolution and AGC. Requires 12VDC, 240mA. Regular price \$199.00



Order #
#82-3015
\$149.00

RF Modulator

Outstanding price on this popular audio/video/surveillance accessory. Accepts standard A/V signal and places it on channel three or four. RCA type inputs, "F" type output. Requires 117VAC. Regular price \$25.75.



Order #
#33-1480
\$19.95

Wide-Band Radio Scanner for Your PC

WiNRADiO™

Integrates advanced radio receiver technology and the power of a personal computer. Tune continuously from 500KHz ~1.3GHz (cellular blocked), FM (wide and narrow), AM and SSB. Hear virtually all police, fire, government, military, overseas broadcasts, HAM radio, citizens band broadcast AM, FM, and television audio. Requires Windows 3.1 or higher (including 95 and NT) and vacant slot for 16 bit ISA card. Regular price \$499.00



Order #
#111-6000
\$399.00

8" Rubber Surround Polypropylene Woofer

MCM AUDIO SELECT™

Popular woofer design is the foundation of many home and auto speaker systems. 70W/100W RMS/peak capacity, frequency response 30Hz~3.5KHz, 8ohm. Other sizes available. Regular price \$13.50



Order #
#55-1180
\$9.99

6½" Shielded Magnet Woofer

MCM AUDIO SELECT™

Great for use in home theater applications. Shielded magnet allows use near TV and computer monitors. Features polypropylene cone and rubber surround. 45W/60W RMS/peak capacity, frequency response 40Hz~5KHz, 8ohm. Other sizes available. Regular price \$14.25



Order #
#55-1186
\$9.99

Pre-Assembled Circuit Modules

CEBEK™

Ideal for repairing old equipment, prototype work or your latest project. These well constructed PC boards are fully assembled, tested and ready to use. Supplied with application instructions and technical specifications. All operate from a single 12VDC source. Call your MCM Sales Representative for more information on over 120 available modules.



Order #	Description	Reg.	Sale
28-4795	1W audio amplifier	\$7.49	\$5.99
28-4796	5W audio amplifier	13.95	11.15
28-4800	5W x 2 stereo amplifier	24.95	19.96
28-4801	15W x 2 stereo amplifier	39.95	31.96
28-4851	88~108MHz FM transmitter	24.95	19.96
28-5115	Flip-flop relay	14.95	11.96
28-4825	VOX relay	17.95	14.36
28-4815	Electric guitar preamplifier	8.95	7.16

To take advantage of special pricing on the items listed, please provide this code: **NVM23**

32 Piece Security Bit Set

Ideal for all of those difficult service applications including computer monitors, cable, telephone and vending equipment. Removes most types of security screws including security hex, torx, spanner and tri-wing. Regular price \$15.39.



Order #
#22-1875
\$8.99

Aluminum Tool/Equipment Case

Clarke



Order #
#21-3462
\$34.95

Includes one tool pallet and pre-cut foam bottom. Ideal for carrying test equipment with small hand tools and accessories. Black finish, measures approximately 19" x 14" x 6". Regular price \$51.50.

Multiple DC Outlet Strip

Valuable accessory to any benchtop power supply. Eight pairs of RF bypassed binding posts allow easy connection and disconnection of multiple accessories. Features analog voltmeter, power switch, built-in fuse and 15A capacity.



Order #
#11-2974
\$44.95

12V/2.3 AH Sealed Lead Acid Battery Pack

Panasonic

Original Panasonic battery is commonly used in bag phones, full size camcorders and all types of portable equipment. Uses standard clip, such as MCM #28-3135.



Order #
#7-PV-8P88A/3H
\$38.95

DMM With Logic Function

TENMA™

3½ digit DMM measures AC/DC voltage from 200mV~600V, resistance to 2000Mohm, capacitance to 20µF, transistor hfe gain and audible continuity test. Requires 9V battery (#290-080) not included. Dimensions: 2½" (W) x 5½" (H) x 1½" (D). Regular price \$65.95.



Order #
#72-4025
\$39.95

FREE Catalog

Same Day Shipping!

In stock orders received by 5:00 p.m. (YOUR TIME), are shipped the same day.



MCM ELECTRONICS®
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER FARNELL Company

For complete ordering information on the items listed, or a free catalog, Call...

1-800-543-4330
www.mcmelectronics.com

SOURCE CODE: NVM23

What's inside a TV power splitter?

Ever wonder what's inside a TV power splitter? Several events made me curious about how they worked and their performance, so I opened some up and made some measurements. Power splitters have an input port S and two output ports, A and B. Ideally, the signal power going into port S splits equally between the coupled ports.

Some important criteria for power splitters are:

- Port Impedance Matching
- Port Isolation
- DC Power Distribution

TV power splitters for 75-ohm cable should look like 75 ohms at each port. Mismatched ports cause reflections and power losses, and that hurts the signal-to-noise performance. Except for weak signal environments,

rents to be the same ($i_A = i_B$). If the output currents are the same and they both flow into the same output impedance (Z_0), then the output voltages (V_A and V_B) will be the same. Thus, the transformer enforces the basic divider operation by forcing the input current to divide equally between the two output ports.



The transformer is also a voltage divider, so the center-tap voltage is at the midpoint of the two output voltages, $(V_A + V_B)/2$. If the output port impedances are similar, then the output voltages are equal. Consequently, the center-tap voltage also equals the output voltages, and there would be zero volts across the transformer.

The operation of the balancing resistor is subtle. If the output ports are matched, then the output voltages are equal and no current flows through the balancing resistor — it's as if the balancing resistor weren't there. If the output voltages are different, then a current will flow through the resistor. The value of the balancing resistor is chosen so that all of the

by Gerald Roylance

Looking Inside a Power Splitter

Figure 2. Two Power Splitters

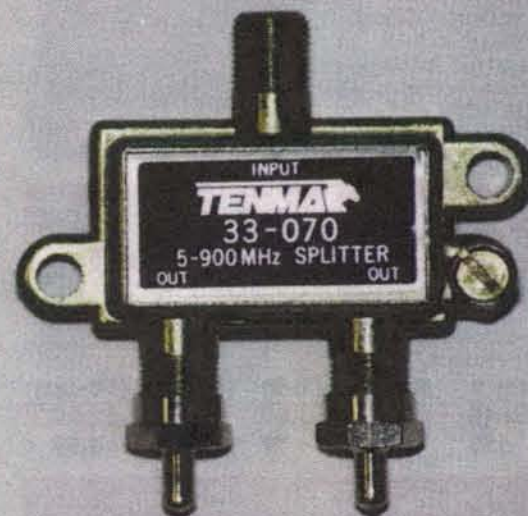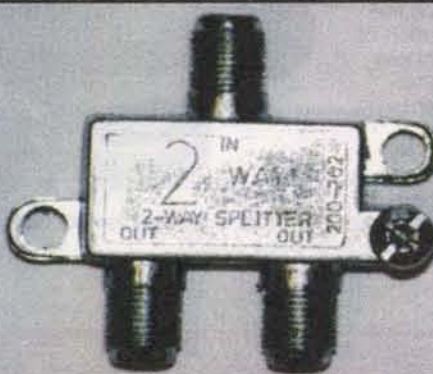

the losses won't mean much (a two-way splitter has an intrinsic 3dB loss already), but the reflections can cause ghosts.

The second criteria — port isolation — helps to keep signals clean even when there are reflections. A signal going into port A of a power splitter should not appear on port B. Port isolation prevents reflections and noise on port A from causing ghosts and interference on port B and vice versa.

DC power distribution is important when a power splitter sits between an inline amplifier and its power source. In low signal strength areas, placing an amplifier at the antenna will eliminate feed line losses and improve reception. To simplify installation, these amplifiers often get their power over the coaxial cable from a power insertion module located inside the house. A power splitter that shorts DC to ground prevents power from getting to the amplifier; a splitter that blocks DC cannot be used between the amplifier and the power source. Three of the four splitters I looked at would pass DC.

Power Splitters

In his book *Introduction to Radio Frequency Design*, American Radio Relay League, 1994, Wes Hayward describes the basic power splitter as seen in Figure 1. The circuit — also called a zero degree hybrid — consists of a center-tapped ideal transformer and a balancing resistor. The circuit operation is clever, but its basic operation follows from a few observations.

Ignore the resistor for the moment and focus on how the transformer splits the power to the outputs. The transformer forces the two output cur-

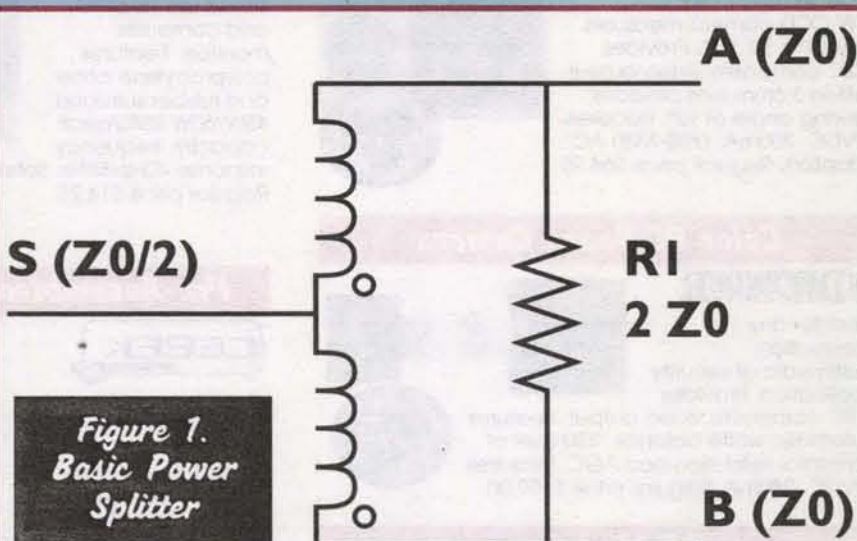


Figure 1. Basic Power Splitter

unbalanced current flows through the resistor and none enters the transformer.

The basic power splitter has unequal port impedances: $Z_S = 0.5 Z_A$ because the two output ports are essentially connected in parallel (when the loads are balanced, all the port voltages are the same). To make the impedances match, the splitter needs an impedance matching network. For broadband performance, that network is a 2:1 matching transformer.

The Power Splitters

Four different power splitters were tested. The first two are shown in Figure 2, and their internal parts are shown later. In addition to these two splitters, two other splitters were electrically tested.

Power Splitter Number One

The first power splitter of the group has model number 200-202 molded on its case. Black Point Products distributes the splitter as a BV-017, Two-Way Splitter, but other companies distribute the same part.

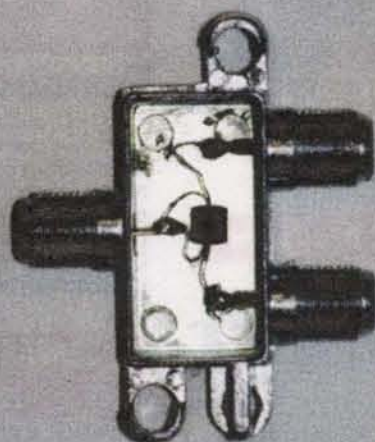


Figure 3. Internal View of 200-202

Figure 3 reveals the inside of the 200-202 power splitter — only the center-tapped transformer of the basic splitter design. This splitter design omits the matching transformer and the balancing resistor. Consequently, the match at the input port and the isolation should be poor. The design easily passes DC current among all ports because the transformer appears as a wire at DC.

Since the design does not have an impedance transformer, the input impedance will be 75 ohms divided by 2, or 37.5 ohms. The mismatch causes reflections at the input port, and the reflection coefficient is $\rho = (75 - 37.5)/(75 + 37.5) = 1/3$. One ninth (i.e., ρ^2) of the input signal power will be reflected and lost. The input mismatch causes a loss of 0.5 dB.

The missing balancing resistor will not affect the power split if the output ports are matched, but it will affect the isolation.

Power Splitter Number Two

The second power splitter is a Tenma model 33-070, 5-900 MHz splitter. The insides are shown in Figure 5, and its schematic is shown in Figure 6. This splitter has a matching transformer, but does not have a balancing resistor. The matching 4:3 autotransformer has a 16:9 impedance ratio, so the transformer converts the 37.5 ohms of the power splitter section to 67 ohms at the input port. The resulting ρ is 0.06 and the mismatch loss is 0.01 dB.




The matching transformer returns to ground through a 1nF blocking capacitor that prevents a DC short. Consequently, this splitter will pass DC power to all ports. The 2pF shunt capacitor tunes out the lead inductance to make the splitter have a broader bandwidth.

Other Power Splitters

Two other power splitters were electrically tested. Power splitter number three is a Gemini Industries, Inc., model number CV60. This model looks similar to the Tenma splitter. The fourth splitter is a Tru-Spec DSV-2, 5-450MHz, and is a splitter that my cable TV company installed.

Electrical Testing

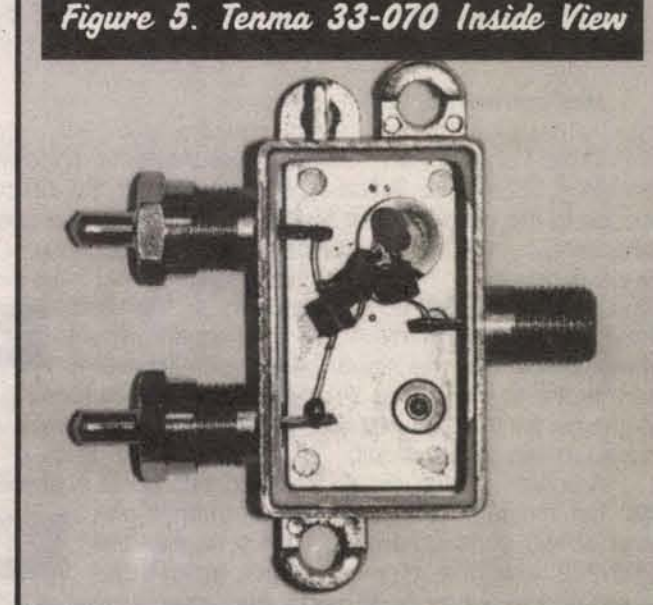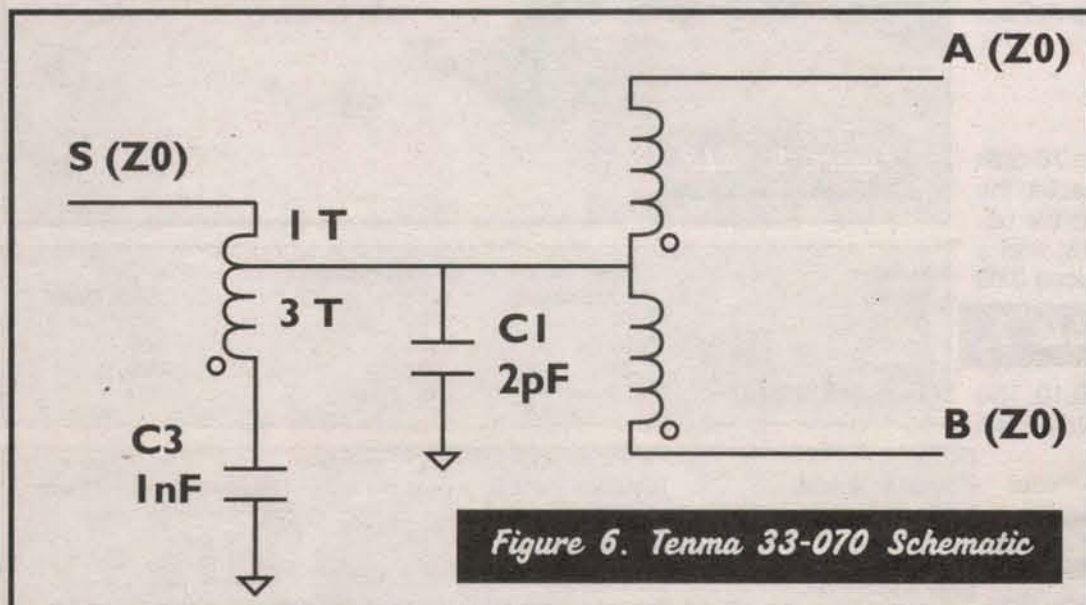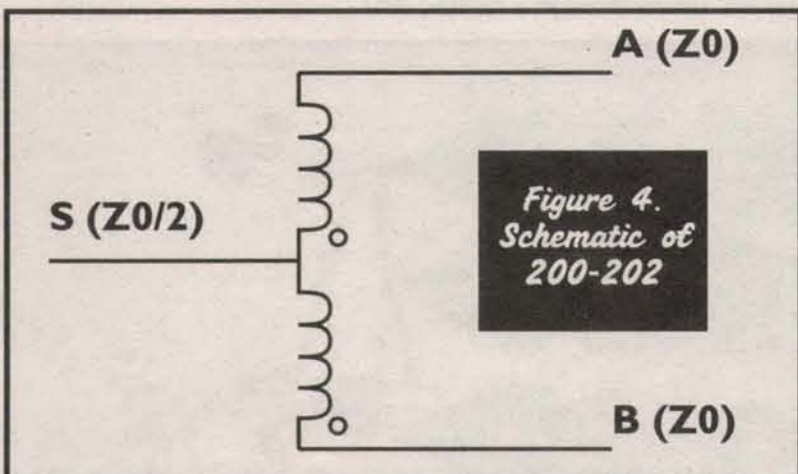Clearly, all power splitters are not created equal. Some are missing



100 WATT AUDIO AMP

GROMMES-PRECISION ST100E AUDIO AMPLIFIER, solid state 100 watt public address amp; response 35 to 20000 Hz 4 ohm output, 0.3% distortion. Volume controls for MIC-1 & -2, AUX input, MUSIC and MASTER plus BASS and TREBLE controls. Also slide switches Loudness bass boost and Lo Filter plus Peak Power/Over-load indicator. Back panel outputs for 4 to 8 ohm and 25 or 70 V speakers, Booster Amp, Mute, 600 ohm telephone line page, two Lo or Hi Z mic select, two XLR 3-pin male mic connections and AC accessory outlet. 4.3x15x12.8, 25 lbs sh. NEW, \$249.50

1950's CAR TACHOMETER

HEYER MODEL 337 TACH / VOLTMETER with 4.5" chrome-rimmed meter. ranges 0-1000 & 0-5000 RPM and +/- 0-18 VDC. Amplifier button plus socket for timing light. With tubes 0A2 & 2D21; 6 or 12 VDC use. Nice addition to a car collector's display! 13x5x5, 9 lbs sh. UNUSED, not tested, \$24.95



1 to 1400 MHz Sweeper

WAVETEK 2001A SWEEP GENERATOR, covers 1 to 1400 MHz sweep and CW in bands 1-500, 450-950, and 950-1400 MHz. Sweep width 50 KHz to 500 MHz. Sweep time: 100 to 0.01 S in 4 decade steps. Markers at 0.2, 1.5 and 20 MHz harmonics and single frequencies 63 MHz, +/-0.35 and +/-0.9 MHz. Marker width 15-400 KHz in 4 steps. RF output continuously adjustable +9 to -81 dBm into 50 ohms. Requires 115/230 VAC 50-60 Hz; 5.3x 11x14.2, 25 lbs sh. USED-repairable w/book, \$395.00

30 FT ANTENNA MAST

AB-1244/GRC MAST KIT, twelve aluminum alloy on steel sections form sturdy, yet lightweight 30 foot 1.7" dia mast. Kit includes five each lower and upper sections, one ea lower and upper adapter sections, gin pole swivel base, four ea 36 and 42 ft guy ropes, four guy stakes, two guy rings plus a 2.5 pound sledge hammer. Part of OE-254/GRC antenna set; 30 lbs. NEW, \$139.50



Prices F.O.B. Lima, Ohio. VISA, MASTERCARD accepted.

Allow for shipping charges. Write for latest Catalog.

Address Dept. NV + Phone 419/227-6573 + FAX 419/227-1313

E-mail: fairradio@wcoil.com Home Page: <http://www2.wcoil.com/~fairradio>

FAIR RADIO SALES CO.

1016 E. Eureka + Box 1105 + Lima, Ohio 45802



Write in 94 on Reader Service Card.

elements such as matching transformers and balancing resistors. Do these omissions affect performance a lot, or are there some subtler design tricks hidden in their design? Running some electrical tests will verify their performance.

To that end, a return loss bridge (RLB) was made for reflection testing, and some isolation measurements were made.

Return Loss Bridge

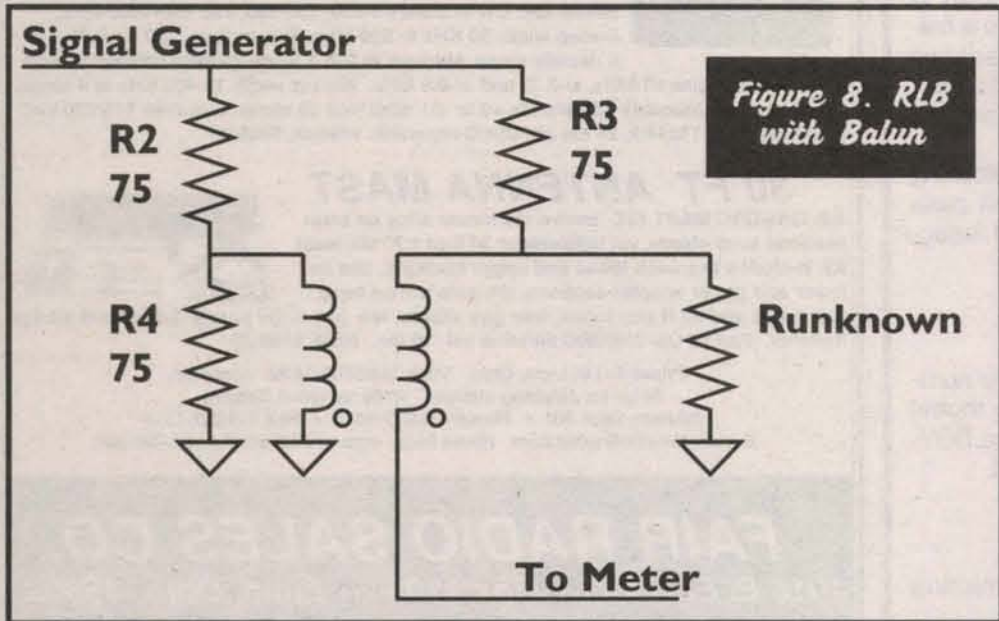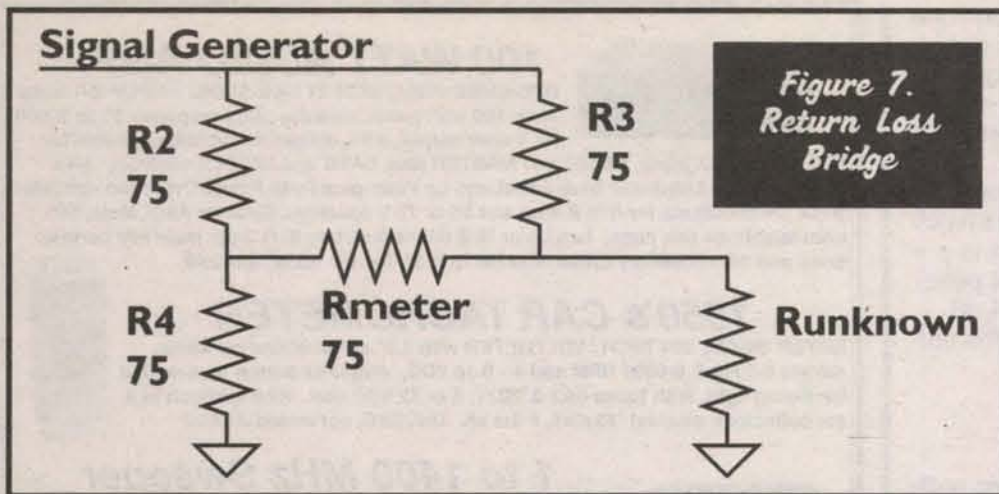Reflection measurements can be made with a return loss bridge (Figure 7). The basic bridge looks like five resistors — four resistors for the bridge and one resistor (Rmeter) across the bridge that represents the



measuring instrument. One of the four bridge resistors (Runknown) is the transmission line that we are trying to measure. If the bridge is balanced, then the voltage across the bridge (between V2 and V1) will be zero and the measuring instrument will read zero. Hayward (c.f. page 151) describes how $V2 - V1$ is proportional to the reflection coefficient $\rho = (1 - y)/(1 + y) = (z - 1)/(z + 1)$.

Unfortunately, the voltage between VA and VB is floating, so it is difficult to measure with a grounded instrument. A balun transformer (see Figure 8) converts the balanced bridge voltage to an unbalanced signal that drives a terminated detector (I used my oscilloscope). The actual bridge is shown in Figure 9.

When making measurements, all ports and lines must be properly terminated. Most of my test equipment is 50 ohm, so I used some 75-ohm to 50-ohm min-loss attenuators in some crucial places, so my 50-ohm generator, cables, and scope would not compromise the measurement. The min-loss attenuator has a series 43.3-ohm resistor on the 75-ohm side and a shunt 86.6-ohm resistor on the 50-ohm side.

Reflection Testing

Table 1 shows the reflection measurements made with a 75-ohm bridge at 138.6 MHz. A two-foot length of foam RG-59 connected the bridge to the device under test. An open circuit was used as the reference ($\rho = 1.0$). A 75-ohm terminator produced $\rho = 0.18$, and a short produced $\rho = 0.89$. The terminator should have produced 0.00 and the short 1.00, so the numbers in the table have some uncertainty. A $\rho = 0.18$ means about three percent of the signal power is reflected. A terminator at the bridge (no RG-59 cable) produced $\rho = 0.10$. The numbers for the 200-202 and the Tenma are what we would expect from looking at the circuit.

A power splitter should be used with ports A and B terminated, but the table includes measurements with one or two ports unterminated. Notice that the 200-202 and the Gemini reflect almost the entire signal when both ports are unterminated. Curiously, the

Table 1

Table 2

Tenma splitter reflection coefficient is not close to one when A and B are open — apparently the splitter consumes about 1/3 of the incident signal power.

Transmission/Isolation Testing

The isolation between ports A and B is tested by injecting a signal into port A while looking at port B. Port S is terminated in 75 ohms. The 200-202 splitter should have poor isolation because its S port is mismatched (remember it is 37.5 ohms). Here is how the S port mismatch hurts isolation. The test signal from port A travels to the S port, where some of it is reflected by the 37.5- to 75-ohm mismatch. The reflected portion travels back through the power splitter, where it divides equally between the A and B ports. Good input match is required for good isolation.


Although the Tenma splitter should have poor isolation because it does not have a balancing resistor, its isolation figure is reasonable. The transmission numbers agree with the reflection coefficients above: Those units with high reflection coefficients show more transmission loss (see Table 2).

Summary

Sadly, some power splitters have mismatched ports. TV splitters do not cost much, so some manufacturers have omitted the matching transformer and/or balancing resistor.

Although the Tenma and the Gemini splitters look almost identical on the outside, the Gemini's poor reflection coefficient suggests the inside is closer to the 200-202. Curiosity got the better of me just now, and my can opener reveals the Gemini is the same design as the 200-202. Maybe the Tru-Spec has all the right components, but it is not mine, so the can opener goes back to the kitchen.

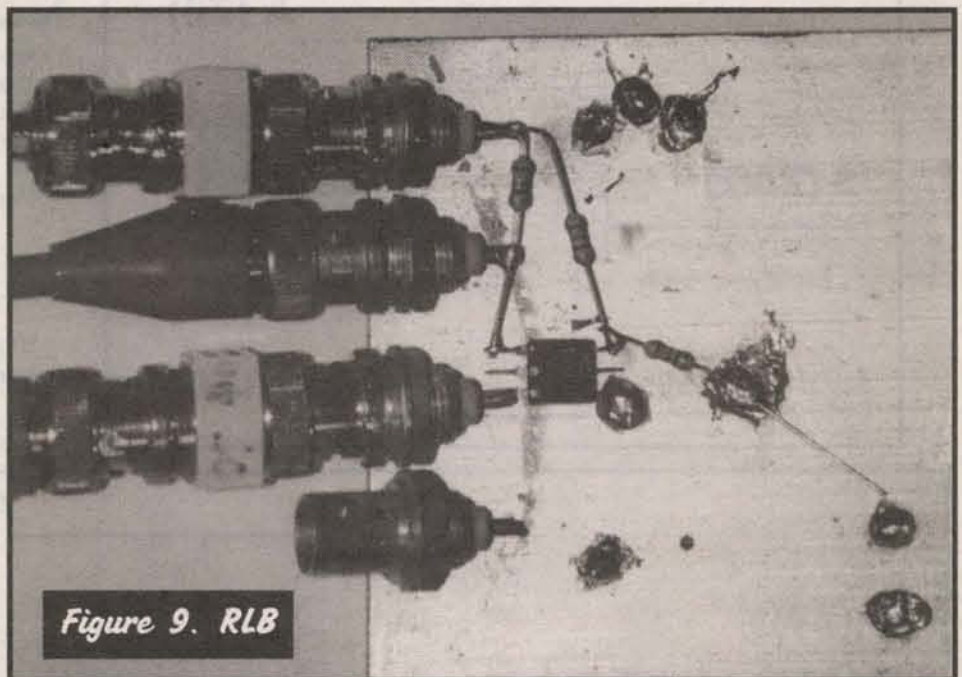All but the Tru-Spec splitter pass DC power among the three ports. The three Tru-Spec ports are DC shorts to ground, so the design is probably similar to the Tenma splitter without the 1nF DC blocking capacitor. Get out your ohmmeter before you apply power through a splitter. **NV**



Splitter Model	A&B Terminated	A Terminated, B Open	A&B Open
200-202	.34	.25	.95
Tenma	.13	.36	.80
Gemini	.32	.48	.98
Tru-Spec DSV-2	.15	.55	.90

Splitter Model	Isolation port A → port B	Transmission — Term
200-202	.17 = 15dB	.68 = -3.4dB
Tenma	.05 = 26dB	.69 = -3.2dB
Gemini	.08 = 22dB	.65 = -3.7dB
Tru-Spec DSV-2	.03 = 30dB	.70 = -3.1dB

reader FeedBack

Dear Nuts & Volts:

I am a long-time subscriber having paid \$25.00 for a lifetime subscription when *Nuts and Volts* was an infant. I saw what I thought was a good opportunity to get a good subscription to a good magazine, and I have never been disappointed with your magazine.

Nuts and Volts has really grown, not just in size, but in quality as well, and rates tops with me!

I have been a ham and experimenter since 1950 and you are "right down my alley."

**Jim Walts
Bruce, FL**

Dear Nuts & Volts:

I have the following comments regarding question #11986 which was posted in your Nov. '98 issue of *Nuts & Volts* magazine, and its corresponding answer which was posted in your Dec. '98 issue.

I also have a RadioShack multi-meter — a Micronta 22-168 — and encountered the same serial communication problems that Grant Fair had with his meter, when I wrote a Windows95/DOS application in Basic to read the meter from my Compaq Pentium laptop.

I wanted to be able to automatically sort various resistors and capacitors that I had obtained at the surplus stores by using the application to read the meter and find the closest standard value to the actual reading.

I read the response given to Grant's question by Roger Omori, in your Dec. '98 issue and tried some of his suggestions which were very helpful in getting my application running.

First, I tried the various serial protocol changes suggested by Roger, using the Procom communications package, but I could not get a reading from the meter.

Next, I coded versions of the example in GW-Basic, Stamp BS2 BASIC, and Borland C++ and could not get any of them to work.

Finally in desperation, I found the number for the RadioShack customer support on the web and contacted them. Their response was to let me know that the Basic program listed in their manual was just an "example" and as such they

could not provide me with any information or support. This included questions I asked them regarding what kind of Basic was used for developing the example, and who the actual meter manufacturer was, so that I could contact them for information.

I tried once more to code the example, this time with Quick Basic, making sure that there were no other Windows 95 applications using the COM1 serial port.

I also checked the serial device driver for COM1 using the Windows 95 control icon under the settings menu, and double-checked all cables.

I specified the serial communications protocol using the following Quick Basic statement: OPEN

"com1:1200,n,7,2,rs,cs,ds,cd" FOR RANDOM AS #2 (see attached listing for more details).

When I turned on the meter, to my surprise, I was able at last to obtain the resistance readings.

To this day, I still don't know why the application did not work. The root cause of the problem could have been due to the fact that the meter may be using hardware handshaking, because the serial cable provided for the meter has five pins instead of the customary three pins used for most serial RS-232 communications. This would certainly explain why the communications software did not work, if it was not setup to use handshaking.

Unfortunately, the manual does not describe the handshaking protocol used. If any of your readers have more information on this subject, I would appreciate hearing from them.

**Daniel F. Ramirez
Amherst, NH**

Dear Nuts & Volts:

Congratulations on 20 years! Great stuff for newbies and old timers in every issue.

**John Capron
Newark, CA**

Dear Nuts & Volts:

Mr. Roylance delivered a great article. I was gratified to read history that escaped me in 50 years of electronics!

Jon

Modern computing and standard surge suppressors... a recipe for disaster.

Almost all surge protection devices use MOV's (metal oxide varistors) as their active element. MOV's are sacrificial/wear/limited life components. Surge suppressors based on this technology are doomed to failure. These surge "suppressors" also don't suppress a thing. They divert powerline surges equally to the ground and neutral wire. When you put current on the common ground wire of interconnected equipment some of that current will flow (through the inherent ground loops) to the data lines. This is a major cause of lock-ups and misoperations that plague today's computer environments. Another fact; all modern computers use switch mode power supplies. During surges the power supply capacitors must charge to the clamping level of the MOV before the MOV turns on. A recent study has shown that it takes a 3000A surge 15 microseconds (15,000 nanoseconds) to charge the typical capacitors of these power supplies to that level. The surge is virtually over before the MOV reacts. (See *five things you probably don't know about your surge suppressor* at www.firethings.com.)

THE POINT: Standard surge suppressors allow too much current to hit the computer. Standard surge suppressors divert surge current to the ground wire and disrupt data transfer. Standard surge suppressors eventually fail without warning. Modern computers have logic voltage levels (the signals that transmit the data) and power supply voltages that are dramatically lower than that of their recent predecessors. Modern computers use integrated circuits with transistors of ever decreasing physical geometries. Modern computers are virtually always interconnected to other computers or peripheral equipment. The bottom line; *modern computers are much more sensitive and susceptible to powerline anomalies.*

INTRODUCING BRICK WALL SURGE FILTERS... The World's Best Surge Suppressor

Initially engineered for critical, non-fail industrial applications, this patented device protects indefinitely and sets a new standard for every measure of surge suppressor and powerline filtering performance.

A Brick Wall 1) Utilizes NO MOV'S or Any Other Sacrificial Components (a two pound inductor and nine capacitors are the heart of the unit) 2) Has No Joule Rating or Surge Current Limitations 3) HAS BEEN TESTED AND CERTIFIED BY UL TO THE MOST DEMANDING CLASSIFICATION OF A NEW GOVERNMENT SPECIFICATION; CLASS I, GRADE A. Which Means: UL PUT ONE THOUSAND 3000A, 6000V SURGES (this is the largest surge an interior environment can experience) THROUGH A UNIT (at 60 second intervals) AND DOCUMENTED NO FAILURE OR PERFORMANCE DEGRADATION OF ANY KIND WHATSOEVER.

i.e.: A Brick Wall Will Not Fail.

We know of no cord connected, MOV based surge protection device that has, or can pass this test.

A Brick Wall possesses UL's lowest Suppressed Voltage Rating (let-through voltage) of 330V. This is the lowest rating they will grant. In that test of one thousand 6000V, 3000A surges, **UL NEVER SAW THE LET-THROUGH VOLTAGE EXCEED 290V. YOU CANNOT DO BETTER THAN THIS FOR A POINT-OF-USE SURGE PROTECTION DEVICE.** Once again, we know of no other surge protection device that could come close to this performance level.

A Brick Wall is a current activated Series Mode device. Since it is not wired in parallel, nor voltage activated, it does not have to wait for the capacitors of the power supply to charge before it becomes effective. **YOUR EQUIPMENT IS PROTECTED INSTANTANEOUSLY (and indefinitely).**

These devices were engineered utilizing a current limiting/surge filtering technology. **THEY DO NOT DIVERT ANY SURGE CURRENT TO THE GROUND WIRE.** They Will Not Cause Your Computer System To LOCK-UP, CRASH OR MISOPERATE as a consequence of surge diversion. Your current surge "suppressor" will.

Powerline Filtering

In addition to all this, Brick Wall Surge **FILTERS** are the best AC powerline filters you can buy (that we have been able to find anyway). Industrial machinery, copiers, coffee makers, laser printers, fluorescent lights, refrigerators, etc., all cause powerline noise that can cause your computer to misoperate. A Brick Wall Surge Filter will make powerline noise related problems disappear.

You Can't Buy a Better Surge Protection/Powerline Filtering Device... Anywhere.

SO... HOW IMPORTANT IS YOUR SYSTEM?



**BRICK WALL DIV.,
PRICE WHEELER CORP.
1-800-528-0313**

Fax: 1-800-528-6623 E-Mail: info@brickwall.com

Web: www.brickwall.com

Visa - MC - AMEX

ASK ABOUT OUR NEW IN-LINE UPS/SERVER PROTECTOR



Available in Modular Form

A SWEETHEART of a DEAL for YOU!

ARGON LASER POWER SUPPLY. THE INDUSTRY STANDARD, AMERICAN LASER 60X

We were fortunate to obtain these unused and factory refurbished ALC 60X power supplies. Always in demand but hard to find. They can power most Argon heads up to 12AMPS. We have no manuals at press time. If you have a 60X series head or similar this is the unit for you. 110VAC power. Rugged anodized aluminum, housing with internal fan. Size: 8"x8"x11", 22 lbs. Don't miss out. Very Ltd. Qty. **ALC60X...\$429ea. or 2 for \$799**



PRICE BUSTER, DSP, COLOR, MINI C-MOUNT, CAMERA,

New, model GM859, Size only: 2" x 2" x 2.5", Latest 1/4" CCD technology. Res. 350 lines, sens., <3lux, auto white balance, AGC. Auto iris connector. 9-12VDC @150ma power BNC video out. Switchable gain. Superior cast aluminum housing with top and bottom mounting. Perfect for general surveillance. Less lens. See lens options below.

Reg. \$299, Save \$100, Special, GM859...\$189ea.

TWO MINI C-MOUNT CAMERAS, The super sensitive,

GM410 or the general purpose GM412, The GM-412 specs: 8&W,

size 1.5"sq. X 2.4"L, 250,000 Pixels, 380 Lines Resolution, Sensitivity 0.3 Lux, The GM410 specs: size only 1.5" SQ. x 1.6"L, >270,000 Pixels, 410 Lines Res., Sens. 0.05 LUX. Both cameras are 1/3" CCD with AGC & Electronic shutter. 12V @110mA power. NTSC out. IR SENSITIVE, BNC video out, Both use std. DC pwr. jack. Aluminum housings with dual threaded top and bottom mounting. True performance not hype! These cameras will outperform ANY camera in this magazine. Multi-lens options are available to exploit their superior performance. **GM412, less lens...\$119, GM410, less lens...\$169**

C-MOUNT LENS OPTIONS TO ENHANCE YOUR IMAGE:
Fast Lenses for Low Light or General Purpose Normal Light

16mm, f1.6, 15° FOV	\$39	4mm, 80° FOV	\$24
8mm, f1.3, 40° FOV	\$49	8mm, 40° FOV	\$24
4mm, f1.4, 78° FOV	\$49	12mm, 28° FOV	\$24

SUPER! UNDERWATER (60 ft.) "LIPSTICK" CAMERA with INTEGRAL INFRA-RED ILLUMINATOR!

Sleek black anodized, BRASS, housing is O-Ring sealed & WATERPROOF. Adjustable mount included. Specs: 1/3" CCD, 400 Lines resolution, 0.05 Lux sensitivity, AGC, Auto Shutter. Operates on 12VDC @225mA, 3.6mm, 92° FOV lens. A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Great for general outdoor use also. **REG. \$299, GM-300KIR...\$219**



WE GOT THE SHAFT and YOU BENEFIT! TINY, PRECISE, PORTESCAP, SWISS, GEARMOTORS.

These mini motors are state of the art "ironless" type. Model A: 1219E-012-G-400 with 1044:1 Planetary gearbox. Size: 12mm diam. x 44mm L (above) Model B: M11-210-54-0 with approx. 40:1 spur gearbox. Size: 16mm diam. x 43mm L (right) Both have 2d x 6mm L, flattened shaft, solder terminal for power.

	VIN	INL	RPM
Type A:	6V	5mA	68
	12	5mA	145
Type B:	6V	8mA	141
	12V	12mA	290

LIMITED QUANTITY

TYPE A: \$19ea. or 2 for \$34

TYPE B: \$15ea. or 2 for \$27

MOTORIZED LINEAR SLIDE, with Z AXIS DRIVE

Heavy duty 3/8" diameter chromed steel rods provide up to 9 inches of linear travel. X drive is via a toothed belt powered by a SLO-SYN M061-LF-409, 1.25V@3.8A stepper motor with 200 steps per rev and 75 oz. in. hold. The Z axis is attached directly to the slide, provides 2 inches of travel and is powered by its own Rapidsyn 23E-6108BH 1.25V@3.8A stepper. 200 steps per rev and 60 oz. in. of hold. Very precise motion is possible due to the approx. 4:1 ratio toothed belt drive. Nice quality, suitable for gen'l use. Not recommended for light load applications. Removed from precision optical equipment. Overall size: 17"L x 6"H x 5.5"D. Complete assembly mounted on a rigid 1/4" thick base. Limited Quantity. **X Z-200 DRIVE SYSTEM...\$69ea. or 2 for \$99.**

NEW MICRO CAMERA, w/audio

1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Pwr. from 9 to 12VDC @100mA, 250k PIXELS, Std. model, 3.6mm, 92° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 once! SENSITIVE to IR. Size Std: 1.25"sq. x 1.0" H x 0.6"d. Both with 6' leads. **WARNING:** Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS. Six models to choose from:

GM-1000A-STD...\$80	GM-1000A-STD/Aud...\$85
GM-1000A-PH...\$80	GM-1000A-PH/Aud...\$85
GM-1000A-CMNT...\$80	GM-1000A-CMNT/Aud...\$85

2.5mm, 150°.....\$22	8.0mm, f2.0.....\$22
4.3mm, 78° f1.8.....\$22	12.0mm, f2.0.....\$22
6.0mm, f2.0.....\$22	5mm, 70°-PH.....\$22

Micro Lenses for GM1000 series

NEWPORT, PRECISION TRANSLATION STAGES. for those with a NEED to PERFORM!

Model 495A MOTORIZED, ROTARY STAGE,

Bidirectional 360° continuous rotation, 0.001" res. Integral DC motor & encoder. Load independent velocity servo. Mount in any orientation. Capacity: 55lbs. Size: 4.75"x5"x1.35" with 2" clear aperture. **NEWPORT price \$2141, Our Price \$795**

Model 400 or 406 X-Y Platform,

Two orthogonal positioners in one low profile unit. Super stable pre-loaded linear bearings can support up to 100 lbs. Provides 1/2" travel. <200urad deviation. Model 400 has solid top plate. The model 406 (shown left) has a 2.25" diam. clear aperture though the unit. Both include 2ea. SM-13 vernier micrometers with 0.001mm resolution. Size: 5.5" x 5.5"

NEWPORT price \$600, Our Price...\$349ea.

Model 436 Translation Stage,

Crossed roller bearing design for precision movement and load capacity. Lockable, stackable, reversible for left or right hand operation. Hardened carbide actuator insert. Pre-loaded against backlash. An array of 1/4-20 and M6 topped holes provided. <125 urad deviation. Supplied with the SM-13 vernier micrometer actuator with 1/2" travel and 0.001mm resolution. Max. stage travel: 1". Max load 125lbs. Size: 3.5" x 6"L **NEWPORT PRICE, \$600, Our Price...\$349ea.**

NEW, SONY, CCM-PCS COMMUNICATIONS CAMERA HIGHLY RATED, TELECONFERENCING CAMERA

Originally sold for \$400! Now available for a fraction of that price. Great looking styling (doesn't look like a toy camera!) Very stable, adjustable tilting base, front panel LED pwr. indicator and sensitive built in electret mic, combine to provide excellent audio and video performance from one compact package. Designed to fit unobtrusively on top of your monitor. Adj. focus 6mm lens. (1" to infinity, macro capable) Auto power off when the privacy shutter is closed. Powered by 7-13VDC. (adapter included) RCA out for video & audio. 1/3" CCD, 330Lines res. 35% better than standard VHS! Size mm: 119 W x 95 D x 60 H. Sony quality. **SPECIAL CCM-PCS...\$99ea. or 2 for \$169**



SCIENTIFIC, 1/2" COLOR CCD CAMERA

All parameters adjustable from outside camera! Perfect for microscopy, inspection, capture or surveillance. Features internal or external sync, Interlaced or N/I, Adj. shutter, 1/60 to 1/10000 Sec., Auto White balance with three steps, Auto iris output, C or CS mount, Manual/auto gain or ext. variable gain. BNC video out, 12V@250mA pwr., via std. barrel jack. The GM470-C has it all! Aluminum housing. Size: 50mm W x 50mm H x 145mm L. New, **GM470C, less lens...\$499ea.**

SEE in TOTAL DARKNESS! WEATHERPROOF IR FLOOD,

48 powerful LED's project a 40 deg. FOV beam up to 45 feet. Automatic on at dusk off at dawn! 110VAC power. Rugged anodized aluminum, housing with adjustable mtg. bracket! Size: 4"x5"x6.3" Commercially made. Brand New! **WPIR...\$179ea.**



CHECK THIS! ULTRA MINI and WEATHERPROOF

Our "LIPSTICK" camera sets new standards. Sleek black anodized, aluminum, housing is O-Ring sealed & RAINPROOF. Adjustable tilting mount included. Specs: 1/3" CCD, 380 Lines resolution, 0.3 Lux sensitivity, AGC, Auto Shutter. Operates on 9 to 12VDC @100mA, 3.7mm, 90° FOV lens. A real glass lens. NTSC video out. 1/2 once! SENSITIVE to IR. Ultra small Size only: 23mm diam. X 50mm long. With 36" cable with BNC video and DC barrel jack. **GM-200KSTD...\$119 pwr. adapter...\$4.95**

"EMBEDDABLE", PINHOLE LENS, "BULLET CAM" it's INCREDIBLE! So tiny you can install it right into a door with merely an 0.9" diameter hole. Sleek black anodized, extruded aluminum housing. Similar construction as the lipstick camera above only smaller! 1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Power from 9 to 16VDC @100mA, 250k PIXELS, 90° FOV Pinhole lens. A real glass lens. Std. NTSC video out. 1/2 once! SENSITIVE to IR. Size only 23mm Diam. x 35mm long. With 36" leads. Think of the places you could put this little jewel. **GM-200KPH lens...\$119**

WORLDS SMALLEST ... 100mW ... VIDEO TRANSMITTER, Incidentally only

0.98" x 0.8" x 0.037" in size. Transmits crystal controlled hi-res. Images with 100mW output! The transmitter you've been waiting for. **Shown actual size.** Much smaller than the 9V battery which powers it. Draws only 35mA! Factory tuned ready to receive on cable channel 59. Will work with color & B&W cameras. UHF Bow tie antenna with balun and 3' F cable for TV Included. Perfect with our GM1000A cameras. Both will fit in a cigarette pack...with the battery! The best deal anywhere. **TVX-100.\$189. with GM1000A-PH CAM...\$259.**



YOU CAN NEVER BE TOO THIN

or TOO POWERFUL. Unique "ThinLine Energy Cell from Portable Energy Products. Their model PLA02V50. A super thin, high performance, patented technology, sealed lead acid battery. Each cell provides 2V@5AH. Their size is an amazing 3.1" x 5.3" x 0.3" thick! They can be mounted in any orientation. Can line the bottom of a briefcase or be covertly worn on the body. 30% higher energy density than conventional lead acid batteries. **Price 6 cells for \$15 or 24 for \$49**

MOTORIZED ZOOM LENS SPECIAL, 6X mag. and auto iris!

New, fabulous hi-res. optics with std. C-Mount. Superior Fujinon and Vicon lenses. Normally cost from \$600 to \$1500. There is no substitute for a good lens! All drive motors will operate from 6-12VDC. The Auto iris has a built in amp which works with any cameras video output for control. **Type B-6, 12.5 to 75mm, 6X, f1.2 \$189 or 2 for \$349**
ZOOM LENS CONTROLLER, NEW \$169



6V@12AH SEALED, RECHARGEABLE, LEAD ACID BATTERY

Brand new Panasonic type LCR6V12PI, tough to get at a discount. Very compact. Use two for a 12V@12AH pack. Two top mounted 1/4" faston connectors. Perfect for robotics and other high drain applications. Size: 5.9"L x 3.7"H x 1.97"D **2 for \$20, or 10 for \$89**

TEKTRONIX 2465A-DM, 4 Chan., 300MHz, O'Scope, on screen waveform stats & DMM READOUT

One of the most popular & powerful scopes available at a reasonable cost. Features: 500ps/Div sweep, 2mV/Div. vertical sensitivity, 1Mohm / 50-ohm input, 500MHz trigger bandwidth, four channels. On-screen waveform cursors provide vert. & horiz. scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. Plus complete DMM! Complete with 2 probes, pouch, cover and manual. Mint condition. 90 day warranty. **\$2695.**

WEATHER RESISTANT Camera Enclosure

Solid, extruded aircraft aluminum. Glass window. Strain reliefs for cables. Size: 3.5"w x 3.7"h x 14"L

Special Price...\$59ea.
with 110VHEATER...\$69ea.



RESOURCES UN-LTD.

300 BEDFORD STREET, MANCHESTER, NH 03101

VISA, MC, AMEX, DISCOVER, COD. ORDER: 800-810-4070 TECH. 603-668-2499 ORDER FAX: 603-644-7825 E-MAIL unltd4u@tiac.net

by Joseph J. Carr

Open Channel

Lightning Observing

Lightning is a familiar and often feared natural phenomenon. Although lightning is seen in all areas of the country, southern Arizona and central Florida are areas of extremely high flash density (i.e., the number of cloud-to-ground strikes per square mile per year). When lightning strikes, property can be damaged, fires started, trees can be split in two (or, oddly, the bark can come off leaving the tree core intact), and, sadly, sometimes people are killed. It's not surprising that the electrical power industry is a leader in lightning research because of the damage done to their power lines by lightning.

Human casualties are common. The daughter of a former governor of Virginia was struck at the National Guard Camp at Pendleton (Virginia) beach in southeast Virginia. Florida saw 298 confirmed lightning deaths in the 30-year period 1959 to 1989. Between 1940 and 1989, there were 8,103 confirmed lightning deaths in the United States (SIRS 1990, Earth Science, Article 67). According to the National Oceanic and Atmospheric Administration (NOAA), lightning killed 88 people in 1995.

About 30 percent of the people struck each year are killed. I would have guessed that nearly all of them would have been killed, with only a few survivors. But the statistics apparently suggest otherwise. Those people who are killed usually succumb to cardiac arrest. The survivors frequently suffer serious heart problems thereafter, and most have to be treated for severe burns. One source claimed that there are cases on record where lightning did not even break the skin, but traveled the wet surface of their body to ground. The skin was said to be severely burned, after the manner of scalding.

It is estimated that the earth is struck by lightning 20 million times per year. And if you believe the old myth about "lightning never strikes the same place twice," then consider the fact that the Empire State Building in New York City takes about 12 strikes per year. Radio and television antenna towers are also

struck frequently, although I hasten to add that they do not "attract" lightning that would not have come anyway (they tend to act as lightning rods).

The lightning is generated under up to 15,000,000 volts of electrical potential. According to one source, there is normally an atmospheric potential cloud-to-ground of 200,000 to 500,000 volts, and a constant but miniscule current of 10^{-12} amperes. The temperature inside the lightning bolt is 15,000 to 60,000 degrees Centigrade, which is several times the temperature on the sun. The lightning bolt travels at speeds up to 100,000,000 feet per second. A lightning bolt is actually a series of strokes, averaging about four. Durations vary from a few nanoseconds upward, but about 30 microseconds (30 μ s) is said to be average. The average peak power per stroke is 10^{12} watts.

Many people struck by lightning were in unsafe situations. For example, on an open beach or in an open field such as a golf course. It is also not smart to be in a boat on the water. Standing next to a tree or other tall object (e.g., radio tower) is also rather dangerous, as the lightning may easily be attracted to that tree. In one case, a group of golfers in Massachusetts were struck when lightning struck a nearby tree, then traveled underground to a covered pavilion where they had taken refuge from the storm. Carrying an umbrella with a metal tip above the canopy has caused lightning injuries, presumably because it looks to the lightning like a lightning rod ... and you look like a ground wire!

As a general (but not absolute) rule, as long as you can hear thunder, the danger of strike is small. Lightning travels at the speed of light (3×10^8 meters/second), while sound travels at 331.3 meters per second at 0°C (sound velocity changes a bit with air temperature), or 1,087 feet per second. As a result, the flash of light arrives instantaneously, while the sound of thunder arrives a short time later (measured in seconds).

A "rule of thumb" is to count the seconds between the flash and thunder clap, and then divide by five, to find the number of miles to the lightning bolt. One reason why I doubt validity of the "can hear thunder" advice is that I've been under thunderstorms where the lightning flash and thunder were very

nearly simultaneous, indicating it was right overhead.

More precise measurements of distance can be done using a good stopwatch to measure the time of arrival of the thunderclap. From that data, you can calculate the distance from $D = VT$, where D is the distance and V is the velocity (if you use m/s for T , then D is in meters, but if ft/s is used, T is in feet). You can further refine your measurements by consulting a table of sound velocity related to temperature and atmospheric pressures.

Some Lightning Detection History

Before we talk about early lightning research, let me hasten to add a caution: **DON'T EVEN THINK ABOUT DOING THESE EXPERIMENTS YOURSELF!** People who've tried to duplicate these experiments have been killed in the attempt.

Electrical phenomenon was researched starting in the early eighteenth century. It was noticed that certain substances, when rubbed, produced static electricity arcs. It was also found that a type of capacitor called a Leyden Jar could store an electrical charge. It was believed — correctly, of course — that these sparks looked enough like lightning to suggest a connection.

In May 1752, Thomas Francois D'Alibard in France performed an experiment that Benjamin Franklin had failed at the year before. The experimenter stood on an electrical stand, holding an iron rod in one hand. The idea was to produce an electrical arc between that rod and another rod in the other hand connected to a grounded iron wire. In an attempt to repeat the experiment in July 1753, Swedish physicist G.W. Richmann, working in Russia, was killed by the lightning.

Benjamin Franklin conducted his famous kite experiment in 1752. He used a rain-damped kite string connected to a key at the bottom. The lightning traveled down the string, and jumped from the key to a dry silk ribbon tied to Franklin's knuckles, and then through his grounded body. Others who attempted this experiment were killed. It's interesting to wonder what the American republic would look like if Franklin, having been killed in 1752, was not alive to provide wisdom to the Constitutional Convention (his compromise suggestion, which reconciled the "large states vs. small states" controversy, is supposedly how we got the bicameral Congress).

When photography and spectroscopy were invented in the nineteenth century, additional facts were learned about lightning. Time-resolved photography was used to count the number of strokes per lightning strike. Current measurements were made by Pockels in Germany during 1897-1900. He analyzed the magnetic fields induced by the lightning currents to estimate the current level from basic electrical fundamentals. C.T.R. Wilson (ca. 1920s), who also invented the cloud chamber, used electric field measurements to study lightning. Wilson hypothesized that the electrical fields cause such great ionization, that it's

JFETS

ULTRA LOW NOISE

LS843 - 3nV/Hz typ

TIGHT MATCHING

LS843 - 1 mV max

- ◇ N & P Channel
- ◇ Duals & Singles
- ◇ Custom Screening
- ◇ Die, SMT, Thru-Hole
- ◇ No Order Minimum
- ◇ COD's Accepted

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court
Fremont, CA 94538
510-490-9160/510-353-0261(Fax)
E-mail: 3629671@MCI.COM

Write in 59 on Reader Service Card.



The RF Connection
213 North Frederick Ave.
Suite 11N
Gaithersburg, MD USA
20877

<http://www.thefc.com/>

Complete Selection of MIL-Spec Coax, RF Connectors and Relays

UG-21B/U N Male for RG-213/214.....\$5.00
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90

UG-176/U Reducer RG-59/8X .25 or 5/\$1.00

UG-175/U Reducer RG-58/58A .25 or 5/\$1.00

Silver Teflon PL-259/Gold Pin.....

.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with

High Density PE Foam dielectric, stranded

center cond. and Duobond III Jacket.....

.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket

Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50

8 Pin Mike Male Panel.....\$2.50

13 Pin DIN for Kenwood.....\$2.75

8 Pin DIN for Icom.....\$1.00

8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666

Info 301/840-5477

FAX 301/869-3680

Write in 60 on Reader Service Card. 15

Most Common Activities Leading to Lightning Strikes on Humans

(derived from NASA web site)

<http://www.thunder.msfc.nasa.gov/primer.html>

1. Working, playing, or walking in open fields.
2. Boating, fishing, swimming.
3. Working on heavy farm or road construction equipment.
4. Playing golf (!!!).
5. Talking on the telephone.
6. Using electrical appliances.

IndustroLogic™

Fast, friendly project development!



SBC-1 80C51
Single Board
Computer
\$179

Menu based monitor and BASIC in ROM. 50 I/O, A/D, RTC, serial, I/O rack interface, up&download to EEPROM. Includes software.



SMD-12 Stored
Message Display
\$179

Display & enter messages with switch closure or serial port. 12 messages of up 32 characters. 6"W x 3"H x 6"D Steel case.



SIO-1000 RS-232
Data Acquisition
Interface Board
\$179

8 TTL in, 8 TTL out, dual 12 bit A/D & D/A channels. counter in, frequency out, WINDOWS/DOS software, cable, case & supply. 4.25" x 6.5" x 1.5" high. 12 oz.

Industrologic, Inc.
3201 Highgate Lane
St. Charles, MO 63301

(314) 707- 8818
9AM-5PM Central

Full technical info on the Web!

www.industrologic.com

Write in 62 on Reader Service Card.

WE ARE LOOKING FOR NEW DISTRIBUTORS FOR NUTS & VOLTS MAGAZINE.

If you are interested in selling Nuts & Volts in your store or on your newsstand, we have a great deal for you!

FOR COMPLETE INFORMATION, ASK FOR OUR NEW DISTRIBUTOR FLYER.

Nuts & Volts Magazine

430 Princeland Court
Corona, CA 91719
phone 909-371-8497
fax 909-371-3052
E-Mail
distributors@nutsvolts.com

possible for discharges to occur between the clouds and the upper atmosphere. Seeming confirmation of the 1925 theory was provided on April 28, 1990 when Shuttle mission STS-32 videotaped a single luminous discharge in the stratosphere.

Modern lightning research still measures electrical and magnetic fields, but adds other techniques to their armamentarium. Cameras with electrically-triggered shutters can be used with photosensors to make photographs of lightning strikes. High-speed movie cameras are also used, although the invention of charge coupled device (CCD) sensors (which are used in video cameras) has allowed a number of new instruments to emerge.

Other researchers rely on radiowaves, especially the whistlers, spherics, and broadband RF noise generated in the ELF/VLF/LF portions of the radio spectrum. This type of research is also easily conducted by amateur scientists.

At a site in Florida, researchers fire three-foot high solid fuel rockets into thunderclouds. The rocket trails a grounded wire that conducts the stroke to earth (**AMATEUR ROCKETEERS: DON'T DO THIS!**). The Space Shuttle and satellites are also being used for lightning research. Some hauntingly beautiful video clips of space shuttle lightning are available from NASA web sites. High altitude aircraft lightning research revealed newly discovered phenomenon called sprites and jets.

Types of Lightning

Cloud-to-ground lightning passes from a cloud overhead to the earth beneath. Most cloud-to-ground strikes occur in the higher latitudes, although recent research indicates a more important variable is cloud top height. Cloud-to-ground lightning is what causes injury and damages. Cloud-to-cloud or "inter-cloud" lightning passes from one cloud to another. Intra-cloud lightning appears within a single cloud. The "jagged" lightning that we see so often is called chain lightning, while sheet lightning is a generalized bright flash.


Other types of lightning may or may not be little more than myths, poor observations (e.g., optical illusions), variations on other types, or real, depending on who you consult. These include ball lightning, tubular lightning, bead lightning, silent lightning, cloud-to-air lightning (as opposed to cloud-to-cloud), and heat lightning.

Storm Scope


Lightning research can be terribly dangerous, especially if it puts you out in the open or if you are foolish enough to mimic professional methods such as ground wire tethered rockets. There are, however, some instruments that are easily built and relatively safe to use. The storm scope is one such instrument.

Figure 1 shows the basic configuration. This project was originally published by Thomas P. Leary in the June 1964 QST magazine (although his implementation used vacuum

Open Channel

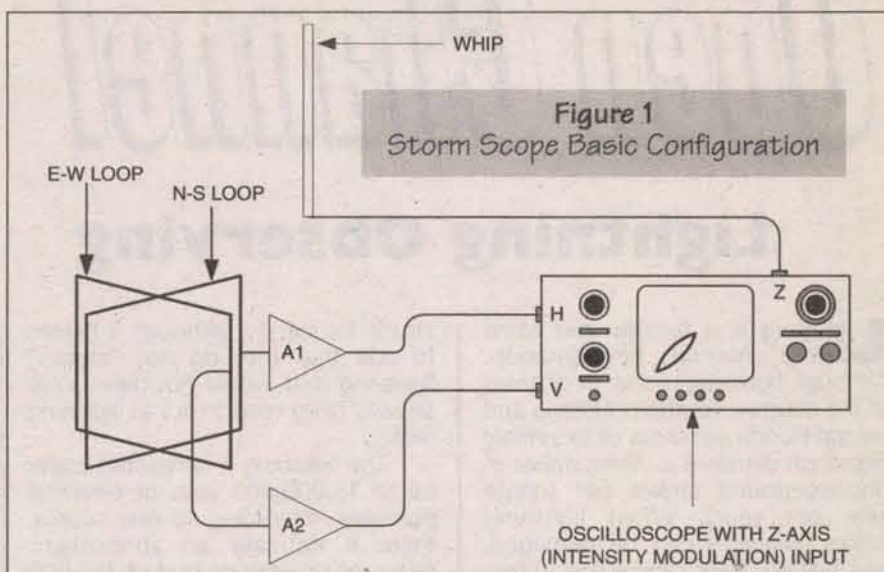

tube amplifiers). The storm scope consists of a pair of orthogonal small loop antennas; one oriented North-South (N-S loop) and the other East-West (E-W loop). Keep in mind that a small loop antenna (e.g., < 0.18λ wire length) shows a figure-8 pattern with nulls broadside to the loop plane, and maxima off the ends. Align the ends of the loop (maximum sensitivity direction) in E-W and N-S directions. A compass will make the accuracy better.

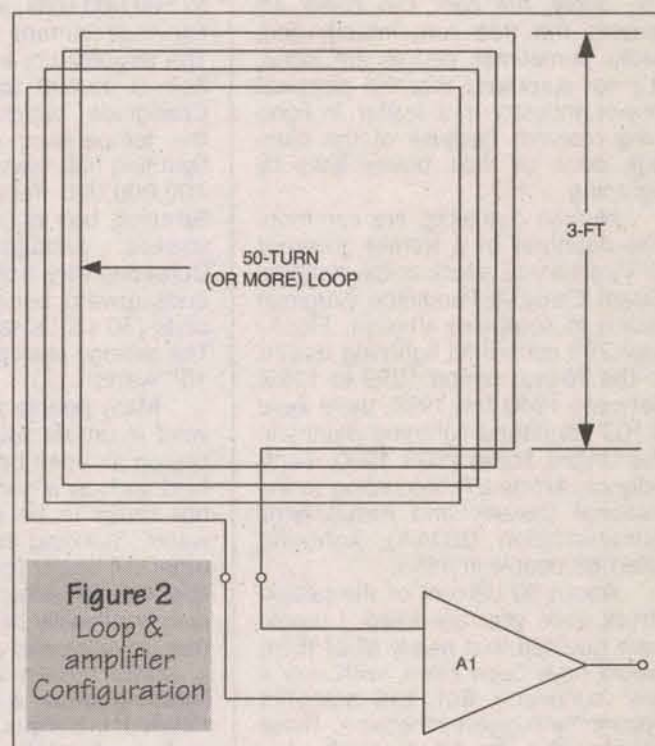


The loops are fed through differential amplifiers, with gains in the 20 to 80 dB range, to the vertical and horizontal plates of the oscilloscope. The reason for the wide gain scale is that oscilloscopes vary. The original project connected the amplifier outputs directly to the oscilloscope deflection plates. Modern two-channel oscilloscopes can be used in the X-Y to form a vectorscope, of which the storm scope is a variation on the theme.

Although any two-channel 'scope with an X-Y mode is usable, a directional ambiguity exists unless the 'scope also has a Z-axis (a.k.a., intensity modulation) input. This input is often present, but hidden on the rear panel of the 'scope. The Z-axis is used to intensity-modulate the screen with a signal from a sense whip or vertical antenna near the two-X loop. It may be necessary to amplify the Z-axis input signal, but in that case a single-ended rather than

differential amplifier is used.

Figure 2 shows the loop and amplifier configuration. The loop consists of at least 50 turns (50-t.) of small gauge insulated wire in a three-foot (3-ft.) loop. Either square or circular loops can be used, although it appears to me that the square is more easily constructed. The loop is untuned. The output of the loop is applied to the input terminals of the differential or push-pull amplifier.

It is critical to shield the loops. Wrap either copper foil or aluminum foil (or tape) over the entire loop, except for a small quarter inch or so gap along the top edge (this prevents the shield from acting like a single-turn shorted loop itself). The shielded loop will be less prone to pattern distortions from capacitive coupling. In addition, it responds largely to the magnetic component of the lightning electromagnetic field. It is less sensitive to electrical fields, so will not pick up as much locally-generated

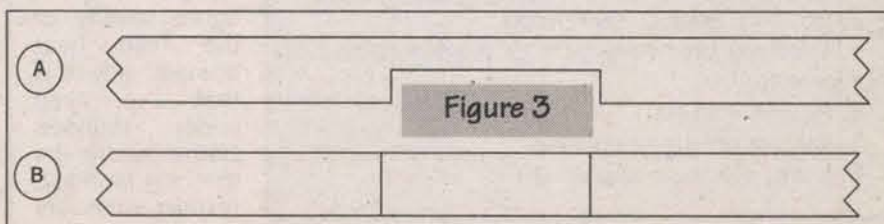

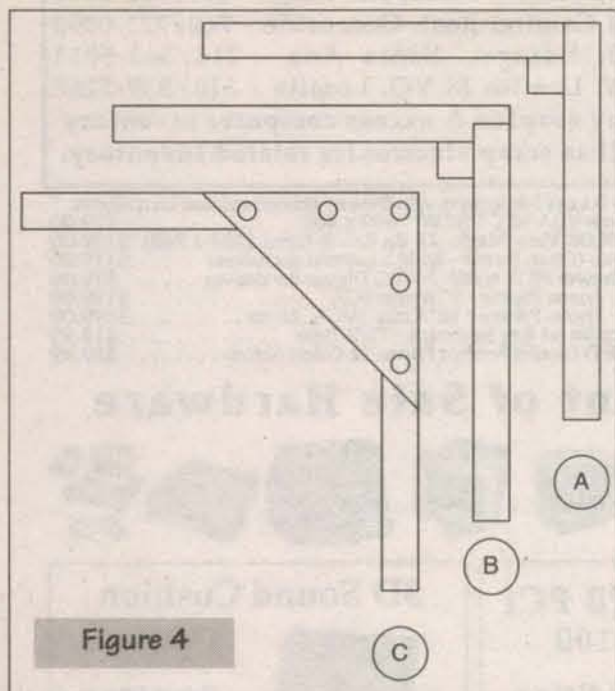


Figure 4

power line and appliance noise.

I constructed a loop pair using 0.75" x 4" x 36" lumber. Although my own woodworking skills leave something to be desired (polite for "atrocious"), others are able to make a better job of the method shown in Figure 3. A notch (Figure 3A) is cut at the center of the top and bottom members of each loop. The depth of the notch is the thickness of the lumber, while the width is sufficient to snug-fit the other piece of wood in it (Figure 3B).

The square loop will tend to

"trapezoid" out of shape

if left to its own devices. As a result, some or all of the methods of Figure 4 are used at the four corners of each loop. In Figure 4A, the wood elements are butted together, glued, and nailed (or screw fastened). A small block, about 0.5 inch square and as wide as the loop arm, is glued in the corner to give strength. In Figure 4B, the same method is used, but the joint between the wood members is a bit different. I am told this method is stronger, even though

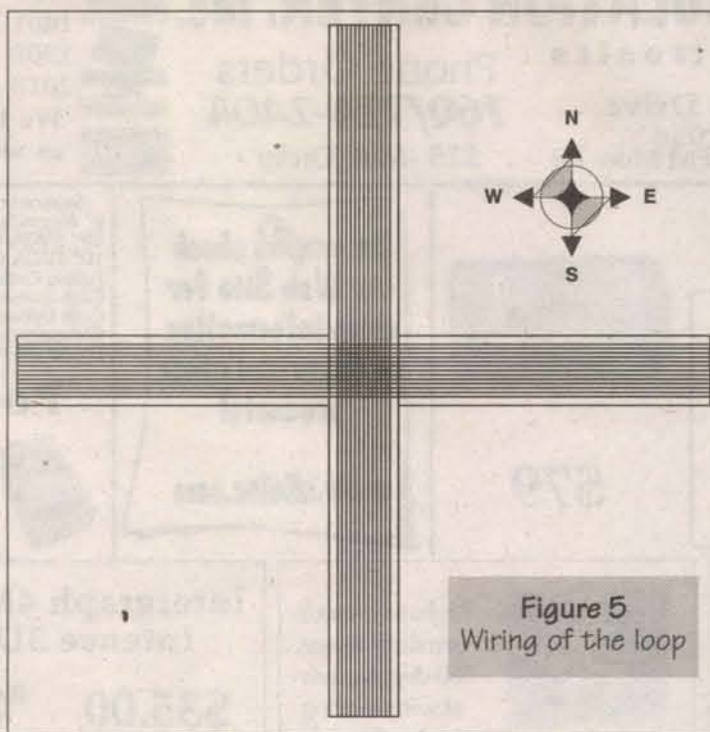


Figure 5
Wiring of the loop

it is more difficult. Finally, a triangular gusset plate cut from a thin sheet of plywood or spruce modeling lumber is shown in Figure 4C.

Figure 5 shows the wiring of the loop. I used 50 conductor ribbon cable, although one continuous loop of #26 (or so) enameled wire could be used as well (it takes more than 600 feet of wire per loop for this approach!). You can also use 60 or 64 conductor cable. The sensitivity of the loop is improved with more turns

or a larger length per side. You can, for example, build a four-foot or five-foot loop, or use multiple runs of 50 conductor ribbon cable. In one case, a whistler/spheric hunter used 126 conductors made from intercom cable.

If you opt for the simpler ribbon cable method, then cross connect adjacent turns so that one continuous loop is formed. This is a tedious chore, but it's made a lot easier if you use printed circuit perf-board (or some of the project boards from RadioShack) to make the connections. It is okay to lay the N-S and E-W loops over one another because their orthogonal geometry makes them minimally interactive.

Results to Expect

The original article claimed detection to distances of 500 miles, but I doubt that figure is practical. I would more likely guess tens of miles, or 100 miles, but further experimentation is needed to confirm the longer distance claim. Figure 6 shows typical patterns. These patterns are representations of what is observed, but are a bit more distinct and less ragged than actual 'scope photos (I am no longer able to photograph 'scope screens ... until I find a new hand-held Polaroid 'scope camera). I was able to create the patterns in Figures 6A and 6B, but those of Figures 6C and 6D are cribbed from the Leary article cited earlier.

The pattern in Figure 6A is what to expect when there is no Z-axis input to receive the vertical sense antenna signal. It shows the line of the storm, but has the directional ambiguity found on loop antennas. In other words, the storm could be in either direction from the loop. Figure 6B shows the pattern to expect when the sense antenna is used, and the Z-axis intensity is correctly adjusted. This is essentially the same concept as a sense antenna producing a cardioid pattern on a radio direction finding (RDF) antenna. The actual pattern will be a lot more ragged than shown here.

Leary claims that patterns like Figure 6C are produced with horizontally polarized cloud-to-cloud discharges (the others were essentially groundwave signals). The pattern in Figure 6D represents what might be seen when a groundwave and cloud-to-cloud pattern co-exist. I was not able to confirm these patterns, but that might be the particular thunderstorm I observed several years ago when I was active in building loops while researching a forthcoming book (Joe Carr's *Loop Antenna Handbook*, Universal Radio Research, Reynoldsburg, OH). NV

A - Figure 6 - B

C - Figure 6 - D

Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJJ@AOL.COM.

COMPUTER CIRCULATION CENTER, Inc.

dba: Alltech Electronics

2618 Temple Heights Drive.
Oceanside, CA 92056
Phone Order Hours 9AM - 5:30PM Mon-Fri

Phone Orders
760/724-2404
\$25 -Min. Order -

9350 Clairemont Mesa, San Diego - 619/573-0411
1401 El Camino Real, Oceanside - 760/721-0093
1300 E. Edinger, Santa Ana - 714/543-5011
2018 W. Lomita BLVD, Lomita - 310/539-2260
We buy surplus & excess computer inventory
as well as scrap electronics related inventory.

Mitsubishi DJ-1000 Digital Camera

Pocket Size

Holds up to 15 images
320 x 240 or 504 x 378
PCMCIA Required for image
downloading.
Windows 3.1/95 Compatible
See the web for more details




\$79

Be sure to check
our Web Site for
more information
on these and other
products!

www.allelec.com

Save on your Point of Sale systems with these refurbished and new components.
9" Monochrome VGA NEC **NEW** 640 x 480 \$79.00
10" SVGA COLOR View Magic .26 dp Refurb (upto 1024 x 768) \$139.00
10" SVGA Color (Open Frame - Build a custom enclosure) \$119.00
Fujitsu Cash Drawer NEW w/till. 24VDC Trigger for drawer \$79.00
Cash Drawer - Epson Printer - 9" Mono VGA \$199.00
Cash Drawer - Epson Printer - 10" Color SVGA .26 dp \$299.00
Compact footprint 83 Key keyboard - PS/2 Type \$14.95
Epson TM300PD Parallel Receipt Printer (2 Color) Refurb \$89.99

Point of Sale Hardware

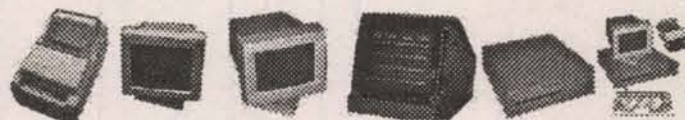

NEC Mini 486



Need a Linux Box?

\$29.00

Mini footprint
3.5" x 11.5 x 13
486 SX 25 CPU
4MB On board
2 ISA Slots
IDE, FD, 2
COM, 1 LPT &
512K VGA
UPGRADABLE
to DX2/66



8 for \$20

1.75" Dia. Lt Wt Wheel

Light to It-medium
duty usage.
360 degree swivel
with locking
brake. Smooth
rolling action.

Intergraph 4MB PCI Intense 3D 100

\$35.00

Rendition
V1000e




3D Accelerated
Video Card for
Windows 95/NT
See Web for
more details

3D Sound Cushion



\$39.95

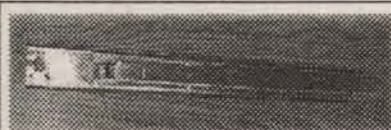Bring Life to
your games
and music
experience.
See the web for
more info.



6 pair for
\$29.00

Extends to 2'
past. Two slide
telescopic
extension

Ball Bearing Drawer Slide

10" Color SVGA!

Up to 1024 x
768 pixels
110V AC
operation.

Refurb:
\$139.00

ViewMagic



\$9.95

Small DC Motor
w/gear box & Wheel

Robotic
Attachments?
Arms, etc?
With rubber o-
ring on 5" dia.
disc.

External SCSI Cases \$29.00 & Up



5.25" Closed HH \$29.
5.25" Open HH \$35.
5.25" Open FH \$45.
3.5" Open for Zip,
Syquest, etc \$29.
3.5" Lunchbox \$19.
All cases have two 50
pin centronics
connectors.

Small 105V 40 RPM Motor. 2.7W

\$9.95



Motor with spin-
dle. Items can be
press fit. Shaft
has a through
hole with a rod
stuck in it.

Motorola Flip Phone Data Adapter



\$39.00

RJ-11 (Dial Tone)
Generator and Ring
Generator. Use any
standard land line
device with your cell
phone. Modem, credit
card terminal,
answering machine...

Large AC Motor.
Use for robotic
drive or ??
Has 5" disc
attached with a
rubber O-Ring.

\$9.95



Reversible 110V AC
Motor with brake



\$69.00
24 pcs

Used 3" Dia. Wheels

360 degree
rotatable. Ball
Bearing for
durability.
These were
from heavy
duty mobile
storage units

CPUs


486SX 25/33\$3.00\$5.00
486SX2-66\$5.00\$8.00
486DX25/33\$5.00\$8.00
486DX2-50/2-66\$14.00\$19.00
486DX4-100\$39.00\$49.00
Pentium 75/90\$39.00\$49.00
Pentium 100 / 133\$59.00\$69.00
Pentium 166\$79.00\$99.00

Upgrade
Your
System



EPROMs

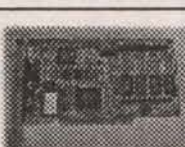2716 /2732\$1.25
2764 /27128\$1.25
27256 /27512\$1.50
1Meg\$2.50
2 Meg\$2.50



\$39.00

Macintosh 2MB PCI
ATI Mach64 Video Card

Supports both
Macintosh and
SVGA Monitors.
Upgradable to
4MB

IDE Hard Drives

420 Meg\$49.00
320 Meg\$39.00
270 Meg\$29.00
120 Meg\$20.00
80 Meg\$15.00
40 Meg\$10.00



PC Oldies but Goodies

EGA/CGA Card -or- ISA Super I/O\$14.95
2 Meg AT Memory Card - or - Parallel/Mono Card\$9.00
Floppy Controller -or- Serial / Parallel Card\$6.95
VLB 1 Meg VGA Card - or - 386 Motherboard w/2 Meg\$19.95
16 Bit (ISA) VGA w 256/512/1 Meg\$9.00 / \$12.00 / \$14.95
VLB Super I/O\$12.95
8 Bit VGA Card - or - XT Motherboard w/640K\$9.95

See Our Website for
for more details on these
industrial surplus items.

Robot Competition? Feeling
creative? Build something!

CD ROM & Sound Cards

4x IDE Internal\$19.00
8x IDE Internal\$29.00
24x IDE Internal with Yamaha Sound Card (ISA)\$49.00
4x SCSI Internal\$25.00
4x SCSI External\$49.00
Universal Audio Cable (CD ROM to Soundcard)\$4.95

[HTTP://WWW.ALLELEC.COM](http://www.allelec.com)

VISIT OUR WEB PAGE DAILY FOR SPECIALS & MORE INFO. ON THESE ITEMS

Help! I'm Lost!

Being lost is frustrating. It happens to most of us; lost in the country, driving for miles through endless grids of farmland, or lost in an unfamiliar big city, wandering through

address. Figure 2 illustrates the basic software components and their interaction in a typical system.

Vehicle Positioning

Data comes in from various

correlation to a set of map coordinates.

There are several common vehicle speed and direction sensors used for position calculation. The most common of these are gyroscopes, wheel speed sensors, odometer

This article explains the inner workings of automotive navigation systems.

varies fairly dramatically with temperature. This drift translates directly into positioning error produced by the vehicle positioning module, since the gyro is used primarily to determine vehicle direction. The gyro output, to be accurate, needs to be frequently calibrated. GPS data is used for correcting the accumulated dead reckoning error.

Just knowing when and how fast a vehicle is turning isn't enough to determine position. The vehicle positioning module needs to know the distance traveled over a period of time. That's where wheel pulse sensors and odometer pulses come in. Wheel pulses come from one or two wheels, and are usually the output of Hall-Effect switches. The incoming pulse rate is proportional to wheel speed, which is proportional to vehicle speed.

Wheel pulses can even be used

Automotive Navigation

deserted, and possibly dangerous, city blocks. All the time being low on gas. Being lost may soon become an unpleasant memory with the emerging availability of automotive navigation systems.

Automotive navigation systems require sophisticated hardware and software and are somewhat expensive, but I believe they'll be as common as air conditioning in the vehicles of the near future. This article examines and explains the major software components of a typical automotive navigation system.

Navigation System Components

There are six major components in a automotive navigation system. These components include a vehicle positioning module, a map matching module, a digital map database, a dynamic route guidance module, a static route planning module, and a user interface. These components are listed in more detail in Figure 1.

Automotive navigation systems do a lot of work when they're running. Global Positioning System (GPS) receivers intercept and condition GPS satellite signals, A/D converters digitize analog signals from gyroscopes or accelerometers, and buffers hold direct digital speed pulse data. On-board digital map databases and route guidance software prompt the driver to stay on course, and route planning engines calculate a route from a vehicle's starting position to a destination

vehicle motion sensors to a Vehicle Positioning module. Within the Vehicle Positioning module, software reads the conditioned signals, keeps track of time, and performs a form a navigation called dead reckoning. The output of the Vehicle Positioning module is the current position of the vehicle, along with the rate of speed and heading. In the simplest case, dead reckoning can be accomplished with a watch, a compass, and a known speed. Time, speed, and direction are recorded at periodic intervals. With a known speed, direction, and starting point, it's easy to determine the distance traveled and make a crude

pulse indicators, and GPS receivers. Gyroscopes, or turn rate sensors, are classed as inertial sensors, as are accelerometers. A quartz resonance gyro outputs a tiny voltage proportional to its input axis rotation. If a vehicle is making a sharp, fast turn, then the output is higher than when the vehicle is making a slow, widely arcing turn. Gyroscopes are great for dead reckoning, but have a few flaws.

The major problem with inexpensive quartz resonance gyros is temperature sensitivity. The output

to detect turns. If the vehicle is making a left turn, then a right wheel travels a greater distance than a left wheel. Wheel pulses vary with tire pressure and slippage which, in turn, create positioning errors. Odometer pulses generally come from an existing in-vehicle computer. There are typically a fixed number of pulses per mile or kilometer, so the distance traveled is simply a matter of counting pulses. Error is still accumulated with slippage, but not as severely as with wheel pulses.

by Jeff Stefan

Where It's At and Where It's Going

LASERS & ACCESSORIES

HELIUM NEON LASERS

- ✓ Complete Systems
- ✓ Plasma Tubes
- ✓ Power Supplies

ACCESSORIES

- ✓ Optics
- ✓ Electro-Optics
- ✓ IR Viewers
- ✓ Books & More



INEREDITH
INSTRUMENTS

Phone: 602-934-9387 • Fax: 602-934-9482

DIODE LASERS

- ✓ Visible / IR
- ✓ Complete Modules
- ✓ Collimating Optics
- ✓ Drive Circuits

FREE CATALOG

WEB SITE:
www.mi-lasers.com

SATELLITE TV – HACKERS 'BIBLE'!

The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

www.baylin.com
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$4 s/h to:
Baylin Publications, 1905 Mariposa, Boulder, CO 80302
MASTER, VISA & AMEX /COD orders accepted



576 pages, 6" x 8-1/2"

NEW!
5th Edition

Telephone: 303-449-4551
FAX: 303-939-8720

FREE CATALOG – Satellite TV books, videos and software

Navigation System Components

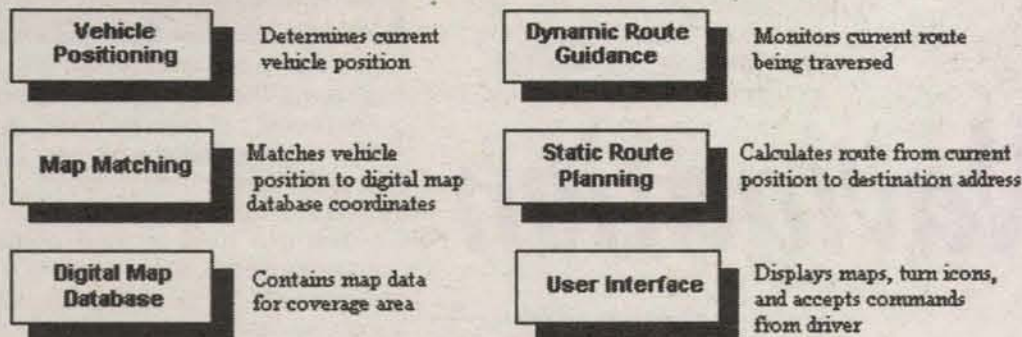


Figure 1

GPS has opened the door to highly accurate vehicle positioning systems, but GPS all by itself isn't really reliable for accurate, full time turn-by-turn navigation. There are two levels of positioning accuracy built into GPS, called SPS and PPS.

SPS stands for Standard Positioning Service and PPS stands for Precise Positioning Service. PPS is used primarily by the military, where SPS is used for civilian applications. Originally, SPS turned out to be very close to the positional accuracy of PPS, so to widen the performance gap, SA, or Selective Availability, was introduced. SA intentionally degrades the GPS positioning accuracy to 100 meters horizontally and 160 meters vertically.

This means that in a vehicle, there is an inherent 300 foot error in any GPS positional reading, and that makes map matching a lot tougher. GPS signals are also often blocked by trees and foliage. In a city with tall buildings, GPS may be blocked, or the signals may bounce

around the buildings then enter the receiver, giving erroneous position readings. This is called multipath error. As it stands now, for robust and consistent navigation, GPS is

the map matching module. Map matching consists of matching the position received by the positioning module to a road segment position from a digitized map database. The digitized map database contains road segment information, such as the latitude and longitude, the type of road, the shape of the road segment, and speed and direction

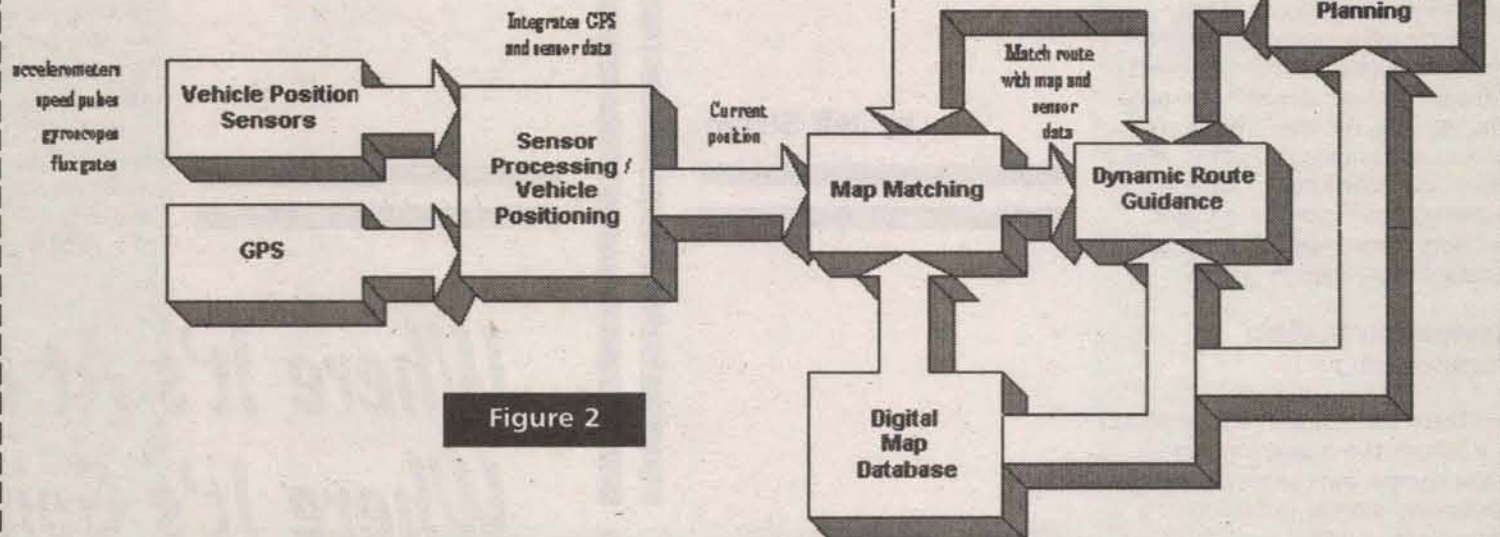


Figure 2

used as a calibration source for dead reckoning and is not the central source of vehicle position information.

Map Matching

The next major component is

attributes. An automotive navigation system is essentially worthless without a good digital map database. Map matching itself is a form of positioning. If the positioning module reports a position that is reasonably close to a road segment, then the position is corrected to the

Weeder Technologies

ON-LINE CATALOG

www.weedtech.com

Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

Voice/Fax 850-863-5723

Stackable RS-232 Kits

Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32**

Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49**

Home Automation (X-10) - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. **\$39**

Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ASCII character string. Example: *12/31 08:45 850-863-5723 Weeder, Terry <CR>. Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$35**

Touch-Tone Input - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. **\$34**

IR Remote Control Receiver

Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. **\$32**

Telephone Call Restrictors

Two modes of operation; either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.

Block out selected outgoing calls. Bypass at any time using your password. **\$35**

Block out selected incoming calls. Calls identified using Caller ID data. **\$48**

Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49**

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$55**

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS... get back to your **BASIC** Cable Needs

Call 1-800-577-8775

For information regarding all of your **BASIC** cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS [COMPATIBLE WITH ALL MAJOR BRANDS]
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

We handle **NEW** equipment ONLY - Don't trust last years **OBSOLETE** and **UNSOLD** stock!
COMPETITIVE PRICING - DEALERS WELCOME



**BASIC
ELECTRICAL
SUPPLY &
WAREHOUSING
CORPORATION**

P.O. BOX 8180 · BARTLETT, IL 60103-8180 · 847-584-2099

digital map position, and not to the position reported by the positioning module.

There are four "truths" regarding position, and only one of them is really true. The vehicle speed and direction sensors report one positional truth, GPS reports another, and the map matching module reports yet another. All of them are inaccurate to a certain degree with respect to where the vehicle is at any given moment, which is the real positional truth.

Route Guidance

The next module is Route Guidance. Route Guidance monitors the vehicle and map matched position and determines if the vehicle is correctly traversing a pre-planned route. It does this by checking whether the current road segment being traversed matches the current segment in the pre-calculated route. Figure 3 illustrates the output of a typical automotive navigation system map display. The triangle icon indicates the vehicle.

The actual reported position may not be exactly on the current road segment of Normandy Road, but it is close enough to snap the vehicle icon onto the road display. It's annoying to a driver to see the icon travel along a route next to the road, but not on the road. Many navigation systems allow the driver to manually adjust the icon.

The Route Guidance module's main responsibility is to present upcoming maneuver data to the User Interface. The next maneuver — such as a right turn or left turn — is presented to the User Interface at a threshold distance from the maneuver. If the maneuver is missed, then at another threshold distance, an error is announced. The driver then

has the option of canceling the route, or calculating a new route from the vehicle's current position.

Route Planning

The Route Planning module is

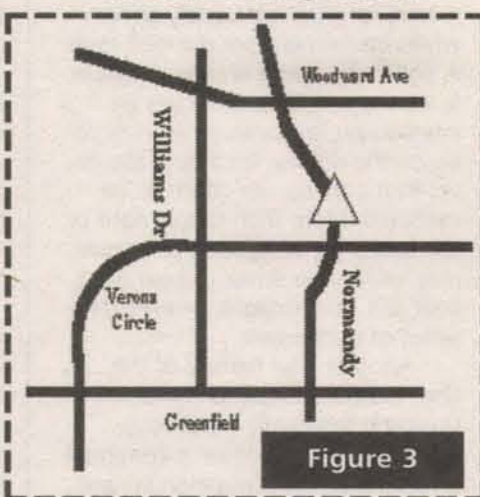


Figure 3

responsible for generating a list of road segments to traverse from the vehicle's current position to a destination. The driver enters a destination address using optional criteria, such as least use of freeways, shortest distance, or shortest time, among others. The Route Planning software links together the road segments into a list based on the driver's preferences and makes this list available to the Route Guidance module.

Route planning, which is essentially a search problem, has its roots in classical computer science and artificial intelligence. Roads and intersections can easily be modeled as graphs, which are commonly used in computer science.

Graph theory is used to illustrate and solve many computer science related problems, from network development to operating system deadlock detection. A typical graph

is shown in Figure 4. The nodes, or circles, are called vertices, and the lines that connect them are called edges. The words node and vertex are used interchangeably.

A method called Dijkstra's Algorithm systematically determines the least-cost path in any graph, given a source and destination node. It can reliably calculate the least-cost path from any node to any other node. It's not a giant leap to translate vertices to intersections and edges to roads.

Note that in Figure 4, the least-cost path from vertex A to vertex E is through the path A to B to D to E, and not from A to C to E. Geometry has nothing to do with it; everything is dependent on the cost value, or weight, assigned to the edges. In a

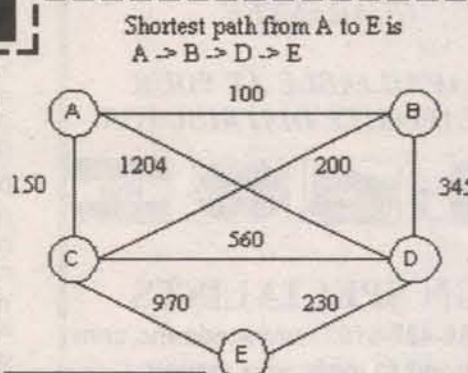


Figure 4

road network, the cost value can be based on speed limit, type of road, or some other criteria that would affect traveling down the road.

Dijkstra's Algorithm blindly and systematically searches for the least-cost path from any source node to any destination node. What

if the search could be sped up if additional information was known ahead of time? This is called a heuristic search, and falls within the domain of artificial intelligence. A heuristic — or rule-of-thumb — helps in making a decision. A simple example of a heuristic is deciding which checkout line to go to in a store. A short line at a checkout usually equates to getting through the line faster. This isn't necessarily true if someone in a short line has a lot of items to buy but, in general, a shorter line means a faster exit.

Heuristics are used with the best-first search algorithm. Best first searches revolve around searching nodes that are estimated to be close to the destination node. In the case of the checkout line, using the heuristic that a shorter line means a faster exit, we would scan all of the lines to determine which line was shorter.

We're looking for the shortest, least-cost distance to our goal, which is getting out of the store in the minimal amount of time. There's no guarantee that the decision will be correct, but it will be correct most of the time.


The heuristic applied to route planning estimates the distance

from a source node to a destination node. What best-first search really does is restrict the search space. Where Dijkstra's Algorithm is able to search a complete network, best-first search restricts the search to a single source and destination.

This translates into less processing time and returning a route to the driver much faster.



Figure 5



EPROM+

A device programming system for design, repair and field service

◆ EXCEPTIONAL POWER FOR THE PRO
◆ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F, 29C, 29EE, 29F)(32 MEG), NVRAMS (1220, X2210/12) 8 PIN SERIAL EEPROMS* (24, 25, 85, 93, 95, 80011A) PLUS ERI400/M58657* BIPOLAR PROMS* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS*(89S, 90S)(AVR) PIC MICROS* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

□ Includes step-by-step tutorial plus explanation of EPROM fundamentals

□ 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE

*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

\$289

\$5.00 SHIPPING - \$5.00 C.O.D.

VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150

(513) 831-9708 FAX (513) 831-7562

website - www.arlabs.com email - arlabs@worldnet.att.net MADE IN THE U.S.A.

5 Axis Robotic Arm Kit

\$195.00 Plus S&H



We make it easy!

You can build this Robotic Arm! Impressive, fast, accurate, and repeatable motion. Any computer capable of sending 2400 or 9600 baud serial data can control the arm, even a Basic Stamp. This arm makes a great foundation for AI and motion control experiments. Position the arm in an X, Y, Z, grid with a joystick or keyboard using the new RoboMotion for Windows. The kit includes the hardware, structural components, Hitec servos, pre-assembled SSC servo controller, DOS and Windows software, and an illustrated assembly manual. Camouflage paint not included.

We have many more cool robots, check out our web page or ask for our free catalog!

3 Axis Version \$155.00 • Mobile Version \$250.00 • Mobile Robots Book \$48.00




Lynxmotion, Inc.
104 Partridge Road
Pekin, IL 61554-1403 USA
<http://www.lynxmotion.com>




Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com

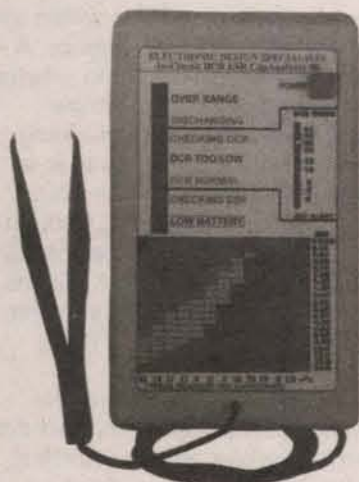CHECK CAPACITORS IN-CIRCUIT WITH 100% ACCURACY



CapAnalyzer 88 \$179

- Automatically discharges cap;
- Checks for low DCR and shorts;
- Checks high-frequency ESR and displays on 20-segment LED meter
- 3-color chart shows typical values.
- Includes gold-plated tweezer probe
- Portable... Batteries included!

LOCATE ANY SHORTED or LEAKY COMPONENT TO THE EXACT SPOT



LeakSeeker 82A \$179

Locates shorted & leaky parts to the exact spot on the PCB without cutting up the board or unsoldering any parts!

• 60 DAY SATISFACTION
OR MONEY BACK
GUARANTEE

• AVAILABLE AT YOUR
FAVORITE DISTRIBUTOR



ELECTRONIC DESIGN SPECIALISTS

4647 Appalachian St, Boca Raton, FL 33428 561-487-6103 www.eds-inc.com
we make test equipment designed to make you money.

Write in 76 on Reader Service Card.

Celebrating our 16th Year Of Service !!

COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

STOCK	1-9	10-24	25+
LSLENS Lens Assembly	24.99	23.74	21.37

DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK	1-9	10-24	25+
DT100K	24.99	23.74	21.37

ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK	1-9	10-24	25+
SB1102	1.99	1.89	1.70

EPROMS

STOCK	1-24	25-99	100+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.39	5.12	4.61
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	3.79	3.60	3.24
27C020-15	4.49	4.27	3.84
27C040-12	6.29	5.98	5.38
27C080-12	12.99	12.34	11.11

7400 SERIES I.C.'s

STOCK	1-24	25-99	100+
7400	.29	.28	.25
7402	.19	.18	.16
7404	.29	.28	.25
7406	.27	.26	.23
7407	.33	.31	.28
7408	.33	.31	.28
7410	.19	.18	.16
7411	.55	.52	.47
7414	.27	.26	.23
7420	.24	.23	.21
7432	.33	.31	.28
7447	.89	.85	.77
7473	.79	.75	.68
7474	.33	.31	.28

FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK	1-9	10-24	25+
K30	11.99	11.39	10.25

What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vises
- Resistors
- Capacitors
- Connectors
- Trimpots
- Kits
- Vises
- LED's
- Transistors
- And more!

GADGETEER'S GOLDMINE

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

• By Gordon McComb

STOCK	1-9	10-24	25+
TB3360	21.99	20.89	18.80

User Interface

Finally, the User Interface accepts commands and presents the navigation data to driver. Maps are displayed with a vehicle icon, as shown in Figure 3, and turn-by-turn maneuver icons are usually shown when traversing a pre-planned route. A right turn icon is shown in Figure 5. As the vehicle approaches an intersection, a maneuver icon pops up on the display, informing the driver that a maneuver needs to be executed. More than simply right or left turns, the navigation computer may inform the driver to bear right, bear left, stay straight, or execute a series of maneuvers.

Another vital feature of the User Interface is speech output. Driving is inherently hazardous, especially when a driver is continually looking at the navigation system and not at the road ahead. Speech output helps to minimize this potentially dangerous and litigious situation. In the simplest case, canned phrases are enunciated. Canned phrases do not recognize road names. To announce the maneuver in Figure 5, canned phrase software will say something like "right turn ahead." More sophisticated text-to-speech software will actually announce the road name. A text-to-speech module will actually say "turn right onto Woodward Avenue."

There are some inherent difficulties with text-to-speech. One major problem is storing the road name in the form that a text-to-speech module understands. It generally can't be simply the English spelling of the road name. Chances are the road name will be mispronounced. The road name needs to be stored as a phoneme.

A phoneme is not so much the way a name is spelled, but how it sounds. This adds more data to an already dense database. Pronunciation is also difficult, since road names are predominately proper nouns. Canned phrases simply involve comparing a key word, such as "right" or "left," and indexing into a ROM location to extract the phrase.

Driver input needs to be minimized so the driver isn't too distracted from keeping his or her eyes on the road. Speech recognition is ideal, but very expensive. Touch screens are good, as are a simple and intuitive button layout.

The Future of Intelligent Transportation Systems

What happens when an accident occurs somewhere on the route you're traveling? Even if you know about the accident, how do

you re-route around it? This is where real-time traffic information and server based navigation comes into play. Similar to an Internet service provider, a vehicle information service provider can monitor traffic and provide real-time traffic updates to the subscribers. If an accident occurs on your route, the service provider can alert your vehicle and download a new route, avoiding the obstacle or accident. Vehicles can even be used as traffic probes. A service provider can call your vehicle, determine its position, and compare the vehicle's speed to the speed on the road segment it's currently on.

If the road segment speed is supposed to be 65 mph, and the vehicle is only going 5 mph, then there is a possibility of traffic incident or construction. If many vehicles on the same road segment are stopped or moving slowly, then the probability of an incident is extremely high, and real-time traffic notifications can be broadcast to other vehicles. If your vehicle is involved in a traffic incident or simply breaks down, then the information service provider can provide emergency and breakdown services, ranging from calling an ambulance or tow truck. These features and services fall under the umbrella of Intelligent Transportation Systems, or ITS.

Think of the early days of aviation. You would pull an old plane out of the hanger, gas it up, check the wind direction, and look up to see if any other air traffic was around. If the sky was clear, you'd take off. No flight plan, very few instruments, and a compass and a map in your lap. There's a certain glamour and appeal to the unrestrained freedom that early aviation offered. That's the way driving is today, without a supporting information infrastructure, and essentially autonomous and unrestrained.

Traffic information systems of the future will offer important driver information, but at a cost. With the increased security and convenience comes a loss of autonomy. Opening a vehicle to allow two-way communications with the outside world opens the door to malevolent hacking. If an information service provider can remotely unlock your car doors, so can a hacker. Hacker proofing a vehicle requires data encryption technology which increases cost and complexity, and there are always back doors to everything.

The road to the future via ITS is bright, but there are a few technological potholes along the way. Being aware of the problems and benefits — both potential and real — can help designers and drivers develop and use reliable, practical, and safe intelligent transportation systems. **NV**



ROBOT ARM TRAINER KIT

The Robot Arm Trainer teaches the basic robotic sensing and locomotion principles while testing your motor skills as you build and control the arm. You can command this unit to grab, release, lift, lower, rotate wrist, and pivot sideways 350°. After assembly, observe the dynamic gear mechanisms through the transparent arm. Five motors and five joints allow for flexibility and fun! Power source: 4 "D" cells. Ages 10 and up. **BQ00107 \$74.95**

BIPOLAR STEPPER MOTOR DRIVER IC

600mA output current capability per channel. 1.2A peak output current (non-repetitive) per channel. Enable facility. Temperature protection. Logical "0" input voltage up to 1.5V (high noise immunity). Internal clamp diodes. With documentation. **L293D \$3.00 each**

L297 STEPPER MOTOR CONTROLLER IC

20-pin package. Normal/Wave drive. Half/full step modes/Clockwise/anticlockwise direction. Switch mode load current regulation. Programmable load current. Few external components. Reset and enable inputs, and home output. Full documentation on our website. **951004 \$7.90 each**

9 VDC 1.0 A WALLWART

Center positive coaxial connector. **96E009 \$5.95**

REMOVABLE HARD DRIVE

Syquest SO555 44MB removable SCSI cartridge hard drive. (Removed during upgrade) **97C024 \$9.95 each**

24VDC @ 25A LAMBDA SWITCHING POWER SUPPLY

24VDC @ 25A (up to 40°C). Input 187-250 VAC, 790W, 0.7pF (260-350 VDC). Size 4.5" x 5" x 13". Weight approx. 9.5 lb. **98E027 \$74.95**



OCTAL TUBE SOCKET

Porcelain. New old stock. MIL-Spec. Original sealed foil bags. **97J001 \$5.95**



INFRARED KIT

Includes part #97V012 (assembled transmitter unit with forty-seven buttons), detector unit, printed circuit board, detector amplifier IC, and all parts needed to detect the signal from the transmitter and convert it to a serial TTL signal. **93V010 \$19.95 each**

TWIST LOCK CONNECTOR

NEMA L5-20 size, for 125V @ 20A. **98J020 \$3.25 each**

HOLD-VAC® SURFACE MOUNT TOOL

This pen-style vacuum tool is delivered to you with four different size vacuum cups - ideal for handling and manipulating various surface mount components during assembly or repair operations. **HV-800 \$19.95 each**



DUAL FULL-BRIDGE DRIVER IC

Up to 46V operating supply voltage. Total DC current up to 4A. Low saturation voltage. Overtemperature protection. Logical "0" input voltage up to 1.5V (high noise immunity). Multiwatt-15 package. Docs are available at our website. **L298 \$9.95 each**

MINI HI-VOLTAGE POWER SUPPLY

+24 VDC in, -6.3KV @ 0.5 mA out. Use for lasers, photo-multiplier tubes, ion generators, cattle prods, electrostatic air filters, etc. Yamata P/N HVH-C204L-1, with docs. **94E003 \$9.95 each**

50-LB. CARE PACKAGE

Surplus goodies from Silicon Valley. This is not junk, just material we've acquired in quantities too small to catalog - electronic and mechanical subassemblies for everything from robots to rockets. Assortments may include ICs, caps, connectors, bearings, diodes, hardware, circuit boards, cables. Weird and wonderful stuff. Most folks are happy with the assortments we send and we often get re-orders. Try one. **92U034 50 Lbs. for \$49.95**



TV AUDIO DEMODULATOR

Unused unit from cable TV box takes channel 3, 4 or 5 signal and demodulates the audio. Comes with documentation and schematics, plus additional schematics to build add-on video demodulator board. **92A028 \$9.95 each**

SOLAR-POWERED ROBOT BUG KIT

No batteries required! It uses photosensitive eyes to seek light and dual feelers to avoid obstacles. Kit includes circuit board, solar cells, miniature motors, all parts and easy-to-follow instructions. Body approx. 3"L x 2"W. **98K001 \$59.00 each**

CRYSTAL SET PROJECTS: 15 Radio Projects You Can Build

Crystal Set Projects is a collection of radio projects that won a recent building contest run by the Xtal Set Society. Included are step-by-step instructions so you can build and design your own Xtal sets no matter what your background in electronics. The projects are of various designs and difficulty so that everyone can learn something. 6x9 paperback, 160pp. **98X010 \$14.95 each**

'486 MOTHERBOARD

Comes with a 25MHz 486-SX CPU. Board supports SX25, SX33, DX25, DX33, DX40, DX50, DX2-50, DX2-66, DX2-80. Does not support DX4 CPUs. All info silkscreened on board. Seven ISA slots and 2 VESA local buss extensions. Used, tested good. While supplies last... **98C014 \$29.95 each**

DISPLAY MISER

Save wear and tear on your monitor. Save on electric bills with Display Miser. This item automatically shuts down the monitor after a predetermined amount of time. The user can program the time to shutdown from 10 to 42 minutes. Easy connection to PC with diagram printed on bottom of unit. No tools needed - just plug-ins! **98C027 \$4.95 each**

GENERAL INSTRUMENTS UNIVERSAL REMOTE CONTROL

Model XRC110. 44-button transmitter controls up to four units, i.e., TV, VCR, Cable Box, and Auxiliary - second TV, VCR, Digital Audio Tuner or services such as Music Choice (MC) and Digital music Express (DMX). Slim, lightweight, easy to handle. Easily programmed as your needs change. Programmed functions not lost when replacing batteries. Uses two "AA" cells. Indicator lights show which device is being controlled. Volume control may be programmed to work even though the rest of the transmitter is in a different mode. Works with equipment from many manufacturers. Will do a "code search" for the correct code, if needed. Batteries, detailed instructions and device code tables included. **98V011 \$9.95 each**



LED FLASHLIGHT

This flashlight is the newest in portable lighting technology. Three "AA" batteries will give 30 hours of light when you use the PL-W1 with one LED. There's no bulb to replace. This is a great light for cavers, backpackers, boaters and anyone who doesn't want to carry a lot of batteries and wants a dependable light. Put one into your Y2K "survival kit." **PL-W1 (1 LED) \$22.95**
PL-W2 (2 LEDs) \$26.95
PL-W3 (3 LEDs) \$29.95

ULTRABRIGHT WHITE LED

T1-3/4, water clear, 1600 mCd. Docs included. **SE5082H \$4.95 each**

1MB 80nS 30-Pin SIMMs

Three-chip type; matched sets. **97C052 4/\$9.95**

POWER SUPPLY TRANSFORMER

Primary: 208 or 240 VAC, 50-60Hz, 3A. Secondary: 2 x 30 or 24VCT @ 5A each, and 24V @ 3A. Mounted on 6-3/4" x 6-7/8" backing. **98N014 \$19.95 each**

Fantastic Sound!!!

NEC AMPLIFIED SPEAKERS

Size: 11"H x 4.5"W x 4.75"D. Power: ±15VAC @ 1A, 3-pin mini-DIN socket. Input: 1/8" stereo phone jack, line level. Outputs: 1/8" stereo phone jacks, line out & earphone. RCA phono cord connects speakers. Simple schematics to build your own power supply included. **98V013 \$19.95/pr.**

ATARI 1020 COLOR PRINTER

For all Atari 8-bit computers. (Not PC-compatible!) Package includes: printer, power supply, software, pens, paper and interface cable. These are new units in factory sealed boxes. **94C037 \$14.95 each**



ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronic.com>

(408) 943-9773 - Fax (408) 943-9776


Store Hours: 9-6 M-F & 10-3 Sat. - Pacific Visa, M/C, AmEx Accepted.

All Sales Final.

California Residents Add Sales Tax.

Shipping Additional on All Orders.

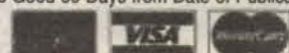Prices Good 60 Days from Date of Publication



Send \$2.00 For Our Latest Catalog!
\$4.50 Foreign. Refundable on First Order.

010299

ELECTRONICS

Q & A

..... With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware and software. This column doesn't replace the Tech Forum that you've grown to love and support. Instead, it will supplement it, so feel free to participate as always with your questions and answers. You can reach me on America Online at TJBYSERS, on the Internet at TJBYSERS@aol.com, or by snail mail at Nuts & Volts Magazine, 430 Princeland Ct., Corona, CA 91719.

What's Up: Two different 12V DC-to-DC voltage converters, two new alarm circuits, and two battery monitor/testers. A reliable fixed-frequency, variable duty cycle pulse generator. And many more web sites to visit, including an interesting look at GeoWorks. Finally, our readers talk back about hard disk fixes and noisy A/D converters. Enjoy!

More Solar Stuff

Q. In your Dec. '98 column, you showed how to trickle-charge a battery from a solar panel using nothing but a diode. What size diode should I use for my solar panel which has a 1-amp output?

Carl Zajac
via Internet

A. Let me reiterate my Dec. '98 answer first: If the charging current is less than 1/10 the capacity of the battery under charge, a charge controller isn't needed. Translated, that means that your 1A solar panel can trickle-charge any battery of 10 AH (amp-hours) or bigger using a simple diode to prevent discharge when the sun doesn't shine. How big is the diode? If you have a 1-amp solar panel, a 1-amp diode like a 1N4001 works. If you have a 3-amp solar array, then the answer is a 1N5400. Both are available from RadioShack for under a buck.


Battery Testing

Q. I'd like to use a voltmeter to check the condition of my 'AA' batteries, but I feel the need to put a load on them while testing. Can I just put a resistor across the battery when I test it? If so, what value of resistor should be used? Also, if I want to discharge NiCd batteries before recharging them, can I put a resistor across them to discharge them completely? What value should I use?

Thomas Wallenmaier
Southfield, MI

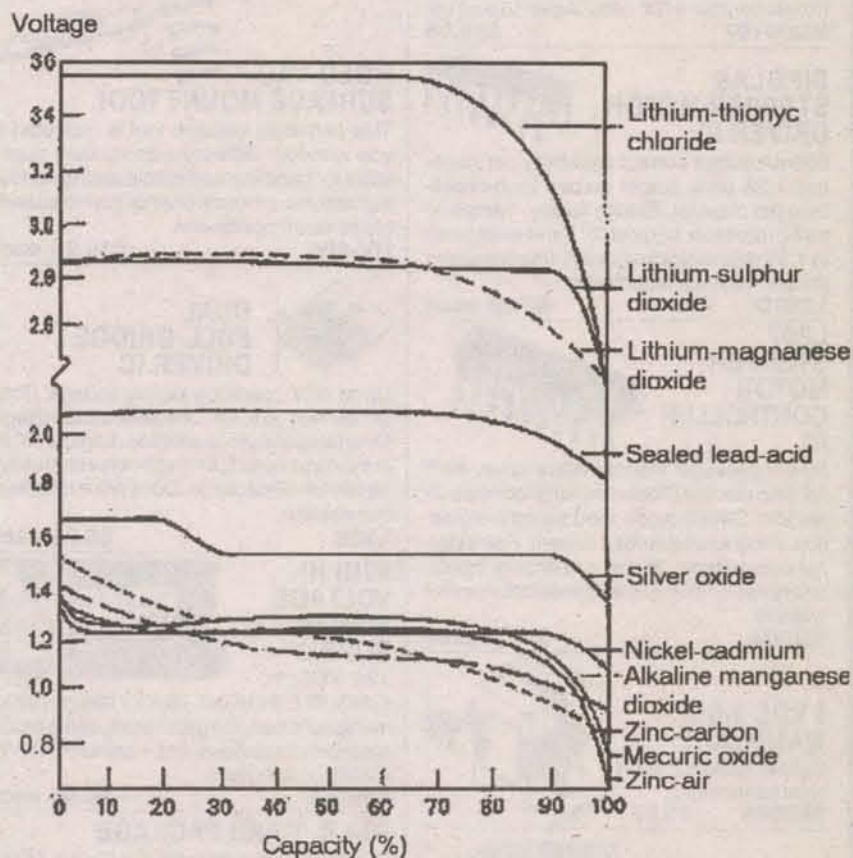A. You're quite right. Measuring the open-circuit voltage (OCV) of a battery to determine the amount of service life will yield but a rough estimate. A more accurate method is to measure the closed-circuit voltage (CCV) of the battery. This is accomplished by putting the battery

under load for one to two seconds, then measuring the CCV. The load is determined by the size and type of battery. In the case of a 'AA' cell, the load should be approximately 8 ohms. A 'D' cell needs a 4-ohm load, and a 9-volt battery is best tested with a 50-ohm load. For an alkaline or carbon-zinc single cell, the cutoff point is 0.9 volts. For example, if the battery voltage is 1.1 volts, the battery has approximately 20% of life left. Different batteries have different discharge profiles, as shown below.



Battery Size	Lamp
AAA	222
AA	PR5
C	PR5
D	PR2
6V lantern	1888
9V	1892

Personally, I prefer to use a flashlight bulb for the load when I test my batteries. In addition to getting a voltage reading of remaining capacity, you get a visual look-see that strikes closer to home. Here's a list of the bulbs that I use for the various batteries — and to drain a NiCd battery for recharging.

'CELLULAR ACCESSORIES'

FROM
M.F.M. COMMUNICATIONS.

No. 1

FOR ALL
YOUR CELLULAR NEEDS

WEB SITES:

English: <http://members.aol.com/mfmcom123/index.htm>

Spanish: <http://members.aol.com/mfmcom123/index2.htm>

EMAIL:

MFMCOM123@aol.com

TELEPHONE:

+44 - 1342 312403

57 Addison Road, Caterham, Surrey, CR3 5LU, UK.

Join us in our 20th Year Celebration!!


We're looking forward to a stellar year in 1999, and we hope you'll be a part of it.

We'll be implementing a lot of new programs this year for both the magazine and the website, plus we'll be giving existing features a face-lift.

We hope you'll be a part of the excitement. As we head toward the millenium, it will be increasingly important to stay on the cutting edge. And that edge is where Nuts & Volts plans to be!!

909-371-8497 • 909-371-3052 FAX
<http://www.nutsvolts.com>

regulator, which you can buy from Digi-Key (1-800-344-4539; <http://www.digikey.com>) or QuestLink (<http://www.questlink.com>) for under \$10.00. (I recommend the LM2577T-ADJ version in a TO-220 package for ease of use.) This regulator is unique in that it has an input voltage range of 3.5 volts to 40 volts, an adjustable voltage output of up to 60 volts at up to 3 amps (at the lower voltages), current limiting, thermal shutdown (in case it gets too hot), and requires only eight external components. Here's the 24-volt version of the DC-to-DC converter you asked for.

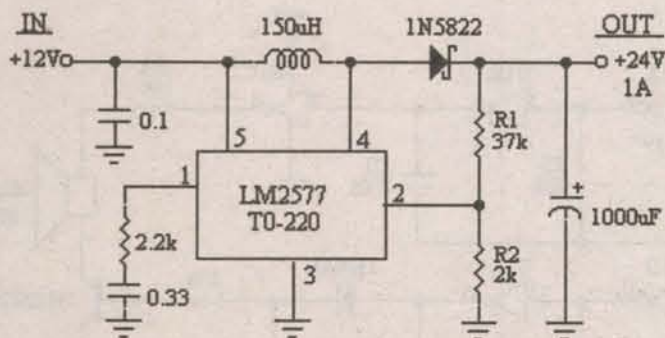

The circuit operates in what's called the "boost" mode, where a magnetic field is built up in an inductor, then allowed to collapse. As the field collapses, it generates a high voltage spike, or kick. This is exactly how the ignition system in your car turns 12 volts into 50KV to fire the spark plugs. On a smaller scale, the LM2577 regulates the boosted voltage between 5 volts and 60 volts. The regulated voltage is determined by the ratio between R1 and R2. Resistors R1 and R2 divide down the output voltage so that it can be compared to the internal 1.23-volt reference. For a given output voltage select the ratio so that

$$\frac{R1}{R2} = \frac{V_{out}}{1.23V} - 1$$

That is, the voltage drop across R2 at the desired output voltage must equal 1.23 volts. Here's how the values of R1 and R2 for a 24-volt output were calculated. Set R2 at 2.0K, then calculate the current needed to produce a 1.23-volt drop.

$$I = \frac{E}{R2} = \frac{1.23}{2000} = 0.615 \text{ mA}$$

Next, calculate the total resistance needed to generate a 0.6-mA current across a 24-volt source.

$$R = \frac{E}{I} = \frac{24}{.000615} = 39K$$

Finally, subtract for R2 to get the value of R1.

$$R1 = R - R2 = 37K$$

You can follow the same procedure for the 19-volt source, or 15 volts, and whatever. The important thing is that R2 has to generate 1.23 volts across it to output the desired voltage. You may have to juggle the values of R1 and R2 to achieve a ratio that equals a standard resistor value, but don't knock yourself out. A 37.4K resistor is plenty close enough for this example. Finally, the input voltage (Vin) can't exceed the boosted output voltage (Vout) — this is a step-up regulator remember? It can't reduce 12 volts to 5 volts, which is why you should get the 13-volt source directly from the 12-volt battery. With a full charge a car battery will measure 12.6 volts; when


charging, the voltage is 13.1 volts. A simple rotary switch will let you select between the sources. For detailed information on designing DC/DC converters with the LM2577, download its data sheet from the National Semiconductor Web site at <http://www.national.com/pf/LM/LM2577.html>.

... DC to DC Conversion, Again

Q. I'd like to use an LM1875 20W IC power amp in an auto audio amplifier. How can I make a bipolar +24VDC/-24VDC power supply from the car's 12-volt power source?

William Silvis
via Internet

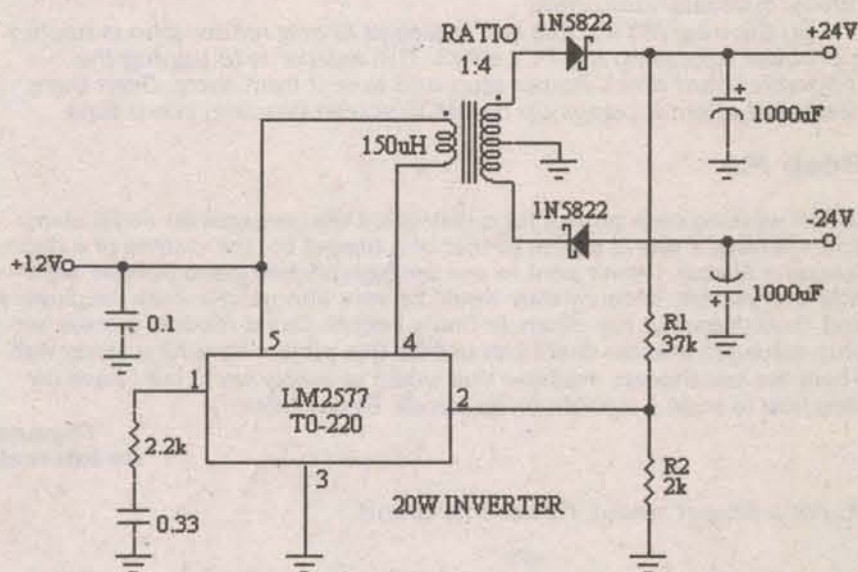A. Like the query above, you, too, can use an LM2577 step-up voltage regulator. For this application we'll use the LM2577 in the flyback mode, as shown below.



In this mode, a transformer replaces the inductor. This time, the energy stored in the primary inductor is transferred to the secondary of a transformer, where — unlike the boost mode — it is transformed to a higher or lower voltage. The amount of energy transfer, that is the resultant voltage at what current, is a product of the two — or total power. Raising the voltage lowers the available current, whereas reducing the voltage increases the output current. Together, the two can't exceed the total dissipation of the IC's output stage — about 30 watts for the LM2577. (An LM2587, a pin-for-pin replacement, can operate up to 60 watts, but runs at a different frequency and uses different inductor and capacitor values. Download the LM2587 data sheet from QuestLink or the National Semiconductor web site (<http://www.national.com>) for details).

Basically, the flyback configuration is the same as that used in your monitor to increase or reduce a DC voltage. In this case, the flyback transformer takes the car's 12-volt source and increases it to ±24VDC. The transformer is a standard center-tapped secondary type with a winding ratio equal to the voltage desired. In your case, you need 48 volts total (24V + 24V) from a 12-volt source, a 1:4 ratio. Should you want to change the voltage to ±5 volts, the ratio would be

PRODUCTS FEATURES ORDER NEWS LINKS

Black Feather Electronics

10841 Noel St. #106
Los Alamitos, Ca. 90720

DIRECT DIAL: (714) 236-1776 FAX: (714) 236-1778 E-MAIL: bjkfea@juno.com

WWW.BLKFEATHER.COM

WE BUY EXCESS/SURPLUS ELECTRONIC SUPPLIES

You Have Tried The Rest
"Now Try The Best"
For all Your Cable TV Converter
"Needs"

Call 1-800-580-3725

Monday Thru Friday 9 am to 6 pm CST
30 day - 100% Money Back Guarantee
One Year Full Warranty • C.O.D.'s also



"Tech 2000"



1:0.8 (10V/12V; quiz later).


As before, resistors R1 and R2 set the output voltage. The output voltage for the bipolar output is derived from the positive leg of the output, which means the outputs aren't tracking. In other words, only the positive output is regulated. If there is a heavier, or lighter, load on the negative supply, its voltage may go above or below the positive. In your case, where you're using a symmetrical Class-B op amp, I wouldn't worry about it. However, if you plan to add single-supply devices, like indicator lamps or a preamp, make sure you hang them on the positive side — the regulated line — to keep the LM1875 in balance. Better yet, use the +12-volt source if you can. (BTW, are you aware that you can operate the LM1875 from a single-polarity (+32V to +60V) power supply?)

Don't Tread On Me Alarm


Q. I have a theft problem that I think could be solved with an inexpensive motion-activated alarm, somewhat like the alarms that go off when you bump into a car. Do you have any advice on appropriate sensors/circuits/sounders?

Steve Scott
via Internet

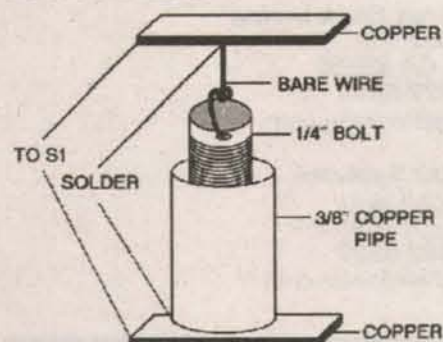
A. What you want is a vibration detector, like RadioShack's 49-406 (\$12.99). This is a 120dB siren that attaches to a door or window and screams its head off when it detects an abrupt shock or vibration. Want to make one yourself? Follow me. It begins with a plumb device, like a 1/4-inch bolt, suspended inside a 3/8-inch copper water pipe, as shown below.



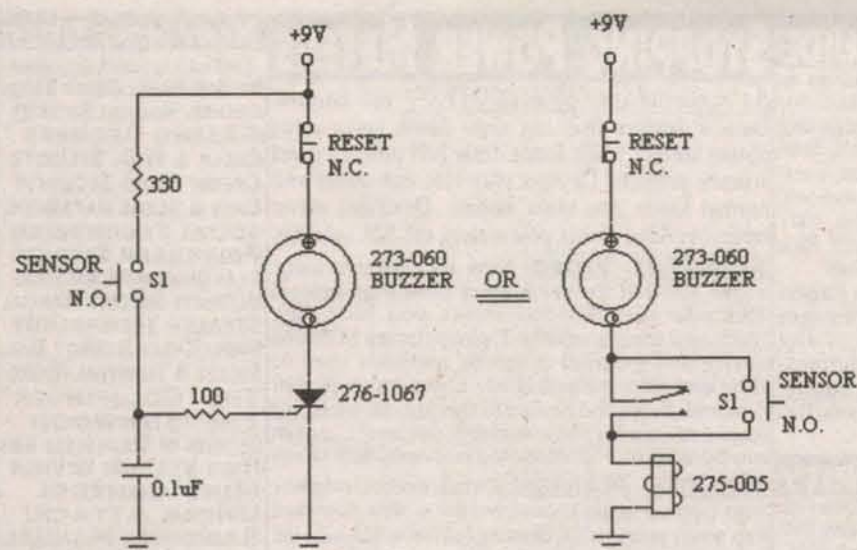This device is identical to those used in pinball machines to trigger the "tilt" alarm. Bump it too hard, and the pendulum hits against the metal guard and sounds the alarm. The sensitivity is adjusted by the size of the pipe, the length of the bare (copper) wire, and the weight of the bolt. The heavier the bolt, the more force it takes to trigger the circuit, which is shown below.



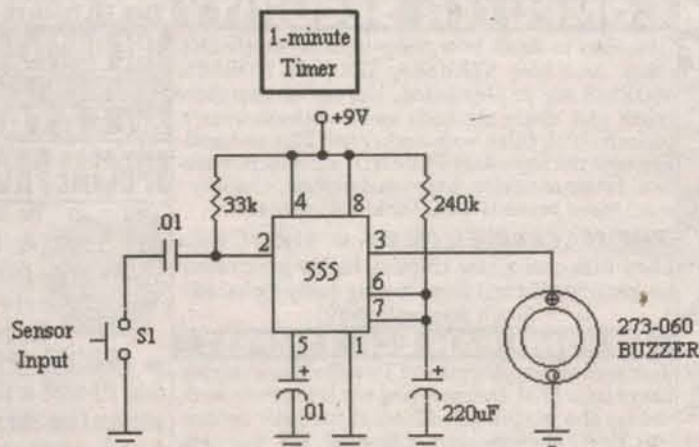I made it simple, on purpose. Once triggered, you have to get your butt out of bed and reset the alarm. If you only want it to scare the thief away and keep warm under the blankets while the alarm does its job, you need an automatic turn-off timer circuit like this.




Battery Gas Gauge Does 36 Volts

Q. I have purchased all of the necessary components, including the printed-circuit board, needed to build the "Battery Gas Gauge" that you described in the July '97 issue. It's my intention to use the gas gauge across two of the 6-volt batteries in the golf cart, which is used as mobility for the disabled, to get a general idea of the charge on battery pack. The thought has come to mind that it may be possible to reconfigure this schematic so that the gauge could be used across the entire bank, which contains six batteries for a total of 36 volts. Can it be done easily?

Joe Dunnett
via Internet

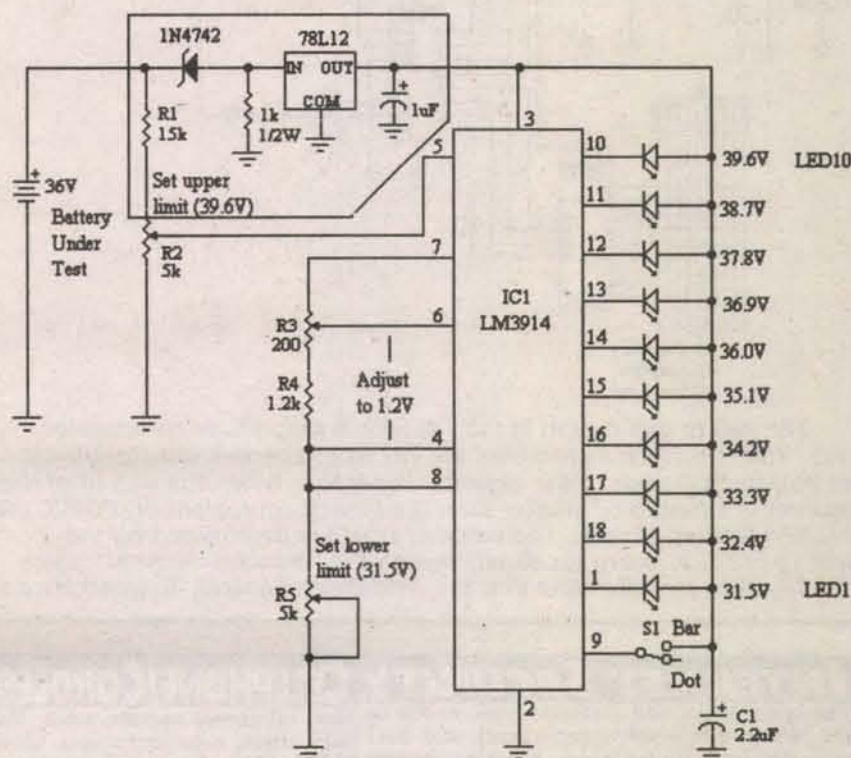A. This is an easy order to fill. All you have to do is separate the power source from the battery under test. Because it's been a while since we published this circuit, and there still seems to be a great deal of interest in it, here it is again with the modification for 36-volt operation.



The changes are highlighted in gray. Basically, you need to change the value of R1 and reduce the 36-volt input to 12 volts via the new 78L12 voltage regulator and its related components. Other than that, it's the same circuit. Make sure that you cut the copper trace on the PC board to pin 3 of the LM3914 and reroute it to the LM78L12 "out" when making this modification. Here's a new table showing the 36-volt battery voltage and charge levels.

Battery Voltage	LED Color	Description
39.6	Green	About 100% of charge remains
38.7	Green	About 80% of charge remains
37.7	Green	About 70% of charge remains
36.9	Green	About 55% of charge remains
36.0	Green	About 40% of charge remains
35.1	Yellow	About 25% of charge remains
34.2	Yellow	About 10% of charge remains
33.3	Red	Caution!
32.4	Red	Danger!
31.5	Red	Dead!


To calibrate the battery monitor, first set the voltage across pins 4 and 6 to 1.2 volts using R3. Apply 31.5 volts to the input and adjust R5 so that LED1 lights. If you don't have a 31.5-volt source, you can measure the battery-under-test voltage with a DMM (digital multimeter) and rotate R5 until that lamp lights with S1 in the dot mode. Now your ambulatory-impaired friends can get to the mall and shop 'til they drop before the golf cart drops dead.

Fixed-Duty Cycle Pulse Generator

Q. Please reference your Sept. '98 article about the LM558: Forrest Mims in his *Engineer's Notebook* shows a variable-pulse generator with a fixed duty cycle that uses two of these timers and a control voltage. This is a very useful circuit, but myself and others find it difficult to start. Would a 556 with a paralleling of the control inputs work better?

S. Chris Early
via Internet

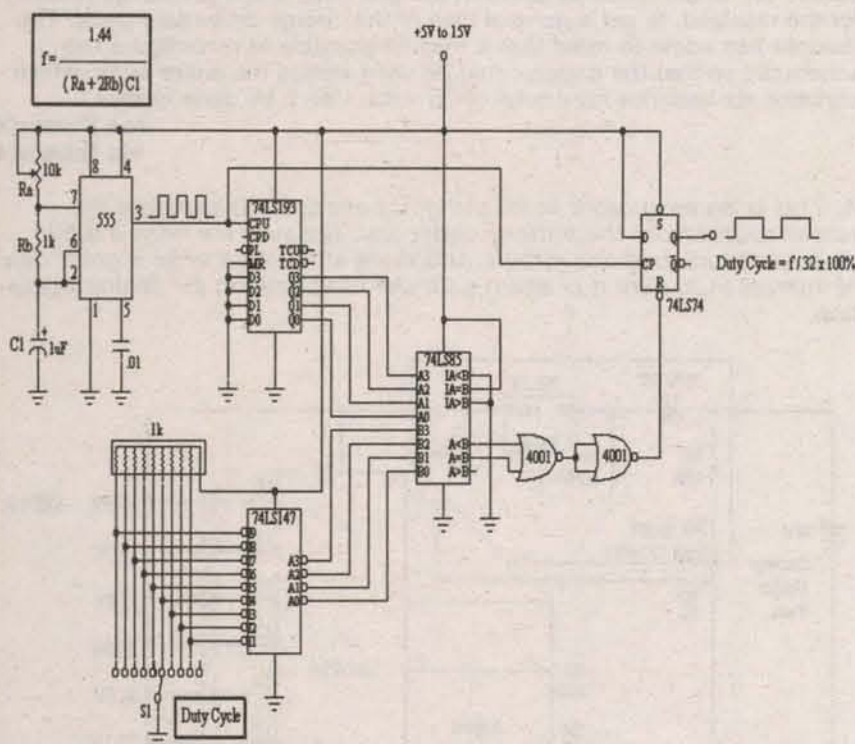A. You, too? I've never been able to make that circuit work short of a swift kick in the rear. Here's a design that I ran across (and slightly modified to include S1), but have never tried. It looks very solid because it uses digital logic to vary the duty cycle, which should make it quite stable.



The key to this design is the 74LS85, a magnitude comparator chip. The 555 clock increments the 74LS193 counter, which outputs its binary BCD code to the digital comparator. When the output of the counter is equal to or greater than the binary equivalent on B0-B3, the 74LS74 flip-flop is reset. The value of B0-B3 is determined by the setting of S1, a rotary (or slider) switch that encodes decimal values of 10%, 20%, etc. into BCD that the 74LS85 recognizes. To generate a

squarewave; for example, simply set S1 to 50% (middle position). While the circuit looks complex, most of the lines are just wires going from one IC pin to another. Total cost is under \$10.00. Like I say, I've never tried this and would appreciate your feedback. In particular, I'm not sure the 1A<B and A<B blocks are properly placed; you may have to exchange the two blocks (six pins in all) to make it work. I recently ran across a single IC function generator, the MAX038 from Maxim (408-737-7600; <http://www.maxim-ic.com>), that claims to have a variable duty cycle pulse generator that's independent of frequency. I haven't looked at it closely, but I suspect it's an upgrade of the venerable Exar XR-2206. Stay tuned for more on this chip.

More POWER!

Q. I plan to build one of your 25-watt inverters shown in the Dec. '98 column, but would like more power, too. Do you have any circuits for 3-4 KW?

Jim Rudholm
via Internet

A. Sure, but not anything you want to tackle unarmed. Once you exceed a couple hundred watts, you can't use a simple squarewave output. You have to use a modified (staircase) wave or a pure sine-wave, which needs at least eight power FETs, which generate a lot of heat, which require special heatsinks, which means you need a drill press, which ... (sorry, sometimes I like playing with words as much as wires) ... makes it cheaper to buy than build. My suggestion? Check out the following retailers.

Alternative Energy Engineering

P.O. Box 339
Redway, CA 95560
1-800-777-6609
<http://www.alt-energy.com>

Sierra Solar Systems

109 Argall Way
Nevada City, CA 95959
1-888-667-6527
<http://www.sierrasolar.com>

INTERNET SECURITY CELLPHONE/CORDLESS GUIDE STOPPING POWER METERS MANY MORE TITLES!

The latest tricks and methods hackers use on the Net to pirate software (warez), and hack websites. Includes examples, countermeasures, password defeats, Packet-Switched Networks, UNIX, Sprintnet, X.25, anonymous FTP, brute force techs, lots of tips. **More!** \$29. wrds=29.4K

INTERNET TRACKING & TRACING: Scammers, spammers, stalkers, infectors, and others hide behind the Internet's anonymity to commit serious offenses. Learn from master hackers best methods to track, trace IDs and origins, and to protect your own privacy. **More!** \$29. wrds=17.0K

INTERNET FRAUDS DATABASE: Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously with impunity. Details how they're done, how to ID them, how to protect yourself. **More!** \$25. wrds=19.1K

THE COOKIE TERMINATOR: Many websites track your every move! Browser cookie, history and cache files contain personal data readily accessible to Internet predators, scammers, spammers and snoops. Your financial, medical, political, habits, lifestyle, future plans data is exposed to the world! Step-by-step how to remove and stop cookies from destroying your privacy. \$25. wrds=8.4K
Any 2 for \$49, 3 for \$64, all 4 for \$79!

PBX SECURITY
PBXs hacking losses of \$5-\$10 Billion/yr! Detailed vulnerabilities (especially for out-dial), countermeasures. Exclusive author interview in Forbes! \$24. wrds=17.4K

ATM SECURITY
100+ ATM crimes, abuses, vulnerabilities, defeats exposed - TEMPEST, mag stripes, false fronts, supercool, **More!** Case histories, labeled internal photos, figures. \$39. wrds=41.0K

TOP SECRET
2430 Juan Tabo, NE, #259, ABQ, NM 87112
P.O. Box 23097 ABQ, NM 87192
Fax: 505-292-4078 (all hours, orders only) Voice: 505-237-2073 (9-7 M-F)

Full Web Catalog: www.tsc-global.com Special Projects: spaf-spp.html
Established in 1971 by John Williams, MSEE, former DOD weapons engineer and NIH physicist. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). Postal MO is fastest! VISA, MC OK. NO CODs. 10% OFF all Orders over \$100; \$2.00 OFF all New Orders over \$20 placed by Mail or Fax. wrds=Estimated Word Count
Sold for legal educational purposes only. Some publications are controversial! We take no responsibility for anything we publish. See Catalog for WARRANTY, SPECIAL PROJECTS and all other applicable policies.

How cellphones operate; mods. Vulnerabilities to hack attack; countermeasures. Cloning details for NAMs, ESNs, etc. control data formats, computing encoded MINs, ESNs, SIDHs, Op Sys, PROMs, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, step-by-step to keypad-reprogram 100+ popular cellphones. One FREE database search. Plus much on Cordless phones. **More!** \$49. wrds=80.0K

PAGER (BEEPER) MANUAL: How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How phreaks hack Pagers; countermeasures. Plus plans for a **Personal Pocket Paging System** (xmitter and receiver). **More!** \$29. wrds=11.7K
Both for only \$69!

CALLER ID & ANI SECURITY
How they work and the many vulnerabilities of Caller ID, ANI, *69, *57, Call Blocking, *67, et al. Describes ESS, SS7, CN/A, CAMA, DNR, Diverters, Centrex! \$25. wrds=15.2K

FAX MACHINE SECURITY
All known methods used to hack Faxes and countermeasures. Includes computer fax modems, crimes, interceptions, fax servers, fax-on-demand, protocols, parameters, compression, encryption, and fax surveillance-type mods. **More!** \$29. wrds=29.0K

VOICE MAIL SECURITY
VMSs are hacked to penetrate PBXs to make outgoing calls, get free VMB usage, secretly read/change/delete messages, control or damage the VMS (or its PBX) itself. Details how hackers do it, countermeasures. A must for users, sysops, security personnel! \$29. wrds=14.2K

CONSUMERTRONICS
CATALOG \$1 WITH ORDER, \$3 W/O

STOPPING POWER METERS

As reported on "60 MINUTES"! 6th Edition! Details devices that can slow down (even stop) power meters while loads draw full power - great science projects! Devices plug into one outlet and normal loads into other outlets. Describes meter creep, overload droop, pole meters, etc. \$29. wrds=10.4K

SPM THE VIDEO: Now it's easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPMEM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM-related manuals! \$29. (20 min)

THE I.G. MANUAL: Details external magnetic ways (applied to meters) outlaws use to slow down and stop power meters while drawing full loads. \$25. wrds=4.9K

KW-HR METERS: How watt-hour energy meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow, stop power meters by others. \$25. wrds=24.2K
Any 2 for \$49, 3 for \$64, all 4 for \$79!

COMPUTER SECURITY
Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39. wrds=49.5K

THE HACKER FILES: Expose 3 HD PC disks filled with choice raw, colorful, highly informative hacker, phreaker text files covering many topics! \$39.
Both for only \$69!

BEYOND VAN ECK TEMPEST
Remote eavesdropping plans of TV video "noise" signals. Range up to 1 KM. Describes how van Eck systems work, and are also used in surveillance of computer systems. Plus TVRO vs phone privacy detailed! \$29. wrds=14.9K. Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

MANY MORE TITLES!

(See Catalog for prices & descriptions)
BEYOND PHONE COLOR BOXES
ANSWER. MACHINE SECURITY
CASINO SECRETS
CHECK & M.O. SECURITY
CREDIT CARD SECURITY
CONS & SCAMS DATABASE
SOCIAL ENGINEERING
POLYGRAPH SECRETS
BY AN ORDER OF THE MAGNITUDE
ULTIMATE SUCCESS MANUAL
STEALTH TECHNOLOGY
SIMPLE/CHEAP SECURITY ELEC.
SECRET & SURVIVAL RADIO
THE "GOLDFINGER"
THE "SILKWOOD"
SECRETS OF SOLDERLESS BBS
HIGH VOLTAGE DEVICES
MIND CONTROL
UNDER ATTACK!
RADIONICS MANUAL
HEAL THYSELF!
SECRET & ALTERNATE IDS
CRYPTANALYSIS TECHNIQUES
GOVERNMENT LAND GRAB
ROCKET'S RED GLARE
SURVIVAL GUNS & AMMO
THE ULTIMATE DRIVER

THE DIRTY-2 DOZEN!
24+ Hot Hack/Phreak Expose Disks!
See CATALOG!

SPECIAL PROJECTS

We will design & build just about anything electronic! Hardware done as SPECIAL PROJECTS. Send #10 SASE or \$1 for SP Application Form, else get at: www.tsc-global.com/spaf-spp.html

GeoWorks Still Lives

Q. In his article "Secrets of Making Attractive Rack Panels" in the Dec. '98 issue, Thomas Henry mentions GeoDraw (Geoworks Ensemble package) as his favorite drafting program software. After checking around the Internet, CompuUSA, and local computer shops, I still haven't found a source for GeoDraw. Any suggestions?

Lee Markmann
San Antonio, Texas

A. First, let me say that GeoDraw runs under the GeoWorks operating system, and isn't a Windows, DOS, or Mac program. GeoWorks, formerly known as GEOS is now sold under the name NewDeal, is like Windows 3.1 in many respects. It's an object-oriented operating system which today we call a GUI (Graphics User Interface) — or Windows. And like Windows, it runs under DOS, and the applications — like GeoDraw — are GEOS specific. In other words, the application programs for GEOS work only with GEOS. Now that you're thoroughly confused, let me say that NewDeal can be installed over Windows, Atari, Commodore, and Apple operating systems. To sort all this out, I suggest you look at James D. Bearden's FAQ (frequently asked questions) on this subject. You can find it at http://www.cis.ohio-state.edu/hypertext/faq/usenet-faqs/html/pcgeos-faq/part1_/faq.html or on our web site (<http://www.nutsvolts.com>) under the name GEOS.TXT. Where can you buy GeoDraw? From New Deal under the name NewDraw.

New Deal, Inc.
P.O. Box 2458
Champlain NY 12919-2458
1-800-985-4263
<http://www.newdealinc.com>

MAILBAG

Dear TJ Byers:

I just read your item in the Nov. '98 issue concerning "Hard Disk Fixes." In my business, I have run into these problems you stated on many occasions, and while you are right on target with the "stickism" problem (we call it "sticktion"), I thought I would share my two cents with you on the third possibility you mentioned.

You stated "... the controller board has died. Unfortunately, there are no fuses to replace." Actually, I have fixed a large number of drives (read many dozens) which have a pico fuse on the controller board. They look like resistors, either standard leads or surface mount, but they are there — most near the power connectors — and they're often totally open.

John Hoyt
South Carolina

Response:

Yep, they are there, indeed, and I knew it. I guess what I should have said is: "If you hear the motor running but can't access the data, then use a DMM to probe the controller board for a voltage — any voltage. If absent, suspect the input fuse, if you can find it. If the voltage is there, then the board is dead." I'm happy to hear that you have repaired dozens of hard disks this way, but I've never been that lucky (sigh ... not even one). Thanks a lot for the input!

TJ Byers
Q & A Editor

The advice in Oct. '98 Electronics Q & A about quiet 2-MHz clocks misses the mark in several places. First, dithering the clock oscillator for a 20-bit ADC is a mistake because it introduces errors into the conversion. To maintain 20-bit (1 ppm) resolution in amplitude, you must also maintain about 1 ppm resolution in time. For a 50-KHz sample rate, the clock should be stable to 20 picoseconds.

Second, the original question is misleading. There are a couple of interpretations. The literal interpretation is the 20-bit ADC is working fine except that the 2-MHz clock causes a lot of radio interference to other equipment. In this interpretation the column's advice about quieter clocks makes sense, but lacks some better advice. Shielding is very effective at killing 2-MHz radiated noise — a 1/16 inch aluminum shield provides more than 150dB of absorption loss. Filtering the

power supply and using bypass capacitors are also important.

A second (and more reasonable) interpretation is the 20-bit ADC outputs a lot of noise and the analog signals show a lot of sharp edges that coincide with the 2-MHz clock. In other words, Steve's project doesn't have the performance he wants. This interpretation is more likely, and it means there is nothing wrong with the 2-MHz clock. The clock and its harmonics are out of the ADC's input band. In this interpretation, the problem is inadequate isolation between the digital and analog parts of the circuit.

For good performance, the analog and digital circuits must be isolated. Otherwise digital currents flowing in the analog parts of the circuit will create IR voltage drops that look like noise. The circuit design needs separate analog and digital supplies, separate analog and digital ground planes, and a single point ground connection between the two systems. The ground plane cuts need careful thought. In addition to isolating the supplies, the designer must also minimize electrostatic and electromagnetic coupling.

In particular, you must keep the digital signals away from the analog signals. Assume that an output bit of the ADC toggles at 16 KHz. If that bit is close to an analog node (say close enough to have 1pF of coupling capacitance), then the capacitive impedance between the two nodes is 10 megohms. Finally, if the analog node impedance is 10K, then the 5-volt digital signal will couple 5mV of noise to the analog node. That 20-bit ADC (whose LSB is about 5 microvolts) just became a 10-bit ADC. To kill the noise, separate the analog and digital traces and use guard rings or other shields to minimize coupling capacitance. (Use low impedance circuits (10K is too large).

Gerald Roylance
Mountain View, CA

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 34501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4935A TRANS IMPAIRMENT TEST SET	\$900.00
HP 34201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 34201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 34200A 50MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$550.00
HP 3370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC. ANALYZER	\$3500.00
HP 3437A 3 5DIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG O-SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP 8558B/181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7880 400MHZ TIME BASE	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7892A 500MHZ DUAL TIME BASE	\$125.00
HP 1740A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7812 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT JO1	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6643A 45VDC-4.3A POWER SUPPLY OPT JO3	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

Write in 75 on Reader Service Card.

Tiny FBasic Computer



(Shown 85% Actual Size - 40 pin DIP)

The TICkit 62 module is like a Parallax Basic Stamp II, but has 4 times the program space installed (expandable to 64K). It also has 4 times the variable space (96 bytes), and uses a modern structured language similar to BASIC only more powerful.

- Only tool you need is a PC
- Inexpensive \$45/module, \$16/IC
- Development Kit only \$45
- Huge library of I/O function
- Structured FBasic Language
- Easy to learn and use
- Powerful enough for large projects

ASK ABOUT OUR STAMP COMPATIBLE PERIPHERAL COMPONENTS

VersaTech
Electronics

PHONE: (303) 828-9156, FAX: (303) 828-9316
e-mail: versatech@csn.net
Web: <http://www.csn.net/versatech>
11170 Flatiron Drive, Lafayette, CO 80026

Basic Stamp is a registered trademark of Parallax, Inc.

TOOLS

TWEEZERS, FORCEPS,
SCISSORS, DREMEL
TOOLS, OPTICAL AIDS,
PLIERS, SCREWDRIVERS,
WHOLESALE & RETAIL

LASER POINTERS



Using high quality laser optics and microelectronics you can cast a 1/4" diameter dot as far as 1600-1800 ft away. Great for professional demonstrations, teachers, and even for amusing your dog or cat. Comes with 3 replaceable LR44 batteries; these are like watch type batteries. Has a wavelength of 630-680nm.
#LS2133 Unit 1 \$10.00

3 LENS HEAD MAGNIFYING GLASS

That's right! Not 1 lens but 3 lenses. This magnifier has many features and its easy operation as follows:
1. Light weight (approx. 110g only). You can get a clear, solid view in wide sight through the double lens two square glass.
2. Velcro head adjustable band to fit your head.
3. Convenient use. There's no need for the users to take off his glasses, and his hands will be free moving.
4. With one touch design, the magnifier is with a 1.8 power to a 2.3 power in just one touch. Then you can change the magnifying time from a 3.7 power to a 4.8 power.
#HM 213 Unit 1 \$19.00



VISIT US AT
WWW.UTOPIATOOLS.COM

UTOPIA TOOLS
CALL FOR FREE CATALOG
TOLL FREE 1-888-UTOPIA-2

WESTERN TEST SYSTEMS

WE BUY AND SELL

Inquiries 303-438-9662 • Fax 303-438-9685

Orders only 800-538-1493

530 Compton St., Unit #C, Broomfield, Colorado 80020

OSCILLOSCOPES & ACCESSORIES

TO 100 MHz	
TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series	\$375.00
ABOVE 100 MHz	
TEK 2465 300 MHz 4-channel Oscilloscope	\$2,500.00
TEK 7104 1 GHz Oscilloscope, with 7A29, 7A29-04, 7B10, 7B15	\$4,500.00
TEK 7844 400 MHz Dual Beam Oscilloscope with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK 7904 500 MHz Oscilloscope, with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK 7A42 4-Channel Logic Triggered Vertical Amplifier	\$500.00
PROBES	
HP 1122A Probe Power Supply	\$150.00
TEK 1101A Accessory Power Supply, for FET probes	\$200.00
TEK P6046 100 MHz Differential Probe	\$750.00
TEK P6150 9 GHz 10X/3 GHz 1X 50 Ohm Probe, SMA(m) output	\$400.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$250.00
TEK P6203 1 GHz 10X Active Probe, for 11000 series	\$375.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW: DC-700 MHz, ST conn.	\$175.00
CALIBRATION	
TEK SG503 Level Generator, 250 kHz-250 MHz, TM500 series	\$600.00

WAVEFORM GENERATORS

FUNCTION	
HP 3310A 5 MHz Function Generator	\$250.00
HP 3310B 5 MHz Function Generator, monochrome & var. phase trigger	\$325.00
HP 3312A 13 MHz Function Generator	\$600.00
HP 3325A 21 MHz Synthesized Function Generator, HPIB	\$1,000.00
HP 3325A-002 21 MHz Function Generator, high voltage output option	\$1,500.00
HP 8165A-002.003 Prog. Signal Source, 1 mHz-50 MHz, log sweep, rear out	\$1,750.00
TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$900.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$1,250.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's	\$275.00
TEK FG501 1 MHz Function Generator, TM500 series	\$225.00
TEK FG502 11 MHz Function Generator	\$300.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$750.00
PULSE	
BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz	\$750.00
HP 8007B 100 MHz Pulse Generator	\$650.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$600.00
HP 8015A-002 50 MHz Dual Output Pulse Generator, gated burst option	\$750.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$800.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8111A-001 Pulse / Function Generator, 1 Hz-20 MHz; burst option	\$1,200.00
HP 8115A 50 MHz Dual Channel Pulse Generator, HPIB	\$2,750.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series	\$275.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$500.00
WAVETEK 802 50 MHz Pulse Generator	\$300.00

VOLTAGE & CURRENT

VOLTMETERS	
FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter	\$500.00
HP 3478A 5-1/2 digit Multimeter, HPIB	\$700.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$900.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,250.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00
CALIBRATION	
FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,000.00
FLUKE 731B DC Reference Standard	\$400.00
HOLT 11 AC Thermal Converter Set, 0.5-1200 V, 20 Hz-30 MHz	\$1,000.00
VALHALLA 2703 AC Volt. Std., 0-120V/10 Hz-100 kHz; 120-1200V/10 Hz-1 kHz	\$1,750.00
VOLTAGE SOURCES	
HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$850.00
KEITHLEY 228 Programmable Voltage/Current Source	\$2,500.00
CURRENT METERS & SOURCES	
HP 4140B Picoammeter / DC Voltage Source, without test fixture	\$2,000.00

HP 6177C DC Current Source, to 50 V, 500 mA	\$500.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186B DC Current Source, to 300 V, 100 mA	\$300.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance	\$500.00
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance	\$800.00
KEITHLEY 261 Picoampere Source	\$375.00
TEK AM503/A6302/TM501 AC/DC Current Probe System	\$1,000.00
TEK CT-5 -opt.05 High Current Transformer for P6021/A6302, to 1000A	\$300.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$275.00

IMPEDANCE & COMPONENT TEST

L.C.R.	
BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
GR 1689-M 5 digit LCR Meter, 12 Hz-100 kHz	\$1,900.00
HP 4262A-101 3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz test, HPIB	\$1,750.00
STANDARDS	
E.S.I. DB62-11K 6-Decade Resistor, 0-11,111.10 Ohms, 0.01 Ohm res.	\$300.00
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step	\$2,000.00
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1432-U 4-Decade Resistor, 0-111.10 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-G 7-Decade Resistor, 0-111.110 Megohms, 0.1 Ohm res.	\$275.00
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms, 1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-111,100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-N 5-Decade Resistor, 0-11,111 Ohms, 0.1 Ohm resolution	\$200.00
GR 1433-X 6-Decade Resistor, 0-111,111.0 Ohms, 0.1 Ohm res.	\$250.00
GR 1482-series Standard Inductors	\$200.00
VALHALLA 2724A Programmable Resistance Standard, 0-11 Gigohms, GPIB	\$1,250.00
HI & LO RESISTANCE	
HP 4328A Milliohmeter	\$1,200.00
CURVE TRACERS	
TEK 577D2/177 Curve Tracer, with standard test fixture	\$1,850.00
T.D.R.	
TEK 1502-opt.04 Time Domain Reflectometer, 0-2,000 feet, chart recorder	\$1,400.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,400.00

POWER SUPPLIES

SINGLE OUTPUT	
HP 6002A-001 0-60 V/0-10 A/200 Watts max. Autorange Power Supply	\$750.00
HP 6010A Autorange 0-200 V 0-17 A Power Supply, 1000 W max.	\$1,400.00
HP 6011A Autorange 0-20 V 0-120 A Power Supply, 1000 W max.	\$1,400.00
HP 6200B Dual Range Supply, 0-20 V 0-1.5 A/0-40 V 0-750 mA CVCC	\$200.00
HP 6201B 0-20 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6256B 0-10 V 0-20 A CV/CC Power Supply	\$250.00
HP 6260B-027 0-10 V 0-100 A CV/CC Power Supply; 208 VAC line	\$675.00
HP 6261B-027 0-20 V 0-50 A CV/CC Power Supply; 208 VAC line	\$675.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$400.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$500.00
HP 6269B-028 0-40 V 0-50 A CV/CC Power Supply; 230 VAC line	\$900.00
HP 6271B 0-60 V 0-3 A CV/CC Power Supply	\$400.00
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply	\$150.00
HP 6284A 0-20 V 0-3 A CV/CC Power Supply	\$175.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 0-4.0-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6434B 0-40 V 0-25 A CV/CC Power Supply	\$800.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP E3610A Dual Range Power Supply, 0-8 V 0-3 A / 0-15 V 0-2 A	\$175.00
HP E3617A 0-60 V 0-2 A CV/CC Power Supply	\$175.00
KEPCO ABC-1500M 0-1500 V 10 mA CV/CL Power Supply	\$125.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
SORENSEN DCR 20-25B 0-20 V 0-25 A CV/CC Power Supply	\$550.00
SORENSEN DCR 600-0.75B 0-600 V 0-750 mA CV/CC Power Supply	\$600.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$400.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$600.00
TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00
MULTIPLE OUTPUT	
HP 6205C Dual Output Supply, 0-40 V 300 mA or 0-20 V 600 mA	\$300.00

HP 6227B Dual 0-25 V 0-2 A CV/CC Power Supply	\$450.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$450.00
HP 6236B Triple Output Supply, to +/-20 V 0.5 A & 0-6 V 2.5 A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$450.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$450.00
LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$650.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00
MISCELLANEOUS	
ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
ELGAR 1751B/461 AC Power Source, 0-135 VAC, 1750 Watts, fixed freq. osc.	\$2,000.00
HP 59501B HPIB Isolated DAC/Power Supply Programmer	\$175.00
HP 6825A Bipolar Power Supply/Amplifier, +/-20 V 2 A	\$800.00
HP 6827A Bipolar Power Supply/Amplifier, +/-100 V 0.5 A	\$800.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A	\$400.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

TIME & FREQUENCY


UNIVERSAL COUNTERS	
HP 5315A-001 100 MHz/100 nS Universal Counter, TCXO reference option	\$450.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$550.00
HP 5315B 100 MHz/100 nS Universal Counter	\$500.00
HP 5316A 100 MHz/100 nS Universal Counter, HPIB	\$600.00
HP 5316A-001,003 100 MHz/100 nS Univ. Counter, HPIB, TCXO, 1 GHz C-ch.	\$750.00
HP 5316B 100 MHz/100 nS Universal Counter, HPIB	\$750.00
HP 5334A 100 MHz Universal Counter, HPIB	\$200.00
HP 5334A-010,030,050 100 MHz Univ. Counter; OCXO, DVM, 1.3 GHz C-ch., rear in	\$750.00
HP 5334B-010,060 100 MHz Universal Counter, HPIB, OCXO	\$250.00
HP 5335A 200 MHz Universal / Statistical Counter	\$500.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$3,000.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$250.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$400.00
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series	\$950.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series	\$275.00
FREQUENCY COUNTERS	
EIP 575 18 GHz Source Locking Counter, GPIB	\$1,500.00
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5340A 18 GHz Frequency Counter	\$450.00
HP 5342A 18 GHz Frequency Counter	\$500.00
HP 5342A-001,011 18 GHz Frequency Counter, OCXO reference & HPIB	\$600.00
HP 5342A-003 18 GHz Freq. Counter, +22 dBm, -20 dBm dynamic range	\$600.00
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00
TEK DP501 1.3 GHz Prescaler, divide by 16, TM500 series	\$225.00
STANDARDS	
HP 105B Quartz Oscillator, 0.1/1.0/5.0 MHz, battery power	\$1,500.00
HP 5087A-opt.033 Distribution Amplifier; 12 outputs at 10 MHz	\$1,750.00

AUDIO & BASEBAND

SPECTRUM ANALYSIS	
HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,500.00
TEK 7L5/L3/R7603 Spectrum Analyzer, 20 Hz-5 MHz, 10 Hz min. res., w/frame	\$1,500.00
DISTORTION ANALYZERS	
HP 339A Distortion Analyzer, built-in low distortion osc.	\$750.00
HP 8903A-001 Audio Analyzer, 20 Hz-100 kHz; rear panel input	\$1,500.00
HP 8903B-001,013,051 Audio Analyzer, 20 Hz-100 kHz; C-message, CCITT	\$1,750.00
TEK DA4084 Programmable Distortion Analyzer	\$750.00
RMS VOLTMETERS	
FLUKE 8920A True RMS Voltmeter, 180 uV-700 V, 10 Hz-20 MHz	\$450.00
FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz	\$450.00
OSCILLATORS	
HP 209A Sine/Square Wave Generator, 4 Hz-2 MHz, 5 VRMS max.	\$225.00
HP 3336C Synthesizer/Level Generator, 10 Hz-21 MHz	\$1,400.00
TEK SG5010 Programmable Oscillator, 10 Hz-163.8 kHz	\$2,750.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$200.00
MISCELLANEOUS	
HP 461A Amplifier, 20/40 dB, 1 kHz-150 MHz, 0.5 V/50 Ohms	\$125.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$350.00



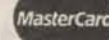90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



KROHN-HITE 3202 Dual HP/LP/BR/BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$450.00
KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$900.00
KROHN-HITE 3750 LP/HP/BR/BR Filter, 0.02 Hz-20 kHz, 6/12/18/24 dB/oct.	\$600.00
KROHN-HITE DCA-10R 10 Watt Amplifier, 20 dB gain, DC-1 MHz, 600-1000 Ohms	\$450.00
ROCKLAND 852 Dual Highpass/ Lowpass Filter, 0.1 Hz-111 kHz	\$900.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series	\$475.00

RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$600.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$1,400.00
HP 8444A-059 Tracking Generator, 0.5-1500 MHz, for 8554, 8568, etc.	\$1,250.00
HP 853A-001 Spectrum Analyzer Display, bench/rack mount config.	\$4,500.00
HP 8565A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res.	\$25,000.00
HP 8566B Spectrum Analyzer, HP calibration certificate	\$7,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$2,500.00
TEK 7L14-039/7603 Spectrum Analyzer, 1 kHz-2.5 GHz, 30 Hz min. res. bw.	\$950.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for Tek 7L12/13/14	\$850.00
TEK TR503 Tracking Generator, 0.1-1800 MHz, for 492/4/5/6	\$1,500.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	

NETWORK ANALYZERS

HP 08748-60010 8748A Reference Plane Extension Cables (set of 6)	\$375.00
HP 08748-60011 8748A-H26 Reference Plane Extension Cables (set of 3)	\$600.00
HP 11650A Network Analyzer Accessory Kit, APC7	\$1,000.00
HP 35676A Reflection/Transmission Test Kit, 5 Hz-200 MHz	\$450.00
HP 8405A Vector Voltmeter, 1-1000 MHz	\$650.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port	\$1,000.00
HP 85021A Directional Bridge, 0.01-18 GHz, APC7 test port	\$1,000.00
HP 85021C Directional Bridge, 0.01-18 GHz, N(f) test port	\$2,000.00
HP 85027A Directional Bridge, APC7 test port, 10 MHz-18 GHz	\$600.00
HP 8502A-H26 Reflection/ Transmission Test Set, 4-2600 MHz	\$1,500.00
HP 85044A Reflection/ Transmission Test Set, 300 kHz-3 GHz	\$3,500.00
HP 85046A S-Parameter Test Set, 300 kHz-3 GHz, for 8753 series	\$2,500.00
HP 8756A Scalar Network Analyzer	\$1,200.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	

SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$2,500.00
FLUKE 6060A/AN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB	\$1,500.00
FLUKE 6062A Synthesized Signal Gen., 0.1-2100 MHz, 10 Hz res., GPIB	\$5,000.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res.	\$4,500.00
GIGATRONICS 600/10-18 Synthesized Source, 10-18 GHz, 1 MHz res., GPIB	\$2,500.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$3,750.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$2,500.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$450.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$3,750.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$1,000.00
HP 8640B-001 Signal Generator, 0.5-512 MHz, AM, FM, var. audio osc.	\$1,750.00
HP 8640B-002.003 Signal Gen., 0.5-1024 MHz, AM, FM, reverse power prot.	\$2,500.00
HP 8656B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., OCXO ref.	\$3,250.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP/IB	\$2,750.00
HP 8660C/86602B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod. w/86635A	\$3,750.00
HP 8660C/86603A-002 Synthesizer, 1-2600 MHz, FM / Phase Mod., w/86635A	\$6,000.00
HP 8672A Synthesized Signal Generator, 2-18 GHz	\$16,500.00
HP 8673C Synthesized Signal Generator, 50 MHz-18.6 GHz	\$12,500.00
HP 8673G-004.008 Synth. CW Signal Generator, 2-26 GHz, >+8 dBm output	\$3,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM, WBFM, Pulse	

SWEEP GENERATORS

HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$1,750.00
HP 83545A RF Plug-in, 5.9-12.4 GHz, +17 dBm levelled	\$400.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$550.00
HP 8620C Sweep Oscillator Frame	\$1,500.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten.	

HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$400.00
HP 86240C RF Plug-in, 3.6-8.6 GHz, +16 dBm levelled	\$700.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86242D-004.008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$500.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$500.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm unlevelled	\$500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$1,750.00
HP 86290A RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled	\$2,250.00
HP 86290C RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled	\$1,250.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$1,500.00
WILTRON 6619A Sweep Generator, 2-8 GHz, +10 dBm levelled	

POWER METERS

ANRITSU MA72B Power Sensor, -20 to +20 dBm, 0.01-18 GHz	\$200.00
ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$2,500.00
BOONTON 4200-01A, 03/8-4A x2 Dual Channel Microwattmeter, w/(2) 1 MHz-7 GHz sensors	\$950.00
BOONTON 42B/41-4B Analog Power Meter, with 1 MHz-12 GHz sensor	\$375.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$500.00
GENERAL MICROWAVE 476/4240A Power Meter & Sensor, 0.01-18 GHz, -35 to +10 dBm	\$300.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 435B/8482B Power Meter, 0 to +43 dBm, 100 kHz-4.2 GHz	\$1,750.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A-002, 022/8481A Power Meter, HP 8477A Power Meter Calibrator, for HP 432 series	\$1,250.00
HP 436A-002, 022/8481A Power Meter, HP 8477A Power Meter Calibrator, for HP 432 series	\$500.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series	\$350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8	\$1,500.00

RF MILLIVOLTMETERS

BOONTON 92B-opt.05 RF Millivoltmeter, 10 kHz-1.2 GHz, 75 Ohms scale	\$500.00
RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$875.00

AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 1W1000 Amplifier, 30 dB gain, 1-1000 MHz, 1 Watt output	\$650.00
BOONTON 82AD-opt.01A Modulation Meter, AM, FM, 10-1200 MHz, GPIB	\$750.00
HP 415E SWR Meter	\$200.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms	\$125.00
HP 8474A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +6 dBm output	\$375.00
HP 8477E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$750.00
HP 8477F Pre-amplifier / Power Amplifier, 0.1-1300 MHz	\$1,200.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$2,500.00
HP 8901B-1.2.3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext. LO	\$3,000.00
HP 8970A Noise Figure Meter	\$5,000.00
HUGHES 1177H02F000 TWT Amplifier, 4.0-8.0 GHz, 10 Watts output	\$1,500.00
MICROWAVE SEMI-CORP. MC5112 Noise Source, 25.5 dB ENR, 1.0-12.4 GHz, N(m), +28 VDC	\$175.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$5,000.00

COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out	\$450.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
CONTINENTAL MW. RAE28-K-M WR28 x K(m) Endfire Adapter	\$225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$125.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
GR 900-Q GR900 14mm Inter-series Adapters	\$125.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33321K Programmable Step Atten., 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,200.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 778D Dual Dir. Coupler, 20 dB, 100-2000 MHz, N test port	\$450.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$150.00
HP 8470B Crystal Detector, 10 MHz-18 GHz, neg. pol., APC7	\$250.00
HP 8472A Crystal Detector, 10 MHz-18 GHz, neg. pol., SMA	\$150.00
HP 8472B Low Barrier Schottky Det., 10 MHz-18 GHz, neg. pol., SMA	\$200.00
HP 8494A-001 Step Attenuator, 0-11 dB, DC-4 GHz, N(f)	\$350.00
HP 8494B-002 Step Attenuator, 0-11 dB, DC-18 GHz, SMA(f)	\$450.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8495G-002 Programmable Step Attenuator, 0-70 dB, DC-4 GHz, SMA	\$300.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA	\$400.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K281C-012 WR42 x APC3.5(m) Adapter	\$300.00

HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz	\$2,900.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,000.00
HP R532A WR28 Frequency Meter, 26.5-40 GHz	\$500.00
HP R752A WR28 Directional Coupler, 3 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$900.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$900.00
HUGHES 45721H-1000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$900.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$400.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz	\$800.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$600.00
HUGHES 47323H-1211 WR19 Flat Broadband Detector, negative, 40-60 GHz	\$650.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$375.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m/f) "NEW"	\$40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
MINI-CIRCUITS ZHL-42 Amplifier, 30 dB gain, 0.7-4.2 GHz, +28 dBm, 15V, SMA	\$400.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$300.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 368BNM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4245-10 Directional Coupler, 10 dB, 4-12 GHz, SMA(f)	\$100.00
NARDA 4799 Level Set Attenuator, 0-15 dB, 4-18 GHz, SMA(f)	\$135.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$135.00
NARDA 769-30 30 dB Attenuator, 150 Watts, DC-6 GHz, N	\$275.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
SPACEK LABS K-2X Frequency Doubler, 9.0-13.25 GHz in / 18.0-26.5 GHz out	\$350.00
SPACEK LABS KA-3X Frequency Tripler, 8.83-13.33 GHz in / 26.5-40.0 GHz out	\$350.00
TRANSCO 705C90100 Latching DPDT Transfer Switch, DC-26.5 GHz, 28 V	\$150.00
TRG B528 WR22 Direct Reading Phase Shifter, 0-360 deg., 33-50 GHz	\$1,250.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHEL 1515 Power Divider, 2-Way, DC-18 GHz, SMA(m/f)	\$125.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00

COMMUNICATIONS

HP 3762A/3763A BER Test System, 1 kHz-150 MHz	\$1,250.00
HP 4935A-003 Transmission Test Set, 20 Hz-110 kHz, battery power	\$600.00
HP 54010A HP1B Bus Analyzer	\$700.00
TEK 1410R NTSC Gen., w/SPG2 sync. generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen., w/SPG12 sync; TSG11 color bars; TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/ SPG12, TSG11, TSG11, TSG13, TSG15, TSG16	\$1,400.00
TEK 1420 NTSC Vectorscope	\$600.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

MISCELLANEOUS

P.A.R. 5206-95.98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
P.A.R. 5209 Lock-in Amp., 0.5 Hz-120 kHz, 130 dB dynamic reserve	\$2,000.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$600.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$275.00

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
QUICKLY ... AT REASONABLE PRICES.

B&K 3020, Sweep/Function Generator, 2MHz (Sine, Square, Triangle).....	\$125
ELP 545, Microwave Counter 19GHz.....	\$500
ESI DP1311, Variable Resistor, 100K max 1K/Step.....	\$75
ESI RV726, Decade Voltage Divider.....	\$275
Fuke 3328, DC Voltage Standard.....	\$350
Fuke 335A, DC Voltage Standard.....	\$275
Fuke 382A, Voltage/Current Calibrator.....	\$400
Fuke 540B, Transfer Standard w/A5-2 Voltage Plug-in.....	\$475
Fuke 760A, Meter Calibrator.....	\$300
Fuke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fuke 845AR, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fuke 893A, AC/DC Differential Voltmeter 0 to 1100 Volts, AC/DC, 0.1%DC, 0.5%AC, 1uV Resolution.....	\$75
Fuke 3330B, Constant Current/Voltage Calibrator.....	\$325
Fuke 5100B, Multifunction Calibrator, Opt. 0305.....	\$3,250
Fuke 5100B, Multifunction Calibrator.....	\$2,700
Fuke 5200A, Programmable AC Calibrator.....	\$1,000
Fuke 5215A, Precision Power Amp.....	\$900
Fuke 6011A, Synthesized Signal Generator, 10Hz-11MHz (7-digit).....	\$350
Fuke 6060B, Synthesized Signal Generator 10KHz-105MHz.....	\$1,600
Fuke 6070A, Synthesized RF Signal Generator 200KHz-520MHz.....	\$1,400
Fuke 8000A, DMM 3-1/2 Digit.....	\$50
Fuke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fuke 8050A, DMM 4-1/2 Digit w/o Battery Pack.....	\$145
Fuke 8520A, DMM 5-1/2 Digit.....	\$275
Fuke 8600A, DMM 4-1/2 Digit w/o Battery Pack.....	\$100
Fuke 8600A, DMM 5-1/2 Digit.....	\$125

INVENTORY REDUCTION SALE PRICES SLASHED UP TO 50%

Fuke 9010A, Micro System Troubleshooter.....	\$375
Fuke 93, Scopemeter (unused).....	\$800
Gould K105-D, Logic Analyzer w/4 Probe Pods.....	\$300
HP 141T, Spectrum Analyzer Mainframe.....	\$475
HP 141T, Spectrum Analyzer w/8552A/8553B, 1KHz-110MHz.....	\$1,000
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8554A, 20Hz-300KHz.....	\$1,100
HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz.....	\$1,700
HP 141T, Spectrum Analyzer w/8552B/8555A, 10MHz-18GHz.....	\$1,900
HP 180TR, Scope Mainframe.....	\$250
HP 204B, Oscillator, 5Hz-1.2MHz, 5VRMS.....	\$100
HP 204C, Oscillator, 5Hz-1.2MHz, 5VRMS.....	\$125
HP 214A, Pulse Generator, 0.8V-100V.....	\$200
HP 334A, Distortion Analyzer.....	\$275
HP 350D, Attenuator.....	\$75
HP 400EL, AC Voltmeter, 10Hz-10MHz.....	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V.....	\$175
HP 415E, SWR Meter.....	\$100
HP 4276A, LCZ Meter.....	\$1,700
HP 432A, Power Meter w/Cable/8478, 0.1-18GHz Sensor.....	\$350
HP 432A, Power Meter w/o Cable/Sensor.....	\$150
HP 435A, Power Meter w/o Sensor/Cable.....	\$100
HP 651B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 652B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator.....	\$195
HP 1630D, Logic Analyzer w/pods.....	\$550
HP 3312A, Function Generator, 1Hz-13MHz.....	\$490
HP 3325A, Programmable Frequency Synthesizer 1Hz-32MHz.....	\$800
HP 3330B, Automatic Synthesizer, 20Hz-13MHz.....	\$295
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V.....	\$125
HP 3403C, True RMS Meter, AC/DC/0.8 100MHz.....	\$275
HP 3406A, RF Voltmeter, 50uV-3V, 1.2GHz.....	\$200
HP 3455A, DMM 5-1/2 Digit.....	\$250
HP 3456A, DMM 6-1/2 Digit.....	\$255
HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function.....	\$175
HP 3575A, Digital Phase Gain Meter.....	\$500
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout.....	\$850
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, Mechanical.....	\$500
HP 3581A, Wave Analyzer, 15Hz-50KHz.....	\$300
HP 3770A, Amplitude/Delay Distortion Analyzer.....	\$300
HP 3779B, Primary MPX Analyzer.....	\$500
HP 3781B, Pattern Generator.....	\$250
HP 332A, LCR Meter.....	\$250
HP 5316A, Counter, 100MHz, HP1B.....	\$350
HP 5328A, Counter, 100MHz w/DVM Opt. 021.....	\$200
HP 5328A, Counter, 500MHz.....	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven.....	\$500
HP 5340A, Counter, 18GHz (mixie).....	\$600
HP 5345A, Counter, 500MHz.....	\$450
HP 5345A, Counter, 500MHz, HP1B.....	\$650
HP 59307A, VHF Switch.....	\$100
HP 6112A, Power Supply, 40V @ .5A (metered).....	\$150
HP 6202B, Power Supply, 40V @ .75A (metered).....	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered).....	\$150
HP 6205B, Power Supply (dual), 0-40V @ .3A, 0-20V @ .8A (metered).....	\$175
HP 6206B, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 6253A, Power Supply (dual), 0-25V @ 3A (metered).....	\$175
HP 6260B, Power Supply, 10V @ 100A (metered).....	\$300
HP 6265B, Power Supply, 40V @ 3A (metered).....	\$200
HP 6266A, Power Supply, 40V @ 6A (metered).....	\$200
HP 6289A, Power Supply, 0-40V @ 1.5A (metered).....	\$175
HP 6294A, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$125
HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$200
HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$300
HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator (1GHz) w/8093A Output Amp w/15401A & 15400A.....	\$1,000
HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$700
HP 8180A, Data Generator.....	\$350

- 60-DAY WARRANTY
- 10-DAY RIGHT OF RETURN
- SATISFACTION GUARANTEED

Newsbytes

Listen to Your E-Mail Instead of Reading It!

Sunnyvale, CA — 4Developers LLC has released Talking E-Mail v. 1.2, a Windows 98/95/NT4 program that notifies you when you've received an E-Mail, and reads it to you. Using nothing more than your e-mail account and sound card, Talking E-Mail's easy-to-understand voice will read aloud your incoming E-Mails, whether they're in plain text, HTML, or RTF formats.

While there are a number of programs that let computers multi-task, Talking E-Mail lets people multi-task. Without interfering with your other work, Talking E-Mail will talk to you, letting you know who is trying to contact you, and what they have to say. You'll hear immediately if your incoming E-Mail is important enough for you to interrupt what you're doing, or if you can respond to it routinely later.

When an E-Mail message arrives, an animated cartoon character pops up on the screen and starts reading the message. Talking E-Mail is highly customizable, allowing you to specify if you want to hear who sent the message, its subject, and how many lines of the message should be read. You can stop the cartoon character at any time, or keep listening while you are working. You can even launch your default e-mail program and reply to the message.

Talking E-Mail's rules system allows you to specify the behavior of the character and what he will say when a message arrives from a specific individual. A variety of animations, sounds, and other settings are available, adding fun and practicality. Talking E-Mail uses Microsoft Agent technology™ to achieve its natural-sounding, understandable voice quality.

In addition to its entertainment value, Talking E-Mail has some very practical uses. You can schedule Talking E-Mail to check your inbox at any time interval, and have the program read your messages aloud, ensuring that critical E-Mails are brought to your attention immediately. It automatically checks for your incoming mail, and makes it easy to hear from your friends and colleagues, without having to stop other activities.

Talking E-Mail costs \$14.95 and can be ordered online from <http://www.4developers.com/talkmail/>. Site licenses are available. You can also download a trial version of Talking E-Mail from <http://www.4developers.com/talkmail/>.

For more information, contact:

4Developers LLC
912 E. Evelyn Avenue
Sunnyvale, CA 94086
E-Mail: sales@4developers.com

Mainstay Releases JustEdit™ Browser-Based Text Editor Speeds Up Web Page Edits

Camarillo, CA — Mainstay today began shipping JustEdit™, a quick and painless way to edit web pages anytime, anywhere, using only a web browser. JustEdit is a Java applet that need only be included in a single web page of a site. A user simply brings up the JustEdit page, enters the path to any web page to edit and clicks "Open." A text editor window opens — displaying HTML code, ready for editing. After making changes, the user clicks "Save" and their web page is modified. JustEdit works on any website and requires no server-side applications, scripts, CGIs, or plug-ins.


JustEdit enables the user to correct a typo, update a headline, price, or date, and even correct a broken or changed link, on the fly, right in a browser. Using JustEdit, there's no need to start an FTP application, find a source file, or download the file from the web, start a web page editor, make the changes, save the changes, then re-upload the file.

Web pages can be changed from anywhere in the world using nothing more than a web browser. JustEdit eliminates the time wasted "round-tripping" web files back and forth to the web server, or needlessly searching for HTML files on a local hard disk. It also eliminates the frantic call back to the office, trying to talk someone through making a simple change.

JustEdit maintains the same level of security enjoyed by web pages today. In fact, JustEdit can be thought of as a transparent FTP client embedded in a web page. Like all FTP clients, both a name and a password are necessary for read/write access to web pages.

JustEdit is now available directly from Mainstay. The special introductory price is \$49.95. JustEdit can be purchased with immediate electronic delivery at: <http://www.mstay.com>. JustEdit works with Windows 95/98/NT, Macintosh and Unix. A free promotional version is also available from www.mstay.com and most popular download sites.

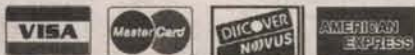Mainstay
591-A Constitution Avenue
Camarillo, CA 93012
<http://www.mstay.com>



Build an Inexpensive Whole-House Temperature/Humidity Monitoring System

Part 1

by Mike Keryan

Transmit data from up to eight monitoring stations on your house's power line, and receive the information on your PC.

In this article, you will see how to build an inexpensive circuit that measures temperatures and humidities. The sensor circuitry is unique in that it requires no calibration whatsoever. It is controlled by a PIC CPU chip that spends most of its time sleeping. Once every five minutes or so, it wakes up and samples the air, and transmits the data onto the house power line using an inexpensive X10 interface. You can place up to eight of these monitoring systems throughout your house, even in your attic and on your screened porch. Somewhere in your house, a PC — connected to an X10 receiver via RS-232 — collects and reports the data. The monitoring software can be extended to make decisions based on the data.

The THX10 remote monitoring system described in this article is inexpensive, accurate, and flexible. You can buy sensors that sample and report accurate temperature and humidity data, but they will probably set you back over \$100.00 apiece. And even if you had the money to buy enough of them to monitor most of the rooms in your house, and to purchase an expensive master monitoring station, you would still have to run a bunch of wires around your house to connect everything.

Or, you can build one or more of

the sensor units described in this article. You can pick up the X10 interface equipment at your local RadioShack. With THX10, you won't have to calibrate anything or string up any wires between rooms. And you can customize the monitor software yourself, because it is written in BASIC.

In Part 1 of this two-part article, we'll talk a little about humidity, describe how the circuit works, and how to build the sensor circuitry. In Part 2, we'll show you how to


connect the sensor circuitry to an X10 interface, and how the X10 receiver and software works.

Why Bother to Measure Humidity?


Ever since we moved from up North to South Carolina several years

ago, my family and I have not been able to adjust to the temperature. Not outside; the temperature outside is nearly always warm to hot and your body seems to become accustomed to that. The problem is inside, where the windows and doors are kept closed and the environment is supposedly controlled. Temperature fluctuations are kept to a minimum thanks to the heating and air-conditioning systems and programmable thermostats. However, it almost never feels ideal. Most of the time, it feels either too warm or too cool, even though the thermostats both upstairs and downstairs swear that the temperature hasn't changed. What they don't tell us anything about is the humidity.

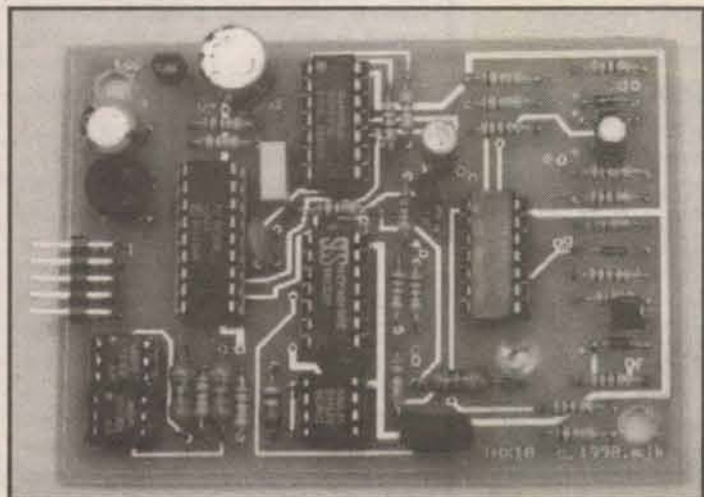Our HVAC systems work very hard to maintain a constant temperature, because our bodies are greatly affected by the temperature. However, human bodies, as well as many other living and non-living things, are also greatly affected by the humidity. Our natural cooling system is dependent on our sweat



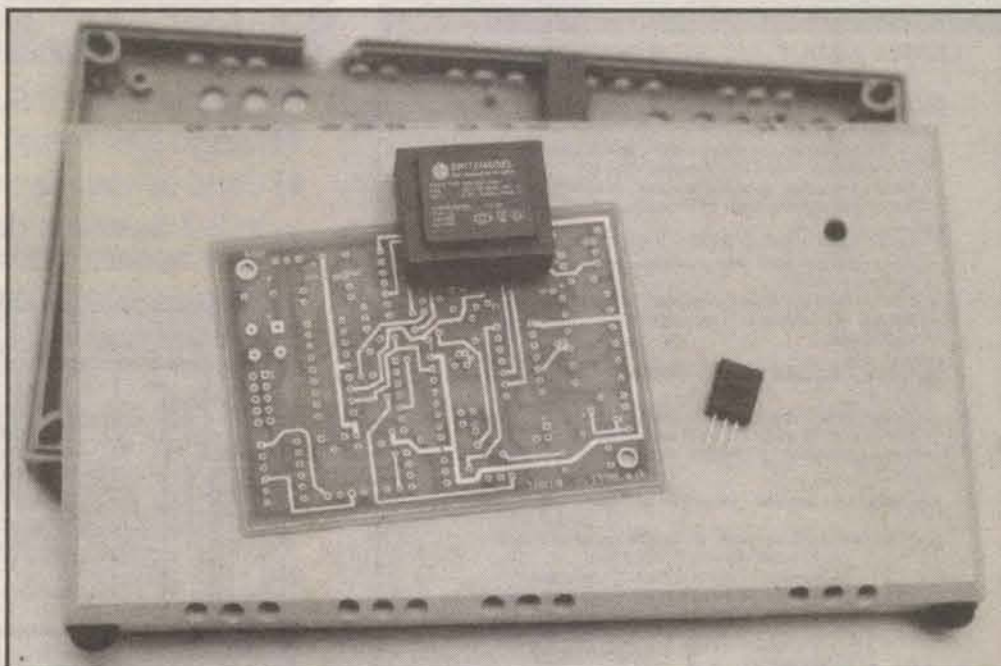The THX10 circuit board with components installed.



The compact 12-volt transformer, THX10 circuit board, humidity sensor, and plastic enclosure. Note the many holes drilled into the enclosure for ventilation.

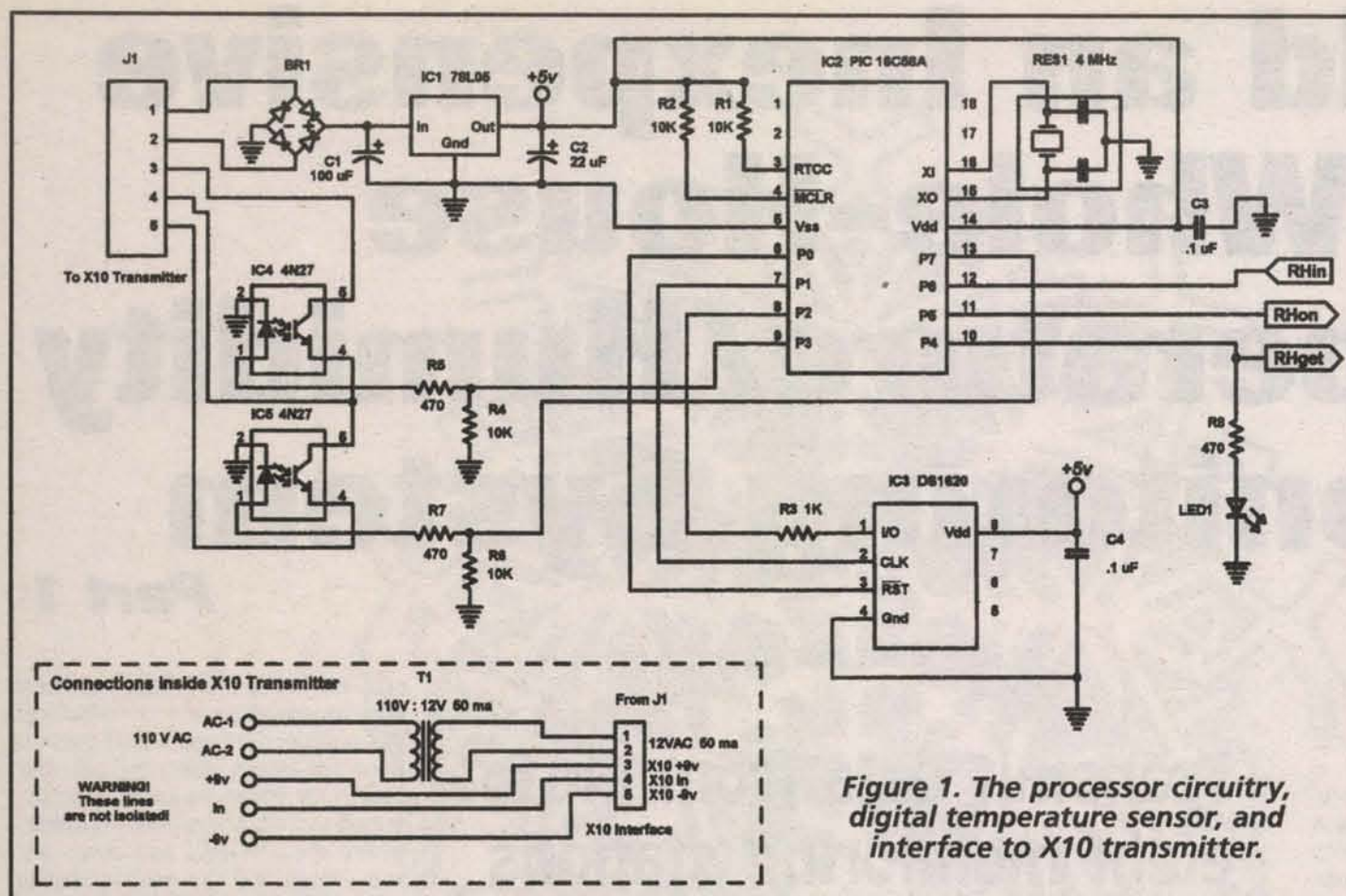


Figure 1. The processor circuitry, digital temperature sensor, and interface to X10 transmitter.

being able to evaporate. If the humidity is very high, the moisture we secrete out of our sweat glands tends to remain on our skin. There is no significant gradient between the moisture on our moist skin to the moist atmosphere, so we experience no cooling effect.

On the other hand, when the humidity is very low, moisture on our skin evaporates very quickly into the relatively moisture-free atmosphere. When this evaporation takes place, a certain amount of heat is given up

from our skin to the environment, and our skin feels cool. When our skin feels cool, we feel cool.

Air at any specific temperature can only hold a finite amount of water vapor. When the air is forced to hold as much moisture as possible, it is said to be saturated. At higher temperatures, the air can hold larger amounts of water vapor, in fact, much larger amounts — it is an exponential relationship. Relative Humidity is defined as the amount of water vapor that is currently present

in the air, divided by the maximum that the air can hold at that same temperature. Therefore, there is a lot more moisture in the air at 90° F, 90% RH, than at 80° F, 90% RH.

It Ain't the Heat, It's the Humidity!

We can generate what is known as the heat index, using both temperature and humidity. The heat index is probably a better indicator of how we feel than either temperature

or humidity alone. The heat index accounts for the ability of moisture to evaporate (low humidity) or to not evaporate (high humidity). Table 1 shows the heat index for temperatures and humidities in 10°/10% increments. Note the example above: 80° F, 90% RH feels like 88°, but 90° F, 90% RH feels like a whopping 122°!

Prolonged exposure and physical activity at a heat index of greater than 90 can cause heat exhaustion, while an index greater than 100 can lead to heat stroke. While the temperatures in our homes are not likely in this high a range, you can see from the chart that humidity does have an affect even at room temperatures, in the 60-90° F range. High humidities in the 80-90° F range make it feel five or more degrees warmer, while low humidities in the 60-70° F range make it feel five or more degrees cooler than a thermostat would say.

So why don't our thermostats measure heat index, rather than just temperature? One big reason is that monitoring and detecting water vapor is much more difficult than measuring other parameters, such as temperature, pressure, etc. Humidity sensors tend to have limited lifetimes, most are highly non-linear and highly temperature-dependent, and they typically have very high part-to-part tolerances, meaning they must be calibrated.

A typical calibration involves placing certain salt solutions in closed containers to give known humidity levels. This is not practical for most manufacturers, and probably nearly impossible for most home tinkerers.

The NH-03 Humidity Sensor

The circuitry in this article is designed around a humidity sensor distributed by Figaro USA, Inc. The NH-03 sensor contains two relative humidity sensitive elements, made from a stable high polymer impregnated in porous ceramic. The sensor also contains two printed NTC thermistors on an alumina ceramic substrate.

The network of humidity and temperature sensors provide temperature compensation, as well as a linear output. The sensor is provided in a small (10 mm x 12 mm x 4 mm) plastic package with three leads, spaced 0.1 inch apart. Figaro states the overall long-term accuracy of the sensor to be ± 10% for 0-40° C (50-104° F) and 30-80% RH, but when used in the self-calibrating circuit (see below), deviations greater than about 3% RH haven't been detected.

Humidity measurement is complicated by the fact that any DC volt-

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS

EASY PIC'n - Beginner

\$29.95

- Programming techniques
- Instruction set, addressing modes, bit manipulation, subroutines, loops, lookup tables, interrupts
- Using a text editor, using an assembler, using MPLAB
- Timing and counting (timer 0), interfacing, I/O conversion

PIC'n Up The Pace - Intermediate

\$34.95

- Serial communication - PIC to peripheral chips and PIC-to-PIC
- Serial EEPROMS
- LCD interface and scanning keypads
- D/A and A/D conversion - several methods
- Math routines

PIC'n Techniques - Intermediate

\$34.95

- 8-pin PICs
- Timer 1, timer 2 and the capture/compare/PWM (CCP) module
- Talking to a PIC with a PC using a terminal program
- Test equipment and data logger experiments

See Table Of Contents: <http://www.sq-1.com>

+ \$4 s/h in US for 1 book, \$5 for 2 books, \$8 for 3 books
VISA, MC, AMEX, MO, Check
CA residents please add 7.25% CA sales tax
PIC and MPLAB are trademarks of Microchip Technology Inc.


SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451
Voice (707) 279-8881 FAX (707) 279-8883
<http://www.sq-1.com>
E-Mail sqone@pacific.net

PCB LAYOUT

Software For Win95 - FREE

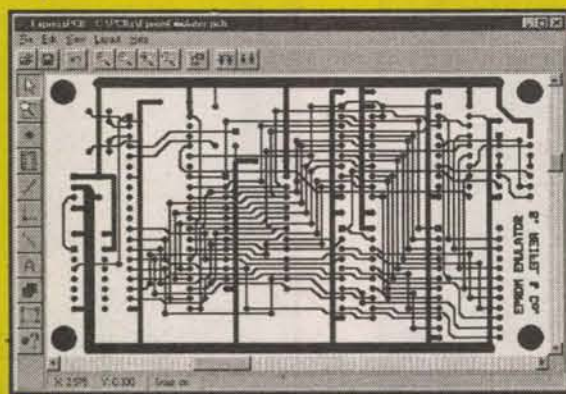- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

age applied to the sensor will degrade the humidity-sensitive elements. In a typical humidity measuring operation, an AC voltage of precisely 1 volt, 1 KHz is supplied across pins 1 and 3 of the sensor. The output is an AC voltage across pins 1 and 2. This AC output voltage is nearly a linear relationship with the % Relative Humidity.

Due to the sensor network, the output is basically independent of fluctuations in temperature and frequency. However, the output is very sensitive to the actual level of input AC voltage, as well as our ability to accurately measure small AC voltages.

A self-calibration technique is used to overcome the problems with the small AC voltages. Circuitry is provided to change the output AC voltage to a DC voltage and then translate the DC voltage to a pulse width. The PIC CPU chip is able to make precise timing measurements of the pulse width.

The measurement process is done twice; the first time measuring the results of the input voltage, the second time measuring the results of the output voltage. Both pulse widths are directly proportional to the corresponding AC voltages: the input AC voltage, a nominal one volt, and the output AC voltage which is a measure of the Relative Humidity and can vary anywhere between 0 volt to 1 volt. Dividing the pulse widths gives the same result as dividing the voltages. This software technique eliminates the need for calibration or for precise AC voltage generation and measurement equipment.

The DS1620 Temperature Sensor

If you read a lot of electronic and PIC literature and magazines, you've probably seen this temperature sensor made by Dallas Semiconductor described before. It is a truly digital chip; it measures the temperature by means of internal oscillators, and outputs data in digital format. It is accurate, stable, and is very easy to interface to a PIC chip. Since it requires no calibration, it is the perfect counterpart for the self-calibrating humidity circuit. Dallas claims the accuracy of the chip to be $\pm 0.5^\circ\text{C}$ (about 1.0°F).

The CPU

PIC microprocessor chips are turning up everywhere nowadays. They are becoming as common as 555 timer chips. The PIC16C58A from Microchip used in this THX10 circuit communicates with the

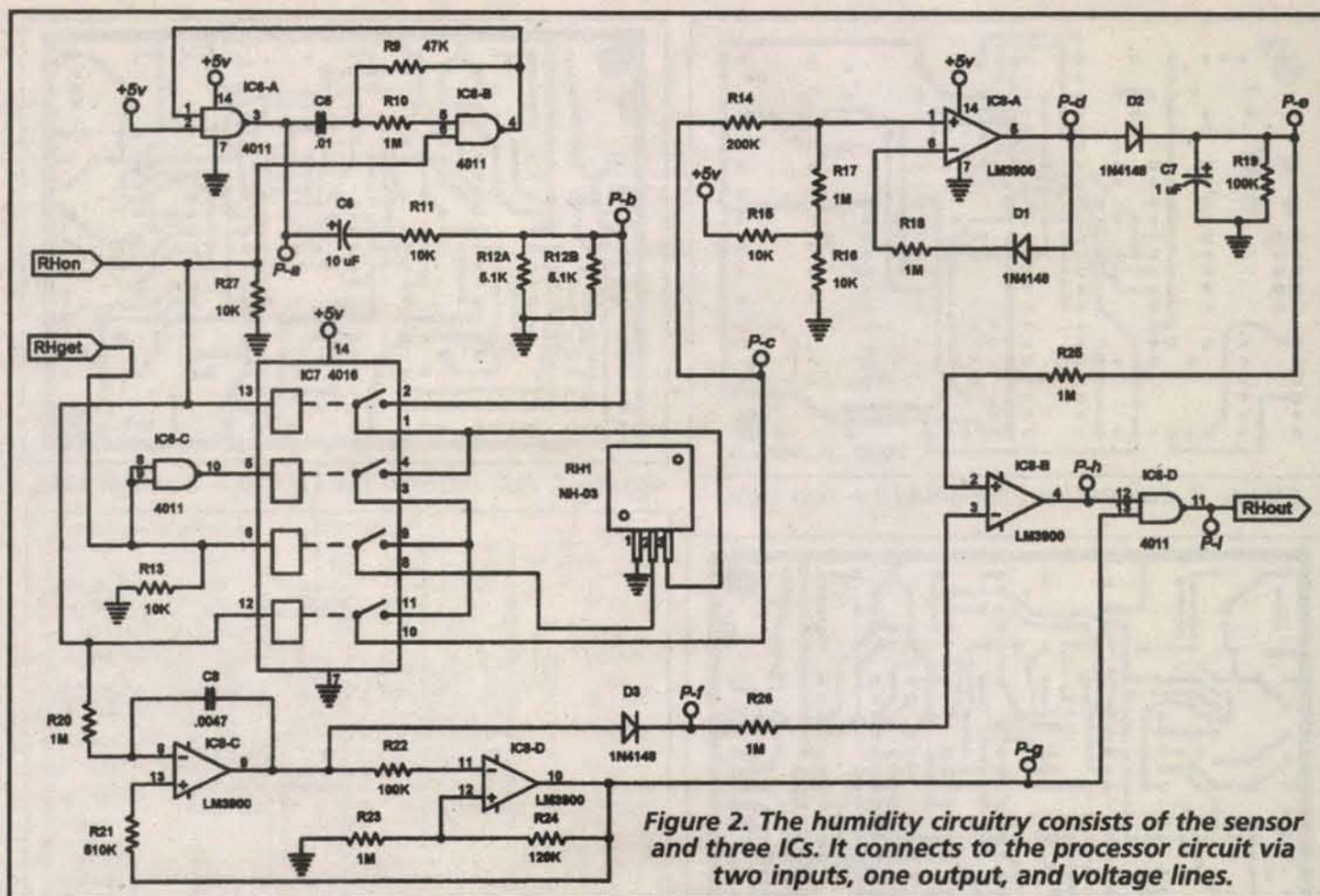


Figure 2. The humidity circuitry consists of the sensor and three ICs. It connects to the processor circuit via two inputs, one output, and voltage lines.

humidity circuitry and with the temperature chip, and does some calculations to convert the data to $^\circ\text{F}$ and % RH. It then sends the data to an X10 transmitter as eight-bit binary sequences, and it communicates the findings on a single LED, used mainly for debugging.

Although any one of these tasks would not be a big problem, developing a circuit built up from discrete logic ICs to handle ALL these tasks would be impractical. The PIC chip

does it all easily, and spends more than 90% of the time in a low power sleep mode.

The Processor Circuit, Temperature Sensor, and Interface

Refer to Figure 1 for details of the processor circuit. The circuit receives a 12-volt AC power input at pins 1 and 2 of J1. BR1 rectifies it, producing a DC voltage that is

smoothed by C1, regulated by IC1, and filtered by C2, producing a 5-volt DC power supply. The total circuit draws at most 20 mA or so (most of the time much less), so the regulator runs cool. IC2 — the PIC CPU — receives the 5-volt supply with an additional capacitor, C3, to reduce high-frequency fluctuations.

RES1 connects to pins 15 and 16 of IC2 to provide a 4-MHz clock pulse. Unused pins 3 and 4 are pulled high by R1 and R2 to avoid

ATTENTION DEALERS/DISTRIBUTORS

BUY DIRECT FROM THE MANUFACTURER

THESE AND OTHER VIDEO SECURITY PRODUCTS NOW AVAILABLE!!! (DEALERS/DIST. ONLY) Minimum Order.



	Qty 5	Qty 10	Qty 20	Qty 50+
CCD Cameras				
B&W Board	\$57	\$52	\$47	Call!
B&W Board/sound	\$62	\$57	\$52	Call!
B&W Mini	\$65	\$60	\$55	Call!
Color - Mini	\$150	\$142	\$135	Call!

*B&W CCDs use Sansone Chips. Color CCDs use Sony.

Guardian Eye

CCD Camera Hidden Inside a "Magnavox" Clock

	Qty 5	Qty 10	Qty 20	Qty 50+
CCD Clock				
B&W Wired	\$144	\$129	\$114	Call!
B&W Wireless	\$289	\$264	\$248	Call!
Color Wired	\$234	\$218	\$199	Call!
Color Wireless	\$387	\$362	\$345	Call!

Wireless use 2.4GHz standard transmitters and receivers.

Call ATN Today for the Best Prices and Quality Security Products.

American Technologies Network Corp.
20 S. Linden Ave. #1B
S. San Francisco, CA 94080
www.atncorp.com


1(800)910-2862
1(650)875-0130
fax: 1(650)875-0129
sales@atncorp.com

Write in 69 on Reader Service Card.

MORE POWER!

68HC11, 80C51 & 80C166

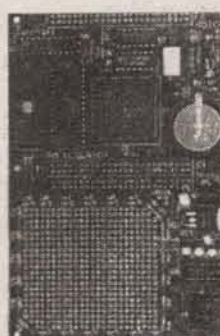AM Research supports over 30 of the most popular Embedded controllers with both hardware and software.



- ✓ More Microcontrollers
- ✓ Faster Hardware.
- ✓ Faster Software.
- ✓ More Productive.
- ✓ More Tools & Utilities.
- ✓ IIC Peripherals.
- ✓ Single Chip Capable.
- ✓ Outstanding Support.
- ✓ Custom designs.

Call or email for a free full line brochure





Orders (800) 949-8051
Info (916) 652-7472
fax (916) 652-6642
www.amresearch.com

AM Research, Inc.
PO Box 43
Loomis, CA 95650

The Embedded Controller Experts

Write in 68 on Reader Service Card.

February 1999 35

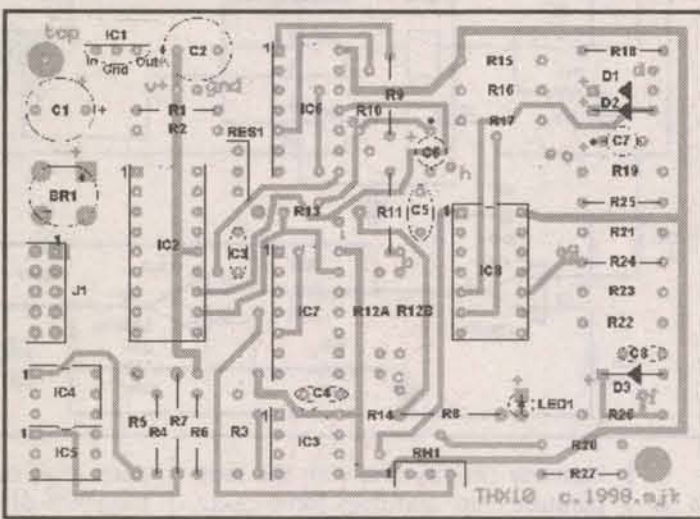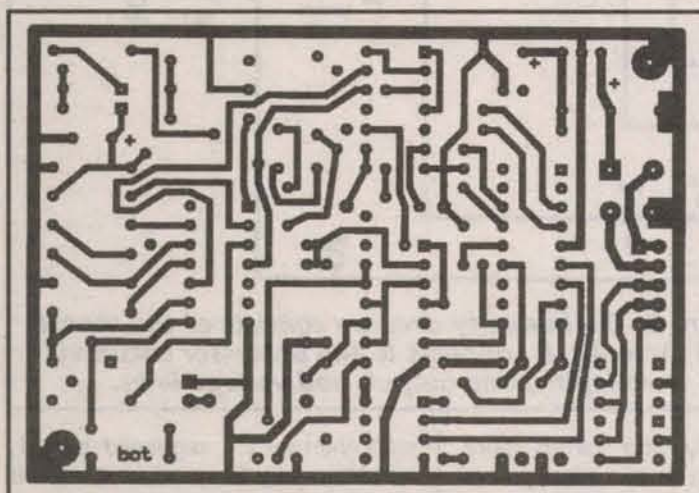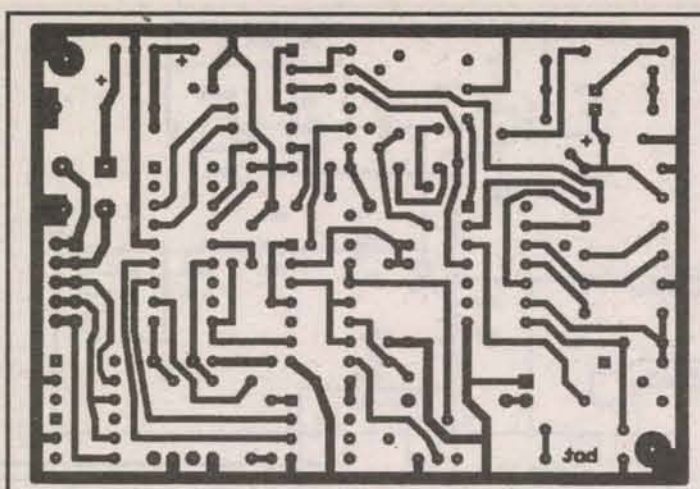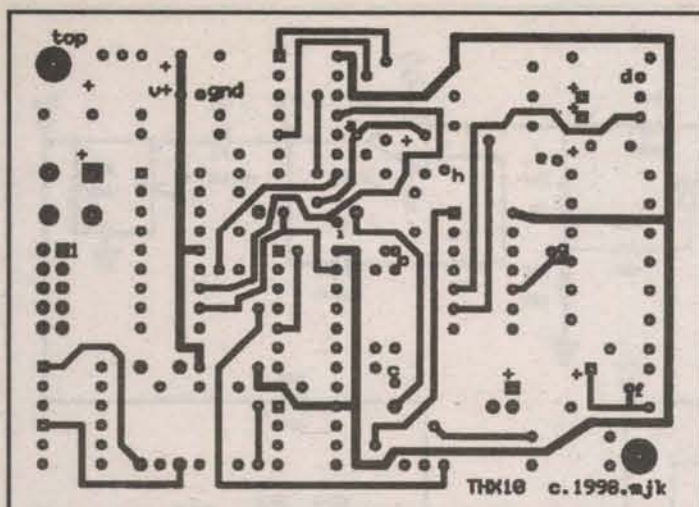

spurious signals that could cause strange reactions. IC2, a programmed Microchip 16C58A PIC chip, uses the other lines to communicate with the temperature sensor, the humidity circuitry, and the X10 interface.

Pins 6, 7, and 8 are used to communicate to IC3, a Dallas DS1620 thermometer IC. This chip contains a built-in temperature sensor and digital circuitry that outputs the data in 0.5° C increments; this precision is approx. 1° F. Typical error for a normal environment (about 0 to 120° F) is well within the 1° F resolution.

C4 is an additional filter capacitor to reduce spurious high-frequency noise. Data is transmitted to/from input/output pin 1 of IC3, while pins 2 and 3 are inputs from IC2. More details on the DS1620 can be obtained from Dallas Semiconductor Corp.

Pins 10, 11, and 12 of IC2 are used to communicate to the humidity circuitry (more on this later). Pin 10 does double-duty by also driving LED1 through current limiting resistor R8. LED1 is used for monitoring and debugging, and as a human

```
' Program T_H_X10.BAS written in PBASIC for BASIC STAMP I  
' For programmed PIC16C58A-04, email mkeryan@pobox.com  
' Copyright 1998 Mike Keryan
```

' Interfaces:	input Dallas DS1620 Digital Temperature IC
	input Figaro NH-03 Humidity sensor and associated
	output single Led, used to display data
	output two relays, one for on-bit, one for off-bit
	these control an X-10 control interface

The system grabs either temperature (from a digital temperature IC) or humidity (from a linear humidity-dependent resistive sensor) alternately every 5 minutes. Each one is updated every 10 minutes. The display is a single Led which blinks the appropriate number of times to count out each digit of the temperature or humid. data. Captured data is output to the X-10 controller as a series of 8 on or off bits. Temperature data is in deg. F., Humidity sent via X-10 is % relative humidity, with the last bit set (+128), so that receiving program monitoring X-10 line can tell which is which.

input/output pins

SYMBOL RST = 0	PIN0 is reset for DS1620
SYMBOL CLK = 1	PIN1 is clock for DS1620
SYMBOL DQn = 2	PIN2 is data i/o for DS1620
SYMBOL DQp = pin2	PIN2 for inputting, outputting a bit
SYMBOL RelayOn = 3	PIN3 is relay output for on state
SYMBOL Led = 4	PIN4 is output to Led
SYMBOL RHget = 4	PIN4 also used to switch between: 0 = applied voltage measured 1 = response voltage measured
SYMBOL RHon = 5	PIN5 high activates RH circuitry
SYMBOL RHin = 6	PIN6 is input pulse for RH
SYMBOL RelayOff = 7	PIN7 is relay output for off state

_____variable storage

SYMBOL DSout = W0	data to DS1620; W0 overlaps B0, B1,
SYMBOL DSin = W0	data from DS1620; and BIT0-BIT7,
SYMBOL DSDat = W0	data in DS format; and BIT8-BIT15
SYMBOL BitOut = BIT0	output data one bit at a time
SYMBOL BitIn = BIT8	input data one bit at a time
SYMBOL SignBit = BIT8	data is negative (deg C) when this bit is set

```

SYMBOL CountSec = B4 ' 8 bit counter for 2.3 second increments
SYMBOL WhichOne = B5 ' 1 = temperature, 0 = humidity
SYMBOL HumiData = B6 ' humidity, % RH
SYMBOL TempData = B6 ' temperature, deg F
SYMBOL LedData = B6 ' data to pulse out on LED
SYMBOL Unused = B7
SYMBOL DataOut = B8 ' data to send to relays

```

SYMBOL Pulses = B9	' 8 bit register for counting pulses
SYMBOL I = B10	' index for loop
SYMBOL J = B11	' temporary variable
SYMBOL ABit = B11	' bit sent to relays
SYMBOL V0 = W1	' pulse width for applied voltage to hum. sensor
	' W1 overlaps B2 and B3
SYMBOL V1 = W6	' pulse width for response voltage from hum. sensor
	' W6 overlaps B12, B13 which are used during
GOSUBS	

GOSUBS

SYMBOL WConfig = \$0C	' code to write to configuration register
SYMBOL CPU = %10	' configuration bit for thermometer mode
SYMBOL OneShot = %01	' configuration bit for one conversion only
SYMBOL StartC = \$EE	' code to start conversion
SYMBOL RTemp = \$AA	' code to read temperature out of DS1620

initialize the DS1620 chip's EEPROM at power-up	
LOW RST	' deactivate DS1620
HIGH CLK	' initially high per specs
PAUSE 2000	' let everything stabilize
DSout = WConfig	' write configuration
GOSUB ShiftOut	' to DS1620
DSout = CPU + OneShot	' thermometer in 1-shot mode
GOSUB ShiftOut	' to DS1620
LOW RST	' deactivate DS1620
Pulses = 3	' send 3 long blinks
GOSUB BlinkLed	' to tell its on and working

'_____continually loop between here and end

```

Loop:  WhichOne = WhichOne + 1 & 1      ' counts 1, 0, 1, 0, 1, ...
      IF WhichOne = 1 THEN Temper

```

```

1_____get humidity data when WhichOne = 0

```

Humid:		
HIGH RHon		' turn on humidity circuitry
PAUSE 2000		' wait till stable
PULSIN RHin, 0, V0		' get pulse width for V0 (applied)
IF V0 < 10 THEN Humid		' eliminate glitches
HIGH RHget		' switch from applied to response
PAUSE 1000		' wait till stable
PULSIN RHin, 0, V1		' get pulse width for V1 (response)
LOW RHget		' shut down V1 output
LOW RHon		' shut down humidity circuit
HumiData = 140 * V1 / V0 + 61 / 2		' % relative humidity
DataOut = HumiData + 128		' set high bit
GOTO Relays		

interface, but is not needed for operation otherwise.

Pins 9 and 13 are used as outputs to the X10 interface. A high (+5 volt) signal on pin 9 is used to send an 'on' signal to the X10 transmitter. A high signal on pin 13 sends an 'off' signal to the transmitter. The lines are kept low when not really sending signals by resistors R4 and R6. Resistors R5 and R7 limit the current to the light-emitting diodes in optoisolators IC4 and IC5. The outputs of these two ICs are NPN transistors that either conduct (send 'on' or 'off' signals to the X10 transmitter) when the LEDs are conducting, or are open circuits when no current

passes through the diodes. The X10 interfacing is explained in more detail in the second part of this article.

The Humidity Circuit

Refer to Figure 2 to understand how the humidity circuit works. It is built around a relative humidity sensor, RH1, an NH-03 from Figaro USA, Inc. It contains two humidity-sensitive elements made from a stable high polymer impregnated in porous ceramic, and two printed NTC thermistors. The elements are manufactured so that when an AC voltage of about 1 volt AC/approximately 1000 Hz is applied to the input (across pins

1 and 3), an output AC voltage is presented (across pins 1 and 2) so that this output AC voltage is proportional to % relative humidity.

The linear, temperature-compensated output greatly reduces the problems that would be present for exponential-type outputs normally found with these types of sensors. However, there are two problems that present themselves: that of the AC input/output and the calibration of the AC signals.

AC voltage is required for input to the humidity sensor. Any DC applied to the sensor will cause permanent damage to the sensor element and render it useless.

Therefore, a simple DC resistance circuit is out of the question. However, AC circuits are relatively difficult to regulate. A 10% deviation in the input signal would translate to an error of 10% or more. A self-calibration technique is used to get around these problems.

Two sections of a CMOS NAND gate (IC6-A and IC6-B) are used to create a 5-volt squarewave generator. Pin 6 is used to gate the oscillator; when it is high (+5 volt), the circuit oscillates, while when it is low (0 volt), there is no oscillation. This gate is controlled by the CPU pin 11 (signal labeled 'RHon'). The R9-C5 combination sets the rate of oscillation.

For the part values shown, it is approximately 1 KHz. Therefore, the output at pin 3 ('P-a' on Figure 2, pt 'a' on the PC board) is a 5-volt, 1-KHz gated squarewave. C6 is used to translate this from a [+5V to 0V] signal to a [+2.5V to -2.5V] (true AC) signal. It is reduced to a 1-volt signal [+0.5V to -0.5V] by the divider made up of resistors R11 and R12. This 1-V 1-KHz AC signal can then be applied to the humidity sensor.

IC7 (a CMOS quad bilateral switch) and gate IC6-C (used as an inverter) form a switch that isolates the humidity sensor when the circuit is not really measuring humidity. They also are used to switch either the input or the output to the measuring circuitry that follows it. When 'RHon' is high (+5V), the 1-V 1-KHz AC signal is applied to the input to the sensor, and an output is sent to

TABLE 1. HEAT INDEX TABLE

To use the table, find the temperature — in deg. F. — along the top, and the relative humidity — in % — along the left. The cell at the intersection of the two is the heat index. This is how hot the combination of temperature and humidity will actually feel.

Relative Humidity	Air Temperature, deg. F.										
	70	75	80	85	90	95	100	105	110	115	120
0%	64	69	73	78	83	87	91	95	99	103	107
10%	65	70	75	80	85	90	95	100	105	111	116
20%	66	72	77	82	87	93	99	105	112	120	130
30%	67	73	78	84	90	96	104	113	123	135	148
40%	68	74	79	86	93	101	110	123	137	151	
50%	69	75	81	88	96	107	120	135	150		
60%	70	76	82	90	100	114	132	149			
70%	70	77	85	93	106	124	144				
80%	71	78	86	97	113	136	157				
90%	71	79	88	102	122	150	170				
100%	72	80	91	108	133	166					

get temperature data when WhichOne = 1

```

Temper:
DSout = StartC      ' code to start a temp. conversion
GOSUB ShiftOut      ' to DS1620
LOW RST             ' deactivate DS1620
PAUSE 2000          ' wait for conversion to end
                    ' and additional second
DSout = RTemp       ' code to get the temperature
GOSUB ShiftOut      ' to DS1620
  
```

```

read data from DS1620 chip
INPUT DQn           ' make pin an input
FOR I = 1 TO 9      ' for 9 bits
  DSin = DSin / 2   ' shift right 1 bit
  LOW CLK           ' falling clock triggers DS1620
  BitIn = DQp       ' get the data bit
  HIGH CLK          ' preset clock high
NEXT I
LOW RST             ' deactivate DS1820
  
```

```

IF SignBit = 0 THEN Skip ' this means neg. deg. C
DSDat = DSDat / $FE00    ' make 16-bit 2's compl.
  
```

```

Skip:
TempData = DSDat * 9 + 325 / 10 ' convert to deg. F
DataOut = TempData
  
```

send data to relays

```

Relays:
FOR I = 1 TO 8      ' for 8 bits
  ABit = DataOut & 1 ' lowest bit
  IF ABit = 1 THEN HiBit
  HIGH RelayOff     ' pulse for off state relay
  GOTO RelayDelay
HiBit:
  HIGH RelayOn      ' pulse for on state relay
RelayDelay:
  PAUSE 500          ' 0.5 second on time
  LOW RelayOff       ' turn off
  LOW RelayOn        ' both relays
  PAUSE 1500         ' 1.5 second off time
  DataOut = DataOut / 2 ' shift to next bit
NEXT I
  
```

display temperature by blinking led

```

Display:
Pulses = LedData / 100 ' hundreds
  
```

```

GOSUB BlinkLed      ' blink that many hundreds
Pulses = Pulses * 100
J = LedData - Pulses ' either 0, 100, or 200
Pulses = J / 10      ' tens and units
GOSUB BlinkLed      ' tens only
Pulses = J // 10     ' blink that many tens
GOSUB BlinkLed      ' units only
                    ' blink that many ones
  
```

loop consumes 5 minutes, mostly in low-power mode

```

Loop5min:
FOR CountSec = 1 TO 130 ' about 5 minutes per loop
  SLEEP 1                ' low power for 2.3 seconds
NEXT CountSec
GOTO Loop                ' redo everything
END
  
```

send data to DS1620 chip

```

ShiftOut:
HIGH RST           ' activate DS1620
OUTPUT DQn         ' make pin an output
FOR I = 1 TO 8     ' for 8 bits
  LOW CLK          ' preset clock low
  DQp = BitOut     ' data bit to DS1620
  HIGH CLK         ' rising clock triggers DS1620
  DSout = DSout / 2 ' shift right for next bit
NEXT I
RETURN
  
```

blink the led a certain number of times

```

BlinkLed:
HIGH Led          ' turn on Led
PAUSE 10          ' at least a short blink
IF Pulses = 0 THEN DoneBlink ' for zero count, skip loop
FOR I = 1 TO Pulses
  HIGH Led        ' do how many times
  PAUSE 500       ' turn on Led
  LOW Led         ' wait 0.5 second
  PAUSE 500       ' turn off Led
  PAUSE 500       ' wait 0.5 second
NEXT I
DoneBlink:
LOW Led           ' turn off Led
PAUSE 1000        ' wait a second
RETURN
  
```

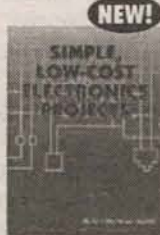

Great Books for Hobbyists, Students, Engineers . . .

Simple, Low-Cost Electronics Projects

by Fred Blechman

Learn electronics with Fred Blechman's exciting new book. Begin with simple designs and progress to more sophisticated projects. Each project comes with a complete discussion of circuit theory and parts list, as well as information on troubleshooting and testing. Build voltmeters and multimeters, inductance and semiconductor testers, variable frequency audio oscillators, a photoelectric counter, and much more!

1-878707-46-9/224 pages/\$19.95



Controlling the World with Your PC

by Paul Bergsman

PC Disk Included! Connect your computer to the real world and make it do useful work like controlling stepper motors, turning appliances on and off, or monitoring fluid levels. PC disk contains software files in ready-to-use form.

1-878707-15-9/208 pages/\$35.00



The Forrest Mims Engineer's Notebook

by Forrest Mims III

This revised edition of Forrest's classic book includes hundreds of useful circuits built from integrated circuits and other parts available from convenient sources.

1-878707-03-5/156 pages/\$19.95



The Integrated Circuit Hobbyist's Handbook

by Thomas R. Powers

Covers the major types of integrated circuit devices—linear, TTL, and CMOS—and provides complete details and theory about their

operation. Contains lots of useful application circuits—an essential reference for every hobbyist. 1-878707-12-4/256 pages/\$19.95



Order on the Web!

For these and other great books
on electronics, visit:

www.LLH-Publishing.com

or

call 1-800-247-6553 to use a
major credit card, or send check or
money order to:

LLH

Technology Publishing
3578 Old Rail Road
Eagle Rock, VA 24085

the rest of the circuit. However, signal 'RHget' (from the CPU pin 10) is used to create a SPDT switch so that the output via pin 10 of IC7 is either the input to the sensor (when 'RHget' is high, the AC signal is passed from pin 2 to pin 1 to pin 4 to pin 3 to pin 11 and then to pin 10) to measure the 'control' signal, or the output of the sensor (when 'RHget' is low, the AC signal is passed through pin 2 through the sensor from its pin 3 to pin 2, to IC7 pin 8 to pin 9 to pin 11 and then to pin 10) to measure the 'test' signal.

The result of all of the above: when 'RHon' is high and 'RHget' is low, the output 'P-c' is the control signal (the input to the sensor), which, at that point, is the 1-V AC signal attenuated slightly by passing through three sections of IC7. When 'RHon' is high and 'RHget' is also high, the output 'P-c' is the test signal (the output from the sensor), which is an AC signal, typically less than 1-V AC and directly proportional to % RH; this signal is also attenuated slightly by passing through three sections of IC7. The CPU then measures two signals: the control signal and the test signal.

Software inside the CPU's program divides the result from the test by the result from the control. This effectively cancels out any effects of voltage loss through IC7, deviations from 1 KHz, deviations from 1-VAC, deviations in the trianglewaves or amps (see below), etc. It completely eliminates the need for any calibration whatsoever.

The rest of the circuit is used to create a signal that the CPU can measure that is in some way directly proportional to the level of AC voltage at 'P-c.' In this case, it is a pulse width which the CPU measures. The signal at 'P-c' is an AC 1-KHz square-wave that varies from approx. 1-V (for 'control' or for 100% RH 'test') to nearly 0-V (for about 30% RH 'test'). The amplifier IC8-A and resistors R14, 15, 16, 17, and D1 rectify the AC signal and amplify it to more measurable levels. D2, C7, and R19 filter it so that the signal at 'P-e' is a DC signal that is approximately 2.5V maximum, about 0.5V minimum.

IC8-C and IC8-D and associated components (R20, 21, 22, 23, and 24, and C8) form a precision trianglewave generator, with a frequency of about 125 Hz. It also is gated (turned on) by a high level of 'RHon.' The output of the trianglewave is dropped a fraction of a volt through D3, so that the high tip of the triangle is at about 2.9V, while the low tip is about 0.4V, at 'P-f.' A squarewave at the same frequency of the triangle is output via pin 10 of IC8-D ('P-g'); the squarewave is high whenever the triangle is increasing (going from 0.4V to 2.9V), while it is low when the triangle is decreasing (going from 2.9V to 0.4V).

Another squarewave is created by IC8-B, used as a comparator. Here this squarewave at 'P-h' is high when-

PARTS LIST FOR HUMIDITY-TEMPERATURE TRANSMITTER

SEMICONDUCTORS

IC1 - 78L05 5-volt 100-mA voltage regulator integrated circuit, TO-92 package
IC2 - PIC16C58A-04, Microchip 8-bit RISC microcontroller integrated circuit programmed with THX10 program (see below)
IC3 - DS1620, Dallas digital thermometer integrated circuit, Jameco #114382
IC4, IC5 - 4N27 (NTE/ECG #3040) optoisolator: diode and NPN phototransistor integrated circuit, Jameco #144240 or Digi-Key #4N27QT-ND
IC6 - CD4011 quad 2-input NAND gate CMOS integrated circuit
IC7 - CD4016 quad bilateral switch CMOS integrated circuit
IC8 - LM3900N or CA3401N quad current-mirror op-amp integrated circuit
BR1 - W02G full wave bridge rectifier, 4 lead molded 200-PRV 1-Amp, Jameco #103018 or Digi-Key W02G-ND
D1, D2, D3 - 1N4148 or 1N914 silicon switching diode 75-PRV 10-mA
LED1 - Light emitting diode, red

RESISTORS

(All resistors are 1/4 watt, 5% units unless noted otherwise)

R1, R2, R4, R6, R11, R13, R15, R16, R27 - 10,000-ohm
R3 - 1000-ohm
R5, R7, R8 - 470-ohm
R9 - 47,000-ohm
R10, R17, R18, R20, R23, R25, R26 - 1.0-megohm
R12A, R12B - 5100-ohm (see text)
R14 - 200,000-ohm
R19, R22 - 100,000-ohm
R21 - 510,000-ohm
R24 - 120,000-ohm

CAPACITORS

C1 - 100-uF, 25-WVDC, electrolytic
C2 - 22-uF, 25-WVDC, electrolytic
C3, C4 - 0.1-uF, ceramic disk
C5 - 0.01-uF, 10% mylar
C6 - 10-uF, 25-WVDC, electrolytic
C7 - 1.0-uF, 25-WVDC, electrolytic
C8 - 0.0047-uF, 10% mylar

ADDITIONAL PARTS AND MATERIALS

J1 - 0.100" right angle male header 10 conductor (2X5), and matching IDC socket connector (such as Jameco S-10)
RES1 - 4-MHz ceramic resonator, Digi-Key PX400-ND or equivalent
RH1 - NH-03 temperature-compensated linearized-AC humidity sensor, available from Figaro USA, www.figarosensor.com (see below)
T1 - low profile transformer 115-V 60-Hz primary, 12-V @ 50-mA secondary, SPK0051200-10001 or equivalent, available from Advanced Components Industries, www.advancedcomponents.com (see below)
Mini-controller - X10 Powerhouse Transmitter MC460 (Tech America #980-0213, Home Automation Systems www.smarthome.com #4030), or Home Controls Inc. www.homecontrols.com #XT460X) or similar products by Stanley (Home Automation Systems #4031) or RadioShack #61-2677c (see text)
PC Interface - X10 Activehome CM11A (Home Automation Systems www.smarthome.com #1140), also available as part of X10 home automation kit at RadioShack stores, Home Controls Inc. www.homecontrols.com #XTCK11A, etc. (see text)

IC sockets, PC board (see below), suitable enclosure, wire, hardware, PC and software, etc.

Note: The following items are available from M. Keryan, 207 Baucom Park Dr., Greer, SC 29650: Preprogrammed IC2 and 3-1/2" diskette with X10 monitoring software, circuit board layout, etc., \$15.00; Etched and drilled double-sided PC board, \$20.00; RH1 humidity sensor, \$14.00; T1 transformer \$10.00. Quantity discounts of 20% for 3 or more of same items. Please include \$5.00 shipping and handling per order (\$10.00 for international orders), check or money order only in US funds. SC residents add 5% sales tax. Source code for PIC controller and for PC monitoring available.

Michael J. Keryan — 207 Baucom Park Drive — Greer, SC 29650
(864) 244-4175 — mkeryan@pobox.com

ever the voltage of the trianglewave is less than the DC level at 'P-e.' The two squarewaves are gated by IC6-D NAND gate to form a pulse, that is at 0V only when the trianglewave is increasing and is at a lower voltage than the DC voltage at 'P-e.' The width of this negative pulse is therefore directly proportional to the DC voltage at 'P-e' and thus also proportional to the AC voltage at 'P-c.'

The humidity circuitry appears quite complex, as is its explanation. However, it uses three extremely inexpensive ICs and a handful of resistors, capacitors, and diodes. It is designed so that the results are virtually independent of any minor deviations in parts values, voltages, or

frequencies. The results are almost totally defined by the precision and accuracy of the humidity sensor itself, and the cost of the circuitry of Figure 2 is also almost totally defined by the cost of the sensor.

Parts and Construction

Except for the oscillator of the PIC CPU, no very high frequencies are involved, and voltages and currents are low. Therefore, any type of circuit construction (breadboarding, wire wrapping, etc.) will work fine. However, to keep the circuit small and to avoid wiring errors, a printed circuit is recommended. Foil patterns for the top and bottom of a double-

sided board are included if you are adept at etching your own boards. For the rest of you, PC boards can be purchased from the author (see the parts list).

A preprogrammed PIC CPU containing the THX10 program can be purchased, as well as the other hard-to-get parts (see the parts list). The humidity sensor is available from the author and through Figaro; there is no substitute for this item. Other transformers can be used to deliver 12 volts to the circuit, but the part shown in the parts list is ideal for making a compact system — it is only 0.6 inch tall, allowing a very thin case to be used. You should have no trouble finding any of the other parts; sources for some of them are shown in the parts list.

The op-amp (IC8) should not be substituted. It uses current-mirror techniques, so other types of op-amps will not work at all in the circuit. It is also about the least expensive op-amp you can find. For the resistors, you should stick to using 1/4 watt to ensure they will physically fit. The same goes for the capacitors; higher voltage caps will work fine, just make sure they will fit on the board. For J1, a 2x5 connector was used because a 10-pin female connector is easier to find than a five-pin connector. If you wish, use a five-pin connector installed in either of the rows on the PC board.

For R12, two 5100-ohm resistors are used in parallel to give a 2550-ohm equivalent. This is close enough to the desired 2500-ohm that would give an exact 1-volt p-p AC signal. If you can find one, use a single 2500-ohm 1% resistor installed in either the R12A or R12B position on the PC board. The only capacitors that are critical at all are C5 and C8. Make sure you use 10% mylar or better here to minimize timing drifts.

A red LED is specified in the parts list, but actually any color will do. You may want to splurge and get a high-brightness LED for about a dollar, instead of a standard brightness 20-cent LED. The brighter ones are easier to see from across the room.


There are no jumpers to worry about. Use IC sockets for all the ICs except the regulator, IC1. When soldering in IC1, the LED, and the diodes, take care to not overheat the leads; you may want to use a hemostat-type heatsink clamped to the leads. If you build your system like the author, you will want to stand the LED off the PCB so that it will fit into a hole drilled in the top side of the case.

Using the placement diagram, solder in all the resistors and diodes (watch the diode orientation — the banded ends all point the same way, toward the left). Similarly, for the items that are partially round but have one flat side (IC1, BR1, LED1) — the flat ends all go toward the top of the board. RES1 can be oriented either way. RH1 must be oriented so that the front (the side with the two little 'M's) faces the closest edge of the PC board.

After all the parts are soldered in, inspect your work to make sure there are no solder bridges and that everything is clean and shiny (no cold solder joints). Then plug in all the ICs, making sure all pin 1s (the end with the dimple or notch) face towards the top of the board. Take the normal precautions to avoid static electricity discharges when handling the ICs.

Testing and Calibration

To test the board after construction, connect either a 12-volt (AC or DC) supply or a 9-volt battery to pins 1 and 2 of J1, with no connections to pins 3, 4, and 5 of J1. After a few seconds, you should see the LED blink three times. This indicates that the CPU and program inside it are working. After about 10 more seconds, you should see the LED blink out the temperature, in degrees F. After about five to six minutes, you'll see the LED come on for about two seconds, then after about 10 more seconds, it will blink out the humidity, in %. Try breathing directly on the humidity sensor just before it takes a reading, and notice the change in humidity.

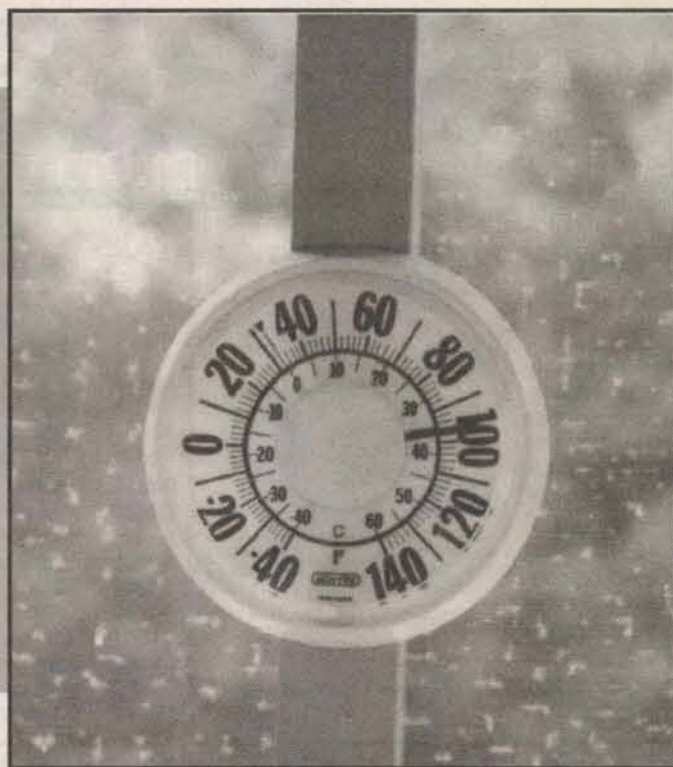

The temperature is only half of the story.

You may be wondering how a single LED can be used to blink out this information to you in a meaningful way. It blinks in one-second intervals — 1/2 second on, 1/2 second off. One blink means 1, two blinks means 2, ... nine blinks means 9.

Between the hundreds and tens digits and between the tens and units digits, there is a longer gap, or pause. For a zero, there is a very short blink, one that is noticeably shorter than the others. For example consider a sequence like this: a very short blink — a pause — 7 blinks — a pause — 3 blinks; this is 0-7-3, or 73. The humidity is preceded by about a two-second long blink to differentiate it from temperature.

What about calibration? There isn't any. The Dallas thermometer chip (IC3) is truly digital; it sends binary data to the CPU. The humidity circuit (see section: 'The Humidity Circuit') uses a self-calibration technique. Any inaccuracies that occur are due to either the sensors themselves, or are due to their placement and the possibility that they might not be ventilated adequately.

The only thing that remains to be tested is the interface to the X10 transmitter. We'll do that when we describe how to connect the sensor board to the transmitter.

For Next Time

This concludes Part 1 of this two-part article. To this point, we have constructed a PC board that contains sensors for temperature and humidity, and a PIC CPU that processes the data and sends the data to an interface. In its current state, it is a self-contained instrument that can communicate its findings via a LED.

Next time, we will explain how to interface this instrument to an inexpensive X10 mini-controller that transmits the data on our house power line. So, between now and then, build the sensor board and have fun watching the LED count. Later on, get the remaining parts: the mini-controller and the serial PC interface that will be used to receive the data on up to eight of the transmitters. Also make sure you have a free serial port on your PC. **NV**

Do You Repair Electronics?

For only \$7.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- UL/FCC number lookup.
- Private user discussion forums.
- Hot tips bulletin board.
- Automated email list server.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878


Write in 71 on Reader Service Card.

Motron
ELECTRONICS

PO Box 2748
Eugene OR 97402-0280
(541) 687-2118

Control your home from your radio!
Only \$99.00 Plus S/H

<http://www.motron.com/>

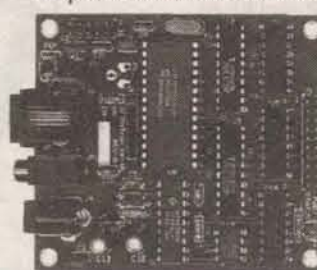

Auto-Kall® AK-16
DTMF Controller Board

The **Auto-Kall® AK-16** DTMF Controller Board features 16 relay driver outputs and DTMF to X-10 house control capability! Control the relay driver outputs, X-10 modules, or both with your radio keypad! X-10 operation requires the PL-513 Power Line Interface (\$20). The **AK-16** mates readily with our **RB-8/10** (\$99) or **RB-16/10** (\$149) relay boards. The 0-12 digit security code is user programmable using your DTMF keypad. Additional features include re-programmable CW ID and several modes of operation, including two with CW response. The **AK-16** is a fully assembled and tested printed circuit board. Price and Specifications are subject to change without notice.



Visa, MasterCard, American Express, Discover
And Government Purchase Orders accepted.
S/H: \$8 USA; \$11 Canada; \$16 Foreign
Se Habla Español. Pida Por Don Moser.



Info: (541) 687-2118

Orders: (800) 338-9058 Fax: (541) 687-2492

CALL TOLL FREE
(800) 292-7711 orders only
Se Habla Español

C&S SALES

EXCELLENCE IN SERVICE

CALL OR WRITE FOR OUR
NEW FREE 64 PAGE
CATALOG!
(800) 445-3201

REPAIR SYSTEM SOLDERING AND DESOLDERING Model SL-916


\$425.00

Top-of-the-line repair system will handle desoldering. Temperature controlled soldering from 300°F to 790°F (150°C to 420°C), desoldering temperature range 410°F to 900°F (210°C to 480°C). The system is based on principle of vacuum absorption of the solder from the PC board.

SL-928 - Desoldering System with Digital Display also available. \$325.00



Elenco Scopes Free Dust Cover and Probes

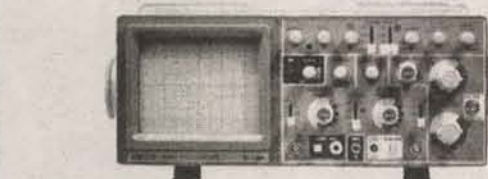

S-1325	25MHz		\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz		\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$895

DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$895
DS-603	60MHz/20Ms/s Analog/Digital	\$995

Four Functions In One Model MX-9300



\$459.95

Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply - 0-30V @ 3A, 15V @ 1A, 5V @ 2A

NEW Tektronix DMMs

- 40,000 count
- High Accuracy
- Tektronix quality
- 3yr warranty

DMM 912	\$169	\$179
DMM 914	\$239	\$229
DMM 916	\$255	\$275



20MHz Sweep / Function Generator with Frequency Counter Model 4040

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep



10MHz Model 4017	\$309	\$399
5MHz Model 4011	\$239	

Fluke Scopemeters



123...NEW...	\$950
92B.....	\$1445
96B.....	\$1695
97.....	\$1695
99B.....	\$2095
105B...NEW...	\$2495

ALL FLUKE
PRODUCTS
ON SALE

Technician Tool Kit Model TK-1500

28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.



\$49.95

Fluke Multimeters			
Model 26III	\$195	Model 12	\$84
Model 70III	\$85	Model 83	\$235
Model 73III	\$115	Model 85	\$269
Model 75III	\$139	Model 87III	\$299
Model 77III	\$154	Model 863E	\$475
Model 79III	\$175	Model 867BE	\$650

B&K Precision Multimeters			
Model 389	\$109	Model 388A	\$99
Model 390	\$127	Model 2707	\$75
Model 391	\$143	Model 2860A	\$79
Model 5360	\$195	Model 5370	\$219
Model 5380	\$265	Model 5390	\$295

DIGITAL LCR METER Model LCR-1810

- Capacitance .1pF to 20MF
- Inductance 1μH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 75°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display



\$99.95

B&K High Current DC Power Supply

- Variable 3-14 VDC
- Thermal Protection
- Current Limiting



Model 1686 12A	\$159
Model 1688 25A	\$239

B & K 13.8V Fixed DC/Power Supplies	
Model 1680 6A	\$39
Model 1682 15A	\$75

Quad Power Supply Model XP-4

4 Fully Regulated DC Power Supplies in One Unit
4 DC voltages: 3 fixed - +5V @ 1A, -5V @ 250mA, +12V @ 500A • 1 Variable 0-12V @ 500mA



\$29.95

Digital Multimeter Model M-1740

\$39.95

Free Holster

11 functions including freq to 20MHz, cap to 20μF.
2 Year Warranty



Family Radio Model FRS-14 by Standard

- 1 Mile Range
- 1/2 Watt Output, 14 Channels
- LCD Channel & Code Display
- 38 Selectable Channel Codes
- Back-Lit Display
- No License Required!

**\$129.95 each or
2 for \$250.00**



Handheld Universal Counter

Features:

- 10-Digit LCD Display.
- 250MHz Direct Count.
- 16 Segment & RF Signal Strength Bargraph.
- NiCad Battery Included.



**Model F-2800
1MHz - 2.8GHz**

\$99

B&K Spectrum Analyzers



500MHz Series

BK2615A	\$1250
BK2620A	\$1675

- 150KHz to 500MHz
- Dynamic Range 80dB (113dB with attenuation)
- +20dBm maximum input
- 12.5 and 400KHz resolution bandwidth
- 150KHz/hour stability
- Built-in tracking generator (Model 2620A)

1.05GHz Series

BK2625A	\$1925
BK2630A	\$2595

- 150KHz to 1,050MHz
- Dynamic Range 80dB (113dB with attenuation)
- AM & FM demod included
- 20 and 400KHz resolution bandwidth
- 150KHz/hour stability
- Built-in tracking generator (Model 2630A)

Simm Module Tester B&K Precision Model 898

- Tests 72 and 30 pin SIMMs to 36 bits.
- Stands alone and portable. No other equipment required.
- Automatically identifies width, depth and speed of SIMMs.
- 10 built-in tests identify most memory defects Pre-heat cycle prior to tests.

\$625



Model XP-581

4 Fully Regulated DC Power Supplies in One Unit
4 DC voltages: 3 fixed +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A



\$89.95

Portable Semiconductor Tester B&K Precision Model 510

- In or out-of-order circuit tests for transistor, FETs, SCRs and darlington.



\$199

Satellite Finder Model SF-01

- Aligns Satellite Dishes
- Range 950-2050MHz
- Compact Size
- Self Power Check



\$39.95



Dual-Display LCR Meter w/ Stat Functions B&K Model 878 **\$219.95**

Auto/manual range
Many features
with Q factor
High Accuracy

Digital Audio Generator SG-9300

\$175



- 10Hz - 1MHz
- Low Distortion
- Sine/Square waves
- Built-in 150MHz Frequency Counter

Guaranteed Lowest Prices

C&S SALES, INC.

15 DAY MONEY BACK GUARANTEE

FULL FACTORY WARRANTY

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710
http://www.elenco.com/cs_sales/



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Events

FEBRUARY 1999

FEBRUARY 1

AZ - PHOENIX - Auction. St. Clement of Rome Catholic Church Social Hall, 15800 Del Webb Blvd. Talk-in: 147.30+ West Valley ARC, Ralph WODNO, 602-582-8208. E-Mail: w0dno@worldnet.att.net

FEBRUARY 6

AR - WEST MEMPHIS - Hamfest. Eugene Woods Civic Center, 212 W. Polk. 9am-4pm. VE Exams. Talk-in: 147.150+. 444.775+. Dixie AR Group, Kellye Farris KB5RCE, 870-732-8724. E-Mail: kb5rce@media-two.com
E-Mail: dixiefest@media-two.com
Web: http://www.media-two.com/DARG
CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

IA - MONTGOMERY - Hamfest. Jerry Morrison NOLE, 515-484-6036. E-Mail: NOLE@WOCX-1.IA.USA.NA E-Mail: lmonster@pcpartner.net
KS - MOUND CITY - Hamfest. Mine Creek ARC, Bill VanKirk WOFT, 913-795-2080. E-Mail: bvkirk@kanza.net
SC - NORTH CHARLESTON - Hamfest. Stall High School. 8:30am-4pm. VE Exams. Charleston ARS, Jenny Myers WA4NGV, 843-747-2324. E-Mail: brycemyers@aol.com
E-Mail: wa4usn@amsat.org

FEBRUARY 6-7

FL - MIAMI - Tropical Hambooree. Fair Expo Center, S.W. 112th Ave. & Coral Way. VE Exams. Talk-in: 146.925, 146.76, 444.525. Dade Radio Club of Miami, Evelyn Gauzens. 305-642-4139. E-Mail: edg@elink.net. 305-226-5346. E-Mail: wd4sfg@bellsouth.net. Web: www.hambooree.org

FEBRUARY 7

OH - LORAIN - Hamfest. Northern Ohio ARS, Mike Willemin W8EU, 440-324-4574
PA - LATROBE - Hamfest. American Legion, 1811 Ligonier St. 8am-1pm. Talk-in: 145.150 (-600). Chestnut Ridge ARC, William Demosky K3AFS, 724-539-1552

FEBRUARY 12-13-14

FL - ORLANDO - Hamfest. Northern FL Section Conv., Tim Starr AE4NJ, 407-850-9258. E-Mail: AE4NJ@aol.com
Web: http://www.oarc.org/hamcat.html

FEBRUARY 13

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves
MA - MARLBOROUGH - Hamfest. Marlborough Middle School, Rt. 85. 10am-2pm. Algonquin ARC, Ann Weldon KA1PON, 508-481-4988
MI - NEGAUNEE - Swap & Shop. Township Hall. Talk-in: 147.27. Hiawatha ARA, Bob Serfas N8PKN, 906-226-9782. John Veight N8RSE, 906-228-9417
NY - WESTFIELD - Hamfest. Westfield Exempt Volunteer Fireman's Assn., 75 Bourne St. 8am-3pm. Talk-in: 145.350 (-). Chautauqua County RAs, Eric Kroon N2PCQ, 716-595-3220. E-Mail: ekroon@netsync.net
PA - OBERLIN - Hamfest. Oberlin Fire Co., Fire Hall. VE Exams. Talk-in: 146.76. HRAC 717-939-4825. E-Mail: n3jnb@juno.com
TX - CANYON - High Plains Hamfest. WTAMU Activities Center. Talk-in: 146.94-88.5Hz, 444.200+ 88.5Hz, 145.35-88.5Hz. ARES, POB 5378, Amarillo, TX 79117. E-Mail: wally@n4bz.org
Web: www.n4bz.org

FEBRUARY 14

CO - BRIGHTON - Hamfest. Aurora Repeater Assn., Wayne Heinen N0POH, 303-699-6335. E-Mail: nrclg@aol.com
IL - ROCK ISLAND - Hamfest. QCCA Expo Center, 2621 4th Ave. Talk-in: W0BXR 146.28/88 and 146.04/64. Davenport ARC, Kent Williams K9UQI, 309-796-0718, 4-9pm only. E-Mail: k9uqi@arcsupport.com E-Mail: k9uqi@netex press.net Web: http://www.arcsupport.com/drac
OH - MANSFIELD - Mid-Winter Hamfest & Computer Show. Richland County Fairgrounds. Talk-in: call W8WE on 146.34/94. InterCity ARC, Inc., Pat Ackerman N8YOB, 419-589-7133 after 2pm EST.

FEBRUARY 20

AR - RUSSELLVILLE - Hamfest. AR River Valley AR Foundation, Margaret Alexander KC5MCS, 501-968-7270. E-Mail: ealexand@cswnet.com
CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052
FL - BROOKSVILLE - Hamfest. Spring Hill VFW

CALENDAR

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine
Events Calendar**
430 Princeland Court
Corona, CA 91719
Phone 909-371-8497
Fax 909-371-3052
E-mail events@nutsvolts.com

COMPUTER SHOWS

AGI Shows, 317-299-8827.
E-Mail: info@agishows.com
http://www.agishows.com

Blue Star Productions
612-788-1901
http://www.supercomputersale.com

Computers And You, 734-283-1754.
www.al-supercomputersales.com

Computer Central Shows
847-412-1900 & 1-888-296-6066.
E-Mail: compcent@megsnet.net
www.computercentralshows.com

Five Star Productions
810-890-0988 E-Mail: jeff@fivestars
www.fivestarsshows.com

Georgia Mountain Productions
706-838-4827.
E-Mail: gamtnpro@blrg.tds.net
georgiamountain.com

PA - CASTLE SHANNON - Hamfest. VFD Memorial Hall, Library Rd. (Rt. 88). 8am-3pm. Talk-in: 146.955- N3RNX repeater. N3SH ARC, Steve Lane W3SRL, 412-341-1043. E-Mail: slane@adelphia.net
Web: http://www.hky.com/~sanfordb/index.htm
VA - ANNANDALE - Hamfest. N. VA Community College, 8333 Little River Tpke. (Rt. 236). VE Exams. Talk-in: 146.91 (-) & 146.685 (-). Vienna Wireless Society, Mike Toia K3MT, 703-757-5021. E-Mail: k3mt@erols.com
Web: http://www.erols.com/k3mt/vws
WV - FAYETTEVILLE - Hamfest. Plateau ARA, Juddie David Burgess KC8CON. E-Mail: kc8con@usa.net Web: http://www.geocities.com/Cape Canaveral/Launchpad/4842

MARCH 1999

MARCH 5

MO - ST. LOUIS - Hamfest. Amateur Radio Auction, Bill Schmidt WA0JCO, 314-544-1515

MARCH 5-6

MS - PASCAGOULA - Hamfest. Jackson County Fairgrounds, Civic Center. Fri: 5pm-9pm, Sat: 8am-3pm. VE Exams. Talk-in: W5WA 145.110. Jackson County ARC, Charles F. Kimmerly, 228-826-5811

MARCH 5-6-7

NE - NORFOLK - State Convention. Fred Wiebelhaus NOVX, 402-379-1929. E-Mail: dfwiebel@sufia.net Web: http://members.aol.com/davidn0xbn/evarc.html

MARCH 6

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052
NJ - PARSIPPANY - Hamfest. PAL Building, Smith Field, Rt. 46 & Baldwin Rd. VE Exams. Splitrock ARA, Mark Turner KB2VKO, 973-347-3195 or 1-888-511-7272. E-Mail: mlturner@bellatlantic.net Web: http://ham.hsix.com/sara
TN - KNOXVILLE - Hamfest. Kerbel Temple, 315 Mimosa Ave. 8am-4pm. Talk-in: 144.83/145.43 or 146.52 simplex. Kerbel Temple, Paul Baird K3PB, 423-986-9562

Gibraltar Trade Center, Inc.
734-287-2000. Taylor, MI.
Gibraltar Trade Center, Inc.
810-465-6440. Mt. Clemens, MI.

MarketPro, Inc., 201-825-2229
http://www.marketpro.com

MarketPro, Inc., 301-984-0880.
E-Mail: md@marketpro.com
http://marketpro.com

Narisaam Computer Show
770-663-0983.
E-Mail: narisaam@aol.com
Web: http://www.showsale.com

Northern Computer Shows
978-744-8440
E-Mail: inquiries@ncshows.com
Web: ncshows.com

Peter Trapp Computer Shows, 603-272-5008. Web: www.petertrapp.com

MARCH 6-7

FL - NEW PORT RICHEY - Hamfest. Fred K. Marchman Technical Educational Center. Sat: 8am-5pm, Sun: 8am-3pm. Talk-in: 146.670 or 145.330. Gulf Coast ARC, Rick Brown KF4QXS, 813-842-2127. E-Mail: rick@gte.net

MARCH 7

FL - ZEPHYRHILLS - Hamfest. Zephyrhills ARC, Ernie Vanselow KD4VRV, 813-783-8389. E-Mail: kd4vrv@gte.net

MA - WESTFIELD - Hamfest. Westfield South Middle School. MTARA, Jim Allen N1RJT, 413-568-1175 days, 413-536-5182 eves. E-Mail: Jim.Allen@the-spa.com
Web: http://www.mtara.org

NY - LINDENHURST - Hamfest. Great South Bay ARC & Suffolk County RC, 516-422-9594. E-Mail: ka2d@li.net Web: http://www.gsbarc.org
WI - WAUKESHA - Swapfest. Waukesha County Expo Center. 8am-2pm. VE Exams. Talk-in: 146.82 PL 127.3. SEWFARS, John Breecher N9NWN, 414-835-7035

MARCH 13

AZ - SCOTTSDALE - Hamfest. Scottsdale ARC, Roger Cahoon KB7ZWI, 602-948-3548
CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves
CA - LINDA - Hamfest. Yuba Sutter ARC, Clara KC6JPP, 530-742-2674. Ron W6KJ, 530-674-8533
FL - EAST ENGLEWOOD - Hamfest. Tringali Community Center, SR 776. Talk-in: 146.700. Englewood ARS, J.R. House K9HUY, 941-475-3005. George KA4JKY, 941-697-3445. E-Mail: gshreve@ewol.com Web: http://www.flnet.com/~crosby/ears/index.html
FL - SEBRING - Hamfest. Highlands County ARC, Phyllis Dibble KD4CQG, 941-465-8176. E-Mail: dibble@strato.net
Web: http://www.strato.net/~hamradio
KY - CAVE CITY - Hamfest. Mammoth Cave ARC, Larry Brumett KN4IV, 502-651-2363. E-Mail: lbrumett@glasgow-ky.com
Web: http://www.scrct.blue.net/mcarc
MO - KANSAS CITY - Hamfest. Ararat AR Shrine Club, Steve Dowdy WJ0I, 816-941-3392. E-Mail: sdowdy@qni.com

Events CALENDAR

ND - WEST FARGO - Hamfest. Fairgrounds. 8am-3pm. VE Exams. Talk-in: 146.76. Red River Radio Amateurs, Mark Kerkvliet KG0FR, 701-282-4716. E-Mail: mbkerk@worldnet.att.net
Web: <http://www.rma.org>

NJ - WEST ORANGE - Hamfest. High School, 600 Pleasant Valley Way. 8:30am-1pm. Talk-in: 146.415 +1.0 85.4T, 224.480 -1.6 no tone, 447.875 -5.0 156.7T, 146.520 simplex. IRAC, Jim Howe N2TDI, 973-402-6066.
E-Mail: n2tdi@juno.com

WA - PUWALLUP - Hamfest. Mike & Key ARC, Michael Dinkelman N7WA, 253-631-3756 or 425-867-4797. E-Mail: mwdink@eskimomail.com

NC - CHARLOTTE - Hamfest & Computerfair. Charlotte Merchandise Mart, 2500 E. Independence Blvd. Mecklenburg ARS, Tim Slay WO4G, 704-382-3234 (W) or 704-948-6283 (H).
E-Mail: wo4g@w4bfb.org

LA - RAYNE - Hamfest. Acadiana ARA, Nolen Griffith K5ARH, 318-989-9039.
E-Mail: k5dpg@aol.com
Web: <http://www.acadiana.net/w5ddl/>

IL - STERLING - Hamfest. High School Fieldhouse, 1608 4th Ave. Talk-in: 146.25/146.85 W9MEP. Sterling-Rock Falls ARS, Lloyd Sherman KB9APW, 815-336-2434.

E-Mail: lsherman@essexl.com
IN - INDIANAPOLIS - Hamfest. State Fairgrounds. Morgan County Repeater Assn., Dennis Bauernfiend WB9ZNZ, 317-996-3782.
E-Mail: dennis.bauernfiend@dfas.mil
Web: <http://www.eb1.com/mcra>
OH - CONNEAUT - Hamfest. Human Resources Center, 327 Mill St. Conneaut ARC, Jack Martilla KA8TUU, 440-593-3353

FL - FT. WALTON BEACH - Hamfest. Playground ARC, Clyde Gowdy KE4FLC, 850-244-0624.
E-Mail: parcfest@aol.com
ME - LEWISTON - ME State Convention. Androscoggin ARC, Ivan Lazure N1OXA, 207-784-

0350. E-Mail: ilazure@gw.net
OK - TULSA - OK State Convention. Maxwell Conv. Center, 700 S. Houston Ave. Talk-in: 145.11 & 443.85. Green Country Hamfest Assn., Merlin Griffin WB5OSM, 918-622-2277. E-Mail: info@GreenCountryHamfest.org
Web: <http://www.GreenCountryHamfest.org>

AR - JONESBORO - Hamfest. Jonesboro ARC, Mike Conley KC5ISI, 870-931-9957. Evelyn Castleberry N5DSY, 870-932-1660.
E-Mail: jsnodgra@insolwrb.net
CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

FL - STUART - Hamfest. Martin County ARA, David Millard KE4AMW, 561-288-7100
MI - MARSHALL - Hamfest. Southern Michigan ARS & Marshall HS Photo Electronics Club, Wes Chaney N8BDM, 616-979-3433.
E-Mail: n8bdm@voyager.net

TX - MIDLAND - Hamfest. Midland ARC, Beverly Harwood KC5BNT, 915-686-1841.
E-Mail: shamrock@apex2000.net
Web: <http://www.lxnet/edge/midswap.htm>

CT - SOUTHTON - Hamfest. Southington ARA, Chet Bacon KA1ILH, 860-628-9346.
E-Mail: hcbacon@connix.com Web: <http://www.connix.com/~hcbacon/sara.html>
NC - KINSTON - Down East Hamfest. Lenoir County Fairgrounds, Hwy. 11 S. 8am-3pm. Doug Burt W4OFO, 252-524-5724

NJ - TRENTON - Hamfest. Tall Cedars of Lebanon picnic grove, Sawmill Rd. Talk-in: 146.67-. Delaware Valley Radio Assn., Darryl Foyuth N2JVP, 609-882-2240 E-Mail: n2jvp@amsat.org Web: www.slac.com/w2zq
OH - MAUMEE - Hamfest. Lucas County Recreation Center, 2901 Key St. 8am-2pm. Talk-in: 147.27+ or 442.85+. Toledo Mobile Radio Assn., Paul Hanslik N8XDB, 419-243-3836.
Web: <http://www.trmhamradio.org>
WV - CHARLESTON - Hamfest. Charleston Area Hamfest & Computer Show, Jimmie Hewlett WD8MKS, 304-768-1143

CT - POMFRET - Hamfest. Eastern CT ARA, Paul Rollinson KB1CNW, 860-928-2456. E-Mail: paulrollinson@worldnet.att.net

CT - WATERFORD - Auction. Waterford Senior Center, Rt. 85. Talk-in: 146.730. RAS of Norwich, Tony Griggs AA1JN, 860-859-0162. Mark Venable N1RSK, 860-572-9380. E-Mail: mvenable@99main.com Web: www.ims.uconn.edu/~rason
IN - MICHIGAN CITY - Hamfest. High School, 8466 W. Pahl Rd. 8am-1pm. Michigan City ARC, Inc., Ron Stahovick N9TPC, 219-325-9089
NY - NEWARK - Hamfest. Drumlins ARC, E-Mail: n2mkt0@aol.com

TX - WEATHERFORD - Hamfest. ARC of Parker County, Elizabeth Hunkele N5ONE, 817-594-1700. E-Mail: eliz@mesh.net

MD - TIMONIU - Maryland State Convention. Sharon Dobson N3QQC, 410-HAM-FEST (Box 3772), 1-800-HAM-FEST (Box 3772). E-Mail: n3qqc@amsat.org Web: <http://www.gbhc.org>

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813

FL - LEESEBURG - Hamfest. Lake ARA, Paul Branch K3NON, 352-343-8729. John Wentz WB8FK, E-Mail: w8hfk@aol.com
NH - HENNIKER - Hamfest. Contoocook Valley RC, Jock Irvine N1JI, 603-428-3476 ext. 256
OH - MADISON - Hamfest. Lake County ARA, Roxanne, 440-256-0320

APRIL 1999

OK - MOORELAND - Hamfest. Tri-State AR Group, Duane Henderson KC5NID, 580-994-2223. E-Mail: kc5nid@pdi.net

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

GA - ATLANTA - Southeastern VHF Conference. Southeastern VHF Society, Dick Hanson K5AND, 770-844-7002. E-Mail: k5and@prestique.net Web: <http://www.svhfs.org.svhfs>

CA - FRESNO - Int'l DX Convention. Gordon Gorton W6NW. E-Mail: gordon@svpal.org

Continued on page 59

OCEAN STATE ELECTRONICS

CALL, WRITE OR FAX FOR OUR FREE 104 PAGE CATALOG 1-800-866-6626

Step back into the past and build a Vintage tube type receiver or transmitter. Each kit comes with all the necessary components to get you on the air vintage radio style. A great opportunity to learn to build, troubleshoot and operate vintage tube type equipment.

THE CAKEPANION RECEIVER KIT 2 TUBES GENERAL COVERAGE REGEN



- Receives AM, SSB, and CW
- Regenerative Receiver Design
- Uses two 6AQ5 Tubes
- Continuous coverage 500 KC - 10MHz using pre-wound plug in coils as in old fashioned regenerative receivers (Coils sold below)
- Smooth Vernier Dial Tuning (No Logging Scale)
- J let front end isolates the antenna and adds RF gain.
- Solid frequency stability.
- Ultra sensitive reception.
- Hi Fi quality audio into 8 ohms. Enough to drive a small speaker (not included)
- Headphone Jack
- Audio clipper circuit eliminates key clicks and heavy static.
- Solid state power supply.
- Complete punched and drilled chassis (tuning caps and solder lugs are pre-installed)
- Well written detailed assembly instructions include color pictorials. Manual included.
- Assembly time approx. 6 hours
- Measures 9" Wide x 9" Deep x 2" High • Weight approx. 5 lbs.

ASSEMBLE A COMPLETE QRP STATION. THE CAKEPANION RECEIVER MATES PERFECTLY WITH OUR PCW-5 TUBE TRANSMITTER

Part No.	Description	Price
CPR-1	2 Tube Receiver Kit	\$119.95
CPR-8	Broadcast Band Coil 500KHz-1800KHz	\$14.95
CPR-160	160 Meter Coil 1.5 MHz-3.0MHz	\$9.95
CPR-80	80 Meter Coil 2.9MHz-7.5MHz	\$9.95
CPR-40	40 Meter Coil 4.0MHz-10MHz	\$7.75

DIGITAL LCR METER - ALSO MEASURES VOLTS, AMPS & FREQUENCY

At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 40H. Capacitors from 1 pfd to 400 mfd and resistors from 1 ohm to 40 meg ohms.
DCV to 1000 V, ACV to 750V
Freq. 1Hz to 4MHz
Great price for this instrument.

LCM-1950 \$79.95

VARIABLE CAPACITORS BROADCAST TYPE - 1/4" SHAFT

1 GANG 14-365PF	\$10.95
2 GANG 10-400/10-400/PF	19.95
3 GANG 15-500PF/SEC	12.95

Many more types available from small air trimmers to large 4KV tuner types.

6146W POWER TUBE

Rugged version of popular 6146B used in many transmitters. MFG. GE

\$17.95 EA. or \$37.00 MP

12BY7A Driver \$15.95

CALL US FOR ALL YOUR TUBE NEEDS.

LEARN COMPUTER THEORY BY BUILDING THIS KIT

DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 micro-processor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

- Uses the 8085 Microprocessor
- Uses the 2816 EPROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS RAM with I/O ports and timer
- Memory expandable option.
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments.

All this for only \$79.95

QRP CW TRANSMITTER KIT 2 TUBES, 3 BANDS



- 3 Band CW Coverage - 160, 80, 40, meters using prewound plug in coils (sold below)
- Crystal Control
- 5 Watts Output into 50 OHMS
- Single Antenna operation with built in TR Switch
- LED Output Power Indicator
- Cathode Keying Circuit
- Solid State Power Supply
- Tube Line Up 6CA Crystal OSC, 6AQ5 Final
- Complete with Pre Wound 80 Meter Coil Included
- Complete Instruction and Color Pictorials
- Use with any Receiver or Transceiver
- Includes 2 Crystals for 80 Meters - 3.64MHz & 3.70MHz
- Complete Punched and Drilled Chassis
- Measures 9"W x 9"D. Weight approx. 5 lbs.
- Assembly time approx. 6 hours

BE UNIQUE! GO QRP VINTAGE RADIO STYLE!

Part No.	Description	Price
PCW-5	2 Tube Transmitter	\$109.95
CPC-160	160 Meter Coil	\$9.95
CPC-80	80 Meter Coil (included)	\$9.95
CPC-40	40 Meter Coil	\$7.95
CY1812	180 Meter Crystal 1.812MHz	\$9.95
CY3560	160 Meter Crystal 3.560MHz	\$9.95
CY7040	40 Meter Crystal 7.040MHz	\$9.95

OTHER CRYSTAL FREQUENCIES IN STOCK. PLEASE INQUIRE.

DELUX CODE KEY



Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

\$16.95

SIGNAL INJECTOR/ TRACER

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.



Kit \$18.95
Assembled \$24.95

CODE PRACTICE OSCILLATOR & MONITOR



3" Speaker, Headphone, Terminal, Volume & Tone Controls. Uses 1 9V Battery

Kit \$19.95
Wired \$24.95

NEW PCDATAK™ SOFTWARE FOR MAKING PRINTED CIRCUIT BOARDS ON ANY WINDOWS 95 OR MS-DOS IBM COMPATIBLE PC!

- Make single or double sided PC Board artwork, up to 30" x 30".
- Print your artwork on any PostScript™ Laser Printer.
- Produces a 1X positive, ready to use with pre-coated board. No other artwork required.
- Produce industry standard solder mask and component layout for silkscreen art.

PCDATAK™ is supplied on one 3.5" diskette with a quick start manual. The full user's manual is larger and must be printed by the user (dot matrix printer ok); approximately 75 pages in length.

The NEW PCDATAK™ software lets you create PC boards ranging from prototypes to hobby projects, and on a par with the pros. You may do the complete printed circuit board layout artwork on your own PC, at a fraction of the cost of other programs. Print the layout on any PostScript™ compatible printer, either on regular paper to be photographed for a positive or negative, or on clear film to be used directly as a positive with other Datak products.

ALL THIS FOR ONLY \$29.95

TO ORDER CALL

1-800-866-6626

Ocean State Electronics

P.O. Box 1458 6 Industrial Drive

Westerly, RI 02891

Phone: 401-596-3080 Fax: 401-596-3590

Mail in orders please include \$5.00 shipping.

CANADA \$10.50 OVERSEAS \$16.00

Minimum order \$10.00 (before shipping)

R.I. Residents add 7% Sales Tax

VISA & MASTERCARD ACCEPTED



VERNIER DIALS

1-1/2" Diameter 0-10 Marking \$11.95
1-1/2" Diameter 0-100 Marking \$12.95
2" Diameter 0-100 Marking \$13.25



VERNIER DRIVE

American made 6:1 vernier drive. Has dual plate mounting flange with two tapped holes (2-56) for dial mounting. Input & output mate with 1/4" shaft.

\$9.95



SIGNETICS NE602AN

Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers

\$2.49



MINI-CIRCUITS SBL-1 DIODE RING MIXER

Double Balance Mixer
LO/RF - 1-500 MHz
RF DC - 500 MHz

\$7.95

OTHER MINI-CIRCUIT PRODUCTS IN STOCK



AM RADIO RECEIVER ON A CHIP (TYPE ZN414)

In a tiny (TO-92) transistor size case, a ten transistor tuned RF circuit that requires no setup or alignment. Nearly a complete circuit; add battery (1.1 to 1.6 volts), tuning coil and capacitor and crystal earphone. Data sheets with circuit examples included.

ZN414 \$7.95



FERRITE "LOOP-STIK" ANTENNA

Hard to find Loop-Stik Antenna. NOW IN STOCK!
For radio receivers.
Tunes the broadcast band.
540KHz-1600KHz

Measures 1/2" Dia. x 3 1/2" Long
Includes mounting bracket. Q=25, L=788µH

LA-540 \$2.25



PLUG IN COIL FORMS

Wind your own coils with these plug in coil forms. Made from Grade XX Phenolic. Equipped with rim, making it easy to insert and pull out. Coils measure 1 1/4" Dia. by 2 1/4" H. Exclusive of the pins. These are like the coil forms used in all the early receivers and transmitters. Hard to find item. Will mount in a 4, 5 or 6 pin tube socket.



MAGNET WIRE

Enamel coated solid copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

SIZE	PRICE	SIZE	PRICE
#14 \$4.00		#24 \$4.25	\$34 \$6.25
#16 4.00		#26 4.25	#36 6.45
#18 4.00		#28 4.85	#38 6.95
#20 4.00		#30 4.85	#40 7.85
#22 4.25		#32 4.85	

TOROIDS

IRON	FERRITE
T-25-2 \$ 40	FT37-43 \$ 70
T-25-6 40	FT37-61 70
T-37-2 55	FT37-77 70
T-37-6 55	FT50-43 85
T-50-2 65	FT50-61 85
T-50-3 65	FT50-77 85
T-50-6 65	FT82-43 1.30
T-68-0 90	FT82-67 1.30
T-68-2 90	FT82-88 1.30
T-68-6 90	FT114-61 2.30
T-80-2 1.20	FT140-43 3.50
T-200-2 6.00	FT240-61 8.75

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.

FM RADIO IC

TDA 7000
Ideal for small mono FM receivers. Features an RF input stage, mixer LO, IF amplifier stage, phase demodulator and muting circuitry. Also useful in LAN, data and SCA receivers.
Data Sheet Included.

TDA7000 \$9.95





Pacific Test Equipment

New Year

BLOWOUT SALE



PACIFIC
TEST EQUIPMENT

	HP 8657A Synthesized Signal Generator 0.1 - 1040 MHz with 10 Hz Resolution, +12 to -143.5 dBm 50W Reverse power protection, internal AM/FM Modulation Note: RF Connectors on rear panel (opt. 002)	Retail \$9,995 Regular \$5,900 Sale \$1,650
	HP 8656B Synthesized Signal Generator 0.1 - 990 MHz with 10 Hz Resolution, +13 to -127 dBm 25W Reverse power protection, internal AM/FM Modulation Note: RF Connectors on rear panel (opt. 002)	Retail \$7,900 Regular \$4,250 Sale \$1,250
	HP 5334B Universal Counter 0 to 100MHz, 9 digit per second resolution, rise/fall time, pulse-width, ac/dc voltage measurement. Frequency, period, ratio and time interval. Front and rear inputs in parallel. HP-IB	Retail \$2,305 Regular \$1,000 Sale \$195
	HP 3457A Digital Multimeter 3-1/2 to 6-1/2 Digit with extended resolution to 7-1/2 digits. dcV, acV, dcI, acI, Ohms, frequency and period. 1350 readings/sec. at 3-2 digits. HP-IB	Retail \$3,260 Regular \$2,495 Sale \$695
HP 3562A Dynamic Signal Analyzer Frequency range 64μHz to 100kHz. Network, spectrum, waveform and transient analysis. 80dB dynamic range. FFT. HP-1B		Regular \$9,500 Sale \$4,550

All above items come with a 90 Day warranty, standard accessories, and FREE UPS Ground shipping within the continental U.S.

We accept VISA, MC and prepayment in advance. Sorry no C.O.D.'s. Quantities are limited to stock on-hand. 20% restocking fee on returns.

We Buy Late Model Test and Measurement Equipment
 from manufacturers such as HP, Tektronix, Fluke, R&S,
 Wavetek, Anritsu, and others . . . Call for availability.
(408) 441-7341 or fax (408) 441-8049

We also carry:
Iwatsu/LeCroy - Topward -LG

For a free catalogue
 or inquires on other equipment
 call:
 (408) 441-7341 M-F 9-6 (PST)
 Ask for Erwin Talavera



PACIFIC
TEST EQUIPMENT


Pacific Test Equipment Corp.
 1450 Koll Cir. #111 • San Jose, CA 95112
 (408) 441-7341 • Fax (408) 441-8049

LOWEST COST LCD'S ON EARTH



VIDEO LCD

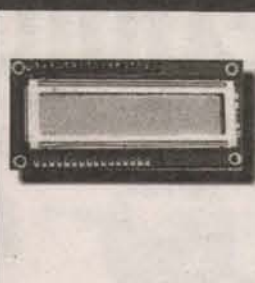4 Inch Video NTSC \$150
Sharp P/N 4LU4E
Composite NTSC & RGB Input
12:00 OR 6:00 Viewing Angle
Integrated Backlight & Inverter
Extended Temp: -10 to +60 C
Brightness: 260 nits
Power Consumption: 4.3 Watts
Contrast: 50 to 1



CHARACTER LCD

OPTREX DMF-5005SN-EW
240 x 64 Graphic EL Backlit STN \$30
OPTREX DMF-5005N
240 x 64 Graphic Reflective STN \$30
SANYO DM2023-7G1
2 x 20 Character Reflective STN \$8
SHARP LM20A21
2 x 20 Character Reflective STN \$8
VIKAY 2035TNLD NOTW-D
2 X 16 Character LED Backlit STN \$8



LCD MONITOR

10.4" DSTN or 12.1" TFT
Analog SVGA Input
Autosync
Auto Sizing
Automatic Expansion of VGA
images to SVGA (On 12.1")
Very Aggressive Pricing
Starting under \$500!



TOUCH MONITOR


EarthVue 10.4
10.4" VGA TFT
Analog VGA Input
105 Nit Brightness
RS-232 Touch Screen Option
Only 9.9"W x 7.7"H x 1.5"D
Ideal For Factory Automation
Fully Articulating Ball Mount
Only \$1095 With Touch



LCD DISPLAYS

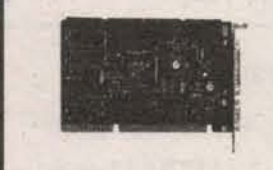6.3" Mono STN \$60
9.4" Mono Reflective \$60
8.4" TFT \$250
9.4" DSTN \$150
10.4" TFT \$350
10.4" DSTN \$240

NoteBook Screens
340 Models in Stock
Obsolete Screens Stocked
Hard To Find LCD? Call!



CONTROLLERS

ISA
PCI
PC/104
NTSC
Analog VGA
Complete LCD Kits with LCD,
Controller & Cable Starting
under \$200



EARTH

Computer Technologies

"The World Leader In LCD Recycling"


Ph: (949) 361-2333 Fax: (949) 361-2121
<http://www.flat-panel.com>

Write In 33 on Reader Service Card.

HAM GEAR FOR SALE

WANTED: ROCKWELL-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net

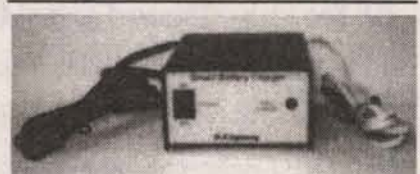HAM EQUIPMENT repair or overhaul Collins, Drake, Swan, Astro, Yaesu, Kenwood, etc. 20 years experience with former Slep Electronics Co. Same excellent service, same reasonable rates, satisfaction guaranteed. Brooks Electronics, 828-349-3503. E-Mail: rwbrooks@dnnet.net



THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.

KK4JK NEEDS to sell Ten-Tec, Mini D transceiver. Not used after factory refurbish. Paid \$800, sell for \$475. Wife ill. 803-534-6868.

NEW PRODUCTS FROM S & S: **UPGRADE YOUR OLD RIGS!** Digital dial (counter) has 10Hz resolution HF, 100Hz VHF and frequency range 50KHz to 230MHz; kit \$99.95; assembled \$149.95. **NEW Digital VFO** with 1Hz resolution to 54MHz; kit \$169.95; assembled \$219.95. S&H \$7 (Continental US). **GUARANTEED TO WORK.** For info send **SASE.** Call/write to order: S & S Engineering, 14102 Brown Rd., Smithsburg, MD 21783. 301-416-0661, E-Mail: N3SAD@aol.com or see <http://www.xmetric.com/sseng>

LML RADIO UHF GRMS repeater 15W programmable 256 channels \$120. 2 meter mobile amp 60 watt \$30. 800MHz scanners \$75 up. Free catalog 909-873-1319. Fax on demand 24 hr. 909-820-1885. Web catalog <http://members.aol.com/hrh6> Write 424 E. Shamrock, Rialto, CA 92376.



MIKEMASTER: A microphone preamplifier with noise gating & compression. Created by Marv Gonsior W6FR, March 1998 QST. Got noise get MikeMaster! For kit order #210-KIT at \$69.95. Assembled & tested (specify Kenwood, ICOM, or Yaesu wiring) order #210-ASY at \$89.95. Shipping for US & Canada is \$6.50, others add 15%. CA residents add 7.75% sales tax. For info send legal size SASE to A&A Engineering, 2521 W. LaPalma #K, Anaheim, CA 92801. P 714-952-2114, Fax 714-952-3280.

HAM GEAR WANTED

CB - SCANNERS

SALES, SERVICE: CB equipment, radios, modifications, power mice, echo-reverb boxes, kits, meters, filters, antennas, noise toys, mounts, hard-to-find items. Partial list \$1, complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492.

SCANNING USA: monthly magazine 100% scanning. All the news and product reviews from the writers you trust. Get more from your scanner. Subscriptions \$24.95, samples \$3. Call 1-800-651-0922 your Visa or MasterCard, or write 2054 Hawthorne, Joliet, IL 60435



ULTIMATE MODIFICATION BIBLE. Mind boggling is the only way to describe this 220 page book. Modification of CBs, channels, power, sliders, talk back and more. 10 meter radios, HAM RADIO, scanners, toys, meters, and more. Only \$29.95 + \$3.25 shipping. Phone orders 1-800-256-9895 (MC-Disc-Visa) No CODs.

ANTTRON 101 CB 10 METER base station antenna with isolation network, no bleedover, no splatter, no TVI tuning sleeve technology 3 piece fiberglass \$69.99. **Twin-Tronics, Inc.** PO Box 2571, Youngstown, OH 44507-0571. Send \$1 for literature, refundable. Ph 330-788-9693. Fax 330-788-7709.

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. www.cbciintl.com

SUPERSTAR, GALAXY, Mirage, Uniden, Cobra, microphones, power supplies, scanners hard-to-find products, picture price sheets. \$1 to cover postage (REFUNDABLE). Galaxy, Box 1202, Akron, OH 44309. Over 10 yrs. in business.

Network Service Tool Set

Popular installation and service tools for networks, modems and telephones. All hand tools are professional heavy duty type.

Use the compact tester on 10BASE-T (UTP & STP), thin Ethernet (BNC), 8-position Token Ring, AT&T 258A and EIA/TIA 568A/B. Automatically scans cables for continuity, wiring sequence and polarization. Tests STP cable ground. Testing installed cables is easy with Remote Terminator and gender changers (UTP and BNC). 9V battery included.

- Coax Stripping Tool, RG-58 & RG-59
- BNC Crimping Tool, RG-58 & RG-59
- Modular Cutting/Stripping/Crimping Tool (4, 6 & 8-Position)
- Multi-Network Cable Tester
- AC Receptacle Tester
- Cable Cutter

Order No. 55625 \$197.00



PC Service Tool Set

Contains all tools needed to troubleshoot & service IBM-compatible PCs. Set includes:

- AMI Diagnostic Software
- POST Card
- Logic Probe
- Digital Multi-Meter
- AC Receptacle Tester
- Serial Adapter
- Serial & Parallel Loopback Connectors
- DIP IC Puller
- PLCC IC Puller
- Grounding Wrist Strap
- Key Top Puller

Order No. 55000 \$198.00



CALL TODAY!

800-854-7393



PC Diagnostic Tool Set

- AMI Diagnostic Software
- POST Card

Order No. 55555 \$89.00

Network Installation Tool Set

- Network Tool Set 55625 without the Multi-Network Cable Tester.

Order No. 55600 \$99.00

Call for your FREE Catalog
Graymark®

P.O. Box 2015 Tustin, CA 92781
<http://www.labvolt.com>

Write In 34 on Reader Service Card.

240+ CHANNEL CB/HAM/COMMER-
CIAL radios: AM/FM/SSB/CW
export/domestic: RCI, Motorola, Uniden,
Cobra, Alinco, Kenwood, Mics, antennas,
linears, meters, books, night scopes, and
tons more stuff! Catalog \$3. MAXTECH,
Box 8086, New York, NY 10150. 718-
547-8244.

CB RADIO EQUIPMENT: Selling all
kinds of equipment! For details E-Mail:
rushead1@juno.com

KONNEX DISTRIBUTING. Call 1-888-
777-7874. PO Box 451372, Los Angeles,
CA 90045. CBs, antennas, meters, trans-
istors. Best prices. Credit card accept-
able.

WANTED: 2057 and 6LF6 electron
tubes. Please call 919-220-5603 or 919-
957-0019.

MUSIC & ACCESSORIES


COMPUTER HARDWARE

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

PENTIUM MOTHERBOARDS, PC100 operation, 1MB cache, on-board sound and 8MB AGP video, 2 ISA/2 PCI, \$96. **CPUs:** Celeron 128K 300/333 @ \$109/119. Pentium II 333/350/400/450 @ \$239/249/345/495. **Cyrix** 300/333 \$85/115. **IBM** 300/333 \$75/99. **AMD K6 MMX** with 3D now 266/300/350/400 @ \$85/99/129/209. **36X CD-ROM**, audio button \$45, 32/64MB SDRAM 10ns DIMM \$49/99, 64/128MB PC-100 DIMM \$101/199. **S3 Trio 3D 4MB (SGRAM)** AGP video card \$34. Call for current pricing, other parts and illustrated catalog, faxback catalog pages, 1-year warranty or better. tech-specialties, Inc., 5703 Heffernan, Houston, TX 77087-4113, 1-800-864-5391 for orders and tech support, fax: 713-307-0314, Internet: www.ts.nu

CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. 3 year warranty. Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in hi-resolution video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.
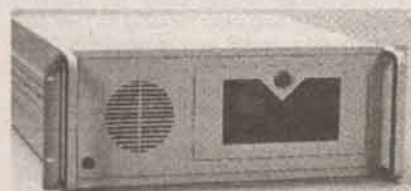
<http://www.pccables.com> **PC CABLES and PARTS.** 100s of hard-to-find new cables and parts, free technical information, low prices, fast online ordering & browsing.



19" RACKMOUNT PC chassis: Heavy duty, 4U, for standard 7 slots ATX motherboard. Optional 8, 12, 14 slots back panels available. Four (three hidden) 3.5"/two 5.25" drive bays, 4.625" front panel fan, power supply not included, \$189 with this ad! Monitor chassis \$269, keyboard chassis \$139. 8255-8253 I/O card with prototyping area \$69, 12-bit ADDA card \$89. Computronics Technology, 972-242-8087.

COLORADO BACKUP tape drives, 350MB, internal, \$35; Summagraphics digitizing tablets, \$95; thermal wire stripers, \$25. 334-889-4637.

CNC! MOTIVITY'S updated website is at: www.motivityusa.com 916-349-8757. A great place to buy CNC.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 OR fax 937-847-2350.

WE CARRY a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at www.rogerssystems.com or call 1-800-366-0579.

EVERYTHING NEW w/warranty! P300MHz MMX \$165, 1.28 gigabyte HD \$65. 15"/17" SVGA monitors \$145/235. Pentium systems from \$350. Also multimedia kits, hard drives, scanners, printers, SCSI adapters \$25. Memory, cases, etc. Call for monthly specials. CCI 714-778-0450. E-Mail: cci@net999.com

MII 300MHz multimedia systems, liquidation \$495. Monitors \$100, laser printers \$175, color inkjets \$95, notebooks \$350, 486DX motherboards + VGA \$30. Closeout prices on software. Call 714-778-0450.

HARD DRIVE liquidation 1,280 megabytes \$60. 8 gigabyte \$155. Mouse \$1.95, SVGA monitors \$135, flatbed scanners \$75, 56K modems 45, 386SX40 \$25, 1.2 floppy \$15, Adaptec SCSI controllers \$45, memory 1.25/megabyte. 714-778-0450.

SONY/AMIGA/MAC/IND. MULTISCANS 15" 0.26 DP 15.7-37KHz TTL/Analog, sync on green, & 150 Blem 15" SVGA's \$85. Expert Sony repair. Refurbished. Pikul & Assoc., 101 Glenfield Dr., Festus, MO 63028. 314-937-0335.

4 MB, 72 Pin SIMMs \$4 ea. Pikul & Associates, 314-937-0335.

Closing Date For Next Issue - February 5th!

WE BUY & SELL!

C and H

50 YEARS IN BUSINESS

SALES COMPANY 2176 E. Colorado Blvd. Pasadena, CA 91107

Take advantage of our special purchase on TEST EQUIPMENT

HIGH PRECISION DIGITAL MULTIMETER

FLUKE, Model 8810A. LED readout. 5-1/2 digit auto-ranging multimeter. Has ohms converter and true rms options. Accuracy AC volts 0.1% to 0.5%, AC rms 0.2% to 0.4%, DC volts 0.01%, ohms 0.02% to 0.2%. Max input voltage 1000 VDC or peak AC. Input impedance to 1 to 1000 meg ohms depending on range. Power input voltage 115 VAC 50/60 Hz. Has built-in carrying handle that can be used as a tilting base. Dimensions: 9-1/4" wide x 14-1/2" deep (including carrying handle) x 3-1/4" high.

Stock #TE9805

\$295.00

3-1/2 DIGIT DIGITAL MULTIMETER

FLUKE, Model 8000A. LED readout. Classic digital multimeter. Ideal companion to our Stock #TE9800 counter. Measures AC/DC volts/milliamperes plus ohms. Input range 0-200 mV to 1200 volts, 0-200 uA to 2000 mA. 0 to 2000 K ohms. Portable unit with carrying handle which also can be used as a tilt stand. Input impedance 10 meg ohms. Max. input voltage 1200 VDC or rms. Accuracy DC volts 0.1% of input + 1 digit. AC volts 0.5% of input + 2 digits 45 Hz to 10 KHz. Input power 115 VAC 50 to 400 Hz 5 watts. Dimen.: 8-1/2" wide x 12" deep (including carrying handle) x 2-1/2" high.

Stock #TE9801

\$75.00

3600 RPM DC MOTOR WITH OPTICAL ENCODER PACIFIC SCIENTIFIC, #4VM82-004-4. 30 volts nom. input voltage. Permanent magnet, reversible servo motor. Has Hewlett Packard optical encoder. Ball bearings. No load speed at 30 VDC input is 4600 rpm. No load current 0.75 amp at 60 oz-in load rpm is 3600, current is approx. 6.6 amps. Torque constant is 9.1 oz-in per amp. Rotor inertia 0.0007 oz-in-sec². Terminal resistance 0.89 ohm. Optical encoder is similar to "HEDS 6000" series. Encoder has 1024 counts per revolution, two channel quadrature output. Outputs are TTL compatible. Encoder requires 5 VDC input at less than 50 mA input current. Dual shafts: front shaft is 3/8" dia. x 3/4" long. This shaft is tapped on the end 8X32 tpi. Rear shaft is 1/4" dia. x 7/16" long. This shaft has dual flats that measure approx 3/16" across. Motor has four 8X32 tpi tapped mounting holes on front. A 3-3/16" dia. centering pilot is also provided on the front face. Dimensions: 4" dia. x 5-1/2" long (excluding shafts.)

Stock #DCME9850

\$79.50

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

TOLL FREE: 1-800-325-9465

Write in 35 on Reader Service Card.

AMAZING PRODUCTS! BOX 716 AMHERST, N.H. 03031

INFORMATION VISIT OUR "ACTION" WEB SITE@
UNLIMITED DEPT GEN 01198 <http://www.amazing1.com>

LASER WINDOW BOUNCE LISTENING SYSTEM

Remarkable concept allows user to hear sounds within a premise over a beam of laser light reflected from a window or similar surface. Experimental device provides hours of interesting and educational use. Utilizes a visible red laser that simplifies alignment and discourages illegal use. Usable range will vary-expect about 20 to 50 meters. Optional lens will increase range 200 to 400 meters! Further range requires expensive optics. Basic system setup requires patience in alignment and a sturdy video tripod (not incl.)



LWB5 Plans.....\$20.00 **LWB5K Kit/Plans.....\$149.95**
LWB50 Basic System Assembled and Tested.....\$199.95
LWB70 Higher Performance Version With High Coherence Laser Gun Sight, Extending Lens, Delux Headsets.....\$299.95

KINETIC ELECTRIC GUN

PIONEER A FUTURISTIC WEAPON!
500 Joules Energy Storage
Constant Current Charging
Triggered Spark Switch
Ballistic Velocities
Handheld Battery Operated
Labeled "Use Caution"

EGUN1 Plans with Parts List.....\$20.00
All Parts are Individually Available

3 MI FM BROADCAST TELEPHONE TRANSMITTER

Tunable On FM Broadcast. Excellent Telephone Project. Only Transmits When Phone is Used
VWPM7K Kit/Plans.....\$39.95
BEEP1K Beeper Alert Kit.....\$19.95

10-14" of Explosive Bolts of Lightning 250KV TESLA COIL

Transmit Wireless Energy Strange and Bizarre pyrotechnical effects. Ion Motors Anti-Gravity Size 20" H x 8" Sq Weight - 25 Pounds 115 Volts/2 Amps AC Labeled "Use Caution"

BTC3 Plans.....\$15.00
BTC3K Kit/Plans.....\$399.95
BTC30 Ready to Use.....\$499.95
BTC4 Plans 24 to 30" Sprk.....\$20.00

HIGH POWER STUNGUNS

STUN100 100KV StunGun.....\$19.95
STUN200 200KV StunGun.....\$39.95
STUN300 300KV StunGun.....\$49.95

LASERS

SUPER BRIGHT VISIBLE RED POINTERS

Signaling Beacon Visible Over 25 Miles!
Over 1/2 Mile Pointing Range
Light Up a Low Level Cloud
Great Fun At The Mo
Drive The Cat Nuts!
6Hrs On AAA Batteries
5 5/8X1/2" All Metal

LAPN65 15 mw equiv 2000ft.....\$24.95
LAPN63 30 mw equiv 4000ft.....\$49.95
LAPN63F Above Focussable.....\$54.95

NEW LASER "LIGHT SHOW" POINTERS

#LAPN6512...12 Design Show.....\$29.95!
#LAPN6524...24 Design Show.....\$34.95!!
#LAPN6540...40+Design Show.....\$39.95!!!

ION RAY GUN

Star Wars Technology Demonstrates Weapons Potential! See Ions in Motion!
IOG79 Plans.....\$10.00
IOG7K Kit/Plans.....\$99.95
IOG70 Assembled and Tested.....\$149.95
HIGHER POWERED DEVICE
IOG9K Kit/Plans.....\$149.95
IOG90 Assembled and Tested.....\$199.95

ATTENTION! HIGH VOLTAGE EXPERIMENTERS

Battery Powered Mini Sized Modules for research in: HOVERCRAFT, ION GUNS FORCE FIELDS, SHOCKERS
MINIMAX4 4KV@10ma.....\$19.95

FM TRANSMITTER KITS

ALL PARTS TO BUILD 6 LONG RANGE WIRELESS DEVICES

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter
- 2 1 Mile+ Telephone Transmitter
- 3 Line Powered Telephone Transmitter Never Needs Batteries!
- 4 Tracking/Homing Beacon "Beeping Transmitter"
- 5 Transmitter Broadcasts Video or Audio Outputs
- 6 Short Range TV/FM Disrupter NEAT PRANK!! Discretion Advised

All 6 Above Kits Plus FREE Info Data Pack on HELPFUL HINTS "Building and Tuning" Wireless Devices
COMBOX Parts and Plans for above.....\$59.95
COMBOP Plans for all the above.....\$10.00

GRAVITY GENERATOR

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build and levitate a small mock space ship from simple materials. Excellent scientific demonstration of a fascinating method of levitation. **Levitate an Object!**
GRA1 Plans and Book.....\$20.00
GRA1K Pwr Sup Kit/Plans.....\$99.95
GRA10 Assembled Pwr Sup.....\$149.95

SHOCK FORCE FIELD/VEHICLE OBJECT ELECTRIFIER

Hand Shock Balls. Wands. Electrify Objects. Great Payback for Those Wiseguys!
SHK1K Kit of Pwr Module.....\$19.95

1 800 221 1705 ORDERS ONLY! FAX 1 603 672 5406 INFO 9-5pm 1 603 673 4730 FREE CATALOG ON REQUEST
Pay by MC, VISA, Cash, Chk, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for PROFORMA

Write in 36 on Reader Service Card.

COMPUTER SOFTWARE

FREE IBM DISK CATALOG of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE <ASP>**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. momnpop@gate.net

MOD CHIPS for Sony PlayStation. Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. www.cconusa.com

LINUX & FREEBSD & LINUX & FREEBSD Linux and FreeBSD distributions on CD-ROM for as low as \$1.99. See our full range of Linux products and books at incredible prices. Use our secured shopping cart system at www.cheapbytes.com Visa and MasterCard gladly accepted. E-Mail: sales@cheapbytes.com fax: 209-367-8518. CheapBytes, PO Box 2714, Lodi, CA 95241.

CAM & MOTION SW/HW: Z-trace, PCB toolpath. Plotcam motion control, step drivers. cmheater@juno.com MSG/FAX 407-452-7197, 407-459-2729. www.me.gabits.net/ddt

MAKE \$\$\$ giving away our software! Business kit \$10 (refundable). RASCOM, 860 E. Carson St. #118-89, Carson, CA 90745.

MINI MAG-Reader. THIS IS THE ONE YOU HEARD ABOUT! Lightweight (67 grams). Compact (approx. 1-1/8 x 1-1/4 x 3-3/8). Operates on 2 or 4 CR2032 lithium batt's. Stores 100 2 track ANSI mag swipes. Easily downloads to DOS based PCs. Mini reader comes complete w/PC cable, software, batteries & instructions. All orders COD (cashier's check or money order only). Orders shipped via Fed Ex. Contact: **LIFELINE ELECTRONIX**, PH: 310-967-5956. LIFELINE9@AOL.COM

LIQUIDATION WIN 95/98, Office97, WindowsNT, 10 PACK CDs \$25, DOS \$25, Lotus SmartSuite \$10, Wordperfect Suite \$35, Antivirus \$5. Call 714-778-0450.

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

HP CALCULATORS wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, rkmmorrow@aol.com

WANTED: TERMINALS + PRINTERS: DEC, Wyse, IBM, ADDS, Okidata, Data South, Epson, C.I.T.O.H., etc. Call for quote on any surplus computer equipment. Call Jeremy, 603-673-8077.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

TEST EQUIPMENT

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

TERRIFIC VALUES: HP 8116A/001 50MHz pulse/function generator with burst, logarithmic sweep, \$4,400; HP 8111A/001 20MHz pulse/function generator with burst, \$2,300; HP 54100D 1GHz digitizing oscilloscope featuring automatic measurements, \$3,100; Tek AM 503, A6302 current probe, amplifier \$825; HP 83522A .01 to 2.4GHz plug-in \$3,750; HP 83570A 18 to 26.5GHz plug-in \$4,500; HP 3488A mainframe \$650 (cards available); HP 8161A/020 100MHz dual channel pulse generator \$2,750; Stanford Research SR 510 lock-in amplifier \$950; HP 8410C, 8410B, network analyzer mainframes \$625, 450; HP 8411A/018, 8411A harmonic frequency converters \$395, 295; HP 8743B/018, 8743A test sets \$575, 300. All in excellent condition with warranty. Pepper Systems (<http://home.earthlink.net/~peppersys>) 214-353-0257 (Fax 214-902-9511). E-Mail: peppersys@earthlink.net

KENTRONIX TEST EQUIPMENT SPECIALS. Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

HP 54602B 4 ch. 150MHz digital oscilloscope, opt 5 (enhanced video trigger), benchlink module/software (RS232 out), training kit probes, transferable HP warranty til 9/99, normally priced at \$5,000, sale price as new at \$2,500. Sorenson DCR-115B DC PS, 0-20V, 0-115A, CVCC, dual meter 220 input, \$800. 201-796-1405. padely@aol.com


NEW HEWLETT-PACKARD 141T CRTs \$195 EACH. We have quantities available. These are double boxed, unopened with late 80's date code, guaranteed. Fits all Kentronix. 732-681-3229 or FAX 732-681-3312. Mailing: Kentronix, PO Box 2444, Farmingdale, NJ 07727 or E-Mail: brian@kentronix.com



EDLIE THE KIT KING

Presents New-Do-

It Yourself Kits from Datak

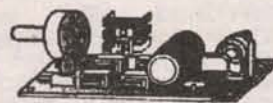

Each Kit comes complete with an educational explanation of the circuit.

Build these useful kits and have! Fun Too! Each kit comes with its own PC Board

Voice Changer (80-1051)

Your voice can be changed to add a vibrato, like those used to disguise secret witnesses. Or you may change your voice upward or downward: women sound like men and vice versa. Includes a very ROBOT voice as well. A microphone and speaker are included on the PC board; all that you need to add is a 9V transistor battery. This is a very novel and entertaining circuit. **\$12.95**

Universal Timer (80-1061)

Another novel circuit, that might be useful for special theatrical effects, or, if you are simply a practical joker! The circuit can produce sounds such as the tick-tock of a grand father's clock, a heart monitor (as ins the hospital) water on a tin roof, a motor boat, cricket, etc. Requires a 9-Volt battery. Includes its own speaker. **\$8.95**

Sound Activated FM Transmitter (80-2801)

A sound activated switch and hybrid sound turns on the transmitter. Sound switch activation level is user settable. Two-state transmitter has excellent range. When no sounds present the transmitter is powered down to save power **\$10.95**

Suction Cup Phone Pick-Up with Amplifier (80-5501)

No electrical connection to the telephone is Required. Attach a suction cup to the handset & turn on the amplifier. This project permits group listening to phone calls, or you can monitor any other oscillating electrical field Dual IC's provide a good quality amplifier. The circuit runs on 6VDC. Everything is included except batteries. **\$10.95**

4 Train Sound Effects (80-9101)

This Cob project will produce 4 very realistic user selectable sound effects that are ideal for model railroad. Throw any of switches to produce a train whistle blowing 3 times, a train chugging along, a level crossing bell & the "clickety clack" of a train crossing a bridge. Kit includes all parts including speaker Easy to assemble. operates on 2.4 to 6VDC. **\$7.95**

Stereo Preamplifier (80-1041)

Amplify any tiny audio signals about 50 times & deliver them to a power amplifier cleanly and undistorted. An AGC control eliminates pops or distortion. This circuit will be useful in boosting the output from tape heads, microphones or a magnetic cartridge etc. For input to an audio amplifier. Requires a 12VDC power supply at about 100mA peak **\$9.50**

Infrared Toggle Switch (80-5801)

Control just about any device using the remote control from just about any TV set. The circuit switches an on-board SPDT relay: Turn it on with the remote, and turn it off with another signal. The relay contacts are rated 1A at 125 V.A.C. The circuit operates any DC supply from 8 to 15v; use as an old calculator supply etc. This circuit can have some very practical Applications, such as turning on a light by an invalid. Your imagination is the limit. **\$15.95**

Variable Power Supply (80-6801)

This is a basic adjustable voltage power supply with a range of about 1.5VDC to 35VDC set by a potentiometer. It is capable of 2 Amps if you ad a simple heat sink. Circuit includes short circuit protection. **\$13.95**

Light Alarm (80-0801)

Detects very small amounts of light and sounds a piezo alarm. Put in your cash box or cupboard. Uses Darlington photo transistor MEL2 & 14011 I.C. A very educational kit. **\$8.50**

2 Stage FM Transmitter

This is an extremely sensitive and powerful FM bug; transmits to upper part of FM band. A two stage, three transistors FM transmitter. It operates on a 9V battery. The most sensitive & powerful that you can legally buy. The circuit employs an Electret microphone for added sensitivity. Unit can run on 6 volts, greatest output at 12V use. Use 9 volts and the short antenna wire included staying legal in U.S. **(80-3201) \$9.50**

Sound Effects Generator (80-103)

Another novel circuit, that might be useful for special theatrical effects, or, if you are simply a practical joker. The circuit can produce sounds such as the tick-tock of a grand father's clock, a heart monitor (as in the hospital) water on a tin roof, a motor boat, cricket, etc. Requires a 9-Volt battery. Includes its own speaker **\$7.95**

Photo Sensor with Control Relay (80-1031)

The most popular usage for this kit is to make you own night light. But you could switch just about any appliance either on or off with either darkness or daylight. Light sensitivity is adjustable over quite a range. The relay can handle up to 10 Amp A.C.. You need to add a 9-Volt transistor battery or a 9V. 25mA supply **\$8.95**

Edlie Has been in business for 52 years. Visit our Store

Call or Write for a
Free

76 page Catalog
800-516-645-4722
Outside the US Please send
\$3.00

Mail your orders to
Edlie Electronics Inc
2700 Hempstead Tpke.
Levittown, N.Y. 11756
Order Toll Free
1-800-645-4722
IN NYS 516-735-3330

Checks, or Money orders are Accepted by mail No C.O.D. Shipping & handling charge \$5 For the continental United States For all Others Including Canada, Hawaii, Alaska, & P.R. must pay full shipping charges

We accept MC, Visa, & AE



To order by Fax Call 516-731-5125
For Info Call 516-735-3330

2539 W. 237th Street, Bldg. F, Torrance, CA 90505
Order desk only: USA: (800) 872-8878 CA: (800) 223-9977
LA. & Technical Info: (310) 784-5488 Fax: (310) 784-7590
OEM INQUIRIES WELCOME

TIMELINE INC.

Over 13 years and 31,000 customers and still growing

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

LIQUID CRYSTAL DISPLAYS

240x64 dot LCD with built-in controller.
AND 4021ST-EO. Unit is EL back-lit. \$59.⁰⁰ or 2 for \$109.⁰⁰ or
OPTREX DMF5005 (non back-lit) \$49.⁰⁰ or 2 for \$89.⁰⁰
20 character x 8 line 7/16" x 2 1/2" H The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface

16x1.....\$7.00	20x2.....\$10.00	32x2.....\$8.00
16x1 (lg. char.).....\$10.00	20x4 (lg. char.).....\$10.00	40x1.....\$8.00
16x2.....\$7.00	20x4 (lg. char.).....\$10.00	40x2.....2 for \$20.00
16x2 (lg. char.).....\$10.00	24x2.....\$10.00	40x4.....\$20.00
16x4.....\$15.00	32x4.....\$10.00	4x2.....\$5.00

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mr.	price	size	Mr.	price
640x480 (backlit)	Epson	\$25.00	480x128	Hitachi	\$10.00
640x400 (backlit)	Panasonic	\$20.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$10.00	240x64	Epson	\$15.00
			160x128	Optrex	\$15.00

6" VGA LCD 640X480, Sanyo LMDK55-22 \$25⁰⁰

MONITORS

9" COLOR SVGA MONITOR \$179.⁰⁰
Fully Enclosed - Tilt and swivel type.

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15KHz • Ability to do 40 and 80 column.
5 inch Amber \$25.00 • 7 inch Amber \$25.00
9 inch Amber or Green \$25.00

5" COLOR MONITOR \$39.⁰⁰

• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
• Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mfr. Samtron

2 for \$89⁰⁰

HACKER CORNER

Encased Spread Spectrum RF Modem \$99.⁰⁰

The ProxLink Radio Module is a small communication device which replaces cables between RS-232 devices with wireless RF (Radio Frequency) technology. Attaching a pair of ProxLinks to any two devices with three wire asynchronous RS-232 ports allows wireless data transmission at rates up to 19.2 Kbaud (full duplex) over a range of 500 - 800 feet. Modules use 900 Mhz spread spectrum radio for communication which does not require an FCC site license. A variety of configuration information (radio channel, baud rate, serial port configuration, etc.) can be programmed into module's non-volatile memory by host PC to provide compatibility and avoid overlapping systems. Configuration changes are supported by menu driven, on-board software. Commonly used Terminal Emulation software and transfer protocols can be used for configuring modules and transferring data between computers. ProxLinks require only 6-9 VDC (350 mA), RS-232 (9 pin sub-D) interface, and small (~4") whip antenna for operation. Unit size is 4.0" x 6.5" x 0.75". Installation schematics and application details available. These are 100 Mw power.

4 INCH LCD MONITOR \$49.⁰⁰

Compact (4.4" x 3.8" x 1.4") TFT active matrix LCD color monitor including fluorescent backlight. Analog RGB and composite sync input with switchable horizontal / vertical viewing. Low power consumption and long life backlight make it ideal for security and door phone use. Single 8 VDC supply and good resolution allow mobile operations or use with laptops. Standard ribbon cable - Molex connector interface. Complete specifications included.

Write in 38 on Reader Service Card.

EFRA TOM FRK-L rubidium oscillators!
10MHz sinewave output at 0.5Vrms. Long term stability: <1 x 10⁻¹⁰/month. Includes optional Mdl EEK-10 heatsink and I/O connector. Used, calibrated, with fresh NIST traceable calibration certificates only \$500 ea. Requires 23VDC to 32VDC at 1.7A max. Full specifications and picture at our website. (Quantities available) **Fluke 732A DC reference standard.** The standard of the industry! Complete with NIST traceable certification with NIST numbers, \$1,950. **Lehman Scientific 1-800-784-8680 Visa/MC. www.lehmanscientific.com**

EQUIPMENT MANUALS we have 1000's of service and operators manuals for all types of test and measurement equipment from 1950 to present. All test equipment manufacturers are represented. Call, write, or fax your want list. Please include mfg.'s manual P/N unit serial numbers if known. **Manuals Plus, Box 549, TAD #601, Tooele, UT 84074. 435-882-7188, FAX 435-882-7195.**

MICROSCOPES: NEW and used! Used B&L StereoZooms! Check our website. **Handheld LCR/DMM/frequency counter, BelMerit DX460L**, all standard DMM functions plus frequency to 20MHz, TTL, and CMOS logic, capacitance meter and inductance meter and more! Comes with holster, battery, test leads and manual. Three-year factory warranty! Special price \$95. **Sencore SC61 waveform analyzer, DC 60MHz**, oscilloscope plus digital readout of frequency, P-P volts, Delta volts, Delta time, etc. Comes with 2 brand new Sencore probes! Fully checked out and guaranteed \$750. **Lehman Scientific 1-800-784-8680 Visa/MC. www.lehmanscientific.com**

AFFORDABLE HP power sensor repair! Most 8481As repaired for \$260 or less. We also handle 478As and many others. Call or fax for more information. **Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.**

WANTED: WESTERN electric test equipment. Tube-type only please. Freq. measuring sets, oscillators, amplifiers, parts, tubes, etc. 1-800-251-5454.

BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING, 3198-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.

POCKET TESTBENCH, tiny, portable, RS-232 instrument. Scope, logic, counter, generator modes. **Oricom Technologies, 303-449-6428 www.sni.net/~oricom**

WANTED: RADIO service monitors, IFR, Motorola, HP, Marconi, also late model HP equipment. 716-763-9104 or Fax 716-763-0371. <http://www.amtronix.com>

BEST PRICES on guaranteed test equipment. Oscilloscopes, Tektronix 305, 454, 475, SC 504, 2225, 2246, & others. Huntron Tracker 2000, Fluke, HP and other fine used test equipment. Check us out at: www.lonemtn.com

SPECTRUM ANALYZER in a probe. \$249. View thru your inexpensive scope. WWW.spectrumprobe.com

WANTED: ELECTRONIC estates. Ham, broadcasting, military, test, public address, tubes, transformers, telex equipment. The bigger the pile, the more worthwhile. We fly anywhere. **Sumner McDaniel 1-800-251-5454.**

POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$78. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. **Science Workshop, Box 310B, Bethpage, NY 11714. http://www.science-workshop.com**


TEST EQUIPMENT for sale/wanted: RF, Microwave, video and fiber optic. Cable TV, Broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. **PTL Test Equipment, Inc. Phone 561-747-3647 FAX 561-575-4635.**



ENGINEER TESTED: Spectrum analyzers, frequency counters, frequency standards, meters, scopes, generators, curve tracers. Temperature, time, weight, light, sound, distance, etc., measurement instruments. **VISA, MASTERCARD, AMEX.** "Performance tested." NIST calibrated. Warranted. **New & used. Gary N62D. HTTP://TECH-SERVICES.COM**

USM 338 HP 1700B/300, \$150; Heathkit frequency counter SM2420 0-512MHz \$29; Tek 191 sig-gen \$50; Call 909-873-1319.

"Let Us Cover Your Parts!"

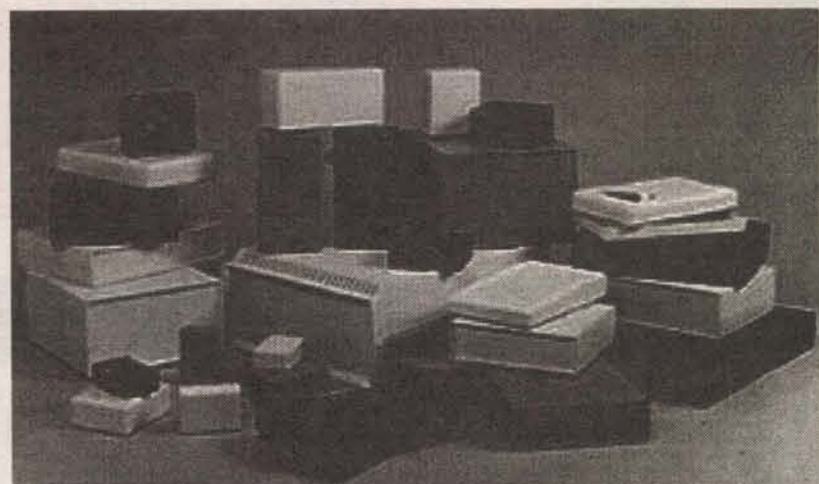

- Eye-Catching Enclosures
- Exceptional Value
- Massive Inventory
- Custom Machining
- Quality Silkscreening
- EMI/RFI Shielding
- Over 50 Sizes

Call, Fax, or Visit On-Line for a
FREE Catalog
email: simco@simcobox.com




SIMCO



(800) 780-9090 www.simcobox.com FAX (941) 452-6200

Write in 39 on Reader Service Card.

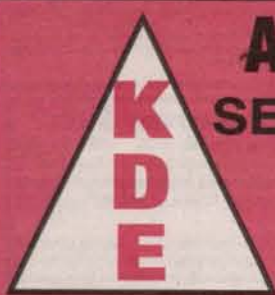

ALL CABLE NEEDS SE HABLAN ESPAÑOL CONVERTERS ALL BRANDS WITH REMOTE

TOLL FREE ORDER LINE:
1-800-361-4586

ALSO

HOOK-UP HELP LINE:
1-847-233-0621

NO ILLINOIS SALES



COD

ON-CARD

KDE ELECTRONICS CORP.
P.O. BOX 1494, ADDISON, IL 60101

Write in 40 on Reader Service Card.

**COMPETITIVE
PRICING**

**PARENTAL
LOCKOUT
AVAILABLE**

**HOURS: Mon. thru Fri.
9-6, Sat. 10-2
30-DAY MONEY BACK
GUARANTEE
1 YEAR WARRANTY**

LARGE ASSORTMENT of used test equipment for sale. Request catalog or visit our website. Stevenson Equipment Company, 609-888-2846, Fax: 609-888-2847. Website: <http://www.stevensonlabs.com>

TEST EQUIPMENT repair or overhaul Tektronix, HP, Wavetek, Boonton, etc. 20 years experience with former Slep Electronics Co., same excellent service same reasonable rates, satisfaction guaranteed. Brooks Electronics 828-349-3503. E-Mail: rwbrooks@dnnet.net

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

DESOLDER STATIONS: own pump, Pace PPS100A/SX25, \$175; MBT 200A desolder/solder, \$350; MBT 250A, \$750; SX25 handpiece, \$75; Ungar 4024, \$200; Weller DS1000 digital readout, \$350; DS100, \$200; Mesel hot tweezer, \$50; soldering: Weller EC2000 digital adj. temp, \$100; WTCP, \$45u, \$60nu; EC1301 pencil \$40u, \$60nu; 1 lb. solder, \$8. 310-515-2058.

TEKTRONIX SALE: 465B \$385; 465B DM44 \$425 2 available; 475A DM44 \$475; 5223 as new \$150; Tek 7104 1GHz frame \$850; 7A13 \$100 LED; 7A18 \$45; 7A19 \$75; 7A26 \$60; 7B53A \$60; 7B80/7B85 \$65 either one; 7B92A \$125; DC504 \$100; PG-507 \$200; PG-508 \$250; P6046 probe \$200; all with money back warranty. **Psitech Plus**, 707-745-4804, www.psitech-plus.com

HEWLETT PACKARD SALE: 1630G logic analyzer with all pods, \$450; 1630D \$300; 3325A synthesizer function generator, \$550; 5335A opt 20,40 \$325; 3586C opt 004 synthesizer/level generator, \$600; as new 1980B oscilloscope meas. sys., \$500; all with money back warranty. **Psitech Plus**, 707-745-4804, www.psitech-plus.com

WAVETEK 178 programmable waveform synthesizer \$725. Racal Dana 9303 true RMS level meter with head as new, \$350; Mod. 9515 opt 01/15/55E 7 digit timer counter \$350; Mod. 6002 opt 10/24/55 7.5 digit microprocess contr. DMM \$400; Fluke 8921A true RMS voltmeter \$300; Philips PM 6654 high resolution programmable timer counter, \$250. **Psitech Plus**, 707-745-4804 www.psitech-plus.com

LOWEST PRICES! Check out Metric's "Current Specials" at <http://www.metric-sales.com> Great deals on top quality refurbished test equipment. Call 1-800-432-3424 for a free catalog.

SUCH A DEAL! Check out Metric's "Current Specials" at <http://www.metric-sales.com> Great deals on top quality reconditioned test equipment. Call 1-800-432-3424 for a free catalog.

WANTED! ELECTRONIC test equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. **1-800-432-3424** Fax: 510-264-0886.

WANTED! ELECTRONIC test equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. **1-800-432-3424** Fax: 510-264-0886.

TEKTRONIX TM504, FG503, 3MHz function gen., PS503A, dual 20V PS, 1A, DM501A 4.5 dig. VM, \$600. A-Comm Electronics, 303-341-2283.

TEK SCOPES: We have most 2200, 2400 series in stock. Competitive prices. Metrowest Technologies PH 508-478-7613, FAX 508-634-3854. www.metrowesttech.com

WANTED! ELECTRONIC test equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. **1-800-432-3424** Fax: 510-264-0886.

SPECTRUM ANALYZERS: Tek 7L5, 7L13 plugins and 490 series in stock. Metrowest Technologies PH 508-478-7613, FAX 508-634-3854. www.metrowesttech.com

TEK PLUG-INS: We have many on the shelf. Metrowest Technologies PH 508-478-7613, FAX 508-634-385. www.metrowesttech.com

HP SPECTRUM analyzers: 8555A, 8558, 8559, others. Performance guaranteed. Metrowest Technologies PH 508-478-7613, FAX 508-634-3854. www.metrowesttech.com

SHOPPING FOR equipment: Metrowest Technologies, Bostons Equipment Supersource. Call for a quote on your next purchase. Metrowest Technologies PH 508-478-7613, FAX 508-634-3854. www.metrowesttech.com

HP 4815A Z-meter: Sandford Associates. **TOTAL** service specialist. Repairs warranted to HP/QA factory specs. Former HP tech/supv with expertise, parts, and tooling. Tel/fax: 908-852-7989, E-Mail: GS_SA4815@compuserve.com

FREQUENCY STANDARDS sales and service. Rack mount or modular rubidium, 16 output distribution amplifiers, inquire. Also quartz modules and disciplined standards. Corby Dawson 805-736-0288.

FOR SALE: HP 141T spectrum analyzer main frame. \$200 plus \$15 shipping. Have 4 left. Phone John Bartholomew 304-525-8793.

HEWLETT PACKARD: 3497A data acquisition/control unit, \$425; 6942A multiprogrammer, \$250; 3400A, \$100; 400E, \$75; 204D, \$80; 7550A plotter, \$175; 5314A, \$75. **Tektronix:** 1230 logic analyzer, \$275; 575 curve tracer, \$125. **Wavetek** III generator, \$75. Kent 515-232-7528.

SPECTRUM ANALYZER, Tektronix 496, \$3,200, also Tek 1502 TDR, Tek 2215 scope, Wavetek 3007, signal generator. 407-423-1365.

HP 8901A modulation ana., \$1,500; HP 3325A synthesizer function gen., \$1,500; HP 8165A, programmable function gen., \$2,000; HP 606A sig. gen., \$300; HP 610C sig. gen., \$300; HP 628A, \$300; HP 8660C, 86632B, 866303A, \$2,000; HP 8640B, opt. 1, 2, \$1,500; HP 8640B opt. 1, 3, \$1,200; Wavetek 1034A power meter AC or DC portable 10MHz, 20GHz, +10dBm, -50dBm, \$450; HP 5245L counter, \$200; HP 8683B sig. gen. 2.3-6.5GHz, \$2,000; A-Comm Electronics, 303-341-2283.

TEST EQUIPMENT for sale: <http://www.a-comm.com>

SENCORE FC51 1GHz counter, \$100; HP 5316A univ. counter HPIB, \$600; HP 5334A 100MHz universal counter opt. 060, \$1,000; HP 5335A DC 1200MHz statistical counter, \$1,500; Boonton 9200 RF voltmeter and probe, \$500; C-Corr 4329E RF amp. 10Hz-70MHz 20dB 250MW PO, \$100; Bird 6735-300 1.2KW RF load and wattmeter, 25-500MHz, \$600. A-Comm Electronics, 303-341-2283.

SECURITY

SURVEILLANCE EQUIPMENT wanted. Audio, video, RF, telephonic, countersurveillance, communications, any other professional equipment. Fax 410-836-1190. E-Mail to Sales@swssec.com Voice 410-879-4035. www.swssec.com/used.html

Metric
Equipment Sales, Inc.

800-432-3424
Fax: 510-264-0886
www.metricsales.com

RENT • BUY • SELL
Yes, we will buy your surplus equipment!


**Scopes, Meters, Analyzers, Power Supplies, Signal
Generators, Counters, Recorders and more**

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu,
Wavetek, Keithley, and more

Test & Measurement Instruments

**Over 7000 Models • 6-Month Warranty
Save 30-90% • 5-Day Free Trial**

Any waveform you want!

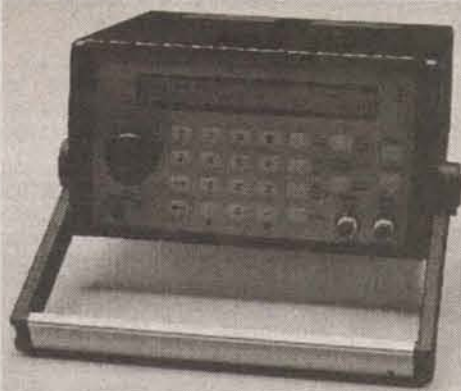

Telulex Inc. model SG-100A

New Features:

- ✓ 21.5 MHz
- ✓ .01 Hz steps
- ✓ multi-unit phaselock

Telulex Inc.

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy!
.01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator


Ramps, Triangles, Exponentials, Noise & more.
0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator

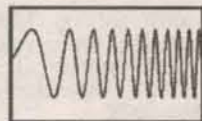
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

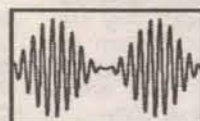


Int/Ext AM, SSB, Dualtone Gen.

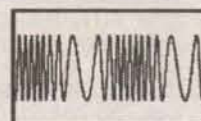

Int/Ext FM, PM, BPSK, Burst

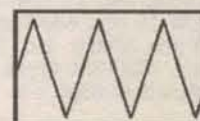


Ramps, Triangles, Exponentials

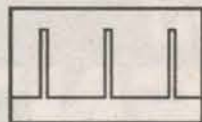

Pulse Generator



Noise

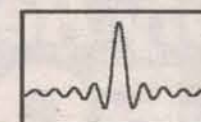

Arbitrary Waveforms



Unlimited Possibilities!

2455 Old Middlefield Way S
Mountain View, CA 94043

Tel (650) 938-0240

Fax (650) 938-0241

<http://www.Telulex.com>

Email: sales@Telulex.com

Write in 42 on Reader Service Card.

8 CAMERA DUO-QUAD DISPLAY BLOW-OUT. 8 camera B+W 2 page hires. real-time quad w/2 video outputs. Selectable display quad/sequencer or both. These units are brand new discontinued American Dynamics AD1475A. Similar units in this magazine are twice the price. Not a China imitation. Industrial unit. Our reg. price \$350, **NOW \$175 EA.** While they last! Pro-Vid Sys. 781-933-0827. E-Mail: RicksVideo@MSN.COM



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.



FACTORY SALE! QVS 104: 4 BNC/RCA 12 pixels, 256 scale. 8.5" (W) x 2" (H) x 5.5" (L). \$169 @ 5 pcs., \$149 @ 10 pcs. Also available: 8-1 video auto-switcher, \$65 @ 5 pcs., \$58 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com



FACTORY SALE! IC 113: PIR motion detector w/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. Matco, Inc. 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com



FACTORY SALE! CNL100, CNP101: 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 1.27" (W) x 1.27" (L) x 1" (H). \$43 @ 5 pcs., \$38 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com



FACTORY SALE! PS 102: Built-in pin hole CCD, lens size: 1.2mm. 5-1/2" (D) x 1.7" (H). \$69 @ 5 pcs., \$65 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com

Subscribe to Nuts & Volts.
Check out our web site and take advantage of our special subscription offer.
<http://www.nutsvolts.com>
For new subscribers OR renewals!

GIANT 50 LED BLINDING OUTPUT OUTDOOR CLUSTER DISPLAY

Now you can attract attention outside even on the brightest day. Make traffic lights, stop signs, attention getters etc. The giant 50 LED cluster display type LT6750 by Sharp consists of 36 jumbo yellow green LEDs connected in series which produce an incredible 8.16 cd output at 19.0 volts and 14 jumbo red LEDs connected in series which produce and incredible 6.8 cd output at 13.2 volts. The LED cluster is mounted in a 2 1/16" Dia. black cylinder with built in sunshade. Features 3 lead (common, (-) red, - green). Viewing angle in the horizontal direction is ± 35 degrees and in the verticals direction ± 15 degrees. We have seen similar units advertised in surplus catalogs for about \$20 and of course the factory sells our cluster display for a fortune, however you can own them for an incredible blowout price while our supply lasts. Brand new prime!

G9987 \$8.95 ea. • 3/\$25.00 • 200/\$1500.00

OMNIFLEX UNI-DIRECTIONAL DYNAMIC MICROPHONE

Super dynamic microphone with long flexible cord and 1/4" mono plug features uni-directional response. Deluxe hand held black case microphone is about 8 1/2" long with 600 ohms impedance and -75dB sensitivity at 1KHz. Great frequency response of 80-12KHz. Has built in ON/OFF switch in handle. Brand new in retail blister package. Perfect for your next Karaoke party! Type OM88 made for St. Louis Music Inc. The wholesale price of these was \$28.95.

G9966 \$19.95 ea.

THORSEN 22 PIECE SCREWDRIVER & BIT SET

Complete set of high quality insulated handle tools with chrome plating and hard vanadium steel tips. Includes 4 different size standard slotted screwdrivers, 5 different size Phillips head screwdrivers, a 10 piece set of torx and misc. insert bit set with insert bit handle, 2 offset Phillips/slotted screwdrivers and a handy wall mounting holder bracket. These are high quality tools not junk sold by others. Brand new in retail blister package.

G9963 \$18.95 ea.

.047 FARAD 5.5VDC SUPER CAP

Small super cap is only 1/2" Dia. x 1/4" Tall but is rated .047 Farad (47,000 MFD) at 5.5VDC. Great for memory backup or tiny robotic applications. Prime!

G1035 \$1.00 ea.

DELUXE ZENITH ALLEGRO MONO WIRELESS HEADPHONE

These are similar to our wireless stereo headphones except they respond in mono. They have the same cushioned headphones but have only one volume control that controls both sides of the headphone. The frequency response is 50Hz to 15,000Hz and we found the sound incredibly good. Transmitter comes with an AC adapter and the wireless headphones require 2 AA batteries (not included). Range is 33ft and these come with 4 different adapters for easy hookup to your VCR, TV, stereo, CD player etc. These are great for those times when you don't want to disturb others in the room. Brand new in manufacturer retail box. Worth much more than our low price.

G9967 \$19.95 ea.

DELUXE STEREO WIRELESS HEADPHONES

Made by Zenith Allegro®, these deluxe stereo wireless headphones feature a powerful IR transmitter, with AC adapter, a deluxe adjustable cushioned band headphone with padded ear cushions, an optional microphone, and 4 different jack adapters. Each side of the stereo headphone has its own volume control. Headphones require 2 AA batteries (not included). The stereo headphones have a tremendous frequency response of 35Hz - 15,000Hz with 1%THD and a S/N ratio of 45db. Operates up to 100 hours from a set of batteries. Has red led on indicator on transmitter and headphones, on/off switch and range of 33ft inside a room. Not only are these simple to hookup and use but also the sound quality is incredible. Now you can enjoy TV, CDs, stereo, VCR etc. without disturbing others. Brand new in manufacturer retail box. Worth about \$100.

G9968 \$39.95 ea.

2 CELL GE FLASHLIGHT

Powerful mini flashlight by GE features a high tech black plastic case and operation from 2 AA batteries (not included). Packed inside each flashlight is a mail in rebate coupon good for up to \$3.00 (expires 9-1-1999) with the purchase of GE/Sanyo batteries. Buy some of the batteries at your local store and it's almost like you'll be getting this nice flashlight for free!

G9961 \$1.00 ea.

ELECTRONIC GOLDMINE
WE ALSO OFFER OVER 150 DIFFERENT ELECTRONIC KITS.
ELECTRONIC GOLDMINE
PO Box 5408
Scottsdale, AZ 85261

<http://www.goldmine-elec.com>

NOTE: All items subject to prior sale; All prices expire 3-31-99

For Phone Orders Call: 800-445-0697
or Fax Your Orders to: (602) 661-8259
For a Free Catalog Call: (602) 451-7454
Foreign catalog request: send \$5.00

Minimum Order: \$10 (plus min. \$5 Shipping and Handling). We accept MasterCard, Visa and personal checks; however, we cannot accept personal checks on orders outside the U.S. Minimum Foreign Order Amount: \$50 (plus a minimum \$10 S&H)

MOTORIZED 20K POTENTIOMETER

Precision made motorized pot by Shokai features a very compact gear reduction assembly with mabuchi motor. The pot has a panel mount bushing with nut and has a long slotted shaft for a knob (if desired). Pot can be manually turned with shaft or automatically turned by applying any voltage from 3 to 12VDC to the motor. Reverse the polarity to cause the pot to turn in the opposite direction. This precision marvel is great for robotics, servo systems, remote control instrumentation, laboratory equipment, etc. Pot has 3 wires connected to it. Motor has 2 wires connected to it. Size about 1 1/2" X 1 1/2". Linear taper 20K rating. Brand new!

G9962 \$3.49 ea. • 10/\$29.95 • 100/\$265.00

Write in 43 on Reader Service Card.



FACTORY SALE! AS 1000, 2.4GHz transmitter & receiver. Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 380 TV line. \$189 @ 5 pcs., \$179 @ 10 pcs. Additional camera \$99 @ 10 pcs. Matco, Inc. 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com

ALARM CATALOG of panels, motion detectors, contracts, CCTV & more. Equipment that only the professionals can buy. Send \$2 to HES Electronics, POB 183, Brick, NJ 08723. Mention this ad and get a \$10 off certificate! Visit www.heselectronics.com

SATELLITE EQUIPMENT

DSS AUTOMATIC LNB cutoff. Very low noise, no adjustments, works with all models. \$60 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

SATELLITE EQUIPMENT available: Receivers \$25 and up; 20-25 LNB \$30; C-KU feed horns \$65. Call 757-599-4408.



FREE BIG dish catalog. Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com Call 1-800-543-3025.

FREE SATELLITE TV CATALOG. Tech books, installation videos, analysis software 1-800-843-2425 or www.baylin.com

USED SATELLITE EQUIPMENT. You name it, we have it. LNAs, downconverters, drives, receivers. Working condition guaranteed. Call 765-385-2305.

FREE SATELLITE TV INSTALLATION TOOLS AND EQUIPMENT CATALOGUE: for complete installation. Consumers, dealers, distributors and technicians welcome. 1-800-646-8665 or www.natropolis.com or fax 651-641-1898. Natropolis, Int'l, PO Box 14115, St. Paul, MN 55114.

L BAND quadrifilar T/R antenna, 55 dB LNA, 20 watt HPA, works great for remote GPS. Info at afstar.com



BEST PRICING on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. www.skyvision.com Call 1-800-543-3025.

1998 DSS SOFTWARE COOKBOOK 700+ CD-ROM COLLECTION CLONING REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIAL: 1ST 500 ORDERS GET 500+ ADDITIONAL PROGRAMS!) WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE!!!). DSS TEST-CARD INFO SOURCE MANUAL \$10. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS, USA. CALL NOW 352-429-5496.

SATELLITE RADIO BOOK AND GUIDE. New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

THE BEST is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at www.acdinc.com for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

DSS TEST CARD information. Call toll free, 1-888-416-7296.

MILITARY SURPLUS ELECTRONICS

MILLIONS \$\$\$ in "scrap gold" from old computers and electronics junk. Message: 603-645-4776 or www.tiac.net/users/quicksand/goldtek.htm

AUDIO - VIDEO - LASERS

MOD CHIPS for Sony PlayStation. Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. www.cconusa.com

SYNC-A-LINK UNIVERSAL VIDEO SYNC GENERATOR restores all horizontal & vertical sync lines, DC level, compensates for inverted video, color phase, from standard or distorted analogue video-type formats. Comes complete with operations manual & 90-day warranty. \$160. 918-479-6451 or write to Sync-A-link Communications, PO Box 4, Locust Grove, OK 74352.

Quality Reconditioned TEST EQUIPMENT

General Radio 1482 Standard Inductors Special \$250.00

Available in 1482B, 1482D, 1482E, 1482F, 1482L, 1482J, 1482K, 1482L, 1482M, 1482P, 1482Q.

Bird 4380A-488 \$300.00

IEEE-488 Interface.

Bird 4410A \$300.00

Wattmeter, Frequency range 0.2 to 2300 MHz, 0.002 to 10,000 Watt. Elements are not included.

Bird 61 \$175.00

Wattmeter, .5/ 2.5 Watts. Elements are not included.

Bird 611 \$175.00

Wattmeter, 15/60 Watts. Elements are not included.

EIP 545 Special \$750.00

Microwave Frequency Counter, 10 Hz to 18 GHz frequency range (3 bands), 12 digit LED display, time base: 10 MHz, aging rate <3x10⁻⁷/month, 50Ω input.

EIP 545A Special \$895.00

Microwave Frequency Counter, 10 MHz to 18 GHz frequency range (3 bands), 12 digit LED display, time base: 10 MHz, aging rate <3x10⁻⁷/month, 50Ω input.

Avcom PSA35A Special \$995.00

Portable Spectrum Analyzer, low bands 10 MHz to 1750 MHz; high bands 3.7 to 4.2 GHz. 60 dB dynamic range.

Hewlett-Packard 5335A Special \$695.00

200 MHz Universal Counter, built-in automatic risetime, duty cycle & pulse width.

Hewlett-Packard 3312A Special \$575.00

Function Generator, 0.1 Hz to 13 MHz in 8 decade ranges, AM/FM, sweep, trigger, gate and burst.

Hewlett-Packard 3325A \$1250.00

Synthesizer/Function Generator, 1 uHz to 21 MHz, 11 digit resolution.

Hewlett-Packard 3488A \$550.00

Switch Control Unit, up to 50 channels, dc to 300 MHz signal switching, can hold up to 5 modules in the 444XX series.

Hewlett-Packard 8350B Special \$2,500.00

Sweep Oscillator Mainframe, 10 MHz to 40 GHz (dependent on plug-in used), 10 mW output power to 26.5 GHz.

Hewlett-Packard 83522A Special \$3,500.00

Sweep Oscillator Plug-In, 0.01 to 2.4 GHz, leveled output >13 dBm. Has opt 004, rear panel RF output.

Hewlett-Packard 83525A Special \$4,500.00

Sweep Oscillator Plug-In, .01 to 8.4 GHz, +13 dBm output. Opt 002, adds 70 dB step attenuator.

Hewlett-Packard 83545A \$3,900.00

Sweep Oscillator plug-in 5.9 to 12.4 GHz frequency range, 50 mW max leveled power, complete HP-IB programmability.

Hewlett-Packard 83592B \$10,950.00

Sweep Oscillator Plug-In, .01 to 20.0 GHz, +13 dBm internally leveled output.

Hewlett-Packard 83594A \$14,700.00

Sweep Oscillator Plug-In, 2 to 26.5 GHz, +4 dBm internally leveled output. Opt 002, adds 70 dB step attenuator.

Tektronix 2213A Special \$600.00

60 MHz Oscilloscope, 2mV sensitivity, 5 nS/div sweep speed, advanced trigger system. Includes 2 probes.

Tektronix 2220 Special \$895.00

60 MHz Oscilloscope, digitizing rates 20 MS/s at 5 uS/div and faster to 20 samples/s at 5 s/div, digital storage/non-storage, single timebase, 4 k record length.

Tektronix 2430A Special \$3,750.00

150 MHz Digital Oscilloscope, 100 MS/s digitizing rate, simultaneous acquisition on 2 channels, envelope mode with 2 ns glitch capture. Has Opt. 05 & 11.

Tektronix 466 Special \$575.00

100 MHz Storage Oscilloscope, dual trace, 5 mV/div, stored writing speed of 3000 div/μs variable persistence. Includes 2 probes.

Tektronix 465 Special \$550.00

100 MHz Oscilloscope, dual trace, 5 mV/div sensitivity, 5 nS/div sweep rate. Includes 2 probes.

Tektronix 468 Special \$1,150.00

Digital/Analog Storage Oscilloscope, 100 MHz nonstorage bw, 10 MHz storage bw, cursors for time/voltage measurements. Includes 2 probes.

Tektronix 475 Special \$750.00


200 MHz Oscilloscope, dual trace, 2 mV/div sensitivity. Includes 2 probes.

Tektronix 485 Special \$895.00

350 MHz Oscilloscope, dual trace, 5 mV/div sensitivity, 1 nS/div sweep rate, 3.0 div/ns writing speed, selectable input impedance. Includes 2 probes.

WANTED USED TEST EQUIPMENT

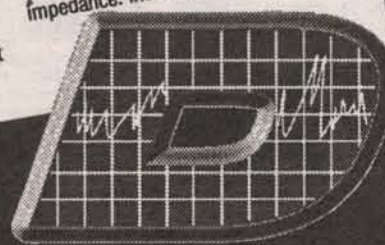(602) 483-6202
Fax (602) 483-6403
14455 North 79th Street, Unit #C • Scottsdale, Arizona 85260



DANBAR SALES COMPANY

CABLE TV

JERROLD UNMODIFIED CONVERTERS FOR SALE. CALL FOR BEST PRICES. NO DESCRAMBLER SALES. CALL BRLD ELECTRONICS 1-800-322-6316.




RAINBOW KITS

TV NOTCH FILTERS
FOR CHANNELS
2 thru 22
ONLY

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DE-222 KIT \$14.95

FM STEREO TRANSMITTER Have your own FM radio station. Any stereo signal you plug into the FMST-100 transmitter kit will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Plug in your CD player, tape deck and have a wireless link to any FM radio, within 200 ft. Listen to your CD while mowing the lawn. Transmit from your car to your camper, or through an auditorium. Transmit music on one channel sing on the other. Compatible with any audio system. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines distance of transmission. Comes complete with left & right input level control as well as a crystal for left & right stereo separation. ANTENNA NOT INCLUDED 9v Battery operation.


 **FMST-100** **Cabinet** **SIZE: 1.5" x 1.6"** **KIT \$29.95**
SIZE: 1.5" x 2.5" x 3" **\$8.95**

RAINBOW MINI-LIGHT Super Bright Flashlight

**Lights up
a complete bedroom
at night**

- LED's don't burn out!
- Battery lasts for years!
- If you have your keys, you'll have a flashlight.
- Replaceable battery!
- Better buy 2, your wife is going to take yours!

Red	MLR	\$9 ⁹⁵
Yellow	MLY	each
Blue	MLB	
White	MLW	
Infrared	MLI	\$12 ⁹⁵ each



**LIE
DETECTOR**



allows you to measure these changes, only a slight amount of change will cause the tone to increase in frequency. Power requirement 6 to 12v DC. Size: 8" x 12"

LD-1

KIT \$9.95

AS-IS converters Oak Sigma, \$20; Zenith, \$7; genuine unmodified DPV5, \$10. Call John 419-243-7856.

CABLE PARTS! Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.



Sweet 16
TOE
DECODER

*Sweet 16 tone decoder
operates great over phone lines, radios
or scanners.*

- 16 TTL Level Outputs
- DTMF Decoder Decodes 16 different touch tones using the phone, radios, or scanners.
- One relay & driver circuit on board.
- 9v battery powered. Size: 2 3/4" x 2 1/8"

TT-16 **KIT \$34.95**



WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless mike that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"

U.S.A.C. **\$14.95**



DC VOLTAGE MONITOR

If battery status is important, you need this kit. This kit uses 7 LEDs to monitor 12V. DC in 1v, 1/2v, or 1/4v steps. Monitor 8v or 5v in 1/4v steps. Great for boats, motor homes, model planes or race car ni-cads. All parts and instructions are included. **SIZE:** 1.3" x 2.7". If you want to switch more power see our Triac (TP-1).

VM-1	KIT \$7.95
For 110 AC VM110	KIT \$10.95

Please add sufficient postage.
US FUNDS ONLY We will
Electronic Rainbow
6227 Coffman Rd
CALL 317-291
INTERNET: www



INDUCTANCE METER

This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7MH. Power requirement 9v DC.

SIZE: 1.75" x 2.5"

IA-1	KIT \$14.95
IA-1 CABINET	\$8.95



DIGITAL THERMOMETER

The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250°F. The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC Size: 2" x 1.35"

DT-3 KIT \$8.95



CAPACITANCE METER

This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <2.2pF to 2.2uF. Power requirement 9v DC. SIZE: 1.80" x 2"

CA-1

KIT \$12.95

VOICE ACTIVATED SWITCH

This VOX circuit can be used to operate a tape recorder, ham radio, CB radio, or turn on an alarm.

The VOX-1 kit has 100MA of output that operates a relay, light, motor, ? What could you do with a sound activated switch? Power requirement 7.5 TO 18v DC. SIZE: 1.5" x 1.3"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

VOX-1 **KIT \$6.95**



PHONE RECORDING SWITCH

This phone line powered switch is small enough to be installed anywhere. Every time the phone is picked up the recorder will record both sides of the conversation automatically. Use it in your office to record all phone calls so you don't lose important information. SIZE: 1" x 6"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TEL-SW1 **KIT \$12.95**



WATER ALARM

Don't ever get stuck with a flooded basement or over fill your water bucket. When the liquid level reaches the sensor it automatically turns the pump on or off. The Water Alarm supplies you with 100 mA of output that activates a relay (that you supply). This relay can turn on a sump pump, or in applications where you are filling a area with liquid it turns off the pump. Sensor included. Size 1.4" x 2"

WA-2 **KIT 17.95**

First lb \$5.50 Canada \$7.50 Additional LB. Add \$1.00
accept telephone orders for Visa or Mastercard

8E

Ind., Inc.
Indianapolis, IN 46268
7262 FAX 317-291-7269
rainbowkits.com




ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS

Altech 360D11, Frequency Syn. .01-2GHz	\$800	HP 86601A, RF Plug-In, 110MHz	\$200
Altech 7615, Noise Source, 28VDC, .01-1.5GHz	\$250	HP 86602A, RF Plug-In, 1300MHz	\$500
Altech Type 32, Precision Attenuator, 0-100dB	\$300	HP 86603A, RF Plug-In, 2600MHz	\$1,500
Argosystems AS210, Frequency Calibration System	\$2,000	HP 86632A, Modulation Plug-In	\$200
Bird 4381, RF Power Analyst, Opt. 832	\$200	HP 8672A/01, Signal Generator, 2-18GHz	\$5,000
Boonton 102B, Signal Generator, .45-520MHz	\$500	HP 8697A, RF Plug-In, 26.5-40GHz	\$250
Boonton 518-A4, Q Standard	\$100	HP 8743A, Reflection Transmission Test Set	\$200
Boonton 82AD, Modulation Meter	\$650	HP 8743A/018, Reflection Transmission Test Set, 18GHz	\$300
Boonton 92BD, Digital RF Millivolt Meter	\$250	HP 8750A, Storage Normalizer, Includes Cable	\$250
Boonton 4200/4E, Power Meter, 18GHz	\$600	HP 8755C, Network Analyzer Plug-In	\$250
Boonton 4200/4G, Power Meter Sensor, .01-26.5GHz	\$200	HP 8756A, Scalar Network Analyzer	\$1,500
Boonton 4220/51013, Power Meter, 18GHz	\$600	HP 8970A, Noise Figure Meter	\$4,000
Boonton 4300, Power Meter w/2-51013 Detectors, Calibrated	\$2,500	HP E3817A, DC Power Supply, 0-40V, 1A	\$250
Brueel & Kjaer 1612, Bandpass Filter	\$250	HP K486A, Power Sensor, 18-26.5GHz	\$100
Calif. Inst. 101T, AC Power Source	\$400	HP P486A, Power Sensor, 12.4-18GHz	\$100
Data Precision 6000/611, Waveform Analyzer	\$350	HP X486A, Power Sensor, 8.2-12.4GHz	\$100
Datron 1062, Digital Multimeter	\$350	Keithley 192, Programmable DMM, 6.5 Digits, HP/IB	\$600
DR Thiedig MILLI-TO2, Ohmmeter, 1 Milliohm-2 Terahms	\$400	Keithley 195A, Digital Multimeter	\$300
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	Keithley 614, Electrometer	\$700
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Krohn-Hite 3202, Filter, LP, HP, BP, Unused	\$350
EIP 545A, Microwave Counter, Opt. 02,05,08	\$1,000	Leeds & North 1091, Capacitor Decade, .001uF-1uF	\$150
ESI 250DE, LCR Bridge	\$200	Marconi 6960, Power Meter with 6920 Sensor	\$600
ESI 296, Auto LCR Meter	\$800	Narda 5082, High Directivity Bridge, 2-18GHz	\$300
Fuke 515A, Portable Calibrator	\$800	Narda 5292 Directional Coupler, 1-18GHz	\$200
Fuke 540B, Thermal Transfer Standard	\$500	PMI 1018B, Peak Power Meter	\$200
Fuke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$300	Racal Dana 1515, Delay Pulse Generator	\$500
Fuke 6080A/AN Frequency Syn. .5-1024MHz	\$4,000	Racal Dana 1992, Frequency Counter, High Stab.	\$500
Fuke 8922A, True RMS Voltmeter	\$250	Racal Dana 9082P, Signal Gen. 1.5-520MHz	\$400
Fuke A55, Thermal Converter	\$200	Racal Dana 9303, True RMS RF Level Meter	\$500
General Microwave 478A, Peak Power Meter	\$700	Racal Dana 9515, Universal Counter, HP/IB, Opt. 41	\$200
General Radio 1557, Vibration Calibrator	\$400	Rohde & Schwarz SPN, Audio Generator	\$300
Gigatronics 600/6-12, Frequency Synthesizer	\$1,000	Sencore TF30, Super Cricket Transistor Tester	\$200
Gigatronics 600/10-18, Frequency Synthesizer	\$1,500	Simco A300, Aerostat Anti-static	\$100
Gigatronics 910, Frequency Synthesizer, .05-26GHz, Opt. 03/06	\$8,000	Tek 067-0681-01, Tunnel Diode Pulsar	\$100
Guideline 9154C, Transvoltage Standard Cell	\$300	Tek 134, Probe Amplifier for P6021 & P6022	\$100
Guideline 9577, Precision DMM, 7.5 Digits	\$300	Tek 1420, NTSC Vectorscope	\$500
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
HP 11590A, Bias Network	\$250	Tek 1502, TDR, Opt. 4, Chart Recorder	\$1,000
HP 11604A, Universal Extension	\$100	Tek 1502B/03/04, TDR, LCD Display, Battery, and Chart Recorder	\$2,500
HP 11605A, Flexible Arm	\$100	Tek 1503/01/05, TDR, Scale in Meters	\$1,000
HP 11638A, Calibration Kit, Type N	\$600	Tek 178, Linear IC Test Fixture, For 577	\$150
HP 11665B, Modulator	\$250	Tek 2336, Scope, 100MHz, Dual Trace	\$700
HP 11712A, Service Kit for 8670 Series Inst.	\$500	Tek 2432, Scope, Digital, 300MHz, 4 Channel	\$2,000
HP 11889A, Adaptor for Plug-In 8350A/B	\$350	Tek 2445B/10/12, Scope, 150MHz, 4 Trace, HP/IB	\$1,800
HP 1600A, Logic Analyzer w/pds	\$400	Tek 2465, Scope, 300MHz, 4 Channel	\$1,800
HP 16500A, Logic Analyzer System	\$2,000	Tek 305DMM, Scope, 10MHz, Dual Trace, DMM, battery	\$500
HP 16510B, Logic Analyzer Card, 16500A System	\$500	Tek 4041, System Controller, GPIB	\$200
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 436/022, Power Meter w/8481A, Cable, GPIB	\$1,200
HP 214B, Pulse Generator	\$1,000	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 33102A, Microwave Switch, 100MHz-18GHz	\$100	Tek 465, Scope, 100MHz Dual Trace	\$400
HP 3312A, Function Generator, 1-13MHz, Sweep	\$400	Tek 491, Spectrum Analyzer w/Meters to 40GHz	\$600
HP 3325A, Function Generator	\$1,000	Tek 492/02, Spectrum Analyzer	\$3,500
HP 3325A/01/02, Function Gen. Opt. 01/02	\$1,500	Tek 496P, Programmable Spectrum Analyzer	\$4,000
HP 33322H, Programmable Attenuator, DC-18GHz	\$250	Tek 5A13N, Differential Comparator	\$250
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$200	Tek 5A20N, Differential Amp	\$100
HP 3455A, Digital Multimeter	\$300	Tek 604, XY Monitor	\$100
HP 3456A, Digital Voltmeter, 6.5 Digits	\$600	Tek 7020, Programmable Digitizer PI	\$600
HP 3468A, Multimeter, 5.5 Digits	\$400	Tek AA501, Distortion Analyzer	\$800
HP 4140B, Picoammeter, DC Source	\$2,000	Tek DC503, Universal Counter Timer TM500	\$100
HP 4274A, Multi-frequency LCR Meter, Opt. 001,002, HP/IB	\$3,800	Tek DC504, Counter/Timer TM500	\$100
HP 438A/022, Power Meter, HP/IB	\$1,000	Tek DM502A, Autoranging DMM	\$150
HP 5004A, Signature Analyzer	\$100	Tek FG501, Function Generator, 1MHz	\$100
HP 5005B, Signature Multimeter	\$350	Tek FG502, Function Generator, .1Hz-11MHz	\$250
HP 5006A, Signature Analyzer	\$300	Tek P604B, Differential Probe	\$300
HP 5182A, Waveform Recorder, Generator	\$500	Tek P6202, Current Probe	\$400
HP 5316A, Universal Counter	\$200	Tek P6204, 1GHz FET Probe	\$300
HP 5328A/021/040, Frequency Counter, DMM	\$250	Tek PG430, Temperature Probe	\$100
HP 5334A/020, Universal Counter w/DVM	\$600	Tek PG508, Pulse Generator, 50MHz	\$300
HP 5335A/010, Frequency Counter	\$600	Tek PS503A, Dual Power Supply	\$150
HP 5335A/030, Frequency Counter, 1300MHz	\$800	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 5340A, Frequency Counter, 18GHz	\$600	Tek SC503, Scope, 10MHz Storage	\$400
HP 5340A, Frequency Counter w/Opt. 01/02/011	\$800	Tek SC504, Scope, 80MHz, Dual Trace	\$500
HP 5342A, Microwave Counter	\$1,000	Tek SG502, Sig. Gen. 5Hz-50KHz	\$200
HP 5350A/010/002, Microwave Frequency Counter	\$2,000	Tek TG501, Time Mark Generator	\$200
HP 5355A, Auto Frequency Converter Plug-In	\$300	Texscan SSG2000, Freq. Syn., 100KHz-2GHz	\$1,800
HP 54100D, Digital Scope, 1GHz	\$2,000	AM, FM	\$250
HP 54200A, Digital Storage Scope	\$800	Ungar 4624, Solder, Desolder Station	\$250
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	Valhalla 2000, Auto Digital Watt-Ammeter	\$200
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Vu-Data 5110, Semiconductor Tester, In/out Circuit	\$150
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,600	Wavetek 143, 20MHz Function Generator	\$200
HP 8350B, Sweep Oscillator Mainframe	\$2,500	Wavetek 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 83540A, RF Plug-In, 2-8.4GHz	\$1,200	Wavetek 180, Sweep/Function Generator	\$200
HP 83545A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wavetek 185, Sweep Function Gen. .0001-5MHz	\$400
HP 8410C/8412B, Network Analyzer	\$800	Wavetek 188, 5MHz Phase Lock Generator	\$200
w/8411A/Opt. 18, 18GHz	\$250	Wavetek 1910, XY Monitor, Dual Trace	\$400
HP 8411A, Frequency Converters	\$250	Wavetek 452, Filter, Dual Hi/Low, 1Hz-10KHz	\$450
HP 8414A, Polar Display	\$300	Wavetek 7530A, FFT Spectrum Analyzer 0-100KHz	\$500
HP 8445B, Spectrum Anyz., Automatic Pre-Selector	\$300	Wavetek 907, Signal Generator, 7-11GHz	\$600
HP 8496B, Attenuator, 110dB	\$250	Wavetek 955, Micro Source, 7.5-12.4GHz, AM, FM, Sweep	\$1,000
HP 8505A, Network Anyz. w/8501A & 8503A, Opt. 05	\$4,000	Wiltron 580A, Network Analyzer	\$800
HP 8553B, Spectrum Anyz., RF Plug-In, 1K-110MHz	\$200	Wiltron 580-97A50, SWR Autotester, .01-18GHz	\$500
HP 8557A/180TR, Spectrum Analyzer, .01-350MHz	\$1,000	Wiltron 610D, Sweeper Mainframe	\$250
HP 8559A/182T, Spectrum Analyzer, .01-21GHz	\$2,500	Wiltron 610D/6237D, Sweep Generator, 2-18GHz	\$800
HP 8559A/853A, Spectrum Analyzer, Digital, .01-21GHz	\$3,500	Wiltron 6213D, RF Plug-In, 10MHz-4.2GHz	\$400
HP 8565A, Spectrum Analyzer, .01-22GHz	\$3,500	Wiltron 6219D, RF Plug-In, 2-8GHz	\$200
HP 8566A, Spectrum Analyzer	\$20,000	Wiltron 6223D, RF Plug-In, 4-12.4GHz	\$250
HP 86222B/H69, RF Plug-In, .01-4GHz	\$1,000	Wiltron 6229D, RF Plug-In, 7.9-18.5GHz	\$300
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400	Wiltron 62FF75, VSWR Bridge, 10-1000MHz	\$150
HP 86260A, RF Plug-In, 12.4-18GHz	\$400	Wiltron 6647A-20/02/03, Programmable Sweep Generator	\$4,000
HP 86290A, RF Plug-In, 2-18GHz	\$1,200	Wiltron 6NF50, Autotester, 1-1500MHz, for 640	\$100
HP 86290B, RF Plug-In, 2-18GHz	\$1,400	Wiltron 7850, Detector, 1-1500MHz, for 640	\$100
HP 8656B, Signal Generator, 1-990MHz, AM/FM	\$3,000		
HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500		

MONTHLY CLEARANCE SALE

HP 54100D, 1GHz DIGITAL SCOPE
RETAIL PRICE \$18,500 • SALE PRICE \$995

HP 8901A MODULATION ANALYZER
RETAIL PRICE \$9,800 • SALE PRICE \$995

PHelps INSTRUMENTS

2631 Hillside Ave., Norco, CA 91760
909-279-7347 • FAX 909-279-7347



Factory Direct
10 HOUR RECORDER

"BUILT LIKE A BATTLESHIP"

• Heavy duty commercial recorder - NOT improvised from consumer models

• 12, 14, and 16 hour models also available

• BUILT-IN voice activation (add \$30)

• Applications information included

• Dimensions: 11.5 x 7.0 x 2.75"

SPECIAL
Nuts & Volts
Price..

\$159

FREE
48-PAGE
SPECIAL EQUIPMENT
CATALOG


COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price includes UPS to 48 States on Pre-Paid Orders

Viking International

150 Executive Park Blvd. #4600 San Francisco, CA 94134

Phone: (415) 468-2066 • Fax: (415) 408-2067 • Web: www.vikingint.com

Write in 46 on Reader Service Card.

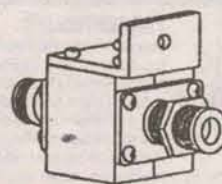

EXPLOSIVE CABLE TV GRAB!
BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middle-man. Let others get fined + zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! LIFETIME GUARANTEE! VISA/MC/AMEX/COD/MO CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). SUPER ZAPPER MODULES ONLY \$16! (3/\$33)! Use SUPER ZAPPERS if you have COX, TCI, WARNER in: CA, TX, FL, NY, PA, MI. DESCRAMBLER PLANS (4=\$5, 20=\$15) 130+ DESCRAMBLER SOURCES (\$5). FREE SHIPPING. OPEN 24 HOURS! 352-429-5496. BRINKER ENGINEERING LABS, USA.

MOD CHIPS for Sony PlayStation. Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. www.cconusa.com

UNMODIFIED ST 1000 and ST 4000, \$20 ea. Bill 419-385-3100.

CABLE PARTS & EVERYTHING. Parts & accessories. Best prices & quantity discount. WE DON'T SELL BOXES. 1-800-MODULE-0.

SONY PLAYSTATION MODCHIPS. Allow you to play CDR backups & imports. \$10 ea. + \$3 shipping. Quantity discounts. 619-590-9320.

BOARD R US, for all your cable needs or computer software, programming service available. 4 MHz resonators 3 pins as low as 34¢. For info call 909-948-3736 or visit us at our web site <http://members.aol.com/BoardRUs>

GENUINE UNMODIFIED JERROLD DPBB7312 FOR SALE 10 LOT MIN. CALL 708-715-6118.

UNMODIFIED CABLE CONVERTERS: JERROLD, SCIENTIFIC ATLANTA, PIONEER, ZENITH, TOCOM. MIN 10 LOT. CALL 708-715-6118

WANTED: GENUINE RAW UNMODIFIED CABLE TV CONVERTERS. TOP CASH PAID. CALL 708-715-6118.

UNBELIEVABLE PRICES. We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, no raw parts. Full technical support. 12pm-7:30pm EST. 1-800-562-8442.

CABLE STOP, one stop for all your cable needs. Quality parts at a low price. 1-800-562-8442 12pm-7:30pm EST

PLAYSTATION MOD chips. Works with all models up to 750x. Color instructions. Five wire hook up, comes with wire. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118.

FOR ALL YOUR CABLE NEEDS: Call Images Electronics, for the best quality parts at the lowest prices. 909-982-2482 or visit our web site at <http://members.aol.com/ImagesCo>

WANTED: TEKNIKA 6510 cable converter boxes/parts. 415-221-5940.

DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.

TELEPHONE/FAX

TELEPHONE CATALOG 160 pages including office automation, voice mail, and all phone accessories. Send \$10 to HES Electronics, POB 183, Brick, NJ 08723. Mention this ad and get a 10% off certificate! Visit www.heselectronics.com

NEW: MEMORECS, provides most important features your answering machine is missing. Oricom Technologies, 303-449-6428. www.sni.net/~ori.com

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.,** 937-847-2300 or FAX 937-847-2350.

COMPONENTS

DON LANCASTER'S ACTIVE FILTER COOKBOOK is back in print. Autographed copies of the seventeenth(!) classic printing \$28.50. **SYNERGETICS PRESS,** Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

MILLIONS \$\$\$ in "scrap gold" from old computers and electronics junk. Message: 603-645-4776 or www.tiac.net/users/quicksand/goldtek.htm

WANT TO Buy: ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoffy Electronic Ent., 818-718-1165, FAX 818-341-5506.

PHOTOMULTIPLIER TUBES, radiosondes, electro-luminescent panels, electronic parts, test equipment. www.lonemtn.com



FACTORY SALE! CNL100, CNP101: 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 1.27" (W) x 1.27" (L) x 1" (H). \$43 @ 5 pcs., \$38 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com

OLD ICs & TRANSISTORS WANTED: HIGHEST PRICES PAID please FAX your list with part number, quantity & condition of any semiconductors to Rick @ ESI, 5363 Broadway Ave., Cleveland, OH 44127. 216-441-8500 FAX 216-441-8503. Since 1946! www.electronic surplus.com



AMAZING! 35¢ ALL TOGGLE SWITCHES. Brand new. Rated 6A/125V. Hardware included. 1/4" panel hole. SPDT or DPDT on-on, or on-off-on. Minimum 100pcs./package. Add \$6 freight. Gateway Products Corporation, PO Box 936397, Margate, FL 33093, 954-974-6864, Fax: 954-974-6818, VISA/MC, no COD.

RF TRANSISTORS, TUBES, 2SC2879, SD1446, MRF455, MRF454, 3SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1419, 2SC1947, 2SB688, 2SD880, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG 4CX250B, 572B, 3CX3000A7, 4CX400A silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.

MICROCONTROLLERS

ATMEL 90S1200/89C2051 PROTOTYPE BOARD. High quality 2x3 bare board with 1x2 prototype area: \$15.50. Supports RS-232 interface, regulated power, connectors. Includes schematics for board and interactive programmer. Free software at WWW.2051BC.COM System manual describing software operation and hardware construction: \$15.50. Send check or money order to: 2051BC, 1826 Lambeth Way, Carmichael, CA 95608. 916-487-2513.



PIC MICROCONTROLLER PROGRAMMER KIT. Super value at \$14.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. <http://www.electron ics123.com>

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

Examples Include:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.
11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: <http://www.emacinc.com>

1985 - 1998
OVER
12
YEARS
OF SERVICE

Write in 47 on Reader Service Card.

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM - SEND THEM FOR REBUILDING! - SAVE \$\$

CUNARD ASSOCIATES, R.D. 6 Box 104, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / 12 YEARS IN BUSINESS.
- WE SAVE YOU \$\$\$ MONEY \$\$\$



- NO JOB IS TOO LARGE OR TOO SMALL. WE OFFER VOLUME DISCOUNTS TO LAW ENFORCEMENT / COMPANIES / FIRE DEPARTMENTS / UNIVERSITIES

GENERAL ELECTRIC	UNIDEN	BENDX KING
MPD/PLS - MPR/MPS/MPX	APH56 APX500 \$21.95	KR105/LAA125 \$34.95
19A704850P(1200MAH) \$34.95	APX650 1050 \$29.95	
19A704860P(1800MAH) \$39.95	1000 1100 1200 \$34.95	KENWOOD
PL19D429763(777)G1/3 \$37.95	BP100/200/205 \$14.95	PB2 / KNB3 \$29.95
	205 inc to 1350 \$22.95	PB21/21H \$14.95
M AXON SA-1155 1160 \$39.95		PB25/H/25 \$24.95
TAD 1450 1510 1520 \$21.95	ICOM	CORDELESS DRILLS
	BP2 / BP3 / BP22 \$18.95	Any brand 7.2V \$18.95
MOTOROLA	BP5 / BP23 / 24 \$24.95	Any brand 9.6V \$29.95
P200 HT600 MT1000	BP7 / CM7 / BP8 \$34.95	Any brand 12.0V \$32.95
NTN 4585 4824 5414 \$37.95	YAESU	Any brand 14.4V \$37.95
NTN 5447 5521 5545 \$37.95		SURVEYING EQUIP.
MIDLAND	FNB 3 4 12 14 16 \$32.95	COMPUTERS - PHONES
70-B10 B16 B19 B21 \$39.95	FNB19 21 26 27 38 \$32.95	Send battery for quote.
70-B32 70-B36 \$39.95	FNB 17 25 35 \$23.95	

FOR INFORMATION ABOUT YOUR REQUIREMENTS CONTACT US:
PHONE OR FAX: (814) 623-7000 E-MAIL TO: PRIMECELL@AOL.COM
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL
DOWNLOAD OUR CATALOG, WEB SITE: <http://users.aol.com/PrimeCell>

BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE - WRITE OR CALL
FREE CATALOG
ADD \$4.50 SHIPPING & HANDLING PER ORDER



Write in 48 on Reader Service Card.

PICWISER LOW cost development system. Rapid prototyping system contains PIC16F84, integrated programmer and solderless breadboard. Write software on PC, program PIC16F84 using parallel port, and test circuits fast. Send \$59 plus \$6 shipping to: Emicros, 25759 Ridgewood, Farmington, MI 48336. 248-477-6639, www.emicros.com

ANTIQUE ELECTRONICS

WESTERN ELECTRIC WANTED: 1927-1960s. Amplifiers, speakers, tubes, etc. Free offer. 1-800-251-5454.

TELEGRAPHY INSTRUMENTS, KEYS SOUNDERS, RELAYS, METERS, VIBROPLEX'S, PRACTICE SETS, INSTRUCTOGRAPHS, CALL BOXES, ETC. GOODMAN 217-345-6771.

ANTIQUE RADIO CLASSIFIED. Free sample copy! Antique radio's largest-circulation monthly magazine. Old radios, TVs, ham equip., 40s & 50s radios, telegraph, books & more. Ads & articles. Free 20-word ad monthly. Subscribe today. Six-month trial: \$19.95. Yearly rates: \$39.49 (\$57.95 by 1st Class). Foreign: write. ARC, PO Box 802-G23A, Carlisle, MA 01741. Phone: 978-371-0512; Fax: 978-371-7129; Web: www.antique radio.com

FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



platt - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95
800T Case Only ... \$121.80




platt - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00
660ZT Case Only ... \$59.45
Optional Sperry meter #DM6510 as shown ... \$65.00



Weller WCC100- Electronically controlled station, temperature adjustable from 350°F-850°F, Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90

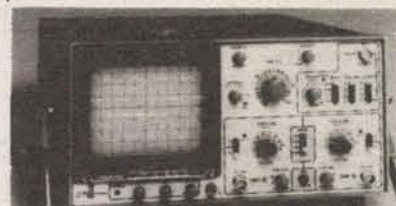
OptiVISOR - Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



GoldStar - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00

Electro Tool, Inc.

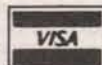9103 Gillman, Livonia, MI 48150
Customer Service: (734) 422-1221
ORDERS ONLY: 1 (800) 772-3455
FAX: (734) 422-3432



"Tools American Made."

CRYSTAL SETS. Parts, plans, books, kits. Largest source in the world. Catalog \$2. MIDCO, PO Box 222288, Hollywood, FL 33022.

WESTERN ELECTRIC WANTED: 1920's-1960's. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

Sell Nuts & Volts
in your store and earn \$\$\$!
Contact us for details. 909-371-8497
E-Mail distributors@nutsvolts.com

SURPLUS TEST EQUIPMENT

HEWLETT PACKARD

11729B, Carrier Noise Test Set	\$3500
11975A, Amplifier, 2-8GHz	\$2000
214B, Pulse Generator, 10Hz-10MHz	\$1000
3312A, Function Generator, 1Hz-13MHz	\$700
3325A, Synthesizer/Function Generator	\$1000
3325A/01/02, Synthesizer/Function Generator	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz	\$5500
w/Opt. 01	\$5500
339A, Distortion Analyzer	\$1000
3456A, Digital Multimeter, 6.5 Digits	\$800
346A, Noise Source, 10MHz-18GHz	\$1100
3478A, Digital Multimeter	\$700
3488A, Switch Control	\$600
3551A, Transmission Test Set	\$600
3562A, Dynamic Signal Analyzer	\$6000
35660A, Signal Analyzer	\$6000
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3577A, Network Analyzer w/35677A Test Set	\$10,500
3580A, Spectrum Analyzer, 5Hz-50KHz, Opt. 2 & 3	\$1000
3581C, Selective Voltmeter	\$800
3585A, Spectrum Analyzer, 20Hz-40.1MHz	\$5500
4192A, LF Impedance Analyzer w/16097A Kit	\$11,000
4193A, Vector Impedance Meter	\$6500
4342A, Q-Meter	\$1800
435B, Power Meter	\$500
436A, Power Meter w/Opt. 022	\$1000
4815A, RF Vector Meter	\$1200
5314A/01/02, Universal Counter	\$225
5316B, Universal Counter	\$1000
5328B, Universal Counter	\$1000
5335A, Frequency Counter, Opt. 10/20	\$850
5340A, Frequency Counter w/Opt. 01/02/011	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz	\$900
5350B, 20GHz Frequency Counter	\$3000
5355A, Frequency Converter	\$1000
5386A, Frequency Counter, 10Hz-3GHz	\$2000
54100A, Digitizing Oscilloscope	\$2500
54100D, 1GHz Digital Oscilloscope	\$2700
54110D, 1GHz Color Digitizing Oscilloscope	\$2500
54120A, Digitizing Oscilloscope Mainframe	\$5750
54201D, Digitizing Oscilloscope	\$2650
6011A, Autorange Power Supply, 20V/120A, 1000 Watt	\$1200
6632A, DC Power Supply, 0-20V, 0-5A, 100 Watt	\$1000
8011A, Pulse Generator	\$400
8011A, Pulse Generator w/Opt. 001	\$500
8012B, Pulse Generator	\$750
8013B, Pulse Generator	\$750
8112A, 50MHz Pulse Generator	\$4000
8116A, 50MHz Pulse/Function Generator, Opt. 001	\$4000
8160A, Programmable Pulse Generator, 50MHz	\$2000
8165A/002, Programmable Signal Source w/AM	\$2200
8347A, RF Amplifier, 100KHz-3GHz	\$3000
8350A, Sweep Oscillator Mainframe	\$1000
8350B, Sweep Oscillator Mainframe	\$1500
83522A, Sweeper Plug-in, .01-2.4GHz, w/Opt. 02	\$4500
83540A, RF Plug-in, 2.0-8.4GHz	\$2000
83540A/002, RF Plug-in, 2-8.4GHz	\$2500
83545A, Oscillator Plug-in, 5.9-12.4GHz	\$1750
8411A/01B, Frequency Converter .11 to 18GHz	\$500
8494H, Programmable Attenuator (unused)	\$800
8495H, Programmable Attenuator (unused)	\$600
8501A, Storage Normalizer	\$1000
8505A, Network Analyzer w/8501A & 8503A	\$4000
8511A, Harmonic Frequency Counter	\$5000
8554B, RF Spectrum Analyzer Plug-in, 500KHz-1250MHz	\$800
8559A, Spectrum Analyzer Plug-in, .01-21GHz	\$2650
8566A/B, Spectrum Analyzer, 100Hz-22GHz	\$22,000
8569B, Spectrum Analyzer, 10MHz-22GHz	\$7000
86222B, Sweep Oscillator Plug-in w/8620C Mainframe	\$1250
8640A, Signal Generator, 0.5-512MHz	\$2100
8640B, Signal Generator, Opt. 002, .5-1024MHz	\$2100
8640B, Signal Generator, Opt. 1, 2	\$2200
8654A, Signal Generator, 10-520MHz	\$450
8656A, Signal Generator, 100KHz-990MHz	\$1700
8660D, Synthesized Signal Generator	\$6000
8672A, Synth. Signal Gen., 2.0-18.0GHz	\$6000
8748A, S-Parameter Test Set w/Opt. 026	\$1350
8754A, Network Analyzer w/8748A Test Set	\$2000
8756A, Scalar Network Analyzer	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz	\$4000
8903A, Audio Analyzer w/Opt. 001	\$900
8970A, Noise Figure Meter	\$4500
K382A, Variable Attenuator	\$2300

TEKTRONIX

1503, TDR Cable Tester w/Opt. 04 Recorder	\$1550
2215, 60MHz Oscilloscope	\$500
2236, 100MHz Oscilloscope	

w/Counter/Timer/DMM	\$1000
2246, 100MHz Oscilloscope	\$1600
2247A, 100MHz Oscilloscope w/Counter/Timer/Voltmeter	\$2500
2337, 100MHz Oscilloscope w/DMM	\$1650
2430A, 150MHz Digital Oscilloscope	\$2850
2432A, 300MHz Digital Storage Oscilloscope	\$3000
2445, Four Channel 150MHz Oscilloscope	\$1500
2445A, 150MHz Four Trace Oscilloscope	\$1850
2465, Four Channel 300MHz Oscilloscope	\$2500
2465B, Four Channel 400MHz Oscilloscope	\$4500
2754P, 10KHz-21GHz Spectrum Analyzer	\$9000
465B, 100MHz Oscilloscope	\$450
466, 100MHz Storage Oscilloscope w/DMM4	\$800
475, 200MHz Oscilloscope	\$650
475A, 250MHz Oscilloscope	\$800
485, Oscilloscope, 350MHz	\$900
576, Curve Tracer	\$2750
577/D2, Curve Tracer, Non-storage w/177 Fixture	\$1750
7D20, Programmable Digitizer	\$400
7L5/L3, Spectrum Analyzer, 20Hz-5MHz	
w/Opt. 025 Tracking Generator	\$1850
7L12, Spectrum Analyzer, 100KHz-1.8GHz	\$1500
7L18, Spectrum Analyzer Plug-in, 1.5-18GHz	
Capable of 60GHz with Mixers	\$2500
7S12, TDR/Sampler	\$450
AFG5101, Arbitrary Function Generator	\$1500
CG5001, Programmable Calibration Generator	\$4000
DSA602, Digitizing Signal Analyzer	\$8500
PG506, Calibration Generator Plug-in	\$600
TM5003, Three Slot Power Mainframe	\$450

VISIT OUR WEBPAGE AT
WWW.RSSURPLUS.COM

TM5006, Six Slot Power Mainframe \$550

MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load	\$850
California Inst. 4500LM3, AC Power Source	\$4000
California Inst. 4503L, AC Power Source	\$4000
Datron 1061A, 6.5 Digit Autocal Multimeter, DC Only	\$700
Datron 1062, 6.5 Digit Autocal Multimeter, DC/AC/Ohms	\$900
EIP 545A, Microwave Frequency Counter	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz	\$3250
EIP 578, Source Locking Frequency Counter	\$2500
ENI 325LA, Power Amplifier, 250KHz-150MHz 25 Watts	\$1850
Fluke 5100B/03/05, Multifunction Calibrator	\$3000
Fluke 5101B/03, Calibrator	\$3000
Fluke 5200A, AC Voltage Calibrator	\$2000
Fluke 8010A, Digital Multimeter	\$175
Fluke 8012A, Digital Multimeter	\$175
Fluke 8050A, Digital Multimeter	\$250
Fluke 8502A, Digital Multimeter, DC Only	\$225
Fluke 8520A, Digital Multimeter	\$350
Fluke 8600A, Digital Multimeter	\$65
Fluke 8810A, Digital Multimeter	\$250
Gigatronics 910, Frequency Synthesizer, .05-26GHz	\$9500
Kikusui PAB18-1, DC Power Supply, 18V/1A	\$100
Kikusui PAB18-3, DC Power Supply, 18V/3A	\$125
Kikusui PAB18-3A, DC Power Supply, 18V/3A	\$145
Kikusui PAB32-2A, DC Power Supply, 32V/2A	\$175
Kikusui PAD16-10L, Power Supply, 16V, 10A	\$300
Kikusui PLZ700W, Electronic Load	\$850
Krohn-Hite 3202/R3202, Tunable Filter/Rack Version	\$500/\$350
LeCroy 9424, 350MHz Oscilloscope	\$3500
Marconi 2019A, Signal Gen., 80KHz-1040MHz	\$2200
Sorensen DCS40-25, DC Power Supply, 40V/25A	\$750
Trans. Devices DLR400 15 3500A, Dynamic Load	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load	\$800
Trans. Devices DLVP 130-110-1000 Electronic Load	\$950
Trans. Devices DLVP 50-120-1000 Electronic Load	\$1000
Valhalla 2703, AC Voltage Standard	\$2350
W & G SNA5, 50Hz-3.2GHz Spectrum Analyzer	\$6000
Wavetek 178, Automatic Synthesizer	\$1850
Wavetek 2001A, Sweep Generator, 1-1400MHz	\$450
Wavetek 3000-200, Signal Generator	\$900
Willtron 560-7K50, RF Detector, 10MHz-40GHz	\$450
Willtron 560-7S50, RF Detector, 10MHz-18.5GHz	\$300
Willtron 560-7S50, RF Detector, 10MHz-26.5GHz, Opt. 2	\$400
Willtron 560-97N50, SWR Autotester, 10MHz-18GHz	\$600
Willtron 560-97S50, SWR Autotester, 10MHz-18GHz	\$600
Willtron 560-98S50, SWR Autotester, 10MHz-26.5GHz	\$900
Willtron 561, Scalar Network Analyzer	\$2500

R & S Surplus
1050 E. CYPRESS STREET, COVINA, CA 91724

(626) 967-0846 • FAX (626) 967-1999

Mr. NiCd

FEBRUARY SUPER SPECIALS!

THE BEST BATTERIES
IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:			
FNB-40xh Sim-NMH	7.2v	650mAh	\$41.95
FNB-47xh (NMH)	7.2v	1800mAh	\$49.95
FNB-41xh (5w NMH)	9.6v	1000mAh	\$49.95
For YAESU FT-51R / 41R / 11R:			
FNB-38 pack (5W)	9.6v	700mAh	\$39.95
For YAESU FT-530 / 416 / 816 / 76 / 26:			
FNB-26 pack (NMH)	7.2v	1500mAh	\$32.95
FNB-27s (5w NMH)	12.0v	1000mAh	\$45.95
For YAESU FT-411 / 470 / 73 / 33 / 23:			
FNB-11 pack (5w)	12.0v	600mAh	\$24.95
FBA-10 6-Cell AA case			\$14.95
Packs for ALINCO DJ-580 / 582 / 180 radios:			
EBP-20ns pack	7.2v	1500mAh	\$29.95
EBP-22nh pk (5w)	12.0v	1000mAh	\$36.95
EDH-11 6-Cell AA case			\$14.95
For ICOM IC-21A / T22-42A / W31-32A / T7A:			
BP-180xh pk (NMH)	7.2v	1000mAh	\$39.95
BP-173 pack (5w)	9.6v	700mAh	\$49.95
For ICOM IC-W21A / 2GXAT / V21AT (Black or Gray):			
BP-132s (5w NMH)	12.0v	1500mAh	\$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:			
BP-83 pack	7.2v	600mAh	\$23.95
For ICOM 02AT etc & Radio Shack HTX-202 / 404:			
BP-8h pack	8.4v	1400mAh	\$32.95
BP-202s pack (HTX-202)	7.2v	1400mAh	\$29.95
For KENWOOD TH-79A / 42A / 22A:			
PB-32xh pack (NMH)	6.0v	1000mAh	\$29.95
PB-34xh pack (5w NMH)	9.6v	1000mAh	\$39.95
For KENWOOD TH-78 / 48 / 28 / 27:			
PB-13 (original size)	7.2v	700mAh	\$26.95
For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:			
PB-6x (NMH, w/chg plug)	7.2v	1200mAh	\$34.95

Mail, phone, & Fax orders welcome! Pay with
Mastercard / VISA / DISCOVER / American Express
Call 608-831-3443 / Fax 608-831-1082
Mr. NiCd - E. H. Yost & Company
2211-D Parview Road, Middleton, WI 53562
CALL OR WRITE FOR OUR FREE CATALOG!
Cellular / Laptop / Videocam / Commercial & Aviation packs too!
E-mail: ehyst@midplains.net

AVIATION ELECTRONICS

BUY, SELL, trade, avionics equipment,
Collins, King, Sperry: test equipment,
IFR, Litton LTN series INUs. 941-625-
3222 P. 941-625-0494 F, E-Mail: avio
nics@afcon.net

SYNCHRO RESOLVER test sets, sys-
tem analyzers, test equipment.
www.lonemtn.com

PUBLICATIONS

START YOUR OWN TECHNICAL VEN-
TURE! Don Lancaster's newly updated
INCREDIBLE SECRET MONEY
MACHINE II tells how. We now have
autographed copies of the Guru's un-
derground classic for \$18.50. Synergetics
Press, Box 809-K, Thatcher, AZ 85552.
520-428-4073. VISA/MC.

THE CASE AGAINST PATENTS. Don
Lancaster's tested and proven alterna-
tives that work in the real world. \$28.50.
Synergetics Press, 3860 West First
Street, Box 809, Thatcher, AZ 85552.
520-428-4073. synergetics@tinaja.com
VISA/MC.

NEW SURVIVAL COMMUNICATIONS
BOOK. How to build complete home
communications systems. Covers all
needs: shortwave radio, amateur radio,
citizens band, scanners, federal, weath-
er, alternate news, satellite radio, equip-
ment sources. How to build and use
alternate emergency power sources,
solar, generators, backup batteries. 200
pages. \$24 Fast delivery Priority Mail.
MC or Visa. Call Universal Electronics 1-
800-241-8171.

ROBOTICS

CNC! MOTIVITY'S updated website is
at: www.motivityusa.com 916-349-
8757. A great place to buy CNC.

ROBOT BOOKS.COM visit our web site
for reviews of robotics books, plus robot
kits, toys, movies, and magazines!
www.robotbooks.com

www.futurerobots.com ROBOTS
are soon coming to our homes. Most of the
technology is now here and their need is
also here. Come see the real future of
home robots.

ARobot KIT from Arrick Robotics uses
the BASIC Stamp II. Quality metal con-
struction. Easy to assemble and very
expandable. \$235. [http://www.robot
ics.com/robot](http://www.robot
ics.com/robot)

PLANS - KITS - SCHEMATICS

HOBBY CATALOG: Broadcasting and
microbroadcasting transmitters, ampli-
fiers, antennas. Start your own radio
station books. Audio, TV, ham, CB, sur-
veillance, science projects, and more.
PAN-COM International, Box 130-V,
Paradise, CA 95967. www.panaxis.com

TEST EQUIPMENT kits. If you liked
Heathkit, you will love Technology
Systems, 4 Prospect Pl., Torrington, CT
06790.

HEATHKIT COMPANY is selling photo-
copies of most Heathkit manuals. Only
authorized source for copyright manuals.
Phone: 616-925-5899, 8-4 ET.

Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Panasonic 175	\$70	\$68	\$65
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65

Call us today to satisfy all your cable equipment needs!

SAM'S ELECTRONICS
1-405-631-1856

All Cable Equipment is unmodified.

THE YEAR 2000 bug (Y2K), do you know what this means to you and your family? Get a complete plan on how to prepare for the least/worse case scenarios, \$10. Contact: Mike, phone/fax, 828-684-7672. [HTTP://WWW.CHIG.COM](http://www.chig.com)

ELECTRONIC KITS, projects and supplies for prototyping, designing or hobby. Call 1-888-GO-4-KITS for catalogs or send \$3 to Quality Kits, 49 McMichael St., Kingston, ON., K7M 1M8. <http://www.qkits.com>

200+ ELECTRONICS PROJECTS. Build for pleasure or make 100% (or more) profits reselling printed plans. \$1 (refundable) for catalog & dealer info. MATCO-A5, PO Box 509, ROSEVILLE, MI 48066-0509.

BUILD THE MENDOCINO MOTOR. This fascinating device is a solar powered, magnetically levitated motor. It will delight and amaze you and your friends. The 27 page plans book includes a list of parts suppliers. The motor uses readily available parts. Plans are \$15 plus \$2.50 S&H. Write to: St. Elmo's Fire, PO Box 141, Stow, MA 01775. E-Mail: tcv@genrad.com

AWESOME KITS: voice changers, levitators, lasers, solar robots, and more! Catalog \$1. **LNS Technologies**, PO Box 67243, Scotts Valley, CA 95067. www.ccnnet.com/~lnstech



CIRCUIT BOARDS. Totally new! Low cost, precision-made PC boards from your Gerber/NC Drill files. Single and double sided. Full details at <http://www.pcbmilling.com> E-Mail: feedback@pcbmill.com FAX: 703-818-0071.



TERRIFIC TIMEPIECES! LED binary clock. LED digital clocks, other kits! Free catalog! WPC, 805-339-0702. www.west.net/~wpc

MOD CHIPS for Sony PlayStation. Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. www.cconusa.com

KITS, CHIPS, quick protoboards, telephone electronics, pocket testbench, RS-232 instrumentation Oricom Technologies, 303-449-6428, www.sni.net/~oricom



SOLDERLESS BREADBOARD SB-147: 3260 tie points, 4 binding posts. \$29.95 plus \$2.60 (2% of subtotal plus \$2) UPS ground delivery. Call 972-242-8087 for 10+ prices. Mail check to: CTI, 1301 West Beltline #105, Carrollton, TX 75006.

HOVERBOARDS, JETPACKS, LIGHT-SABERS. Plans, schematics, and kits for over 100 incredible devices. \$3 for catalog. Future Horizons, PO Box 125, Marquette, MI 49855. www.futurehorizons.net

MANUALS — SCHEMATICS WANTED

CASH FOR your test equipment manuals in good condition for most Tektronix, HP, Fluke, and other test equipment. E-Mail your list and best price to: manu@lonemtn.com

THE YEAR 2000 bug (Y2K), do you know what this means to you and your family? Get a complete plan on how to prepare for the least/worse case scenarios, \$10. Contact: Mike, phone/fax, 828-684-7672. [HTTP://WWW.CHIG.COM](http://www.chig.com)

MISCELLANEOUS ELECTRONICS FOR SALE

CALL FOR a free electronics catalog or visit our web site at www.bgmicro.com B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 1-800-276-2206.

L BAND quadrifilar T/R antenna, 55 dB LNA, 20 watt HPA, works great for remote GPS. Info at afstar.com.

FREE FLYER on cable TV, phones, credit cards info, schematics, project boards, other misc. items. Bill 1-800-879-9657.

NUCLEAR ELECTRONICS (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: oetech@newmexico.com <http://www.oetech.com>

FOR SALE: Test equipment, two-way radios, cellphones, broadcast equipment, mobile repeaters, UNIX workstations. See www.mbay.net/~thor

INVERTERS/UPS. 450 VA inverters, 24 VDC TO 120 VAC, \$10; 450 VA UPS, \$20; 600 VA UPS, \$40; 1250 VA UPS, \$85. Other sizes available. Call for complete price list. 1-800-755-0080.

47pc•kit

\$12.95

MK101
SWEETHEART

Give him or her that special heartbeat. 28 leds form 2 blinking hearts. Power supply : 9V battery



14pc•kit

\$5.95

MK102
FLASHING LEDS

For different applications (such as model construction) and educational purposes. Adjustable flashing speed. Power supply : 9V battery



30pc•kit

\$14.95

MK104
ELECTRONIC CRICKET

This cricket turns on when it gets dark. Great as practical joke. The tone and repetition between two crickets is adjustable. Power supply : 9V battery



34pc•kit

\$9.95

MK103
LED SOUND-TO-LIGHT UNIT

For different funny and practical applications. 4 high-intensity leds light up and react simultaneously on every sound. Power supply : 9V battery



36pc•kit

\$10.95

MK105
SIGNAL GENERATOR

Several signal outputs : square wave, triangle, sine and integrator which are selectable with a jumper. The signal frequency is about 1KHz (fixed) (ideal to learn electronics) Power supply : 9V battery



26pc•kit

\$14.95

MK106
METRONOME

The beats per minute are given by a built-in speaker and by a led. Adjustable volume, beats, and sound. With on/off switch. Power supply : 9V battery



36pc•kit

\$12.95

MK107
LED RUNNING LIGHT

8 leds running light. Different running effects are selectable (by prog push button). Adjustable effect speed. Power supply stand-by by push button. Power supply : 9V battery




8pc•kit

\$7.95

MK108
WATER ALARM

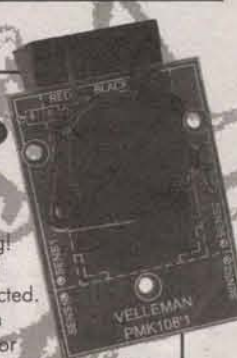Never let you surprise by flooding! Gives alarm sound when water is detected. Incorporated alarm buzzer. Water sensor can be placed at distance by cutting the board and using wires to connect the sensor. Power supply : 9V battery



35pc•kit

\$9.95

MK109
ELECTRONIC DIE

No more cheating allowed! The eyes of the die are leds. Rolls out when the push button is released. Power supply : 9V battery



17pc•kit

\$12.95

MK110
SIMPLE ONE CHANNEL LIGHT ORGAN

With loudspeaker input. The lamp flashes on the beat of the music. Optical isolated loudspeaker input with adjustable sensitivity : 2W to 60W. Maximum load : 120W at 120Vac.



17pc•kit

\$19.95

K5300
STROBOSCOPE

Adjustable flash frequency : 5-15Hz. Power supply : 120Vac. Power consumption : 13W max.



21pc•kit

\$12.49

K2637
SUPERMINI 2.5W AUDIO POWER AMPLIFIER

Superb audio amplifier with incredible tiny dimensions. Integrated circuit has a pre- and power amplifier which can be used separately. Max. output power : 2.5W @ 4ohm. Frequency characteristics : 60Hz to 15KHz. Power supply : 4.5V to 15Vdc / 400mA



Exists also as module : M2637 \$17.49

velleman

7415 Whitehall Street Suite 119
Fort Worth, TX 76118
(817) 284-7785 F : (817) 284-7712
www.velleman.be email : velleman@earthlink.net

Questions ? Contact us for a list of US distributors or to get your **FREE** catalogue

HIGHEND SURPLUS 203-744-4101. OK INDUSTRIES DEMO BLOWOUT. If it is not listed just give us a call, chances are we have it! **SOLDER STATIONS:** total rework, forced convection, hot air. MTR5000 (retail \$4,595) sell \$2,350; MTR4000 (retail \$3,995) sell \$1,750; MTR3000 (retail \$2,495) sell \$1,250; BTR2000 (retail \$1,595) sell \$775; FCR2000 (retail \$1,850) sell \$950; BTR1000 (retail \$825) sell \$400; SMT1160 (retail \$1,000) sell \$450; SA2000 (retail \$395) sell \$185; SA1000 (retail \$295) sell \$150; SA500 (retail \$225) sell \$75. **PUR-AIR:** Fume exactors. EP101 (retail \$1,695) sell \$475; EP051 (retail \$595) sell \$225. **JEM:** Batch ovens JEM310 (retail \$7,995) sell \$3,600; JEM210 (retail \$4,995) sell \$2,200. **PICK & PLACE:** Chip placers, vacuum pencils, fluid dispensers. SMT8001 (retail \$4,000) sell \$1,750; SMT880 (retail \$2,200) sell \$950; FD1000 (retail \$395) sell \$175; VP100 (retail \$395) sell \$175. **BOARD ETCHER:** SSP-75A (retail \$995) sell \$400. **ALWAYS BUYING: VIDEO, RADIO, PHONE SYSTEMS, COMPUTERS, STEREO, AND BROADCAST EQUIPMENT.**

ELECTRONICS PARTS: BELOW WHOLESALE PRICES! Phone, fax, E-Mail for free flyer. Hoffman Industries, 853 Dundee Ave., Elgin, IL 60120. Ph: 847-622-8201, Fax: 847-622-8202, toll free: 1-888-311-4248, E-Mail: hoffind@aol.com Web site & on-line catalog: <http://hoffind.com>



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors cut & strip to spec. If interested, please call **1-800-626-7540**, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: info@anaheimwire.com

OPTO22 LC4A controller with PS115-1.5A supply, B2 and PB8AH brain board and rack, (4) AD3, (2) AD6 and (2) DA3T analog modules, plus (3) Sola Solids AC/DC converters, 115VAC input, 5VDC@300mA ±15VDC@150mA outputs. Removed from working service, \$315 for all. Pioneer Magnetics 500W industrial computer console DC power supply. 115/230VAC, 50/60Hz, 9.8A input. 5VDC@80A, 12VDC@8A, 12VDC@1.5A outputs. NOS, \$195. One each. E-Mail: dahawk@ptd.net

HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE. European and American screwdrivers, nut-drivers, pliers, hex- keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: w2tv@csi.com



SOLAR-POWERED FAN HAT. Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

<http://www.pccables.com> **PC CABLES and PARTS.** 100s of hard-to-find new cables and parts, Free technical information, low prices, fast online ordering & browsing.

Subscribe to Nuts & Volts!
Call 1-800-783-4624

TOROIDIAL ISOLATION TRANSFORMER, 120V TO 120V @ 450 watts with mounting bracket & hardware. \$30 each, 2 for \$50 or 10 for \$200, includes S&H. List price over \$100, 70 pcs. available. Call GS&E, 716-338-7001. VISA & MC NO COD.

MISCELLANEOUS ELECTRONICS WANTED

TESTERS WANTED: Immediate offers made for Ultrasonic, Magnetic Particle, Eddy Current, X-Ray and Borescopes, 24hrs. Leave detailed message with make/model. 1-800-530-3371.

WANTED: ELECTRON tubes, ICs, semi-conductors. Summit, PO Box 810903, Boca Raton, FL 33481. Phone 1-800-226-6960. <http://www.summitelectronics.com>

WANTED: TUBE HiFi/commercial amps, preamps, corner/horn speakers. Altec, Marantz, McIntosh, Western Electric, etc. 405-737-3312 fax 405-737-3355.

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

www.gatewayelex.com

(Electronically Speaking, Gateway's Got It!)



MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

WANT USED or surplus DC motor controls or adjustable frequency AC drives, 1/2 HP and up. DC motors fractional to 3 HP. C. Woodruff, 5507 55th Ave. S., Seattle, WA 98118. Voice/Fax 206-723-8487.

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

RADAR/MICROWAVE equip: Aviation, marine, fire control. Like TPS 21, APS 10, 42 APG 30. Parts, TM's, etc. Radar, Box 10215, Pittsburgh, PA 15232.

OLD ICs & TRANSISTORS WANTED: **HIGHEST PRICES PAID** please FAX your list with part number, quantity & condition of any semiconductors to Rick @ ESI, 5363 Broadway Ave., Cleveland, OH 44127. 216-441-8500 FAX 216-441-8503. Since 1946! www.electronicssurplus.com

WANTED: AVIONICS test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

WESTERN ELECTRIC audio equipment wanted. 1927-1960's. Amplifiers, "pre-amps," speakers, transformers, tubes, etc. 1-800-251-5454.

WESTERN ELECTRIC WANTED: 1920's-1960's. Amplifiers, mixers, pre-amps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.

WANTED: ELECTRONIC estates. Ham, broadcasting, military, test, public address, tubes, transformers, telex equipment. The bigger the pile, the more worthwhile. We fly anywhere. Sumner McDanel 1-800-251-5454.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

WANTED: GR1630AV; GR1620; power resistors (carbon tube, heatsink ww preferred, 50wt); AC capacitors (60 out, .1uF-50uF). 610-932-4019.

HIGHEST PRICES paid for Western Electric tubes, new and used. Also buying many others. Call or send us your list. **Don Singerhouse/Singerhouse Sound, PO Box 321, New Richmond, WI 54017. Toll free tel/fax: 1-888-715-tube. E-Mail: singtube@frontiernet.net**

BBS & ONLINE SERVICES

VISIT DON Lancaster's GURU'S LAIR website at <http://www.tinaja.com> PICs, pseudoscience, PostScript, patents, Tinaja quests, flutterwumpers, book-on-demand, magic sinewaves, money machines, Navicubes, tramways, wavelets, and Webmastering. Online reprints, consultants net, forums, annotated hot links, surplus bargains, great heaping bunches more.

CHECK IT OUT: members.aol.com/corkymoos members.aol.com/corkymoos members.aol.com/corkymoos members.aol.com/corkymoos members.aol.com/corkymoos

Sell Nuts & Volts in your store!
Contact us for complete details.
phone 909-371-8497
fax 909-371-3052
E-Mail distributors@nutsvolts.com

EDUCATION

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

DON LANCASTER'S ACTIVE FILTER COOKBOOK is back in print. Autographed copies of the seventeenth(!) classic printing \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

GRAND UNIFIED THEORY MADE EASY. 110 page book explains a new theory linking gravity, electronics & magnetism. Explores universe mysteries, goes beyond-relativity & quantum theory. \$9.95. To order: send check or M/O to American Science Innovations, PO Box 155, Clarington, OH 43915.

Congratulations Larry Gunseor Winner of our December Drawing!

RAMSEY World's Smallest TV Transmitters

We call them the 'Cubes'... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture!

Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air!

C-2000, Basic Video Transmitter Cube.....\$89.95
C-3000, Basic Video and Audio Transmitter Cube.....\$149.95
C-2001, High Power Video Transmitter Cube.....\$179.95
C-3001, High Power Video and Audio Transmitter Cube.....\$229.95

Super Pro FM Stereo Radio Transmitter



A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require

a whole equipment rack to hold all the features we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'punch' in your audio - without over modulation, LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes cabinet, whip antenna and 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

FM-100, Professional FM Stereo Transmitter Kit.....\$299.95
FM-100WT, Fully Wired High Power FM Transmitter.....\$429.95

AM Band Radio Transmitter



Ramsey AM radio transmitters operate in the standard AM broadcast band and are easy to set to any clear channel in your area. Our AM-25, 'pro' version, fully synthesized transmitter features easy frequency setting DIP switches for stable, no-drift frequency control, while being jumper settable for higher power output where regulations allow. The entry-level AM-1 uses a tunable transmit oscillator and runs the maximum 100 milliwatts of power. No FCC license is required, expected range is up to 1/4 mile depending upon antenna and conditions. Transmitters accept standard line-level inputs from tape decks, CD players or mike mixers, and run on 12 volts DC. The Pro AM-25 comes complete with AC power adapter, matching case set and bottom loaded wire antenna. Our entry-level AM-1 has an available matching case and knob set for a finished, professional look.

AM-25, Professional AM Transmitter Kit.....\$129.95
AM-1, Entry level AM Radio Transmitter Kit.....\$29.95
CAM, Matching Case Set for AM-1.....\$14.95

CCD Video Cameras



If you're looking for a good quality CCD board camera, stop right here! Our cameras use top quality Japanese Class 'A' CCD arrays with over 440 line line resolution, not the off-spec arrays that are found on many other cameras. You see, the Japanese suppliers grade the CCDs at manufacture and some manufacturers end up with the off-grade chips due to either cost constraints or lack of buying 'clout'. Also, a new strain of CMOS single chip cameras are entering the market, those units have about 1/2 the resolution and draw over twice the current that these cameras do - don't be fooled! Our cameras have nice clean fields and excellent light sensitivity, you'll really see the difference, and if you want to see in the dark, the black & white models are super IR (Infra-Red) sensitive. Our IR-1 illuminator kit is invisible to the human eye, but lights the scene like a flashlight at night! Color camera has Auto White Balance, Auto Gain, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. They run on 9 VDC and produce standard 1 volt p-p video. Add one of our transmitter units for wireless transmission to any TV set, or add our IB-1 Interface board for audio sound pick-up and super easy direct wire hook-up connection to any Video monitor, VCR or TV with video/audio input jacks. Cameras fully assembled, including pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens.....\$99.95
CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$99.95
CCDPH-2, Color CCD Camera, wide-angle lens.....\$149.95
IR-1, IR Illuminator Kit for B&W cameras.....\$24.95
IB-1, Interface Board Kit.....\$24.95

FM Stereo Radio Transmitters



Microprocessor controlled for easy frequency programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations.

Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized FM Stereo Transmitter Kit.....\$129.95

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC. Add our matching case and whip antenna set for a nice finished look.

FM-10A, Tunable FM Stereo Transmitter Kit.....\$34.95
CFM, Matching Case and Antenna Set.....\$14.95
AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

RF Power Booster

Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat, professionally finished look, add the optional matching case set.

LPA-1, Power Booster Amplifier Kit.....\$39.95
CLPA, Matching Case Set for LPA-1 Kit.....\$14.95
LPA-1WT, Fully Wired LPA-1 with Case.....\$99.95

BUSINESS OPPORTUNITIES

MILLIONS \$\$\$ in "scrap gold" from old computers and electronics junk. Message: 603-645-4776 or www.tiac.net/users/quicksand/goldtek.htm

INTERNET DISTRIBUTORS wanted. The nation's largest privately-held ISP needs distributors in all areas. E-Mail: rgobel@navix.net for free information.

Treasure Finder Kit



Search for buried treasure at the beach, backyard or park. This professional quality kit can detect metal at a depth of up to 6 inches. Easy to use, just listen for the change in tone as you 'sweep' the unit across the surface - the larger the tone change - the larger the object.

Has built-in speaker or earphone connection, runs on standard 9 volt battery. Complete kit includes handsome case, rugged PVC handle assembly that 'breaks down' for easy transportation and shielded Faraday search coil. Easy one evening assembly. This nifty kit will literally pay for itself! That guy in the picture looks like he found something - what do you think it is - gold, silver, Rogaine, Viagra? You'll have fun with this kit.

TF-1, Treasure Finder Kit.....\$39.95

Binocular Special



We came across these nice binoculars in an importers close-out deal. Not some cheap in-line lens jobs, these beauties have roof prisms, a super nice rubber armored housing over light weight

aluminum. 10 x 25 power with fully coated optics. Includes lens cleaner cloth, neck lanyard and nice carry case. For extra demanding use in bright sun, choose the EX module with ruby coated Objective lens. First quality at a close-out price! We've seen the exact same units with the 'Bushnell' name on them being sold for \$30 more!

BNO-1, Binoculars and case.....\$24.95
BNO-1EX, Ruby Coated Lens Binoculars and case.....\$29.95

Speech Descrambler



Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. Speech inversion technology is used, which is compatible with most cordless phones and many police department systems, hook it up to your scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC. Our matching case set adds a professional look to your kit.

SS-70A, Speech Descrambler/Scrambler Kit.....\$39.95
CSS, Custom Matching Case and Knob Set.....\$14.95
SS-70AWT, Fully Wired SS-70A with Case.....\$79.95
AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

Call for our Free Catalog!

See our complete catalog and order on-line with our secure server at: www.ramseyelectronics.com

RAMSEY ELECTRONICS, INC.

793 Canning Parkway Victor, NY 14564

Order Toll-free: 800-446-2295

Sorry, no tech info, order status at this number

Technical Info, Order Status

Call Factory direct: 716-924-4560

Fax: 716-924-4555



ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

THE CASE AGAINST PATENTS. Thoroughly tested and proven alternatives that work in the real world, \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

Closing Date
For Next Issue - February 5th



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

ROSE AIRCRAFT seeks investors for solar electric 1 pilot helium helicopter. \$5 for info \$100 plans. 619-223-7191 x218. CV, CA 91912-7589.

REPAIRS - SERVICES

PINBALL MACHINES! Books, Magazines, Manuals, Diagrams, Supplies, Parts. \$2 catalog, Marco Specialties, 5290-N Platt Springs Rd., Lexington, SC 29073-9252. 803-957-5500. FAX 803-957-6974. E-Mail: tilt@ix.netcom.com http://pinball machine.com

ENGINEERING CONSULTING. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05xx, HC11xx, and PIC families. Software design for IBM PC, XLINX and Altera FPGA design. In-house schematic capture and PWB. Hicks Electronic Design, PO Box 7366, Loveland, CO 80537-0366. Toll Free 1-888-849-6792 E-Mail: steve@hickseng ineering.com website: www.hickseng ineering.com

(E)PROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

PC BOARDS REPAIRED. Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.

PROFESSIONAL PRINTED circuit design on CAD, over 30 years experience. All types of designs: conventional, multilayer, downhole, fine line. Prototype and production boards fabricated. Reverse engineer existing two layer boards. Quick service with affordable cost. Call now for your quote. Tel 713-952-8623, Fax 713-952-8624.

CABLE CONVERTER REPAIR: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: HIGHENG1@AOL ask for George.

PLAYSTATION MOD chips. Works with all models up to 750x. Color instructions. Five wire hook up, comes with wire. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118.

Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 800 Series, 1000C, 1150C, Copier 120, 210	6	10	6.67	4.00	39.95	39.95
HP 720C, 722C, 890C, 1120C	6	10	6.67	4.50	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Apple StyleWriter 2400, 2500						
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200	10	17	4.00	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK	COLOR
	CARTRIDGE	CARTRIDGE
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$12.00	\$19.00
Epson Stylus Color II, IIs	\$14.00	\$19.00
Epson Stylus Color 500, 200	\$14.00	\$19.00
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	\$14.00	\$19.00

- **BULK Inks, Refill Accessories**
- **Glossy card stock & Coated Paper**
- **School & Government PO's Welcome**
- **2 - 3 Day Shipping**

Quality Inks for:
HP • Epson • Lexmark
Canon • Apple • DEC

Inkjet
Southwest



Call or see us online!

Monday - Friday
7:30 - 4:30 PST 10:30 - 7:30 EST

www.inkjetsw.com

(602) 668-7334 Fax

1-800-447-3469

(602) 668-0959

*You Win
with Nuts
& Volts*

**Subscribe today and be
automatically entered
in our new MONTHLY
PRIZE DRAWING!!!**

To Subscribe -
Just fill in and mail the
enclosed subscription
card or call our toll
free order line at
(800) 783-4624 with a
Visa or MasterCard.

**We now offer
a three-year
subscription
for only \$51.00!!
(USA delivery only)**

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200

• Correct implementation of manufacturer specified algorithms for fast, reliable programming.

• Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.

• Full over current detection on all device power supplies protects against bad chips and reverse insertion.


• Broad support for additional devices using adapters listed below.

Available Adapters

EP-PIC (18C5x, 61, 62x, 71, 84)	\$49.95
EP-PIC64 (16C62-5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (88HC11 E/A)	\$59.95
EP-11D (88HC11D03)	\$39.95
EP-16 (16bit EPROMs)	\$49.95
EP-28 (286E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (IC22v10, 18v8)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

M²L Electronics

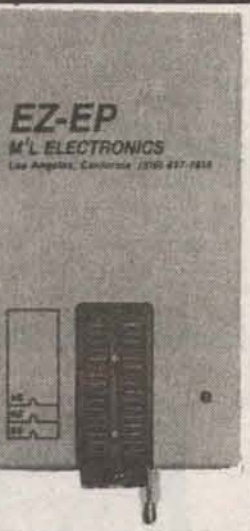970/259-0555
Fax: 970/259-0777
361 S Camino Del Rio #119
Durango, CO 81301
CO orders please add 7% sales tax.
<http://www.m2l.com>



Write in 96 on Reader Service Card.

Events CALENDAR

Continued from page 42

E-Mail: w6nw@amateur-radio.org
Web: <http://www.amateur-radio.org/ncdxc.org>

APRIL 10

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

MA - ROCHESTER - Hamfest. Rochester ARC, John Scott N0HZN, 507-285-6522.

E-Mail: n0hzn@aol.com

Web: <http://members.aol.com/rarchams/>

NC - MORGANTON - Hamfest & Computer Fair. Burke County Fairgrounds, Hwy. 181N (Exit 100 Eastbound, Exit 105 Westbound I-40). 8am-5pm. Talk-in: 147.15 (K4VLY repeater). Catawba Valley, Tom T aylor, 704-433-6205.

E-Mail: kc4qpr@vistatech.net

WA - SPOKANE - Hamfest. Lilac City ARC, Warren Kelsey KJ7BB, 509-534-8443

APRIL 11

NC - RALEIGH - RARSfest. State Fairgrounds, Jim Graham Bldg. 8am-4pm. Raleigh ARS, Wilbur Goss WD4RDT, 919-266-9883. E-Mail: k4hf@juno.com

WI - MADISON - Hamfest. Madison Area Repeater Assn., Paul Toussaint N9VWH, 608-245-8890. E-Mail: n9vwh@hotmail.com

APRIL 17

AL - ALBERTVILLE - Hamfest. Marshall County ARC, Buddy Smith KC4URL, 256-593-2516. E-Mail: kc4url@aimet.net

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

ID - IDAHO FALLS - Hamfest. Eastern Idaho UHF Society, Jay Greenburg WA4VRV, 208-524-1388. E-Mail: wa4vrv@srv.net

Web: <http://www.srv.net/~wa4vrv/hamfest.htm>

KY - MURRAY - Hamfest. Murray State University ARC, Pat Compton KF4FMZ, 502-762-6433. E-Mail: patrick.compton@murraystate.edu

Web: <http://mursuky.edu/clubs/msuarc/hamfest.htm>

MA - BLAINE - Hamfest. Robbinsdale ARC, Jerry Dorf N0FWG, or Harriet Johanson 612-537-1722. E-Mail: jerryd@skypoint.com

MO - JOPLIN - Hamfest. Joplin ARC, Ray Brown KB0STN, 417-781-4967. E-Mail: raybrown@ipa.net

Web: <http://www.joplin-arc.org>

OK - LAWTON - Hamfest. Lawton Ft. Sill ARC, Bob Morford KA5YED, 580-355-6120 or 580-353-8074

APRIL 18

CT - HARTFORD - 1999 Trinity College Fire-Fighting Home Robot Contest. Trinity College campus. Jake Mendelsohn, 190 Mohegan Dr., West Hartford, CT 06117. E-Mail: JMENDEL141@AOL.COM

Web: <http://www.trincoll.edu/~robot>

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

PA - MONROEVILLE - Hamfest. Two Rivers ARC, Michael Kowalcheck, Jr. KV3L, 412-751-9657

APRIL 23-24

AR - LITTLE ROCK - Hamfest. Jim Blackmon K5VZ, 870-246-7833 H, 870-246-6734 W. E-Mail: lrhamfest@usa.net

Web: <http://www.aristotle.net/~ares/hamfest/>

APRIL 24

AR - BENTONVILLE - Hamfest. Benton County Radio Operators, Betty Weiberg N0XWQ, 417-435-

2332

IA - DES MOINES - Hamfest. Des Moines RAA, Duane Bower WB0UCY, 515-287-6542

NJ - HARMONY - Hamfest. Warren County Farmers Fairgrounds, Rt. 519 N. 8am-2pm. VE Exams. Talk-in: 147.375+ 146.730. Cherryville RA II, Inc., Randy Vance N2MQZ, 908-788-4080 or 908-454-4370. E-Mail: n2mqz@aol.com

Web: <mailto://w2cra@qsl.net>

NM - ALBUQUERQUE - Hamfest. Albuquerque ARC & AR Caravan Club, Chuck Opdyke KC5GA, 505-858-0306. E-Mail: n5oqj@worldnet.att.net

VA - CHESAPEAKE - Hamfest. Chesapeake AR Service, Jim Cannon KF4RQQ, 757-382-0193. Web: <http://www.qsl.net/cars>

WA - VANCOUVER - Hamfest. Clark County ARC, Luther Brisky KC7KVL, 360-896-8909 or 360-254-5082. E-Mail: lwayne@e-z.net

Web: <http://www.w7aja.org>

APRIL 25

FL - GAINESVILLE - Hamfest. Gainesville ARS, H. Walter Johnston W4TKE. E-Mail: w4tke@juno.com

E-Mail: w4tke@gator.net

IL - ARTHUR - Hamfest. Moultrie ARK, Ralph Zancha WC9V, 217-873-5287 or 217-543-2178. E-Mail: rzancha@one-eleven.net

Web: <http://home.stlnet.com/~jhdson/hamfest.html>

IL - GALVA - Hamfest. Bill Anderson WB9TEW, 309-932-3023. E-Mail: bill@inw.net

OH - ATHENS - Hamfest. Athens County ARA, Drew McDaniel W8MHV, 740-592-2106.

BLOWOUT SPECIALS

SUPER SAVING UPGRADE KIT

M BOARDS WITH CPU, 8MB AGP & SOUND:

K6-2 300 MHz MMX	\$199
K6-2 333 MHz MMX	\$229
K6-2 350 MHz MMX	\$249
Pentium II Celeron 300	\$199
Pentium II Celeron 300 w 128Kcache	\$199
Pentium II Celeron 333 w 128Kcache	\$219
Pentium II 266 MMX	\$299
Pentium II 300 MMX	\$339
Pentium II 333 MMX	\$339
Pentium II 350 MMX	\$345
Pentium II 400 MMX	\$445
Pentium II 450 MMX	\$675

CASES WITH POWER SUPPLIES

MED TOWER CASE PREMIUM.....	\$29
ATX MED TOWER CASE PREMI.....	\$49

FLOPPY

1.44 Mitsumi.....	\$16.95
-------------------	---------

MONITORS

14" 28 108 N-I, Low Radiation.....	\$119
15" 28 1024x768 N-I, Low Rad.....	\$145
17" 28 1280x1024 N-I, Low Rad.....	\$239

KEYBOARDS

104 Keyboard.....	\$10
Keytronic.....	\$19
Focus 2000.....	\$call

VGA CARDS

SVGA 1MB ISA.....	\$35
PCI 1MB/2MB/4MB.....	\$1425/39
PCI OR AGP 4MB. TV OUT. OPTI.....	\$39
PCI OR AGP VGA 8MB.....	\$69

BANSII 16MB.....\$119

VOODOO II 12MB W/incomming & G-Police.....\$119

ANY OTHER VGA CARDS.....\$CALL

CONTROLLER SCSI

DIAMOND FIRE PORT 40.....\$95

Adaptec 2940/2940UW/2940U2W.....\$149/169/379

MODEM FAX MODEM

33.6K Voice Modem/Fax Modem.....	\$26
56K Voice Modem/Fax Modem.....	\$29
US ROBOTIC 56K Modem.....V90.....	\$69
ISDN.....	\$CALL

BISME COMPUTERS OUTLET

906 N Carpenter Rd. Suite A. Modesto, CA 95351



36X CDROM..\$45

Orders & Price

Tel: (800) 899 6430

36X Bundle

\$69

36X Speed CD
16 Bit Sound Card
with Wavetable.
Amplified Speakers 80W

For ALL kinds of Drives, Sound Cards
Speakers and CD Titles: \$Call

HARD DRIVES SPECIALS

4.3GB..\$136 6.4GB..\$155 8.4GB..\$185 10GB..\$219
13.5GB..\$245 16GB..\$375 21GB..\$555 any other CAL

IBM 6X86

333 MMX

Motherboard

CPU, 8MB AGP

VGA & SOUND

\$199

Will beat any price

Resellers

Dealers

Welcome

3 years Parts &

5 years Labor

Warranty.

Lifetime Tech

Support

All Systems carry

3 years Parts &

5 years Labor

Warranty.

Lifetime Tech

Support

EVERYDAY

LOW PRICES

www.bisme.com

906 N Carpenter Rd. Suite A. Modesto, CA 95351

Write in 97 on Reader Service Card.

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT

Visit www.alfaelectronics.com for complete info

Call 1-800-526-2532 for Order and Free Catalog



DMM

DMM-895 (\$179.00): true rms, AC/DC (V,A), Ω , bar graph, freq, capac, dBm, logic, diode

DMM-237 (\$99.95): 4 1/2 digit, true rms, high resol (10 μ V, 10nA, 10m Ω), hFE, diode, contin.

DMM-20 (\$74.95): AC/DC (V, A), Freq, cont., Capac, Induct., Ω , hFE, diode, duty cycle

DMM-122 (\$59.95): DC/AC (V,A), Ω , hFE, diode, capacitance, freq, logic, continuity

DMM-123 (\$44.95): DMM + capacitance, DC/AC (V,A), Ω , hFE, diode, continuity

DMM-10 (\$19.95): 3 1/2 digit, DC/AC V, Ω , hFE, diode, signal output (+3V, -0.5Vsq, 50% duty)



LCR/COUNTER

CAP-15 (\$49.95): 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution, zero adjustment.

LCR-24 (\$119.95): 0.1 μ H-200H, 0.1pF-2000 μ F, 0.01 Ω -20M Ω , diode test. New Model.

LCR-131D (\$129.95): autorange, 0.1 μ H-10kH, 0.1pF-10mF, 1m Ω -10M Ω , Q Factor, serial/parallel, 120Hz/1kHz testing mode.

FC-1200 (\$129.95): 1.25GHz Handheld, 8 digits display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (440MHz)

FLUKE

12B \$94.95

70-III \$99.00

73-III \$125.00

75-III \$155.00

77-III \$173.00

79-III \$195.00

87-III \$325.00

92B-III \$1,445

96B-II \$1,695

99B-III \$2,095

105B \$2,495

123-III \$1,130

863E \$555

867B \$740

SPECIALTY

AC Current Probe \$34.95

DC/AC Current Probe \$79.95

Mini AC Clamp \$59.95

AC Clamp w/temp \$89.95

DC/AC Clamp \$109.95

Thermometer \$69.95-\$89.95

IR Thermometer \$189.95

Sound Level Meter \$169.95

Tachometer \$169.95-\$219.95

EMF Tester \$69.95

Pressure Meter \$299.95

Watt Meter \$129.95

High Voltage Probe \$59.95

pH Meter \$79.95

Light Meter \$79.95-\$89.95



Single Output DC Power Supplies

• Constant current, constant voltage mode

• Short Circuit and overload protected

Analog Meters Display

PS-303 (\$159.00) 30V/3A

PS-305 (\$129.95) 30V/5A

PS-8112 (\$399.95) 60V/5A

PS-1610 (\$289.00) 16V/10A

PS-8107 (\$

Events CALENDAR

E-Mail: dmcdaniell@ohio.edu

MAY 1999

MAY 1

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

TN - NASHVILLE - Hamfest. Nashville ARC, Bob Malone WB5ZDS, 615-865-6225

WI - CEDARBURG - Hamfest. Ozaukee RC, Joe Holly AA9HR, 414-377-2137

MAY 12

NJ - EDISON - Trenton Computer Festival. NJ

Convention Center, Raritan Center. Sat: 9am-5pm, Sun: 9am-4pm. KGP Productions, Inc., Marin Light, 1-800-631-0062. E-Mail: kgp@mail.com Web: www.tcf-nj.org

TX - ABILENE - West Texas Section Convention, Peggy Richard KA4UPA, 915-672-8889. E-Mail: jimr@swconnect.net

MAY 2

MD - HAGERSTOWN - Hamfest. Community College, Athletic and Recreation Bldg. 8am-3pm. Talk-in: 147.090+. The Antietam Radio Assn., Tina Jones KB8ZQM, 304-728-7769. E-Mail: kb8zqm@intrepid.net

Web: http://www.erols.com/rjlong61/ara

NY - YONKERS - Flea Market. Lincoln High

School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053

WV - RIPLEY - Hamfest. Jackson County ARC, Gary Casto AG8RY, 304-372-2849

MAY 8

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

TX - CHICOTA - Hamfest. Red River Valley ARC & ARES of Lamar County, Kevin "Mort" Winslow N3YNL, 214-894-3088.

E-Mail: 4n3ynl@unicomp.net

MAY 14-15-16

OH - DAYTON - Hamfest. Dayton ARA, Dick Miller N8CBU, 937-427-3109.

E-Mail: chair@hamvention.org

Web: http://www.hamvention.org

MAY 15

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

GA - STATESBORO - Hamfest. Statesboro ARS, Martin Holzman WB4MOG. E-Mail: mart@bulloch.com

MAY 16

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: http://web.mit.edu/w1mx/www/swapfest.html

MAY 22-23

WA - YAKIMA - WA State Convention. Yakima ARC, C. Jo Whitney KA7LJQ, 509-965-3379. E-Mail: kb7hdx@televar.com Web: http://eagle.ykm.com/~w7aq/hamfest.html

MAY 29

CANADA - MANITOBA - WINNIPEG - Hamfest. Winnipeg ARC, Ed Henderson VE4YU, 204-694-0667. E-Mail: edve4yu@pangea.ca

NY - PLATTSBURGH - Hamfest. Champlain Valley ARC, Bernhard Jakobetz KC2ALG, 518-643-9657

MAY 30

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813

JUNE 1999

JUNE 5

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

JUNE 5-6

OR - SEASIDE - SEAPAC Ham Convention. Seaside Convention Center. VE Exams. Randy Stinson K2ZT, 503-297-1175. E-Mail: rastinson@att.net

JUNE 12

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

JUNE 19

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

JUNE 20

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: http://web.mit.edu/w1mx/www/swapfest.html

JULY 1999

JULY 3

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

JULY 10

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

NY - BATAVIA - Hamfest. Genesee fairgrounds. 6am-3pm. Talk-in: W2RCX 147.285+. "Gram," Harold Hay, 716-343-2844. E-Mail: Wa2abq@aol.com

JULY 17

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

JULY 18

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: http://web.mit.edu/w1mx/www/swapfest.html

JULY 25

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813

AUGUST 1999

AUGUST 7

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

AUGUST 14

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 96 Page CATALOG. Outside the U.S.A. send \$3.00 postage.

Interact ProPad GAME CONTROLLER

Interact Game Products # SV-230 PC ProPad works with hundreds of PC games. Very similar to Super Nintendo controllers, it has a four-way direction button on the left, A and B buttons on the right and speed controls and auto-fire controls in the middle. 15 pin D-sub connector plugs into the sound card on most Windows based computers.

\$3.00 each CAT # SV-230
2 for \$5.00

3000 MCD ULTRA-BRIGHT RED LED

Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs now at our lowest price ever. Due to a special purchase of "tape-and-reel" parts we are able to offer these LEDs at an incredibly low price when purchased on the reel. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.

CAT# LED-50
2 for \$1.00
100 for \$35.00
1000 for \$250.00 (25¢ each)

S-VHS Tape (Used)

Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great and cost a fraction of the "new" price.

CAT #S-VHS
\$3.00 each
10 for \$28.00 • 100 for \$250.00

INCREDIBLY CHEAP!! Switching Power Supply

Voltek Corp # SPEC7188B Input: 100 - 240 Vac Outputs: +5 Vdc @ 3.70 A, +12 Vdc @ 0.60 A, -5 Vdc @ 0.05 A, +5 Vdc Trickle @ 0.1 A Metal encased switching supply. Standard three-prong IEC socket power input. 7 conductor, Molex-type connector output. 9" x 2.1" x 1.36". UL recognized. Removed from new equipment.

CAT # PS-27
\$3.50 each

10K THERMISTOR

Semitec # 103AT-2 10K ohm (± 1%) @ 25 deg. C. Rated 10 mW. Time constant: 15 sec. 2 mm x 3mm. 2.5mm lead spacing.

CAT #THR-20
\$1.00 each
10 for \$8.50
200 for \$130.00

3 BUTTON Serial MOUSE

Windows compatible three button serial mouse. Includes 3.5" floppy disk with drivers.

\$3.50 each CAT #MSE-3
10 for \$30.00

Encased Piezoelectric Element

0.82" DIAMETER X 0.15" AVX/Kyocera # PCRT21BGX Black plastic front, vented metal back. Solder loop terminals. Louder than non encased piezo elements. Requires external signal to produce sound.

CAT # PE-38
3 for \$1.00
100 for \$25.00
1000 for \$125.00

BIG Flashing LED

Big, bright red flashing LED. 10 mm diameter. Red diffused lens. Great for attention getting displays. Operates on 3-12 Vdc. Flash rate approx. 2 times per second.

CAT# LED-60
2 for \$1.50
10 for \$6.50
100 for \$50.00

UV Blacklight

New black-light lamps designed by Avon Cosmetics to highlight dry skin. They have a built-in timer that shuts-off the lamp after approximately one minute. Ideal for lighting fluorescence in black-light posters, gemstones, hand stamps and US currency. 5" lamp, F4T5BLB, is housed in a lightweight plastic case. 7" x 3.25" x 2.3" high. Powered by a 12 Vdc, 500 ma wall transformer (included). Individually boxed.

CAT# UVL-1
\$10.00 each

F4T5-BLB Replacement lamp for above fixture. **CAT # BLB-5** \$3.00 each

470 Mfd 450 Vdc

Nichicon #LGQ2W471MHSC 1.375" dia x 2" high. 0.4" lead spacing.

CAT# EC-4745
\$3.00 each
10 for \$22.50

"Hi-8" Video Cassette

SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.

CAT # VCU-8
\$3.00 each
10 for \$28.00 • 100 for \$250.00

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
INTERNET http://www.allcorp.com/
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

Equipment Management Technology

From Acquisition to Disposition

BUY * RENT * SELL

Quality Test and Measurement Equipment

We inventory HP, Tektronix, Fluke, Anritsu, Wiltron, Iwatsu, Wavetek, GenRad and many other manufacturers. Our product lines include RF & microwave, oscilloscopes, generators, supplies, communications, voltage and frequency standards. Call us now for a quote!

Tel 650-631-1700 * Fax 650-631-1200 * email sales@emt1.com

Write in 100 on Reader Service Card.

Events CALENDAR

AUGUST 15

KY - LEXINGTON - Hamfest. National Guard Armory. 8am-4pm. VE Exams. Talk-in: 146.760. John Barnes KS4GL, 606-253-1178. E-Mail: KS4GL@juno.com
MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

AUGUST 21

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

SEPTEMBER 1999

SEPTEMBER 4

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

SEPTEMBER 11

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

SEPTEMBER 18

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

SEPTEMBER 19

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

SEPTEMBER 26

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813.
NY - YONKERS - Flea Market. Lincoln High School. Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network. Otto Supliski WB2SLQ, 914-969-1053

OCTOBER 1999

OCTOBER 2

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

OCTOBER 9

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

OCTOBER 16

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

OCTOBER 17

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

NOVEMBER 1999

NOVEMBER 6

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in.

619-561-0052

NOVEMBER 13

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

NOVEMBER 20

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

NOVEMBER 25

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813

DECEMBER 1999

DECEMBER 4

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

DECEMBER 11

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

DECEMBER 18

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052



REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single Black Refill \$8.00; Triple Refill \$19.00. **CANON BJC-600 (BC-201)** Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJI-481 & BJI-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240 (BC-05 Cart)** 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and **Apple Stylewriter 2400** Black 3-bottle kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70** and **Apple Stylewriter 2400** Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJI-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJI-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049), Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00; **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560** Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C** - Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C** (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP DESKJET 720, 722, 890, OFFICE JET 1170 & 1175 (C1823A)** Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/ExecJet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark ExecJet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.



HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Inforunner \$8.00; Commodore MPS-801 \$5.00; MPS-803 \$7.00; Decwriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannisman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00; Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00.

ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed.

Order directly or send SASE for complete list.

Add \$4.00 per order shipping. California residents add 7.75% sales tax.

On ribbon orders over \$50.00 deduct 10% discount.



H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216



<http://www.extremepay.com/occomp/orr.htm>

Write in 101 on Reader Service Card.

CABLE TV CONVERTERS

WILL NOT DECODE

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

TIMELESS PRODUCTS

New! "TP 125 V"
 128 Channel Converter with Volume

Special Prices for
 TP1550PC
 Call for Details

Panasonic still available!


- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES

Write in 102 on Reader Service Card.

STAMP APPLICATIONS

by Lon Glazner

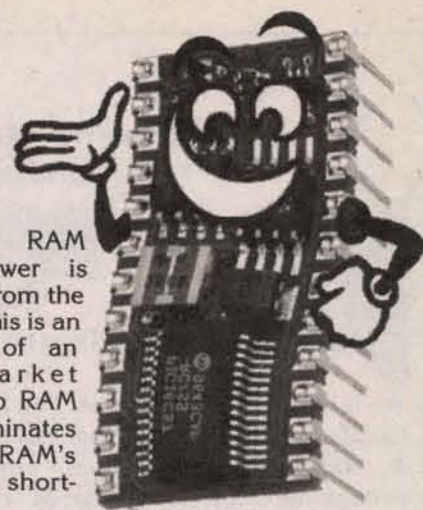

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

Storing Data With The RAMPack B

Overview

A problem commonly faced by Stamp users is how to store data that can sometimes come in overwhelming quantities. We're not talking just a few bytes here and a few bytes there. We're talking about a few hundred bytes — or more — that need to be stored for later use. If you ever wanted to store a text file, and parse the data out to some serial device, or have a string of serial data stored automatically for you, then the RAMPack B may fit the bill.

More importantly, we'll be using this month's RAMPack B (RPB) overview as a stepping stone. Next month, we'll use the serial data storage capacity of the RPB to store graphic bit-map (*.BMP) data files. These files will be downloaded directly from your PC into the RPB. Next month's article will also use the Scott Edwards Electronics, Inc., G12032 Mini Serial Liquid Crystal Display (G12032 LCD). With the RPB and the G12032 LCD, developing graphic displays becomes a relatively simple task. Some limited animation with the graphic display is also possible using these two devices in tandem.

In this article, we will start off covering some of the basic functions of the RPB, briefly discuss data conversion, and finish up with how to use the First-In-First-Out (FIFO) buffer mode to store serial data automatically. But first, an overview of electronic memory "types."

Data Memory Discussion

There are quite a few ways to store data in today's electronic devices. There are typically four areas of concern that need to be addressed when selecting a memory device. These areas are speed, volatility of memory, input/output (I/O) pins required to access the memory, and how often the memory can be written to.

For example, with serial EEPROM (Electrically Erasable PROM), such as Microchip's 24LCxx series, you gain the dual

benefits of a low pin count to access the memory and non-volatile memory (stored data is retained after power is removed). With EEPROM, you can usually access memory with two or three I/O pins depending on the type of memory you use. Parallax provides application notes for interfacing a BASIC Stamp to EEPROM. In fact, the BASIC Stamp has EEPROM on board that can be





accessed through the PBASIC READ and WRITE commands. EEPROM is usually an excellent vehicle for the storage of data in electronic designs. It is low-cost, easy-to-use, and has memory that is retained even after power is lost. There are only three downsides to EEPROM. First, EEPROM is usually only guaranteed for one million erase/write cycles. This may seem like a lot, but if you were to update a memory location every three seconds, the EEPROM could fail after only 35 days of use. Secondly, interfacing to EEPROM is not always the easiest thing for beginners to accomplish. Finally, compared to other memory types, access time for EEPROM is considered slow. For the experienced Stamp user, the second shortcoming is of little consequence, and the third isn't entirely relevant because of the operating speed of BASIC Stamps.

SRAM (Static RAM), on the other hand, has no limitation on how many read/write cycles it can be used for, but requires a large number of I/O pins to address memory locations. In fact, with no additional logic buffers, more than 22 I/O pins could be required. The additional problem of volatile memory (data is lost when power is removed) usually precludes SRAM from being an attractive memory storage device for Stamp-based designs. SRAM, and RAM in general, has one additional advantage of fast access time that makes it attractive to designers using much faster processors than the BASIC Stamp.


There are additional types of RAM including Dallas Semiconductor NVRAM (non-volatile RAM). NVRAM provides a back-up lithium power source to retain

data in RAM when power is removed from the system. This is an example of an after-market addition to RAM that eliminates one of RAM's inherent shortcomings.

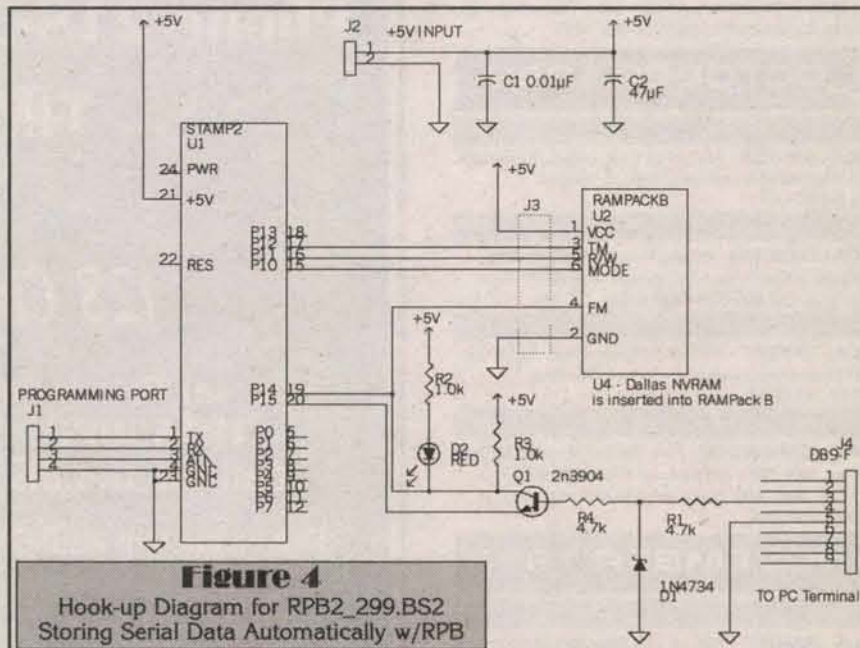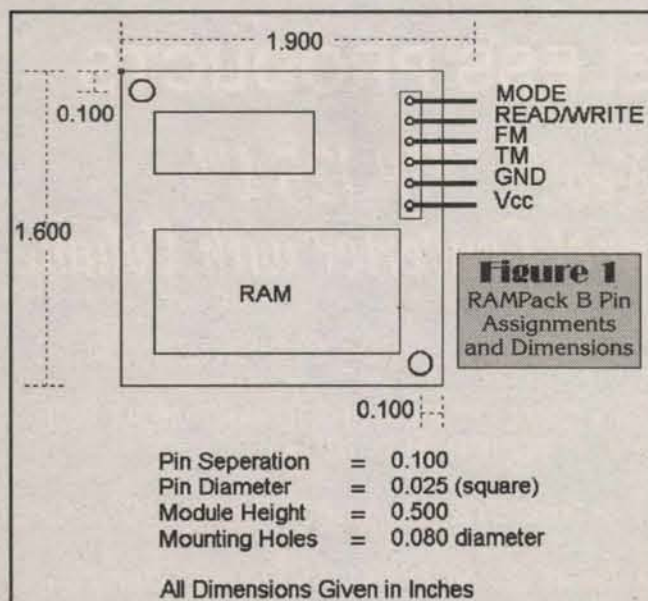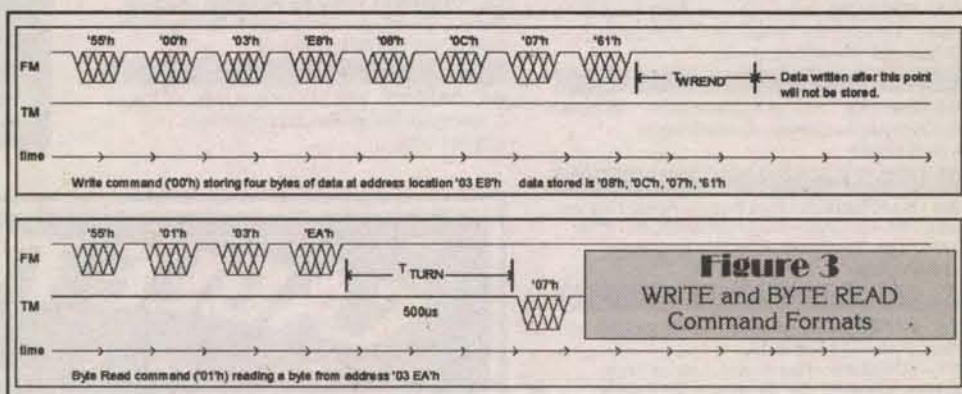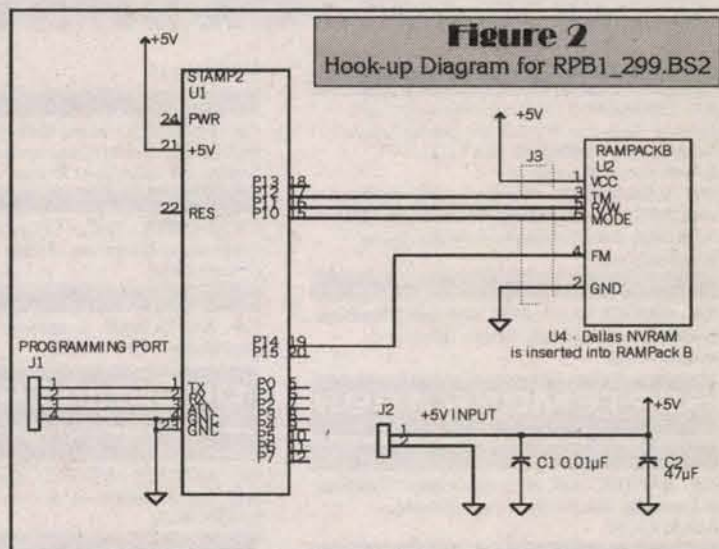The RPB is another such attempt to delete the shortcomings of RAM-based memory. The RPB is kind of like "smart RAM." With the RPB, access to SRAM can be accomplished with a single I/O pin. The communication format used by the RPB is the very common 8N1 (eight data bits, no parity, one stop bit) serial communication.



STAMP APPLICATIONS

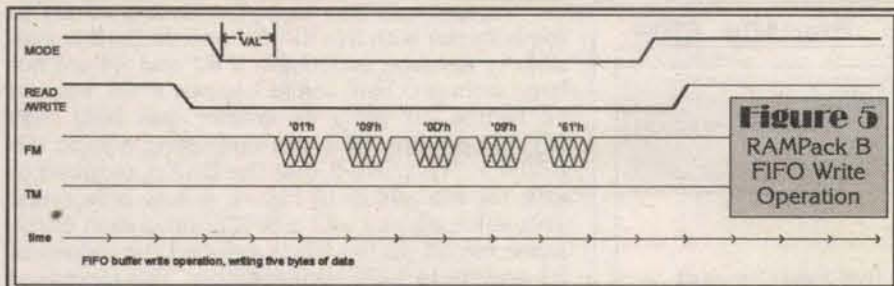

This is the same format as is used in many devices such as serial printers, PCs, GPS receivers, and the BASIC Stamp. In the RPB, SRAM comes socketed in the module. This SRAM can be removed and replaced with NVRAM. The RPB normally comes with 8Kx8 byte SRAM. 8Kx8 byte SRAM has room to store 8,192 bytes of data. The user can replace the 8Kx8 byte SRAM with 32Kx8 byte SRAM and extend the storage capability of the RPB to 32,768 bytes of data.

I used a Dallas Semiconductor DS1230Y-150 32Kx8 byte NVRAM in the RPB used in this design. I tend to keep one of these lying around for test purposes. There is no reason that the 8Kx8 byte SRAM that the RPB is sold with can't be used for any of the functions described in this article.

Using the RAMPack B WRITE and BYTE_READ Commands

To start with, we'll be taking a look at just the WRITE and BYTE_READ commands of the RPB. All commands sent to the RPB must be prefaced with a '\$55', or '55'hex. This is a binary '01010101', and is used by the RPB to calculate the baud rate that the Master unit is using to send

data. In this design, the Master unit is a BASIC Stamp 2. For more information on the RPB data formats, I would recommend downloading the latest data sheet from "www.solutions-cubed.com."

Code Listing 1 —
RBP1_299.BS2 —

shows one example of writing and reading data from the RPB using just the WRITE and BYTE_READ commands. The WRITE command discussed here should not be confused with the PBASIC WRITE command, which accesses EEPROM on-board the BASIC Stamp. All Solutions Cubed Mini-Mods — of which the RPB is one — can communicate using the PBASIC SEROUT and SERIN commands.

In RPB1_299.BS2, part of the ASCII character set is written to the RPB with the WRITE command. These ASCII values are then read back to the BASIC Stamp 2 (BS2) using the BYTE_READ command. Figure 2 can be used as a hook-up, or wiring diagram, if you want to try this yourself. This connection scheme uses two I/O pins to communicate with the RPB. You could connect the TM and FM pin of the RPB together and run this program using one I/O pin on the BS2. Multiple baud rates are used in this code example to display how the communication baud rate to and from the RPB can be changed on the fly.

The RPB WRITE command follows a simple format. Figure 3 displays the serial format in hexadecimal values. The decimal equivalents work for these values as well. The data string for a WRITE command always starts with the sync byte ('55'hex), then the command byte

('00'hex), followed by the high address byte, and low address byte, for the address location that the WRITE is to begin at. For example, to start writing data at address location 1000 ('03E8'hex), you would send '03'hex as the high address byte, and 'E8'hex as the low address byte. After this data is received by the RPB, it will store any subsequent bytes of data sequentially

SOURCES

For more information on the BASIC Stamp, contact:

Parallax, Inc.

3805 Atherton Road, #102
Rocklin, CA 95765
phone (916) 624-8333
<http://www.parallaxinc.com>

Scott Edwards Electronics, Inc.

2700 E. Fry Blvd. Suite A4
Sierra Vista, AZ 85635
phone 520-459-4802
fax 520-459-0623
www.seetron.com info@seetron.com

Solutions Cubed

Lon Glazner
3029 Esplanade Suite F
Chico, CA 95973
E-Mail: lon@solutions-cubed.com
Phone: 530-891-8045
Fax: 530-891-1643

MICRO VIDEO CAMERAS

MB-750U & MB750P
Video Cameras
your Choice
\$89.95

- 1.25" sq.
- .1 LUX
- 420 TV Line

The Best, Smallest, Micro Cameras on the Market Today!
Call and Compare! We Match or Beat All Prices!

WIRELESS VIDEO CAMERAS

NIGHT VISION



GFT-1001



Compatible with
AC or Battery

Transmits
Over
1000 ft.




Wireless Observation System's
GFS-1001 (900MHz) - \$499.95
GFS-1001c (900MHz) - \$599.95
(1.2 Ghz system available)

Wireless 4-Channel B/W &
COLOR Cameras Available!
Plug and Play Readiness

Panasonic Color Camera Sale

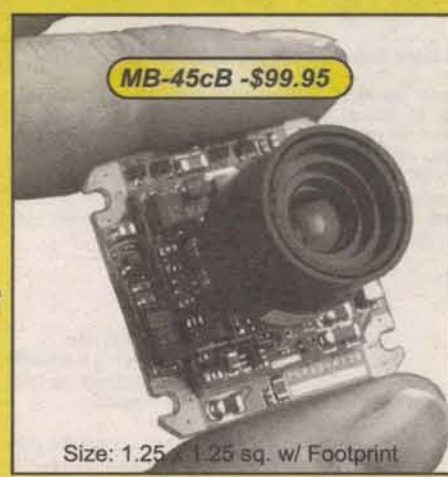MB-950c Panasonic Camera Sale \$99.95 was \$299.95
Sale Ends 12/31/98



Micro Color MB-45cB: \$99.95

- Wide Voltage Range, 5-14 Volts!
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

Specifications: MB-45cB Color Camera

Pick-up device	1/4" Interline transfer
Effective Pixels	512 (H) x 496 (V)
Scanning System	2:1 Interface
	525 lines - 60 fields
Frame per second	30 frames
Synchronization	Internal
Video output	VBS, 1vpp 75 Ohms
Horizontal Res.	More than 330 lines
Min. Required Illumination	40 LUX @ F2.8
AGC	On fixed
White Balance	ATW fixed
Operating Temperature	32°F to 104°F
Ambient conditions	Indoors
Lens	F2.8 Hor. Angle 45° - Ver. Angle 34°

AFFORDABLE LIPSTICK CAMERAS

These cameras are supplied with a PCM-1 Video/Power cable.
The BNC connection is for standard video connection to a Monitor or VCR.




1-800-752-3571

Visit Polaris Ind. Web Site at:
<http://www.polarisusa.com>

Polaris Industries 470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

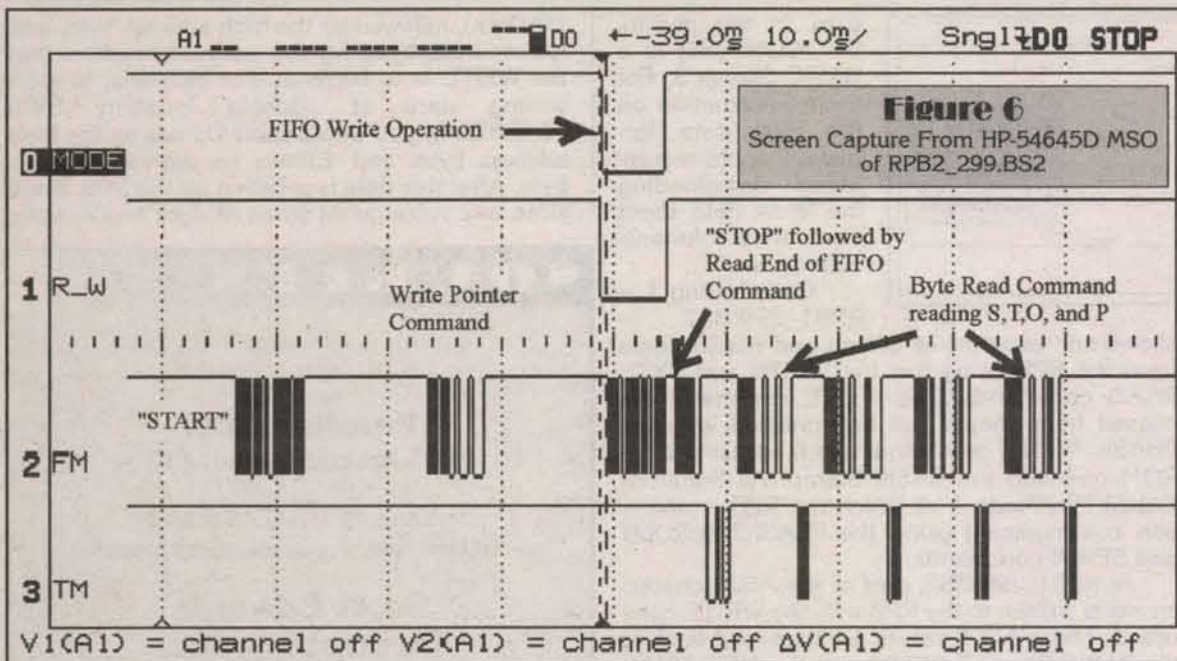Prices, availability and specifications are subject to change without notice. Shipping and Handling are not included with price.



in RAM. The RPB will exit the WRITE subroutine if there is no data received after a period of time. The time it takes for this to occur is based on the baud rate that data is being received at. For 9600 baud, the time the FM line must remain high for a WRITE to end is roughly 2ms.

For the BYTE READ command, the RPB expects the sync byte ('55'hex), then the command byte ('01'hex), and finally the high and low address bytes for the memory location that you would like to read. The RPB will send the data byte requested on the TM line in 500us. Figure 3 displays this function with data displayed in hexadecimal format.

Storing Serial Data Automatically With The RAMPack B

While the RPB WRITE and BYTE READ commands are useful, they don't solve a very common problem Stamp users run into. It's difficult to store large amounts of serial data for later use by the Stamp. Using the circuit in Figure 4 and the RPB's FIFO mode, you can easily inter-

face to the RPB to store serial data from a PC terminal program.

Some explanation of the circuit in Figure 4 is required. The transistor Q1 — along with D1, R1, and R4 — acts to invert and limit data signals from the PC serial port to the BS2 and RPB. This could be considered a "poor-man's" RS-232 converter. Data received at the RPB's FM pin from the PC will be at roughly TTL levels. R2 and D2 just provide a visual indication when data is being transmitted. The red LED, D2, will flash when data is present at the FM pin.

One of the trickier aspects to using the RPB FIFO mode in this configuration lies in the need to send commands to the RPB. Because the Master unit (BS2) has to share the FM pin with the serial data source (PC in this case), the BS2 must have the ability to seize the serial data line. This is accomplished by connecting the P15 (FMEN in code) of the BS2 to the emitter of Q1. If P15 (FMEN) of the BS2 is an output high (5VDC), then Q1 is effectively removed from the circuit. In this configuration, P14 (FMBS2) can be used to send commands to the RPB.

Current can flow from the emitter of Q1 to the collector with this kind of switch. So it is possible to damage an I/O pin if R1 and R4 are not large enough. This would happen if Q1 were to be turned on while its emitter was held high (5VDC) and the BS2 was outputting a logic low (0VDC). The current that the BS2 is required to sink for the circuit in Figure 4 was only 6mA. This value agreed with a SPICE simulation of the same circuit. In the lab, I reduced the values of R1 and R4 to 1.0K ohm resistors. This increased the current that the BS2 had to sink to about 30mA. If you use this circuit, I would recommend sticking with the values in Figure 4. You should also write your code to minimize the possibility of the BS2 writing to the RPB while your serial data source is sending data.

It is also necessary to give the serial data source (PC) access to the RPB. When the BS2 outputs a logic low (0VDC) at P15 (FMEN), it provides a ground path for the emitter of Q1. This effectively places Q1 in the circuit. When P15 (FMEN) is low, then P14 (FMBS2) should be configured as an input pin. P11 (R_W) and P10 (MODE) are also used to place the RPB in FIFO mode. In this application, the FIFO write operation is used to automatically store data sequentially in RAM with the RPB. Figure 5 shows the proper pin configurations for the RPB MODE and READ/WRITE pins for a FIFO write operation. Tval is the time from executing a FIFO write operation until serial data will be accepted. The maximum time to expect here is 20us.

Code Listing 2 — RPB2_299.BS2 — stores data from a text terminal into the RAM residing on the RAMPack B. This routine waits for the ASCII characters "START" to be received by the BS2 before executing a FIFO write operation. Any text typed into the data terminal after the "START" characters are received will be stored sequentially in RAM. When the ASCII characters "STOP" are received, the BS2 will read the data stored in the RPB and display it via the Debug command. The RPB baud rate is set to 9600 baud just after the "START" is received. Up to 8,192 characters could be stored in RAM using this routine and the SRAM that an RPB is sold with.

I should note a sticky point in this design. The "START" that is received by the BS2 is also

Code Listing 2. RPB2_299.BS2 Storing Serial Data Automatically with the RPB

'RPB2_299.BS2 - Storing Serial Data Automatically with the RPB: This program waits for the characters "START" to be received. Once received the RPB has its internal baud rate reset to 9600 by the WRITE "POINTER" command. This command also has the effect of pointing any subsequent FIFO write operations to address location '0000'hex. Data is then loaded into the RPB while it is in FIFO write mode until the 'BS2 receives the characters "STOP". The READ END OF FIFO command is used to find the last address pointed to by the FIFO write operation. This value is always the same as the number of bytes stored during the FIFO write operation. The last byte of data written during a FIFO write operation will be at one less than the value returned by the READ END OF FIFO command.

Program Variables

Address	VAR	Word	
Addr_lo	VAR	Address.lowbyte	
Addr_hi	VAR	Address.highbyte	
DataByte	VAR	Byte	
End_Addr	VAR	Word	
End_Addr_lo	VAR	End_Addr.lowbyte	
End_Addr_hi	VAR	End_Addr.highbyte	

Pin Assignments

Pin	CON	Value	
FMEN	CON	15	'Enables/disables data from serial data source
FMBS2	CON	14	'From Master pin: sends data/commands to the RPB
TMBS2	CON	12	'To Master pin: receives data from the RPB
R_W	CON	11	'Read/Write pin: selects type of FIFO operation
MODE	CON	10	'Mode pin: enables/disables FIFO mode

Communication Constants

Constant	CON	Value	
Sync	CON	\$55	'Sync byte
B_Read	CON	\$01	'Byte Read command
W_Pointer	CON	\$05	'Write Pointer command
EOF_Pointer	CON	\$07	'Read End of FIFO command
Baud	CON	84	'9600 baud

Initialization of registers

Initialize:	High	Low	Value	
FMEN	High	Low	0	'Disable data from serial data source
MODE	High	Low	0	'Disable FIFO mode
R_W	High	Low	0	'Default to FIFO read
Pause	High	Low	500	'Allow RPB time to power up

debug CR,CR,"Initialized",CR

MainProgram:

'Wait for "START" from serial data source, display message when received

Low	FMEN	'Enable data from serial data source
Serout	FMBS2,Baud,[wait("START")]	
debug	"START Received",CR	
High	FMEN	'Disable data from serial data source

'At this point the RPB has reset itself due to the "START" data and has returned to a default baud rate of 2400. The Write Pointer command is used to reset the address that the FIFO write operation will start at, and reset the RPB baud rate to 9600 for further data.

Address	= 0	'Pointer will be reset to '0000'hex
Serout	FMBS2,Baud,[Sync,W_Pointer,Addr_hi,Addr_lo]	
Input	FMBS2	'Make FMBS2 an input pin
debug	"Resetting FIFO Pointer",CR	
debug	"Entering FIFO Buffer Mode",CR	
Pause	100	

'Enable FIFO write operation and wait for "STOP" to be received

Low	FMEN	'Enable data from serial source
Low	R_W	'Select FIFO write
Low	MODE	'Enable FIFO buffer
Serout	FMBS2,Baud,[wait("STOP")]	
High	MODE	'Disable FIFO buffer after "STOP"
High	R_W	'Default to FIFO read
High	FMEN	'Disable data from serial source
Debug	"STOP received",CR,CR	

'The Read End of FIFO command is used to determine how many bytes of data were stored during the FIFO write operation. This value is used to set up a For...Next loop to read back all of the data and display it using the Debug command.

Serout	FMBS2,Baud,[Sync,EOF_Pointer]	
Serout <td>TMBS2,Baud,[End_Addr_hi,End_Addr_lo]</td> <td></td>	TMBS2,Baud,[End_Addr_hi,End_Addr_lo]	
Debug	"Number of bytes in message = ",Dec End_Addr,CR	
Debug	"Data received after START is... ",CR	
For	Address = 0 to End_Addr-1	'Read data from '0000'hex to (End_Addr - 1)
Serout	FMBS2,Baud,[Sync,B_Read,Addr_hi,Addr_lo]	
Serout	TMBS2,Baud,[DataByte]	
Debug	DataByte	'Display data read

Next	Initialize	'Start over
Goto	Initialize	
END:		

STAMP APPLICATIONS

received by the RPB on its FM pin. Since these characters do not meet the typical command structure that the RPB expects (sync byte, then command byte, etc.), the RPB will execute a system reset. This reset returns the RPB to a default condition which has the baud rate set to 2400. Sending any valid command from the BS2 to the RPB at 9600 baud prior to executing a FIFO write operation resets the internal baud rate of the RPB to 9600 baud.

In RPB2_299.BS2, this is done by resetting the RPB's internal address pointer with the WRITE POINTER command ('05'hex). This command resets the internal address pointer to '0000'hex, as well as setting the RPB baud rate to 9600.

The hassle of dealing with the effects that the "START" characters have on the RPB can be easily removed. The BS2 could simply execute a FIFO write operation, and then wait for the "STOP" characters. In this manner, all received data would be loaded into the RPB. Since this design interfaces to a human typist, through the PC, adding additional Debug routines and commands can be accommodated. The Debug commands used in this routine might cause unnecessary delays and can be removed in designs where timing is critical.

In instances where data is received as one long string — such as from GPS receivers — it is best to execute a FIFO write operation immediately and wait until a particular end-of-string message is received. In this design, the "STOP" constitutes the end-of-string message.

Figure 6 displays a screen capture from an HP-54645D MSO (Mixed Signal Oscilloscope). This image is of a slightly-modified version of RPB2_299.BS2. From it, you can see how the data flows from the serial data

source to the RPB, and then from the RPB to the BS2. I should note that my serial data source was a PC utilizing a common terminal program found on most IBM-style computers available today. The communication parameters that I used were 8N1 serial data, 9600 baud, no-handshaking, and local-echo "on."

In Closing

Most of the difficulty in interfacing the RAMPack B's FIFO mode to the BS2 concern the pin-sharing requirements for TM and FM pins. These difficulties can usually be overcome with a minimum of additional electronic parts. Often times, the BASIC Stamp is expected to operate as kind of a "traffic director" for serial data. In these instances, the RAMPack B can be effectively used to buffer serial data.

Next month, we'll take a look at pin sharing with the TM pin, as well as the FM pin. Sharing both pins allows the BASIC Stamp and RPB to act as traffic director and data buffer in a myriad of configurations. One such configuration will be covered in the March installment. Next month, we'll trap serial data from a PC, and then send the data to the Scott Edwards Electronics G12032 LCD. The same circuitry we used in Figure 4 will be added to, to accommodate the sharing of the TM pin, and to convert from non-inverted serial data to inverted serial data. The end result will be a device that records bit-maps from your PC and can then display these bit-maps to a graphic LCD. **NV**

Lon Glazner is a partner and engineer at Solutions Cubed. Solutions Cubed is an innovative group of design engineers who specialize in embedded control design. They also produce a line of BASIC Stamp compatible products called Miniature Engineering Modules.

Code Listing 1. RPB1_299.BS2 ASCII Loop Program

'RPB1_299.BS2 - ASCII Loop Program: this Basic Stamp2 program writes part of the ASCII character set to the RAMPack B at 4800 baud. It then reads the data back in reverse order at 2400 baud. This data is displayed using the Debug command. Finally, the data is read back at 9600 baud in the order in which it was stored, this data is also displayed via the Debug command.

Program Variables

Address	VAR	Word	'Stores address in RAM to write or read from
Addr_lo	VAR	Address.lowbyte	'Address is broken into bytes for sending to the RPB
Addr_hi	VAR	Address.highbyte	'Address is broken into bytes for sending to the RPB
Baud	VAR	Word	'A word variable is used to store the data rate
DataByte	VAR	Byte	'Used to hold data to be sent or received
A	VAR	Byte	'For...Next variable

Program Constants

FMBS2	CON	14	'From Master pin: sends data/commands to the RPB
TMBS2	CON	12	'To Master pin: receives data from the RPB
B_Write	CON	\$00	'Write command for the RPB
B_Read	CON	\$01	'Byte read command for the RPB

Initialization of registers

Pause	100	'Allow some time for RPB to power up
Address	= 0	'Default address is 0
DataByte	= 33	'Start data at ASCII "I"

Main Program:

'Write data to RPB at 4800 baud

Baud	= 188	'Write data at 4800 baud
For	A = 1 to 58	'Send ASCII "I" through "Z"
Serout	FMBS2,Baud,[\$55,B_Write,Addr_hi,Addr_lo,DataByte]	
Pause	20	'Allow time for WRITE to end
DataByte	= DataByte + 1	'Point to next ASCII character
Address	= Address + 1	'Point to next address
Next		

'Read data from RPB at 2400 baud, reads data in reverse order of how data was written to RAM

Baud	= 396	'Read data at 2400 baud
For	A = 1 to 58	
Address	= Address - 1	'Read starting at last byte written
Serout	FMBS2,Baud,[\$55,B_Read,Addr_hi,Addr_lo]	
Serin	TMBS2,Baud,[DataByte]	
Debug	DataByte, **	'Display byte received
Next		

'Read data from RPB at 9600 baud, reads data in the same order as data was written to RAM

Baud	= 84	'Read data at 9600 baud
Debug	CR,CR	'Place a blank line between data sets
For	A = 1 to 58	
Serout	FMBS2,Baud,[\$55,B_Read,Addr_hi,Addr_lo]	
Serin	TMBS2,Baud,[DataByte]	
Debug	DataByte, **	'Display byte received
Address	= Address + 1	'Read data start at first byte written
Next		

END: 'End of program

Look Ma, No BASIC Stamp*

PicBasic Compiler - \$99.95

Put BASIC Stamp I programs right into a PIC microcontroller - no BS1 module necessary! The programs run faster and can be longer. You also get more variables and extra instructions. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

PicBasic Pro Compiler - \$249.95

PicBasic Pro is BASIC Stamp II compatible, and like the standard compiler above, eliminates the need for a BS2 module. Pro adds built-in LCD support, interrupts in BASIC, arrays, program size to 8K, real If..Then..Else and I/O to any PIC pin. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

*BASIC Stamp is a trademark of Parallax Inc.

EPIC Plus PIC Programmer - \$59.95

Programs PIC12C50x, 67x, 16C55x, 6xx, 7xx, 8x, 9xx. Optional ZIF adapters for DIP, SOIC, MQFP, PLCC. Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

PICProto Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds 5V reg, caps, osc, DB9-25, large proto area. \$8.95 - \$17.95


microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933
(719) 520-5323 (719) 520-1867 fax

<http://www.melabs.com>
email: info@melabs.com

Write in 64 on Reader Service Card.

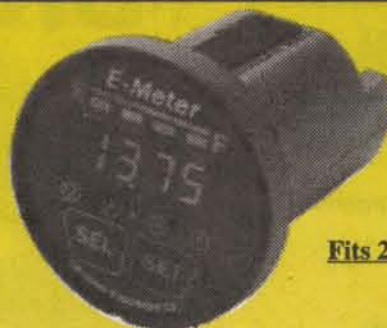Y2K PLANNING? USING BATTERIES? GET AN E-METER™



From \$200

OEM's: Call for free applications assistance.

Fits 2" hole Up to 1000 Amps @500 Volts!

Here's why every Y2K battery bank needs an **E-Meter** - the world's most popular DC energy monitor. The multi-color bar graph shows battery status at a glance. The bright digital display reports Volts, Amps, Amp-hours, Time Remaining, - even Kilowatt-hours. Reports historical information including battery Charge Efficiency, number of discharge cycles, deepest depth of discharge and average depth of discharge. The optional Low Battery contact can optimize your generator run times for charging and RS232 output is available for remote sites.

Don't be afraid of Y2K - be ready with an E-Meter!

Cruising Equipment

5245 Shilshole Ave. NW, Seattle, WA 98107
(206) 782-8100 Fax: (206) 782-4336
<http://www.cruisingequip.com>


Write in 65 on Reader Service Card.

Nuts & Volts Magazine/February 1999 65

AMATEUR ROBOTICS

NOTEBOOK

by Robert Nansel

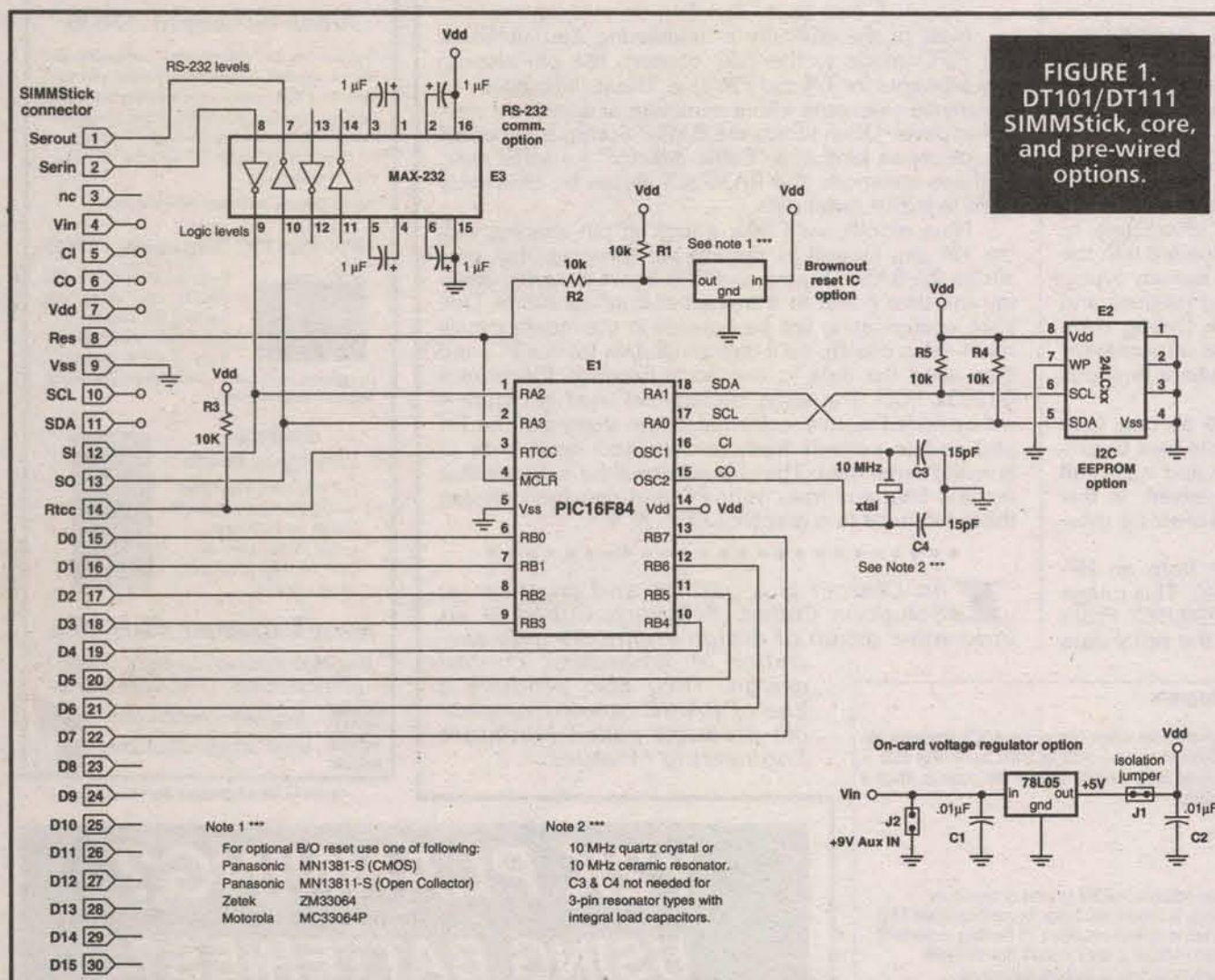


This month, I'm going to start a project a bit different from past Breadbot projects. Over the last seven columns, I've shown three different versions of Breadbot: The first used a Parallax BASIC Stamp 1 (the BS1-IC Breadbot was covered in this column in the June and July '98 issues of *Nuts & Volts*); the second used a BASIC Stamp 2 (the BS2-IC Breadbot was covered in the September '98 column); and the third used a homebrew BS2-IC clone based on the PIC002 SIMMStick PCB (the BS2 SIMMStick project was covered in the October '98 column, and SIMMSticks were covered in the August '98 issue). The common thread for these projects, of course, is that they are all programmed with some variant of PBASIC or another.

The BS-2 SIMMStick project was the most complicated of the three projects in terms of the wiring, soldering, and debugging involved, but with a little VROC methodology, it wasn't difficult to get the thing to work.

If you will recall, VROC stands for Voltage + Reset + Oscillator + Communications — the essentials of getting any embedded microcontroller system to work. I stated then that when all four of these elements are working properly — assuming the software is already debugged — then the embedded microcontroller system will work. Debugged software is always the big "if," but using known-good firmware in the form of a pre-programmed BS2 PIC chip ensured no trouble from that front.

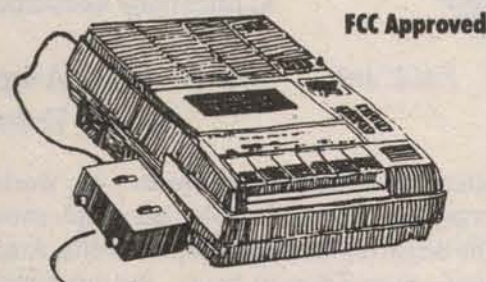TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00
Call 407-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

BIG POWER LOW COST



Dominos are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominos are true plug-and-go control.

Dominos 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5V @ 15 mA

Dominos 2 has:

- everything in Dominos 1 plus
- 16 more bits of high-current parallel I/O
- Hardware clock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**



4 Park St., Vernon, CT 06066
(860) 871-6170

Over the Falls

In this project, however, I won't be starting with the known-good firmware of PBASIC, so beyond getting the VROC details nailed down, there's the issue of bringing up an embedded system with untested software. When you have to debug hardware and software at the same time, the potential complexity isn't doubled, it's squared; software bugs can masquerade as hardware bugs and vice versa, and if you venture out in these waters unprepared, you have paddled out into a swift stream indeed. That thunder you hear up ahead is white water, and you find yourself going over the falls with PIC assembly language as the barrel.

To make the plunge survivable — and even enjoyable — we need to start with the simplest hardware and software combination possible, the bare minimum needed to tell that both hardware and software are functioning as designed.

With PCs, the usual first program you write is the good old "Hello World" program which prints (big surprise) "Hello, World!" to an appropriate text display such as an LCD screen or a laser printer. Breadbot doesn't

have any text device to print to — not yet, anyway — so we'll need some other output device. Among embedded control programmers, the output device of choice for the microcontroller equivalent of "Hello World" is the LED. If you can get a microcontroller to blink an LED on demand, you'll survive going over the falls.

It may sound trivial, merely blinking an LED, but the first time you program any new microcontroller — especially one in a homebrew system — you'll discover how incredibly difficult it can be to get all the I/O, status, and configuration registers properly programmed just to make that LED blink. In effect, you are using the microcontroller as a tool to help build and debug itself. And a blinking LED gives you one very important thing: success. If you can make that LED blink, it means you've got the hardware working — half the battle.

The Hardware

The hardware, in this case, is a PIC16F84 built on a DonTronics DT101 or DT111 PCB (Figure 1). I'm not going to present the detailed assembly instructions for the DT101 as I did for the PIC002 I used in the BS2 SIMMStick project. The DonTronics board has a clear component placement silkscreen (unlike the PIC002), and you can ftp summary instructions for building the DonTronics DT101 from Wirz Electronics at dtp://wirz.com/3rdParty/DT101/dt101.pdf.

For your initial tests, you will need nine components, those marked by

asterisks in the parts list.

First solder in J8, the 30-pin right angle header connector. In addition — although they aren't required — I do recommend soldering in high-quality, machined-pin IC sockets for all the ICs you install. These sockets are more expensive than the regular ones, but they are much more rugged and reliable. For the minimal system, though, all you need is the 18-pin socket for the microcontroller.

If you are using the DonTronics DT001 development board to program your SIMMSticks directly in-circuit, you can dispense with the socket for the MCU, and just solder it in (see my Dec '98 column for more on the DT001). If you are using another programmer, such as the Parallax PIC programmer, you'll need a socket on the SIMMStick so you can plug and unplug the MCU each time you program it.

Even though the PIC16F84 uses flash erasable program memory, and thus can be permanently soldered into the circuit, I don't recommend doing this if this is your first microcontroller project. Few things are more frustrating than frying a brand new MCU, but having to then unsolder and replace it before work can continue — and possibly damage the PCB in the process — is one of them.

After you've familiarized yourself with the characteristics of PICs and SIMMSticks, then it might be a good idea to solder the MCU to the board. It will be a more reliable connection when subjected to the vibration of a moving robot, and it will also be cheaper. If you choose to install the

Go Wireless With Our Modules

SILRX/TXM

SILRX — \$26.00 ea.
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multi-node wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz
AVAILABLE JAN '99

RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a

low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ lemosint@ma.ultranet.com

All products available in either 418 or 433 MHz

Write In 212 on Reader Service Card.

BRIGAR ELECTRONICS

7-9 ALICE ST.

BINGHAMTON, NY 13904

SEND FOR
FREE
CATALOGUE

Open 7:30 To 4:30 PM
Monday thru Friday
Saturday 7:30 AM to Noon

PHONE: (607) 723-3111

FAX: (607) 723-5202

E-MAIL: BRIGAR2@aol.com

Web address: <http://members.aol.com/brigar2/brigar.html>



WELDEX Video camera # WDPK-2000
1/3" CCD Board camera B&W Pinhole lens
compact 30mm x 30 mm (Approx 1"sq.)
High performance & picture quality of a full
featured camera on a compact board.
0.03 Lux min. illumination - RCA connectors
for power & Video connections.
430 lines
resolution.
input.
Brigar
Special
\$85.95



NMB 12 VOLT DC FAN 28 CFM
Model # 3110KL-04V-B17
size: 80mm x 25mm 0.13 Amp
7 blade - Phenolic Blade & housing
DC Brushless - Ball bearing -
12" wire leads - UL & CSA - 25 dba
BRIGAR
PRICE
.... \$4.25



**120 VOLT AC 10 AMP TOROID
ISOLATION TRANSFORMER**
Mfg: BANNER MAGNETICS # 159257
INPUT: 120VAC (Blk, Gry)
Output: 70v 12 amp (Red, Red)
120vac 10amp (Violet, White)
12 V 1amp (Brown, Brown)
Size:
3-1/2"H x 5"Dia.
Weight: 12 lbs.
PRICE...
\$59.95



AC TO DC WALL TRANSFORMER
MFG: AUDIOVOX PART# CNR405
INPUT: 120VAC 60Hz 11W
Output: 12 VDC 300mA
Polarity: Center pos. with 6'
zip cord 2.5 mm Female
receptacle. UL & CSA
SALE PRICE \$1.50



40 PIN
CPU 8 BIT 256
BYTES RAM,
Timer/counter and
I/O PRICE... \$1.75

INTEL # P8052AH



ROTARY VANE AIR COMPRESSOR
GAST Model# 0522-P167-G451DX
Oil-less rotary vane air compressor directly
connected to motor. Compressor rated at
3.2 to 4 Cfm @ 10 psig max.
Motor rating:
3/4 H.P. 60 Hz 115 Vac 1 PH 1725 RPM
Code H - 7.40 A - SF 1.00 - FR 56 Cz Amb 50 c
Time Rating: Cont. Insul Class B - Thermally Prot.
Motor Size: 14"L X 6-1/2"Dia. Weight: 40 Lbs.
Shaft Size: 2-1/8"L x 5/8"dia. (Flated)
BRAND NEW FACTORY BOXED \$119.95



LCD DISPLAY ASSEMBLY #HG416
4 DIGIT 16 Segment display (the lcd
contains 126 segments - some of the
segments are fixed with words such
as play, scan, loud, rdm, pgm etc...)
9 vdc - white back light with orange
characters. Smart display with SMD
components.
DISPLAYS COMES COMPLETE
WITH 3.5" DISKETTE. FILES
CONTAIN 68HC11 PROGRAM,
LIST OF COMMANDS AND
SCHEMATICS



PRICE
\$3.95

**POWER PRODUCTS
PART # HE381**
Linear power supply module.
Size: 2-1/4"W x 4-3/4"L x 1-1/2"D
Input: 115vac 50/60hz 271 ma.
Output: 5vdc 5000ma.
Price... \$19.95 ea.



ULTRASONIC LIGHT SWITCH MFG: LITRONIC
Replaces existing wall switch - Great for home alarm
systems or controlling lights & small appliances, ON-
OFF Switch-LED TRIP Indicator COLOR: WHITE
SIZE: 5"W x 5"H x 1-3/8"D
● VOLTAGE 120 OR 277VAC 50/60HZ
● MIN LOAD 80 WATT 120V
● MAX LOAD 1000W 120V
Sensor Low Power Ultrasonic 25KHZ
● ADJUSTMENT: Sensitivity &
Time out (0 TO 25 MINUTES)
● Documentation & schematic
Included. Energy Savings
30 TO 60%
ORIGINAL PRICE \$100.00
SPECIAL SALE PRICE
\$6.95

SALE




MOTION SENSING
AUTOMATIC SWITCH

Write In 213 on Reader Service Card.

Nuts & Volts Magazine/February 1999 67

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

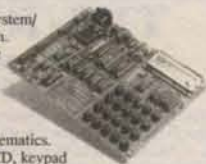with the AES learning system/
embedded control system.
Extensive manuals guide
you through your
development project.
All programming
and hardware details
explained. Complete schematics.
Learn to program the LCD, keypad
digital, analog, and serial I/O. for
your applications.



THREE MODELS AVAILABLE.
Choose from an Intel 8051,
Intel 8088, or Motorola 68HC11
based system.
All models come with:

- 32K Byte ROM, 32K Byte RAM - 2 by 16 Liquid Crystal Display - 4 by 5 Keypad - Digital, Analog, and Serial I/O - Interrupts, timers, chip-selects - 26 pin expansion connector - Built-in Logic Probe - Power Supply (can also be battery operated) - Powerful ROM MONITOR to help you program - Connects to your PC for programming or data logging (cable included) - Assembly, BASIC, and C programming (varies with model) - Program disks with Cross Assembler and many, well documented, program examples - User's Manuals: cover all details (over 500 pages) - Completely assembled and ready to use - Source code for all drivers and MONITOR - Optional Text Book.

Everything you need. From \$279

Money Back Guarantee

Call for Free Info Pack, or see

WEB at <http://www.aesmicro.com>

714-550-8094, FAX 714-550-9941


Call 1-800-730-3232

AES
Advanced Educational Systems

AES 575 ANTON BLVD., SUITE 300, COSTA MESA, CA 92626, USA

FIGURE 2.
SIMMStick test
circuit.

DT101/DT111 SIMMStick

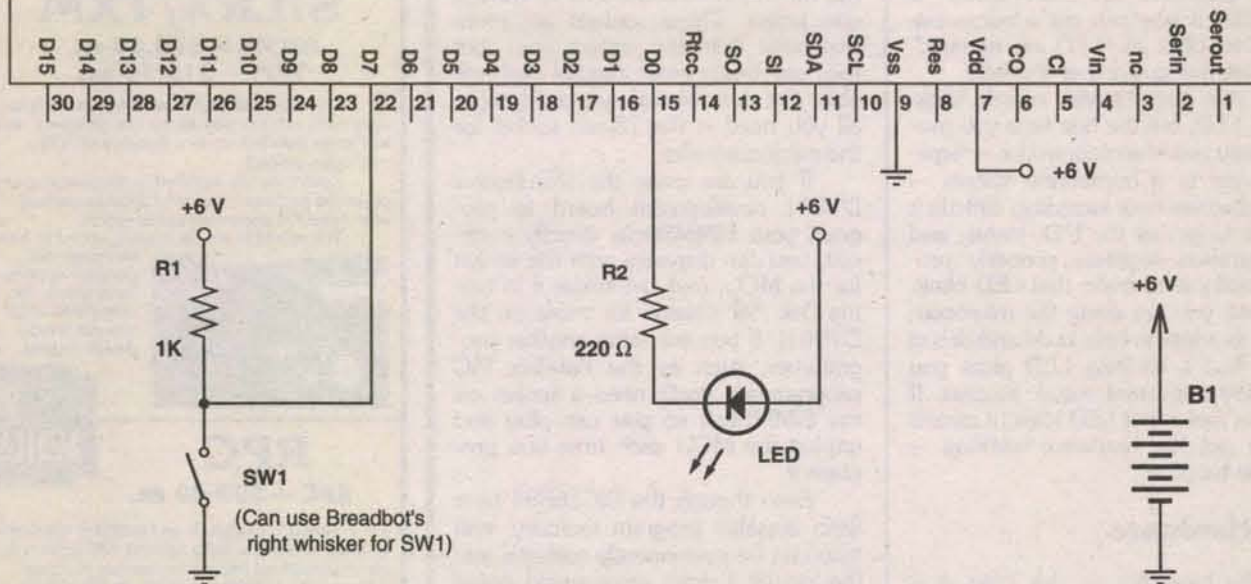

RS-232 communications option, you should at least use a socket for the MAX-232 because it's pretty easy to accidentally zap it when you're working out serial cable problems.

Power Supply

You can power this circuit either directly at Vdd (pin 7 of the SS-Bus) from Breadbot's six-volt battery pack, or at Vin (pin 4 of the SS-Bus) from a nine-volt battery. For the latter, you'll need to install the on-card voltage reg-

ulator option.

To install this option, you'll need C1, C2, J1, and VR1. The +5V regulator VR1 isn't labeled on the DT101 silkscreen (not enough room), but it goes between C7 and J1 with the flat of the TO-92 package facing J1. If you are installing this option, after you solder in VR1, I recommend that you cut the trace on the solder side of the board that shorts the pads of J1 together, solder in the J1 header, and place a shorting jumper between its pins.

The reason for this is that the DT001 programmer automatically switches SS-Bus pin 7 between its own +5V Vdd and +13V Vpp supplies during programming, so if you have VR1 installed on the DT101, its output must be temporarily isolated from the programmer during programming. Otherwise, VR1's +5V will fight against Vpp's +13V, and the result may be curls of blue smoke from one


or both voltage regulators.

At the very least, the programmer won't be able to burn the program into the PIC. A sign that the SIMMStick's Vdd supply isn't isolated from the DT001 programmer's Vdd is that the DT001's Vdd indicator LED will be lit when you plug the SIMMStick in the programming slot and switch the Run/Load switch to the "Load" position; when you switch to "Run," the Vdd LED will go out. I'll talk more about using the DT001 later.

If you are using a separate PIC chip programmer, then install the J1 isolation jumper option if you want, though it's only really necessary in this case if it's possible you will ever apply voltages to both Vin (SS-Bus pin 4) and Vdd (SS-Bus pin 7) simultaneously. As with the BASIC Stamps, use one or the other, but not both.

Next, solder in C1 and C2. With the SIMMStick oriented component side up and the SS-Bus connector fac-

RF Data Modules

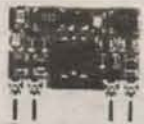

AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current: 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10



AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery. CMOS
- Low current. 2.4mA typical
- 2kHz data rate. CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95



FM TRANSCEIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCEIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to ± 15 kV
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair. (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

Transceiver..... \$247.90
Transmitter..... \$ 87.15
Receiver..... \$105.52



ABACOM
TECHNOLOGIES



Tel: (416)236-3858
Fax: (416)236-8866
www.abacom-tech.com
abacomech@compuserve.com

title "test1 - Poll a Bit"

Constantly polls input bit for switch closure, indicates result with LED

LIST P=16F84, F=INHX8M, R=DEC
errorlevel 0,-305
INCLUDE "pic\mpasm\16F84.inc"

; Registers

_CONFIG _CP_OFF & _WDT_OFF & _HS_OSC & _PWRTE_ON

PAGE

org 0

bsf STATUS, RP0
bcf TRISB & 0x07F, 0; Set RB0 to Output
bcf STATUS, RP0

wait_ON

btfsc PORTB,7 ; Wait for switch press
goto wait_ON

bcf PORTB,0 ; Turn LED ON

wait_OFF

btfss PORTB,7 ;
goto wait_OFF ; Wait for switch release

bsf PORTB,0 ; Turn LED OFF

goto wait_ON

end

Questions & Answers


TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

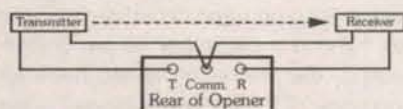QUESTIONS

I would like to hook-up a circuit that is similar to the beam-breaking safety part of my garage door opener. It is a Chamberlain unit.

I want to use this system in conjunction with a burglar alarm system. There is no schematic with the opener. Refer to the following schematic for wiring information.



Can someone supply a simple circuit that I can try? What kind of sender unit and optical detector is required?

2991 Roger W. Hamel
Cedarville, MI

In most projects that use crystals, they never specify series or parallel. What is the difference between series and parallel crystals? Are they interchangeable?

For example, a 20 pF capacitance of the parallel crystal, is this internal or external and is this a set value or minimum or maximum?

The capacitance in most projects vary from 10 to 30 pF, is this for series or parallel and how do you calculate the value?

2992 Marvin Saij
Ontario, Canada

Is there a simple circuit modification to add to a triac light control to provide "soft-on" function to increase bulb life? Is it known what the bulb makers believe is possible here? I wonder if the relatively new axial disposed filaments are more prone to failure from mechanical shock?

2993 John Connell
San Francisco, CA

Are ZN416 (preferred) or ZN414 available somewhere? These are simple AM radio receiver ICs. I would like to purchase some, but haven't been able to locate any of either type.

2994 David Rowe
Sacramento, CA

I would like to have the pinout for an Analog Device AD2038 temperature meter. It was described in the

Send all material to **Nuts & Volts Magazine**, 430 Princeland Court, Corona, CA 91719, OR fax to (909) 371-3052, OR E-Mail to forum@nutsvolts.com

1987 short-form selection guide.

Through experimentation, I have resolved many of the interconnect requirements, but not all. A pinout would be helpful.

2995 Kenneth Keck
via Internet

I am looking for a circuit that I can use to calculate the time between two vehicles in motion.

Vehicle 1 will have the circuit installed, and needs to calculate how far behind (in seconds) vehicle 2 is following.

2996 Mike Ciotti
via Internet

I have a gasoline 120V AC 8KW generator that I use at job sites. The thing just rip-roads whether I have a power tool plugged into it or not.

Can anyone direct me to a circuit that can do load sensing to see if a load is on-line, which would then run a servo motor, or solenoid to open the throttle on the engine, and when the load is removed to idle it back down?

It does have a 12V battery to provide sensing voltage.

2997 John Jones II
via Internet

Is there an antenna for short-wave radio? Where can I find it or them?

2998 Nelson Ortega
Tampa, FL

I have a project underway that uses two separate inexpensive Elenco sine/squarewave generators.

On these, the frequency output is controlled by a simple potentiometer. I need to be able to control these pots using a computer/Visual Basic 6. Does anyone know how I can accomplish this? I wish to use a mouse, where pressing the left mouse button assumes control of generator 1, allowing mouse movement to control frequency. Pressing the right button would adjust generator 2.

Also, once frequency 1 is set, I would like things set up so that pressing the right button would start up the second generator at the same frequency as generator 1. I am sure all this could be done in software, perhaps directly controlling a Sound

Blaster card, but currently I am trying to control those pots via RS-232.

2999 Tom Moore
via Internet

I am looking for a circuit that will interface with the data port of a number of automobile on-board computers.

My immediate need is for a 96 Jeep Cherokee. Once I get to talk to the computer, I would need to figure out what I'm seeing. Possibly using a BASIC Stamp and or a laptop to help decode the information?

Trying to troubleshoot a newer vehicle now is much harder than it was back before the days of the on-board computers.

29910 Joe Reed
Charlotte, NC

I am looking for a device that would protect equipment from voltage sags during brownouts and from power going on and off quickly as often happens during blackouts.

This device would pass power from the AC mains to the load device(s) as long as the AC supply remains inside an acceptable range of voltages (from 100 to 130 VAC). But, if voltages drops (or goes too high), then it disconnects the devices from the mains (both sides, hot and neutral) and keeps them disconnected until the voltages on the mains have returned to normal values and have stayed there continuously for at least 100 seconds.

The device must be able to support inductive and non-inductive loads of up to 15 amps. The device could be completely prepared for consumers (like a power strip is) or could be a component that requires the addition of power plugs and sockets.

29911 Nelson Bolyard
via Internet

I have a DBS receiver that is capable of controlling a VCR via an IR emitter.

Due to my shelf arrangement and room conditions, the DBS receiver does not reliably control the VCR.

I would like to build a simple 'repeater' circuit in which an IR sensor placed in front of the emitter of the DBS receiver would transmit, via

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

a short cable, to an IR emitter placed in front of the VCR's IR receiver.

I am sure there are some inexpensive IR modules available from distributors that might do the job easily, but I am not very familiar with them.

29912 Lee Roth
Columbus, OH

I am looking for a device for a telephone line that has the Caller Line ID (CLID) feature.

One side of this device would hook to the telco line, the other side

ANSWER TO #1996 - JAN. 1999

What you are describing is a frequency detector. It should be fairly simple to construct using a couple of LM567 tone decoders.

Referring to Figure A, U4 is set up to detect an input frequency of 60 Hz and with a little logic, turn on D2. When the input frequency is less than 60 Hz, D1 is on and D2 is off. When the input frequency is greater than 60 Hz, U5 turns on D3 and disables oper-

ation of D1 and D2 through the nand gates U2A and U2C.

To set up U4, monitor the center frequency of the decoder on pin 6 with a scope or frequency counter and adjust R4 for an output of 60 Hz. Likewise, to set up U5, monitor the center frequency of the decoder on pin 6, adjust R6 for an output of 62 Hz. See Figure A for circuit details.

Kevin Goodwin
Oceanside, CA

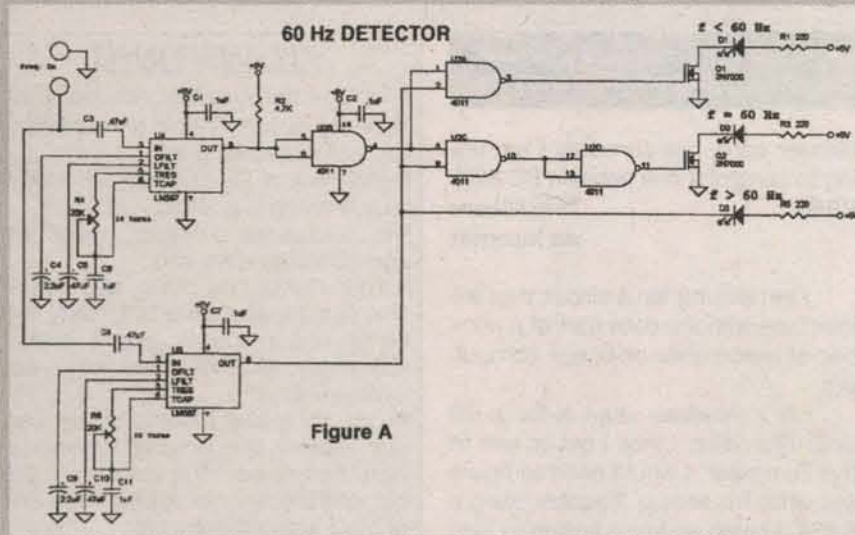


Figure A

would be connected to the phone(s).

The device would prevent the phones from ringing unless and until CLID information containing a number was supplied by the telco. The device would not ring the phone for incoming calls that have no CLID information, nor for calls whose CLID info indicates P (private) or O (Out of area), or any other non-numeric info for the phone number.

The phones that connect to this device must still be able to get dial tone and/or answer calls merely by

lifting the receiver, and the telco line features that require flashing the hook (e.g., call waiting, three-way calling) must continue to work with those phones.

29913

Nelson Bolyard
via Internet

ANSWERS

ANSWERS TO #19917 - JAN. 1999

You can solve this problem by getting a device known as the

"ymouse" manufactured by P. I. Engineering, 2296 Williamston Rd., Williamston, MI at 1-800-628-3185 or 517-655-5523.

This adapter will handle either two mice or one mouse and a touchpad device, or one mouse and a trackball, and connects to the computer's serial DB9 port.

They also manufacture adapters for PS2, keyboards, and laptops.

The website can be found at <http://www.ymouse.com>

Arthur Hazboun
Harbor City, CA

ANSWERS TO #19917 - JAN. 1999

You may want to consider purchasing a Y-splitter which would allow two pointing devices to be used simultaneously by your PC.

A mail order business called Cyberguys sells these Y-splitters for both serial and PS/2 pointing devices. They are advertised to work with standard mice, trackballs, and other pointing devices such as touchpads. The catalog number is 104-0520, and they are priced at \$45.95 each. Check them out on the web at www.cybererguys.com or by voice at 1-800-892-1010.

John McMichael
Laramie, WY

ANSWER TO #1998 - JAN. 1999

It sounds to me like a case of AGC overload with resultant cross-channel modulation. That's a fancy way of saying those two channels are way too strong for your TV set, and your high-gain antenna is not helping one bit.

If the antenna has a pre-amplifier in it, that will just make things worse.

Here's a simple test: instead of your big antenna, connect a halo loop or maybe just a couple of paper clips to the antenna terminals of your TV set. The picture may look weaker, but the bars should go away.

Once you have determined that too much signal level is the problem, then you can address how to reduce the signal on those two channels while still receiving other stations in the area.

Tuning stubs used as notch filters would be one approach. Turning off the pre-amplifier (if there is one) might do the trick, or pointing the antenna in some other direction, such as 90 or 180 degrees off-course.

Harry Boling
Garland, TX

ANSWERS TO #1999 - JAN. 1999

You want a set of cascaded timers. This should be easy using 555 ICs. Connect pin 2 (trigger, active low) on each timer via resistor to +V and a capacitor to pin 3 (output) on the preceding timer. The trailing edge of the output pulse will spike the trigger low starting the next timer.

To start the timers properly, you should probably set up a momentary switch to all the resets (pin 4, active low), and a momentary switch to pin 2 of the start timer.

Peter Hanely
via Internet

ANSWERS TO #1999 - JAN. 1999

CEBEK recently released a three-timer circuit designed to simulate the operation of a traffic light. Time settings are adjustable from 4 to 50 seconds for the "Red" and "Green" outputs. The "Yellow" output is automatically set to 1/4 of the time setting.

This circuit operates at 12V DC and can switch up to 2A. This will easily control relays to operate the light at 120 VAC.

Best of all, the price of this board level unit is under \$20.00 available from MCM Electronics, 1-800-543-4330. Order number is 28-6215.

Alex McIlwain
Lakeland, FL


ANSWERS TO #1999 - JAN. 1999

Rather than using discrete components to generate timing signals for the traffic light, have you considered using a PIC microcontroller from Microchip Electronics?

A PIC 12C508, for example, has six I/O pins and sells for under \$2.00 in single quantities. It also has its own clock which runs at 4 MHz and should be accurate enough for your application.

If you don't mind setting the delay values in software, you should literally need no external components to get the timing signals, since three of the six I/O pins could be pro-

The Pocket Programmer

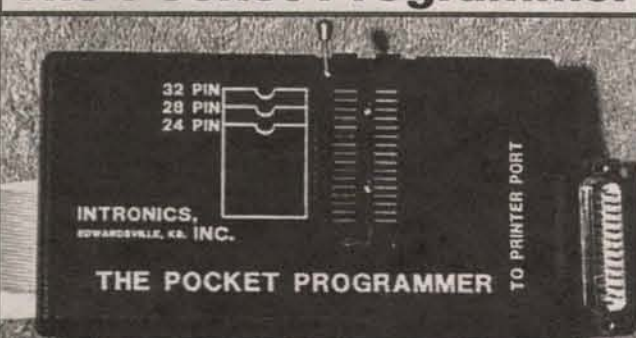

The portable programmer that uses the printer port of your PC instead of a internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.

Only \$129.95

Same Name, Address & Phone Number for 16 Years....
Now isn't that Amazing ?

Intronics, Inc.

Box 13723 / 612 Newton St.

Edwardsville, KS 66113

Tel. (913) 422-2094

Add \$5.00 COD

Add \$4.00 Shipping

Fax (913) 441-1623 Visa / Master Charge / Amex



CABLE CONVERTERS

Our converters are designed for your specific needs.

- **Volume Control**, 135 Ch, Ch-3/4, AFT/MFT, P/G Lock, HRC/STD and Sleep Timer
- **85 Ch Plain Converter** Ch-3, AFT, PG Lock, HRC/STD and Sleep Timer

UNBEATABLE PRICES

FREE BROCHURE

CALL (310) 515-5085

PCW CO

Fax (310) 538-3636

ANSWERS TO #19915 - JAN. 19915

You can make a dual channel oscilloscope act like a Huntron Tracker (characteristic curve tracer) by using an external sinewave generator and a resistor. The signal generator (or scope) must have a floating common.

Channel-A of the scope measures the voltage across the component under test, Channel-B measures the current.

Set the scope time scale to X vs. Y (or A vs. B). Apply a 5Vpk (10Vpp) 1KHz sinewave to the component under test in series with a 1,000 ohm resistor. Connect the scope's CHA-COM and CHB-COM to the junction of the component under test and the resistor.

Connect CH-A to the junction of the signal generator output and the component under test, connect CH-B to the junction of the signal generator and the resistor.

Be aware that some tiny diodes have very low I_{max} . The above circuit will put up to 5mA through your component. Lower the signal voltage or increase the resistance appropriately.

Use a relay or toggle switch to place other components into this circuit automatically for comparison of "good" vs "bad" components.

Anthony Tekatch
Ontario, Canada

ANSWERS TO #19915 - JAN. 1999

We have a .pdf file on our web site that shows a curve tracer that may be added to most oscilloscopes like the one requested by the reader, Joe Farley. <http://www.wenzel.com/pdf/curve.pdf> (A copy is reprinted here, to the right.)

The simple version may be all that you need, but the multi-voltage design has enough voltage and power to look at the behavior of power devices and enough sensitivity to non-destructively characterize delicate components. Just make sure the switch settings are right.


I also like the built-in diode for single-polarity testing when high-reverse voltage can cause damage.

Charles Wenzel
Austin, TX

grammed to provide the timing signals for the lights.

If you are new to programming PICs, check out the Microchip web site at www.microchip.com and invest some time in learning. If you do a lot of work with electronic circuit design, the time you are able to save on projects like this should more than make up for the time you invest in

V/I Curve Tracer

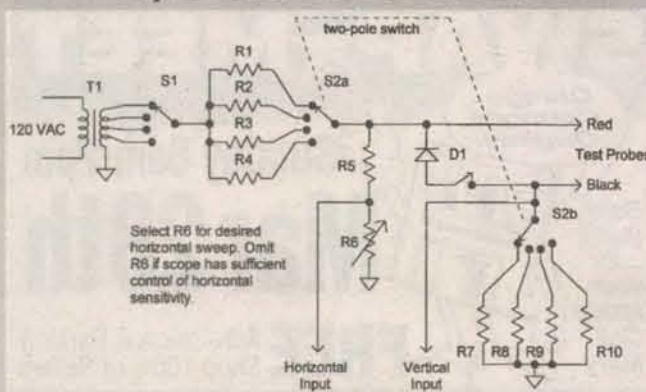

The V/I Curve Tracer is an indispensable tool for troubleshooting circuits and testing components. The circuit traces the current versus voltage curve for the component under test on an ordinary oscilloscope. The peak-to-peak test voltage is adjusted by selecting different taps on a power transformer and the test current is limited by a selected series resistor. The voltage and current ranges are not critical and a single voltage version built with no switches will prove quite useful. The "deluxe" version shown in the schematic provides four test voltages with current ranges from a few hundred microamps to a few hundred milliamperes. An optional diode is included in the output to limit the voltage swing to a single polarity to prevent reverse breakdown when checking delicate devices.

T1: Unless you plan to test high-power devices, T1 may be a small power transformer with a few different secondary voltages. The prototype depicted in the schematic has four secondary taps but a center-tapped 24VAC transformer will give two useful test voltages of about 17 and 33 volts peak. Avoid voltages much above 24VAC to reduce risk of shock.

S1: A single-pole switch with enough positions to accommodate the desired number of test voltages.

S2: A two-pole switch with enough positions to accommodate the desired number of test current ranges. Note that the switch selects resistor pairs: R1 & R7, R2 & R8, R3 & R9, R4 & R10.

R1 - R4: These resistors limit the test current. R1 could be a 100 ohm, 10 watt resistor for a high power range capable of testing incandescent lamps (and quickly zapping semiconductors!). R1 works with the current sensing resistor R7. The current sensing resistors should be

about 1000 times smaller than the series resistors so R7 should be 0.1 ohms if R1 is 100 ohms. The power dissipated in the current sensing resistors will be small so any style may be used.

Try R2 = 1000 ohms, R3 = 10,000, and R4 = 100,000 ohms.



Following the 1/1000 guideline gives R8 = 1 ohm, R9 = 10 ohms, R10 = 100 ohms. Note that these current sense values give four ranges from 100mA to 100uA with about 10 mV per vertical division for the oscilloscope. If the oscilloscope does not have a vertical sensitivity of 10 mV per division, the current sense resistors (R7 - R10) may be increased.

D1: A silicon diode capable of handling the highest test current and voltage. A 1N4002 should work well for most applications. When the diode is in the circuit, it will limit the negative swing to under -1 volt.

Here is a simple version with a single voltage range of about 18 volts peak and a current limit of about 18



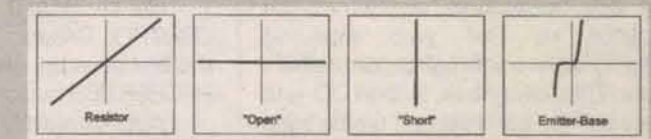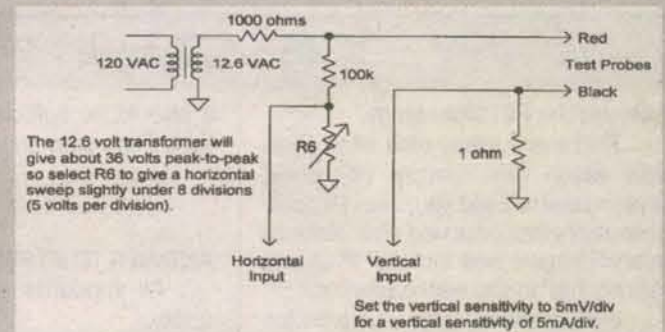milliamperes peak. The transformer is an ordinary "filament" transformer or similar with a single secondary. This one-range tracer is quite useful for quick checking of zeners, transistor junctions, LEDs, and most other semiconductors.



COMPUTER PARTS

www.lapazusa.com

MEMORY UPGRADES

1Mx9-70 SIMM	\$10
4Mx9-70 SIMM	\$19
1Mx32/36-70 72-pin SIMM (4MB)	\$10/15
2Mx32/36-70 72-pin SIMM (8MB)	\$19/25
4Mx32/36-70 72-pin SIMM (16MB)	\$39/44
8Mx32/36-70 72-pin SIMM (32MB)	\$65/72
64Mx64 EDO/PC 100 DIMM	\$89/95

VIDEO

1MB KIT (2-256x16) 2CAS SOJ/ZIP...	\$18/35
1MB KIT (2-256x16) 2WE SOJ/ZIP...	\$19/36

CACHE

64Kx1-15ns 22-DIP	\$5.50
32Kx8-25/20/15ns 28-DIP	\$3/2/2.50
64Kx8-15ns 32-DIP	\$6
128Kx8-15/20ns 32-DIP narrow	\$12 & up
128Kx8-15/20/25ns 32-DIP wide	\$12 & up

CPU

INTEL 486DX2-66 (5v) CPU	\$30
INTEL 486DX4-100 (5v) CPU	\$69
INTEL PENTIUM 83Mhz OVERDRIVE	\$85
INTEL PENTIUM 133/166 CPU	\$65/79

MISC.

LBA CARD: Upgrade your hard drive beyond 540MB without the expense of a new Bios. \$29.95

486DX4 KIT: Upgrade your old 5V 486 CPU with this kit. AMD DX4-100 CPU+5v Adaptor+CPU Fan. \$65.00

MMX ADAPTOR: Allows 3v Pentium boards to accept MMX CPU. Adaptor for Intel or Cyrex CPU. \$30.00

PENTIUM MOTHERBOARD/SYSTEMS SPECIALS
Pentium M/B 133Mhz Intel, 512K, 32MB RAM. \$195.00

Pentium II - Intel Celeron 300A, ATX M/B, 1.44 FDD, 2GB HD, 8MB Video, 56K Fax Modem, 36X CD ROM, Mid tower ATX case. Best value! \$595.00
1-YEAR WARRANTY ON PARTS & LABOR

PACKARD BELL

486 to Pentium motherboards

PRICES SUBJECT TO CHANGE WITHOUT NOTICE - TERMS: COD, VISA/MC - MINIMUM ORDER \$20 - SHIPPING & HANDLING: \$7 MIN.
ORDER LINE: (800) 586-4199

LA PAZ ELECTRONICS INT'L
P.O. BOX 261095, San Diego CA 92196
TEL (619) 586-7610 FAX (619) 586-1482
e-mail: lapazusa@pobox.com

TONER CARTRIDGE RECHARGE

& Laser Printer Supplies

CALL NOW FOR YOUR FREE CATALOG #13!



Instruction Manual Free with starter kit
Video Training Tapes choose from our library
Catalog #13 100 pages FREE!
Marketing Flyers with customized pricing
Printer/Copier/Fax Cross Reference 68 pgs-Free with any order

■ Black, Color & MICR Toners
■ Tools and Accessories
■ Technical Support
■ Cartridge Parts
■ Video Training Tapes
■ OPC Drums and Belts
■ InkJet Refill Supplies
■ Graphic Black Toner Kits
■ MICR Toner Kits

Fast, Same Day Shipping
Mail-in Cartridge Service
Export Orders
Monthly Sales Specials
Marketing Flyers

Visit our website at
www.chenesko.com

for all the free tech documents, Sales Specials and the latest industry news!



Chenesko Products Inc.
2221 Fifth Ave., Suite 4,
Bronx, NY 10457
Tel: 516-467-3223
E-Mail: chenesko@aol.com
<http://www.chenesko.com>

800-221-3516

When Visiting Disney World And Sea World...
Come To The World Of Electronic Surplus!

SKYCRAFT

PARTS & SURPLUS, INC.
ORLANDO, FLORIDA



Located At The Intersection Of I-4
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial
And Government Electronic Surplus Including:

- ★ WIRE
- ★ SWITCHES
- ★ RESISTORS
- ★ TRANSISTORS
- ★ TRANSFORMERS
- ★ TEST EQUIPMENT
- ★ NI-CAD BATTERIES
- ★ COAX
- ★ RELAYS
- ★ HARDWARE
- ★ CAPACITORS
- ★ PANEL METERS
- ★ CIRCUIT BOARDS
- ★ INTEGRATED CIRCUITS

HOURS:

Monday - Friday 8:30-6:00
Saturday 8:30-5:00

★★★★★★★★

We Buy Surplus
Electronic Parts —
FAX your list.

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186



ACP's 90th GIANT COMPUTER SWAP★MEET

Orange
County's
Original!

Be a
Seller
...for
your
space
Call
Mary



All Day
Sunday 8am-2pm

Mar 28th

FREE Admission & Parking
Shop 100's of Sellers

in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.

ACP SUPER★STORE

Since 1976

1310 E. Edinger
Santa Ana, CA
714-558-8813



call waiting) in the box, if it does,
delete ONLY the *70 click ok and
close the other windows. That should
fix your problem.

If this does not fix it, you should
check that you do not have your calls
automatically forwarded when the
number is busy.

Gregg Berkholtz
Portland, OR

ANSWER TO #1992 - JAN. 1999

You are probably suffering from
two separate problems, but both of
them are related to the current the
motors draw.

First, your power supply probably
cannot provide enough current when
the motors are first turned on.
Although the motors may say they
are 5 amperes, the current the
motors draw when they are first
turned on could be much higher. If it
is high enough, then the supply volt-
age may dip low enough that the
microcontroller gets upset. The
motor supplies and the logic supplies
should be separate, you don't want
the dip on the motor supply to affect
the microcontroller.

If you must use one supply, then
connect the motor to the supply
directly, but use a series diode to
connect the positive supply to the
microcontroller. If the motor supply
dips, then the diode will reverse bias
and prevent the motor from pulling
down the microcontroller supply.

The microcontroller power sup-
ply (not the motor) should have some
large capacitors so it can coast
through the dip in the motor supply.
Use a scope to look at the power sup-
ply.

Second, you probably have a
wicked ground loop. You must
arrange your ground wires so none
of the motor current flows through
any of the microcontroller ground
connections. The microcontroller
ground connections include the
grounds used for the power devices
that turn the motors on and off.

You may need transformer or
optoelectronic coupling. The general-
ized notion is called single point
grounding.

Here's what happens: Say the
motor current does flow through the
microcontroller ground. Say the
resistance of the ground connection
is 0.1 ohms. If the motor startup cur-
rent is 20 amperes, then the voltage
drop across the ground connection
is 2 volts — more than enough to
change a logic state from false to
true.

You may also want to add some
capacitors, diodes, and resistors
across the motor, but these compo-
nents are usually added to reduce
the stress on the power switching
components or to reduce RFI.

Gerald Roylance
Mountain View, CA

ANSWER TO #1991 - JAN. 1999

There are several PLL ICs that
can be used for a 100-1000 MHz
synthesizer.

TECH FORUM

learning the PIC technology.

There are many web sites avail-
able which give sample PIC code,
explain how to build your own PIC pro-
grammer, etc. Just use your favorite
search engine and include "PIC" and
"Microchip" in the search terms.

If you want to simply buy a device
for this application, check out the
"Lights to Go" web site at
<http://www.trafficlights.com/e5ad.htm>. This describes a \$44.00 unit
they sell for controlling a traffic light.

It should be sufficient to control the
light if you plan on using it indoors.

Mark Winters
Orem, UT

ANSWER TO #1993 - JAN. 1999

All modems should have that
ability.

Go to START — SETTINGS —
CONTROL PANEL — MODEM. When
the box pops up, choose the DIALING
PROPERTIES button.

Approximately 2/3 down the

newly displayed window is a check
box for "Call Waiting" make sure it is
not checked. If it is not, go to START
— PROGRAMS — ACCESSORIES —
DIAL-UP NETWORKING. Highlight the
"Entry Name" or "Connection Name"
you connect to.

Now choose FILE — PROPER-
TIES.

In the windows that pops up, ver-
ify that the "Telephone Number" box
does not have a *70 (or whatever
your phone company uses to disable

ELECTRONIX EXPRESS

WELLER SOLDERING STATION — MODEL WLC 100

- Variable power control (5 to 40 watts)
- Replaceable heating element
- Quality light-weight pencil iron

\$3695



DUAL-TRACE OSCILLOSCOPE

W/HIGH RESOLUTION, BLUE CRT
INCLUDES PROBES, POWER CORD
2 YEAR WARRANTY
Goldstar 5020
20MHZ \$349.00



SCOPE PROBE 60 MHZ

SWITCHABLE X1, X10 \$1295

DIGITAL MULTIMETER

WITH CAP/FREQUENCY
TRANSISTOR TESTER
Model DM645 \$3495



PAD-234

DIGITAL/ANALOG TRAINER

Complete
portable
workstation.
Variable and
fixed power
supplies, function generator,
digital I/O, rugged design,
high impact case.

Assembled \$150.00 Kit \$110.00



HIGH QUALITY TOOLS

With Cushion Grips and Return Spring

Needle Nose Pliers \$295

Wire Stripper \$150

Diagonal Cutter \$295

ON-ON

POWER SUPPLIES

0-30 VDC, 0-3 Amp. Built-in current
limiting, overload protected, constant
voltage and current operation.

01PSGP4303A Analog Display \$165.00

01PSGP4303D Digital Display 189.00

SOLDERLESS BREADBOARD

830 tie points. MB102PLT
model features 3 binding posts
and aluminum backplate.

Part No. 1-9 10+

MB102 5.95 5.00

MB102PLT 8.95 8.00

HELPING \$350

HAND

WITH

MAGNIFIER

#060836

\$395

MOTION DETECTOR

\$2 ea. — 10 For \$15

LM555 10 Min. 22¢ ea.

LM741 10 Min. 27¢ ea.

74LS00 10 Min. 18¢ ea.

7805 Regulator 10 Min. 30¢ ea.

2N3904 10 Min. 6¢ ea.

PN2222 10 Min. 6¢ ea.

Red LED T 1 1/4 10 Min. 6¢ ea.

Green LED T 1 1/4 10 Min. 7¢ ea.

Yellow LED T 1 1/4 10 Min. 8¢ ea.

Photo Cell 10 Min. 65¢ ea.

100K Pot., 1" Shaft PC ML 10 Min. 15¢ ea.

SOLDERING IRON 3-WIRE

HIGH PERFORMANCE \$525

#060501

SOLDERING IRON STAND

W/SPONGE \$350

#060842

1 LB. 60/40 Solder Roll .031" \$595

DESOLDER PUMP W/TIP \$350

#060820

15 TURN POT 69¢ ea.

7 SEG. DISPLAY 60¢ ea.

Bourns 3006P series. All standard values available.

MAN72 C.A Red 0.3"

MAN74 C.C Red 0.3"

FREE CATALOG

MORE

Low-Priced

Items In Our

FREE

216-Page Catalog

Electronix Express

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

216-Page Catalog

TERMS: Min. \$20 + shipping. School Purchase Orders, VISA/ MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020
FAX: 732-381-1572

365 Blair Road • Avenel, NJ 07001-2293

800-972-2225

<http://www.elexp.com>

email: electron@elexp.com

TECH FORUM

Motorola's MC145200 will work to 2 GHz. National has an LMX2315, and Harris has an HFA3524. Even better for this application would be a fractional-N chipset, but I don't have any data handy. All these chips are programmed serially, so the interface to a computer is simple.

Unfortunately, the problem in building such a synthesizer is not the IC, but the oscillator. It is tough to build an oscillator that covers one octave, but you want to cover about 3.5 octaves.

The simplest way around the oscillator range problem is a heterodyne design. Use a VCO that covers 5.1 to 6.0 GHz, mix it with a 5.0 GHz local oscillator, and use the 0.1-1.0 GHz result as the synthesizer output. The frequencies are a little scary, and the performance won't be great.

An alternative is to build a 250-500 MHz VCO to cover the middle octave. Other octaves are derived from this signal. Switch in a doubler if you need the top octave, or use one or two dividers to get the lower octaves. You will need six or seven half-octave filters to clean up the output signal.

There are a lot of switches, so we are not talking about something simple. The performance should be better than the heterodyne design.

Building a one-octave VCO is difficult, and building a good one is an art. The good ones are bandswitched and vary the oscillator bias conditions in different bands. They also use pre-tuning and compensate for changes in PLL loop gain.

For low-noise oscillators, the VCO tuning sensitivity is often less than 500 KHz/volt and the VCO will have 32 tuning bands.

Good (but expensive) texts are: Manassewitsch, *Frequency Synthesizers: Theory and Design*, and Rohde, *Microwave and Wireless Synthesizers*.

Gerald Roylance
Mountain View, CA

ANSWER TO #129818 - DEC. 1998

I recall that one of the hobby electronics magazines did a construction project a while back on building a GPIB interface, perhaps *Electronics Now*, or *Popular Electronics*.

However, Computerboards, Inc. in Massachusetts sells a GPIB interface for \$249.00 new. Their phone number is 508-946-5100.

You can probably get the spec for the GPIB interface from the National Instruments or Hewlett-Packard web site.

Joe Heck
Wrentham, MA

ANSWER TO #129817 - DEC. 1998

It is very simple to construct a linear, 10X amplifier, for this application. It is also very inexpensive (total cost is about 45¢).

Build the non-inverting amplifier exactly as drawn in the book, *The Art of Electronics*, by P. Horowitz and W. Hill.

For instance, one could use a LM 358 op-amp, a 1 Kohm resistor, a 3.3 Kohm resistor, a 5.6 Kohm resistor, and a 7-32 volts DC power supply (or just an ordinary 9-volt battery).

1. Connect the positive terminal of the power supply to pin #8 of the LM 358.

2. Connect the negative terminal of the power supply to pin #4 of the LM 358.

3. Connect the end of the 5.6 Kohm resistor to pin #1.

4. Connect one end of the 3.3 Kohm resistor to the free end of the 5.6 Kohm resistor. (5.6K + 3.3K = 9K. This is R2 on the drawing.)

5. Connect one end of the 1 Kohm resistor to the free end of the 3.3 Kohm resistor. (This is R1 on the


drawing.)

6. Connect the free end of the 1 Kohm resistor to the negative terminal of the power supply.

7. Connect the junction of the 3.3 Kohm and the 1 Kohm resistor (that made in step #5) to pin #2 of the LM 358.

8. Be sure to connect the negative terminal of the power supply to the ground of the sensor (s).

Continued on page 81



Roger's Systems

Computer - Telecommunication
Network - Audio - Video
"We Have Great Connections"
Accessories - Connectors
Tools - Adaptors

Specialist

www.rogerssystems.com

Video Cable

- RCA Connectors for VCR/Camcorder to TV Monitor or A/V Receiver.
- Highest quality 75 ohm video cable for a superior picture.
- Molded connector with gold plated contacts improves the quality of the connection.
- Push-on connector for easy installation.

Part #	Length	Price
VC-7003.....	3'	\$2.00 ea.
VC-7004.....	6'	\$3.00 ea.
VC-7005.....	12'	\$4.00 ea.

Audio Cable

- RCA Connectors for CD Player or Cassette to Amp/Receiver.
- 100% foil shield for reduced interference and superior sound.
- Molded connector with gold plated contacts improves the quality of the connection.
- Color coded for easy connection of left and right channel.

Part #	Length	Price
VC-7009.....	3'	\$2.00 ea.
VC-7010.....	6'	\$3.00 ea.
VC-7011.....	12'	\$4.00 ea.

"F" Video Cable

- Push-on connector for easy installation.
- Connects VCR/Cable Box to TV
- Highest quality 75 ohm video cable for a superior picture.
- Molded connector with gold plated contacts improves the quality of the connection.

Part #	Length	Price
VC-7000.....	3'	\$2.00 ea.
VC-7001.....	6'	\$3.00 ea.
VC-7002.....	12'	\$4.00 ea.

"S" Video Cable

- Push-on connector for easy installation.
- Connects SVHS/Laser Disc/Hi 8 Camcorders to TV Monitor or A/V Receiver
- Highest quality 75 ohm video cable for a superior picture.
- Molded connector with gold plated contacts improves the quality of the connection.

Part #	Length	Price
VC-7007.....	6'	\$3.00 ea.
VC-7008.....	12'	\$5.00 ea.

A/V Connection Kit

- Triple RCA Male to Male Cable for Audio and Video.
- Best connection from VCR/Laser Disc/Camcorder to TV Monitor or A/V Receiver.
- 100% Foil shield for reduced interference and superior reception.
- Color coded for easy installation.
- Molded connection with gold plated contacts improves the quality of the connection.

Part #	Length	Price
VC-7012.....	3'	\$4.00 ea.
VC-7013.....	6'	\$6.00 ea.
VC-7014.....	12'	\$8.00 ea.

In-Wall Volume Control

- Controls volume of remote speakers.
- Easy installation terminal block.
- 10-position range.
- Mounts in standard electrical J-box.
- Accepts up to 14 awg wire.
- 30 watts average- 55 watt peak.
- Ivory colored.
- Includes Mounting screws.

Part #	Price
AS-7020.....	\$10.00 ea.

1-800-366-0579

24895 Ave. Rockefeller, Valencia, CA 91355

Local 805-295-5577

FAX 805-295-8777

\$20.00 minimum order required • Add \$4.50 shipping for prepaid orders • Prices subject to change without notice. All major credit cards accepted • Special offers only valid on items in stock
California residents add 8.25% tax • eMail sales@rogerssystems.com. Call for quantity discounts • No out of state checks accepted • Most orders shipped same day! • Not responsible for errors in typesetting.
Trademarks are the property of their respective companies. All photographs are for illustration purposes only and may not be a true representation of actual products.

HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 91719.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your *Nuts & Volts* account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

ADVERTISER'S INDEX

Abacom Technologies	68	Davilyn Corp.	7	KDE Electronics Corp.	48	Roger's Systems Specialist	73
ABC Electronics	29	Decade Engineering	86	La Paz Electronics Int'l.	71	Sam's Electronics	54
ACP Super Store	72	DeMar Electronics	87	Lemos International Co., Inc.	67	Scott Edwards Electronics	8
Advanced Educational Systems	68	Digital Products Co.	86	Linear Systems	15	Seabird Technical	87
Alfa Electronics	59	Earth Computer Technologies	44	LLH Technology Publishing	38	Shreve Systems	86
All Electronics Corporation	60	Edlie Electronics, Inc.	46	Lynxmotion, Inc.	21	SIMCO	47
Allison Technology Corporation	81, 86	E.H. Yost & Co.	54	M2L Electronics	59	Skycraft Parts & Surplus, Inc.	72
Alltech Electronics	18	ELECTRO MAVIN	8	Matco, Inc.	87	Square 1 Electronics	34
Alltronics	23	Electro Tool, Inc.	53	MCM Electronics	9	Surplus Traders	86
American Technologies Network Corp.	35	Electronic Design Specialists, Inc.	22	Meredith Instruments	19	Synergetics	79
AM Research, Inc.	35	Electronic Goldmine	49	Metric Equipment Sales, Inc.	48	Tech 2000	26
Andromeda Research	21	Electronic Rainbow Ind., Inc.	51	M.F.M. Communications	24	Tech 2000	26
Antique Radio Classified	87	Electronix Corp.	39	microEngineering Labs	65	Techniks, Inc.	86
AST Global Electronics	32	Electronix Express	72	Micromint	66	Technological Arts	86
Aventrade	86	EMAC, Inc.	53	Motron Electronics	39	Telulex, Inc.	49
Base2	87	EPS	87	Mr. NiCd	54	The RF Connection	15
Basic Electrical Supply		Equipment Management Technology	61	MSC Electronics	87	Timeless Products	61
& Warehousing Corporation	20	ExpressPCB	34	Netcom	85	Timeline, Inc.	47
Baylin Publications	19	Fair Radio Sales	11	Northwest Cable & Connector Co.	25	Ultra Link	87
Bilcon Corp.	87	Foss Warehouse Distributors	86	Ocean State Electronics	42	Unicorn Electronics	22
Bisme Computers Outlet	59	Gateway	56	Optoelectronics	94	USI Corp.	66
Black Feather Electronics	26	General Device Instruments	86	Pacific Test Equipment Corp.	43	Utopia Tools	29
Brick Wall Div., Price Wheeler Corp.	13	Glentech, Inc.	86	Parallax, Inc.	Back Cover	V&V Mach. & Equipment, Inc.	86, 87
Brigar Electronics	67	Graymark	44	PARAMAX, INC.	83	Velleman	55
C & S Sales, Inc.	40	Halted Specialties Co.	3	PCW, Inc.	70	VersaTech Electronics	29
C and H Sales Company	45	H.T. Orr Computer Supplies	61	Phelps Instruments	52	Vesta Technology, Inc.	87
Chaffin Electronics	78	Hyatt Electronic Surplus	87	Pioneer Hill Software	81	Viking International	52
Chenesko Products, Inc.	71	IndustroLogic	16	Polaris Industries	63	Visitect, Inc.	82
Communications Surplus	87	Information Unlimited	45	Prairie Digital, Inc.	87	Weeder Technologies	20
Consumertronics	28	Inkjet Southwest	58	Pulsar, Inc.	25	Western Test Systems	30-31
Corporate Systems Center	2, 95	Intronics, Inc.	70	R & S Surplus	54	Wholesale Cable	78
Cruising Equipment	65	Jade Products, Inc.	86	Ramsey Electronics, Inc.	57	Worldwyde	77, 86
Cunard Associates	53	James' Electronic Services, Ltd.	84	Resources Un-Ltd.	14		
Danbar Sales Company	50	J-Works, Inc.	77	R.E. Smith	86		

AMATEUR RADIO & TV

Abacom Technologies	68
Alltronics	23
Communications Surplus	87
Gateway	56
Jade Products, Inc.	86
Lemos International Co., Inc.	67
Ocean State Electronics	42
Ramsey Electronics, Inc.	57
The RF Connection	15

BATTERIES/CHARGERS

Aventrade	86
Cruising Equipment	65
Cunard Associates	53
E.H. Yost & Co.	54
Jade Products, Inc.	86
Mr. NiCd	54

BUSINESS OPPORTUNITIES

Cheneko Products, Inc.	71
------------------------	----

BUYING ELECTRONIC SURPLUS

ABC Electronics	29
Alltech Electronics	18
Black Feather Electronics	26
C and H Sales Company	45
Earth Computer Technologies	44
EPS	87
Equipment Management Technology	61
Metric Equipment Sales, Inc.	48
Roger's Systems Specialist	73
Skycraft Parts & Surplus, Inc.	72

CABLE TV

Basic Electrical Supply & Warehousing Corporation	20
Foss Warehouse Distributors	86
James' Electronic Services, Ltd.	84
KDE Electronics Corp.	48
PCW, Inc.	70
Sam's Electronics	54
Tech 2000	26
Timeless Products	61
Wholesale Cable	78

CB/SCANNERS

USI Corp.	66
-----------	----

CCD CAMERAS/VIDEO

American Technologies Network Corp.	35
Black Feather Electronics	26
Decade Engineering	86
MSC Electronics	87
Polaris Industries	63
Ramsey Electronics, Inc.	57
Resources Un-Ltd.	14
Seabird Technical	87
Timeline, Inc.	47
USI Corp.	66

COMPONENTS

Communications Surplus	87
Electronic Goldmine	49
Electronix Express	72
EPS	87
Hyatt Electronic Surplus	87
La Paz Electronics Int'l.	71
Linear Systems	15
Ocean State Electronics	42
Pulsar, Inc.	25
Skycraft Parts & Surplus, Inc.	72
Unicom Electronics	22
Visitect, Inc.	82

COMPUTER

Hardware

ACP Super Store	72
Allison Technology Corp.	81, 86
Alltech Electronics	18
AM Research, Inc.	35
Base2	87
Bisme Computers Outlet	59
Brick Wall Div., Price Wheeler Corp.	13
Chaffin Electronics	78
Consumertronics	28

Corporate Systems Center	2, 95
Earth Computer Technologies	44
ELECTRO MAVIN	8
General Device Instruments	86
Halted Specialties Co.	3
La Paz Electronics Int'l.	71
MCM Electronics	9
Northwest Cable & Connector Co.	25
Roger's Systems Specialist	73
Shreve Systems	86
Techniks, Inc.	86
Ultra Link	87
Worldwyde	77, 86

Software

AM Research, Inc.	35
Bisme Computers Outlet	59
Electronix Corp.	39
Pioneer Hill Software	81
Ultra Link	87

Microcontrollers / I/O Boards

Abacom Technologies	68
Advanced Educational Systems	68
AM Research, Inc.	35
Bisme Computer Outlet	59
EMAC, Inc.	53
IndustroLogic	16
La Paz Electronics Int'l.	71
Micromint	66
Motron Electronics	39
Parallax, Inc.	Back Cover
PARAMAX, INC.	83
Prairie Digital, Inc.	87
R.E. Smith	86
Scott Edwards Electronics	8
Square 1 Electronics	34
Technological Arts	86
VersaTech Electronics	29
Vesta Technology, Inc.	87

Printers/Printer Supplies

Cheneko Products, Inc.	71
H.T. Orr Computer Supplies	61
Inkjet Southwest	58

DESIGN/ENGINEERING SERVICES

ExpressPCB	34
Pulsar, Inc.	25
V&V Mach. & Equipment, Inc.	86, 87

EDUCATION

Advanced Educational Systems	68
Electronix Corp.	39
EMAC, Inc.	53

EVENTS/SHOWS

ACP Super Store	72
-----------------	----

KITS

Alltronics	23
C & S Sales, Inc.	40
Digital Products, Inc.	86
Earth Computer Technologies	44
Edlie Electronics, Inc.	46
Electronic Goldmine	49
Electronic Rainbow Ind., Inc.	51
EMAC, Inc.	53
Gateway	56
Hyatt Electronic Surplus	87
Information Unlimited	45
Inkjet Southwest	58
Jade Products, Inc.	86
Ocean State Electronics	42
Ramsey Electronics, Inc.	57
Scott Edwards Electronics	8
USI Corp.	66
Velleman	55
Weeder Technologies	20

LASERS

Information Unlimited	45
Meredith Instruments	19
Resources Un-Ltd.	14
Unicom Electronics	22

MISC./SURPLUS

All Electronics Corporation	60
Alltech Electronics	18
Black Feather Electronics	26
Brigar Electronics	67
C and H Sales Company	45
Chaffin Electronics	78

FIND
what you need ...

FAST
BY PRODUCT
OR
CATEGORY

Communications Surplus	87
Consumertronics	28
DeMar Electronics	87
Electronic Goldmine	49
Electronic Rainbow Ind., Inc.	51
EPS	87
Equipment Management Technology	61
Fair Radio Sales	11
Gateway	56
Halted Specialties Co.	3
Hyatt Electronic Surplus	87
Linear Systems	15
Resources Un-Ltd.	14
Shreve Systems	86
SIMCO	47
Skycraft Parts & Surplus, Inc.	72
Surplus Traders	86
Timeline, Inc.	47
Unicom Electronics	22
Viking International	52
Visitect, Inc.	82
Weeder Technologies	20

PROGRAMMERS

Andromeda Research	21
General Device Instruments	86
Intronics, Inc.	70
M2L Electronics	59
microEngineering Labs	65

PUBLICATIONS

Antique Radio Classified	87
Consumertronics	28
LLH Technology Publishing	38
Netcom	85
Square 1 Electronics	34
Synergetics	79

ROBOTICS

Abacom Technologies	68
Lemos International Co., Inc.	67
Lynxmotion, Inc.	21
PARAMAX, INC.	83

SATELLITE

Baylin Publications	19
---------------------	----

SECURITY

American Technologies Network Corp.	35
Information Unlimited	45
Lemos International Co., Inc.	67
Matco, Inc.	87
MSC Electronics	87
Polaris Industries	63
Visitect, Inc.	82

SOLAR EQUIPMENT

Cruising Equipment	65
--------------------	----

STEPPER MOTORS

Alltronics	23
PARAMAX, INC.	83

TELEPHONE

Bilcocon Corp.	87
Digital Products, Inc.	86
M.F.M. Communications	24
Telulex, Inc.	49
Weeder Technologies	20

TEST EQUIPMENT

ABC Electronics	29
Alfa Electronics	59
Allison Technology Corp.	81, 86
AST Global Electronics	32
C & S Sales, Inc.	40
C and H Sales Company	45
Cruising Equipment	65
Danbar Sales Company	50
Davilyn Corp.	7
Digital Products, Inc.	86
Electronic Design Specialists, Inc.	22
Equipment Management Technology	61
Electro Tool, Inc.	53
Glentech, Inc.	86
Intronics, Inc.	70
J-Works, Inc.	77
MCM Electronics	9
Metric Equipment Sales, Inc.	48
Optoelectronics	94
Pacific Test Equipment Corp.	43
Phelps Instruments	52
Pioneer Hill Software	81
R & S Surplus	54
Seabird Technical	87
Telulex, Inc.	49
Western Test Systems	30-31

TOOLS

C & S Sales, Inc.	40
Electro Tool, Inc.	53
Graymark	44
The RF Connection	15
Utopia Tools	29

WIRE/CABLE & CONNECTORS

Northwest Cable & Connector Co.	25
Roger's Systems Specialist	73
The RF Connection	15

Magnifiers come in many sizes, shapes, and prices. To put a numerical value on the property we call magnification, you need to go back to 1800's England when they defined the near point. The near point is the closest distance from the eyes most adults can comfortably focus and is defined as 10 inches (250mm).

This is the basis for determining the property we call magnification of near subjects. If you look at one line 10mm long from 10 inches, and it covers a particular angle, and compare it to another line 5mm long with a magnifier, and it covers the same angle, you have a 2X magnifier.

Under the same viewing conditions, a 0.1mm line covering the same angle would mean you are using a 100X magnifier. Not all manufacturers use this definition of magnification and use the term power instead. Power is not that rigorously defined and often refers to the increase in area. In this case, the magnification factor is the square root of the power. A 9X power lens would have a magnification factor of about 3X.

When you focus your eyes from infinity to 10 inches, it's similar to introducing a four diopter lens into the view. My old eyes don't come close to the 10-inch focus of the average adult, so I have

Figure 1



a different size image on the retina. Individual differences and preferences support the thousands of different magnifiers in the marketplace.

Simple Lens Magnifiers

Simple lens magnifiers use one lens group between the eye and the subject under observation. These simple magnifiers may be a single lens, several lenses cemented together and, in rare cases, air-spaced lenses. They may yield magnifications from a little over 1X to over 300X. In the current commercial market, you can find magnifiers that provide slightly over 1X to about 25X. Higher magnifications are now provided by the more easily used compound magnifiers.

Compound magnifiers differ from the simple magnifiers in that they use a second set of lenses to magnify the image of the primary group. Representatives of compound magnifiers are microscopes, binoculars, and telescopes. There are image magnifiers that use infrared, ultraviolet, X-ray, and electrons, but we will only cover the visible frequencies.

A popular form of simple magnifiers in Figure 1 is an oversized 5X and a focusing 8X model. When you look through these magnifiers, you will find that for practical purposes, the visual linear magnification is about half the stated value. If you put the magnifier on a piece of quadrille paper, you can easily see the degree of magnification. You can increase the magnification by lifting it from the surface of the subject and increasing the distance to your eye, however, a little bit goes a long way as the image is quickly distorted beyond use. The ones shown cost about \$5.00 to \$10.00.

Some magnifiers include a measuring reticle (a glass scale) at the focal plane for accurate measurements of length, angle, or thread pitch. More highly corrected optics can increase the price up

MMM
AAA
GGG
NNN
III
FFF
III
EEE
RRR
SSS
1X to
1000X

by John C. Little

to \$250.00 for special applications such as photo retouching. Most of the simple magnifiers on the market today use clear bodies so you can view either opaque or transparent subjects.

Another simple magnifier is the eyeloupe shown with a spring retainer in Figure 2. It is difficult to find eyeloupes with a spring retainer now, but plain loupes from 2X to 5X are available at less than \$10.00.

Bi-ocular Magnifiers

Your local drugstore carries a very economical bi-ocular magnifier called reading glasses. The strongest sold is usually 3.25 diopter that give a little less than a 2X stereo view and are priced at \$8.00 to \$15.00. (The diopter is one meter divided by the focal length of the lens.) The "half glasses" allow quick orientation of your subject by looking over the top. Some people may be uncomfortable trying to converge the sight lines and maintain a stereo view so close to the face.

A solution is the head-mounted magnifiers, some with flip-up lenses that are available in 2X to 8X. These are designed with wedge shaped lenses to ease the strain of the converging sight lines. They are priced in the \$20.00 to \$50.00 range.

Shown in the background of Figure 2 is an inexpensive compound microscope that is found in magnifications from 20X to 100X. The higher mag-

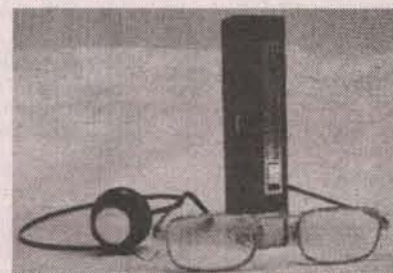


Figure 2

nifications do not seem to have a consistent, good image quality so they should be carefully examined before purchasing. This type of microscope usually includes a "flashlight" to illuminate an opaque subject. They are particularly useful in the field for simple tasks. They are priced from \$5.00 to \$20.00. Some models can be focused below the plane of the foot. With these, you can examine a few of the problems on PC boards.

Compound Magnifiers

When you look into a compound microscope, you see the image at the end of a dark tube. How far away the image appears is determined by the eyepiece. How much of the subject you can see is determined, in part, by the focal length of the objective and the diameter of the field stop in the eyepiece. The field stop is a disk located at a focal plane within the eyepiece. It gives a sharply-defined limit to the image and also limits the image projected up the tube to the optically-corrected area.

As the focal length of the objective gets smaller, you get higher magnification and a smaller field of view. The common plan achromats (color-corrected objectives), when used with 10XWF eyepieces, have these approximate field diameters: 40X 4.5mm, 100X 1.75mm, 400X 0.45mm, 1000X 0.18mm. When you look at a printed circuit board and need a larger field of view or a greater depth of field, you must increase the focal length of the objective(s). Changing from a 10X eyepiece to a 5X will only make the image look farther away while the area covered by the image stays about the same.

The approximate magnification of the compound microscope is determined by multiplying the magnification factor marked on the objective by the factor on the eyepiece. This is only an approximate value due to manufacturing variations

and the settings of the eyepiece diopter adjustment. For accurate measurements, you will need the optics calibrated using a stage micrometer and a reference reticle mounted in the eyepiece.

Stereo Microscopes

Stereo microscopes are two compound microscopes mounted so that the sight lines converge at about a seven-degree angle. A typical fixed magnification stereo microscope is illustrated in Figure 3. This arrangement provides an apparent depth perception similar to that of the near point. These microscopes are designed primarily for those applications where there is a need to manipulate the subject. Image erecting prisms or mirrors are introduced into the optical train without which a direct stereo image could not be obtained.

Applications for stereo microscopes include: electronic surface mount placement and attachment, repair of fine mechanisms, quality control, and a long list of other applications. A single magnification model will cost from \$125.00 to over \$300.00. Two or more fixed magnifications will cost \$250.00 to \$1,000.00. Remember that at magnifications above 10X, hand/eye coordination and tremor will bring more frustration than satisfaction for many placement tasks. It is the same problem you would have controlling handheld binoculars.

Locating solder faults and other QC work is more easily done at higher magnifications. Most of the current manufacturers provide good optics except for some of those sold in toy and hobby stores. The primary difference among different models and manufacturers is the quality of the illumination system and the quality of the mechanical work. The graph (Figure 4) illustrates the diameter of the field of view with different values of magnification. It should only be used as a rough guide because of the variations from manufacturer to manufacturer. You would not be able to see a whole 16-pin DIP or the top of a TO-8 can at 30X.

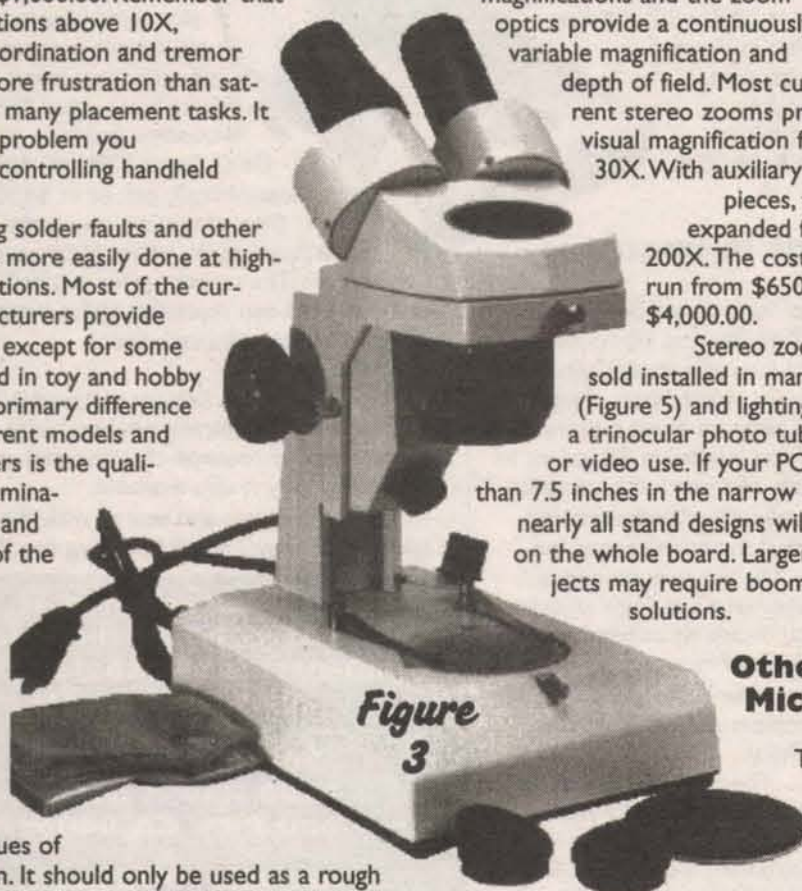


Figure 3

In my experience, perhaps one-half to one percent of users have difficulty attaining or maintaining a fused stereo image from a stereo microscope. This is usually an example of the strong habit of combining the eyes focus and the convergence of the sight line. This is a learned response and can be overcome with practice. It often helps to focus the instrument on a subject, lift your head, and focus on a distant object, close your eyes, and place your head over the eyepieces and opening the eyes. The stereo view pops into view in most cases. Those who need to wear corrective glasses for astigmatism should look for designs providing high eyepoint eyepieces. The near or farsighted can usually use a microscope without glasses.

Zoom Stereo Microscopes

Stereo zoom microscopes are the industry standard for electronic assembly. As assembly people become more experienced, they like to work at increasing magnifications and the zoom optics provide a continuously variable magnification and depth of field. Most current stereo zooms provide visual magnification from 7X to at least 30X. With auxiliary lenses and eyepieces, the range can be expanded from 3.5X to over 200X. The cost of new instruments run from \$650.00 to over \$4,000.00.

Stereo zoom heads (pods) are sold installed in many designs of stands (Figure 5) and lighting systems, as well as a trinocular photo tube design for camera or video use. If your PC boards are less than 7.5 inches in the narrow dimension, then nearly all stand designs will allow you to work on the whole board. Larger dimensional subjects may require boom stands or other solutions.

Other Compound Microscopes

The average student and research grade compound microscope (under \$2,000.00) has a maximum visual resolution of about 900X when using air to glass or oil immersion objectives in visible light. This is a result of



Figure 5

the physical limitation of the phenomenon of diffraction. For the technologist, the real question is not the

degree of magnification but how much information is retained in the image. With a microscope set at 1000X visual magnification, you can take a photograph and print the image on a billboard at say 10,000X. There would not be any more information than at 900X, in fact there would be a lot less.

Magnification alone will rarely be the main factor in microscopy.

There are no universal compound microscopes (those useful for every type of subject), although some in the \$50,000.00 range may come close. The purchaser must decide what information they are seeking, what lighting is needed, and the effort and type of sample preparation they are willing to perform to acquire a useful image.

There are hundreds of useful books on microscopes and dozens of excellent ones to help in the selection of the proper microscope for your application. You should be aware, however, that the selection of a specific microscope brand is like selecting a brand of automobile. If you ask an experienced professional for a recommendation, most will quote the brand they are using although the basic microscope has changed little in the last 75 years. All well-designed microscopes should last a lifetime with a reasonable amount of care while a good warranty will cover that rare one that slips through the quality control checks.

One, Two, or Three Eyes?

You would think that a binocular microscope would be inherently better than a monocular model; they certainly cost more. For short term use, it is hard to say. You need to balance the

USB Relay Module

Model JSB-210

Controls 8 to 16 "form C" relays over the USB (Universal Serial Bus). Program the module with simple commands in any program language that supports USB Communications. Driver and sample code provided

J-Works, Inc

12328 Gladstone St., Unit 4
Sylmar, CA 91342
(818) 361-0787 Voice (818) 270-2413 Fax

Other Products

RS-485 Remote I/O
ISA Waveform Generator
RS-485 to DS-1820
RS-485 Temperature I/O
DS-1820 Probe

Visit our Web site for
Information on all our products
<http://www.j-works.com>
E-mail sales@j-works.com

Fixed Frequency or Workstation Monitor?

Now, use **ANY** monitor on your PC with the new **Avalanche 3D** from Worldwyde.com!



- Easiest installation of any card in its class!
- Supports all resolutions and frequencies:
- from 320 x 200 to 1280 x 1024
- 15KHz to 120KHz
- Available in PCI or AGP

To order, call Worldwyde.com
1-248-473-1182
21365 Randall Street • Farmington Hills, MI 48336
Visit us on the web at www.worldwyde.com
Dealer/Quantity Discounts Available

Special!
\$109⁰⁰

image degradation of at least four air to glass surfaces in a binocular head against the discomfort of using a single eye. If you do not plan intense viewing sessions lasting longer than an hour at a time, a monocular model should work very well.

Do you need a third eye (a trinocular head)? It is difficult but not impossible to obtain excellent photomicrographs or videomicrographs with binocular heads. Because of the angle of the eyetube, it is difficult but you can configure a copy stand for photography. You need to figure about \$200.00 more for a trinocular head over the binocular. A good copy stand will cost a little less. Some trinocular heads blank out the two viewing eyepieces when in the photo mode while others allow a small portion of the light to be projected to the eyes to track moving subjects.


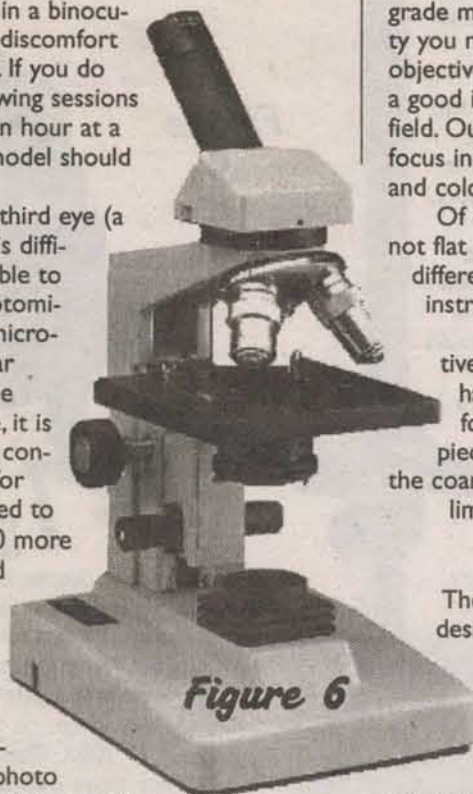


Figure 6

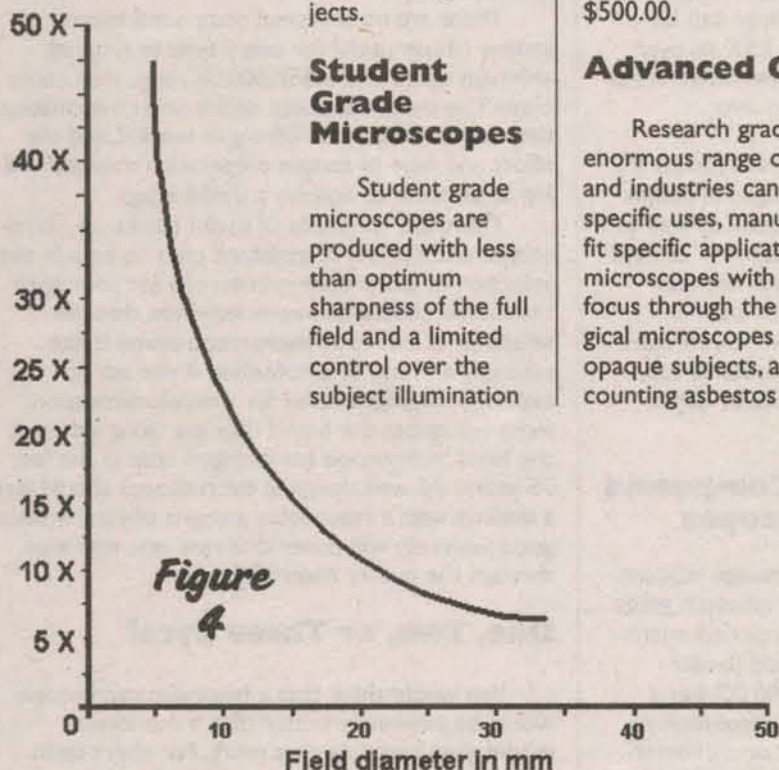

Student Grade Microscopes

Student grade microscopes are produced with less than optimum sharpness of the full field and a limited control over the subject illumination

compared to a research model. However, student grade microscopes may provide all the image quality you need for non-critical use. The achromatic objectives used in this class of instrument provide a good image in the central 60% of the image field. Outside that area the image is not in focus in the same plane as the central area and color fringes increase.

Of course, if your subject is not flat it may not make much difference. Most of these instruments come with 4X, 10X, and 40X objectives. They may or may not have both coarse and fine focus control. With 10X eyepieces and 40X objectives (400X), the coarse focus mechanism has reached its limit so adding a 100X objective to the instrument is not very practical.

These instruments are designed with only transparent subjects in mind, however, in a pinch, you can view an opaque subject up to about 100X with a strong sidelight. Shown in Figure 6 is one of the few student microscopes designed to be upgraded. Student grade microscopes cost from about \$125.00 to \$500.00.

Advanced Grade Microscopes


Research grade microscopes are available in an enormous range of designs. Because laboratories and industries can afford instruments designed for specific uses, manufacturers modify their designs to fit specific applications. There are tissue culture microscopes with extended clearance objectives to focus through the bottom of a petri dish, metallurgical microscopes with reflective illumination for opaque subjects, and polarizing microscopes for counting asbestos fibers. The list goes on and on.

Wherever and from whoever you decide to purchase an advanced microscope, make sure they know your imaging problem and will help you solve it.

The cost of a quality full-sized biological microscope is about \$700.00. Such an instrument would have 4X, 10X, 40XSL, and 100XSL oil

objectives, a binocular head with 10XWF eyepieces, a mechanical stage, an Abbe' condenser, and a variable intensity light source. In Figure 7, is an unusual current product in that it has a vertical illuminator built into the trinocular head for viewing opaque subjects as well as transparent ones. Someone somewhere has a magnifier to solve your imaging problem in the range of 1X to 1000X.

Figure 7

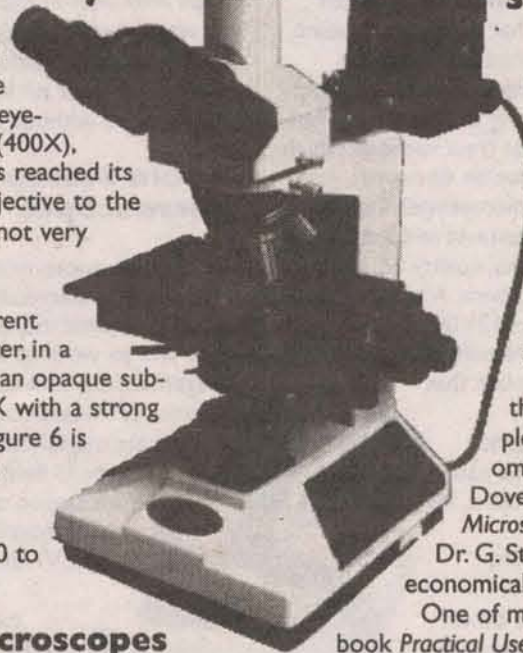

Books and Other Sources

To decide the specifications for your new microscope purchase the book *Exploring with the Microscope* by W. Nachtigall/Sterling Publishing Co., ISBN #0-8069-0867-x; a winner at \$14.95. This book has over 100 color micrographs.

To familiarize you with the nomenclature and simple sample preparation, I recommend you invest in a Dover book titled *The Microscope and How to Use It* by Dr. G. Stehli, ISBN #0-486-22575-5; economically priced at \$4.95 (1996).

One of my favorites is the 1958 book *Practical Use of the Microscope* by G.H. Needham. The current price is \$99.00. This book has just been reprinted and is available through McCrone Accessories at www.mccrone.com.

The Microscope Society of America has a website (www.msamicroscopy.com) with information on local microscope chapters, and an extensive bibliography is also available.

Get on the web and search with the words "light microscopy;" it will be a long list. **NV**

I can be reached at jlittle@netwizard.net for comments or brickbats. You can also write me at:

Seabird Technical
3580 Haven Avenue
Redwood City, CA 94063-4603
www.seabirdt.com

\$\$\$ We Can Save You Money \$\$\$

Computers	PCB Manufacturing	PCB Assembly Services	Full Line Of Electronic Components
Custom Built PC's at the Lowest Prices Computer Accessories	Single & Double Sided	Board Stuffing Wave Soldering Acquisition of Parts	IC's Semiconductors Capacitors Resistors Sockets Relays Transistors & More

Call **Chaffin Electronics** Toll Free at (800) 442-2330

WE WANT YOUR BUSINESS!!! BIG OR SMALL

Phone	Fax	Email	Internet
(800) 442 2330	(740) 354-9462	ceinc@zoomnet.net	www.chaffinelectronics.com

WHOLESALE CABLE

COMPLETE LINE OF CABLE PRODUCTS

- ✓ Quality merchandise by brand name manufacturers
- ✓ Satisfaction guaranteed
- ✓ Free gift on first order
- ✓ Technical support
- ✓ 2 year warranty on new converters
- ✓ COD shipping & overnight shipping by request
- ✓ Experience where it counts
- ✓ Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES

WHOLESALE CABLE M-F 11am-6pm EST (800) 909-4333
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.

Tell us the best price you were offered, where you got it from, and let us try to beat it.



RESOURCE BIN

number eighty five

Another look at some favorite websites.

Our usual reminder here that the *Resource Bin* is now a two-way column. You can get tech help, consultant referrals, and off-the-wall networking on nearly any electronic, *tinaja* questing, personal publishing, money machine, or computer topic by calling me at (520) 428-4073 weekdays 8-5 Mountain Standard Time.

Be certain to frequently check out my new *Guru's Lair* web site you'll find at (where else?) www.tinaja.com. This is the place you'll go for instant tech answers. Among the many files in our library, you will find complete reprint sets for all of the *Resource Bin* and other columns. Plus a brand new Research InfoPack Service.

You will get the best results if you have both *Netscape Communicator* and *AcrobatReader 3.0* installed.

Where to go for what?

Quite a bit has happened since we last surveyed great places to visit on the web. So I thought it was way past time for an update. Needless to say, the web is where *everything* technical or electronic now seems to be coming down. You simply cannot afford to miss out. You can easily sample the web at your local school or library if you are not yet online.

We saw how to get yourself on the web in RESBN78.PDF. And secrets of web-based research in RESBN71.PDF.

You'll need a newer computer that supports *Netscape* or another modern browser. Perhaps a Pentium running Windows 98. Or a *Linux* box. While you can use Web TV (I feel this is an outright joke) or any national service such as AOL, I strongly believe a local ISP or *Internet Service Provider* is often your best way to go. Typical charges are around \$19.00 per month or less. This usually includes a CD-ROM or similar startup software.

You can pick up that latest *Netscape Browser* free at www.netscape.com. One useful

local ISP is www.zekes.com.

Tip: Do look into the new wireless services being offered by a few ISPs. These can end up 400K fast, leave you connected all the time, and tie up no phone lines or have any telco or cable fees. But the transceivers are costly and you'll need line-of-sight.

If you are brand new to the web, you go to a site by booting Netscape and then entering a url address into the *Location* box.

NEXT MONTH:
Don explores the denizens in the pseudoscience morass.

When you find sites you like, you save them by clicking on the *Bookmark* button. Much more on web use, from bare startups to fancy advanced home page design are at www.tinaja.com/weblib01.html.

You will find untold zillions of web sites active today. How do you locate the better ones? My choices here are simply based on the sites that I use most often. Instant "hot buttons" for linking most of these are now found at www.tinaja.com. Here are several of my current favorites ...

www.questlink.com

This is *the* place to go for electronic data sheets and all application notes. They are industry wide, and represent pretty near anybody and everybody. They also let you instant order small quantities of many harder-to-get ICs and semiconductors.

As with my own site and just about any other source of decent tech info on the web, you will need an *Acrobat Reader* to let you view their ap notes and data sheets. You get this free from www.adobe.com. For Acrobat utterly and totally blows HTML away on all counts. More info about this superb PostScript extension can be found at www.tinaja.com/acrob01.html and at my www.tinaja.com/post01.html.

Additional electrical engineering links and link farms can be found at www.tinaja.com/ee01.html. Since the link farms do such an incredibly good job here, I personally provide ee links only to the farms and the actual sites I have a repeating need for.

www.hotbot.com

This one is my favorite web search engine. You'll go here to find what is where on the web. Just type in some keywords, and dozens to hundreds of results get listed. Put the keywords in quotes when searching for a name or other exact match. You can also make use of their "links to this url" search as a great ego trip to find out just who is linking your own site.

There are hundreds of other search engines. The www.altavista.digital.com is quite popular, although I use it only for emergency backup. There's also an "inference engine" that tries to gather together larger concepts for you up at www.infind.com. When this works, it performs very well. When it misses, it does so badly. An example of a *meta* search engine master site which links hundreds of others is www.kresch.com. They also offer all sorts of webmaster tools, free search engine submissions, and bounces more.

Books

My very favorite online bookstore is www.lindsaybks.com. Who specialize in republishing the "lost technology" titles on everything from old machine shop practice to his early radio books. The quickest way to reach them is to click through on one of their banners found on my website. More info on banners at www.tinaja.com/advt01.html.

That 800-pound gorilla, of course, is *Amazon Books*. Who have now become *the* place to go to get *any* book on *any* topic. Reach them by way of www.tinaja.com/amlink01.html. I have also placed a few carefully selected book recommendations on dozens of topics here.

By the way, your use of this exact www.tinaja.com/amlink01.html link to Amazon supports both your *Resource Bin* and the *Ask the Guru* web pages at zero additional cost to you.

Oxbridge Media Finder

The fastest, cheapest, and the most convenient way to get up to speed on most any technical topic is by use of those industry insider

new from DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. \$28.50 each.

RESEARCH INFOPACKS

Don's instant cash-and-carry flat rate consulting service. Ask any reasonable technical question for a detailed analysis and complete report. See www.tinaja.com/info01 for specifics. \$75.00

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. \$18.50

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Tech Musings V or VI	\$24.50
Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$34.50
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Technical Insider Secrets	FREE

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. 28.50

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. \$24.50

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Check Don's *Guru's Lair* at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com

FREE US VOICE HELPLINE

VISA/MC

SYNERGETICS

Box 809-NV

Thatcher, AZ 85552

(520) 428-4073

trade journals. Find these at www.mediafinder.com.

Online and E-Mail publisher linkings often do get provided in their listings. But sadly, Oxbridge does not give you complete snail-mail addresses as a free service. Instead, you may have to use the backwards phone finders found at in-123.infospace.com or at www.anywho.com to pin these down.

Additional phone number sources and other useful web utilities appear at www.tinaja.com/webwb01.html.

RESOURCE BIN

SOME RECOMMENDED WEBSITES

www.adobe.com www.tinaja.com/acrob01.html www.terraserver.microsoft.com www.anywho.com www.icmaster.com	Acrobat readers and PGML info Acrobat independent support Aerial & satellite photos Alternate backwards phone list Alternate chip info source	www6.MapsOnUs.com www.kresch.com www.drms.com us.imdb.com www.tinaja.com/dntkwb01.html	Maps and trip planning Meta search engine site Military surplus electronics Movie reviews Non-technical site favorites
www.drebes.com www.bigfoot.com www.infospace.com www.altavista.digital.com www.tinaja.com/amlink01.html	Alternate people finder Alternate people finder Alternate people finder Alternate search engine Amazon book access	www.ebay.com www.tinaja.com/patnt01.html www.whowhere.com www2.shelf.ac.uk/~chem/web-elements www.tinaja.com/post01.html	Online real time auctions Patent and patenting alternative People finder Periodical table of chem elements PostScript independent support
in-123.infospace.com www.tinaja.com/adv01.html www.tinaja.com/beewb01.html www.netscape.com www.classifieds2000.com	Backwards phone directory Banner advertising secrets Bee's favorite links Best Internet browser Buy or sell a car	www.ups.com www.tinaja.com/webwb01.html www.hotbot.com www.lindsaybks.com www.zakes.com	Real time package tracking Resource links for the web Search engine site Source for "new-old" books Southeastern Arizona ISP
www.tinaja.com/consul01.html www.craftsfaironline.com www.unitedmedia.com/comics/dilbert www.tinaja.com www.questlink.com	Consultant's network Crafts links Dilbert Eclectic computer & electronic info Electronic data sheets & ap notes	www.daztcn.wr.usgs.gov www.etrade.com quote.yahoo.com www.tinaja.com/barg01.html www.tinaja.com/dtekwb01.html	Stream gauge realtime info Stock buy/sell/trade Stock quotes Surplus test equipment Technical web site favorites
www.tinaja.com/eewb01.html www.mohotta.com www.healthy.net www.weavespindye.org www.infind.com	Electronic engineering sites Essential hacker nutrients Free Medline access Handweaving links Inference search engine	www.thomasregister.com www.bsinet.com/map1 www.horizons.com/suremaps www.mediafinder.com www.internic.net/cgi-bin/whois	Thomas registry of manufacturers Topographic map CD ROM's Topographic maps online Trade journal directory Url finder
www.tinaja.com/info01.html www.internic.net datamation.com/PlugIn/jobs/jobs.html www.monster.com www.kbb.com	Infopack research service Internet url registration Job links Job opportunities Kelly Blue Book car values	www.usps.com www.virtualflorist.com www.ghgcorp.com/stilgar/shuttlelinks www.tinaja.com/weblib01.html www.usps.gov/ncsc	US Post Office Virtual flowers Weaving links Webmastering secrets Zip code directory

www.drms.com

This is your main site to go to for military surplus sales. As we've seen, there's all sorts of incredible surplus bargains these days. It is now super easy to bid on the web and pay by VISA. We saw lots of details on the access secrets a few months back in RESBN81.PDF and RESBN82.PDF.

Examples of the gettable goodies are at www.tinaja.com/barg01.html.

For convenience, I've split this site access up into these four hot buttons at www.tinaja.com ...

DRMS1 — DOD stuff for sale
DRMS2 — Preliminary results
DRMS3 — Final sales results
DRMS4 — Master search engine

What I'll personally do is grab the info off the web. Then I print it and stash it in a time ordered box. First the descriptions, then their offerings, and finally a search on items of any special interest. The latter to find their condition and acquisition cost. I will also try to actually inspect their lots when and where feasible. Or have them inspected for me. I'll then worry about and revise the bids for a week before submitting them.

The general object of the game is to buy for a penny on the dollar, sell for a dime, and then try to make a nine percent profit. But lately, I have been bidding far lower. When you win too often, you're paying way too much.

The feds are experimenting with private surplus sales. An outfit called *Levy-Latham* is now handling some of the federal surplus auction offerings.

Be sure to check out their website at www.levylatham.com.

Maps and Aerial Photos

I have long been a topo map freak. Besides having handled my share of underground cave mapping. There's a wide variety of map-related websites that are good and getting better.

Start off with www6.MapsOnUs.com. These folks sell "roadmap" style maps and trip planning routes. I've found them to be exceptionally useful.

I recently got off on the wrong 4WD track near the Galiuro Wilderness. I was utterly amazed to find this trail online, and was quickly able to "fly" on over to the Powers Hill trail I was really looking for. On the other hand, *Maps On Us* seems to refuse to let you go over Mule Creek pass or through the "tunnel" in Lordsburg.

A useful second alternate here is *MapQuest* at www.mapquest.com. Who I have found almost as good.

The actual USGS topo maps are still at their "stumbling first steps" stage. Although I'd expect a superb quality free site shortly. That seamlessly lets you print and map to high res.

Meanwhile, there is a new USGS map site up as *Map One* and found at www.horizons.com/suremaps. This one seems more interested in selling stuff than presenting it online. They seem to have missed the essential fact that web success depends on giving a lot away to sell a little.

Somewhat poorly scanned versions of the USGS maps themselves (sadly with those infuriating borders intact) are sold by www.bsinet.com/map1 and a few others. Prices are around \$16.00 for 64 quads and a viewer.

Yet another "almost but not

quite there" is the outrageously fascinating *Terra Server* image base that's up at www.terraserver.microsoft.com. This one offers free "flyby" topographic and satellite maps. Down to one meter per pixel resolution, even. There are over four terabytes of data here!

But even with the latest additions, the coverage remains limited. It does take a lot of practice to interpret aerial photos. Especially if they are in black and white and lack a stereo viewing. Things sure get confusingly fuzzy and blobby at maximum resolution. But I would expect hires stereo color maps online within a year or two at most.

Runway maps and other pilot info for airports is at www.airnav.com.

These are especially handy if a pilot is going to visit you. But they seem to have left Thatcher International off their list. Probably because there's a few old refrigerators and other minor debris where the runway used to be.

Finally, I have found the USGS real time stream gauge site to be quite interesting. White water folks consider this data essential, while I've found it handy to spot out which remote 4WD crossings are and are not passible. It is also fun watching floods move down through the Gila Valley.

Try out www.daztcn.wr.usgs.gov or some similar page for your state. Be sure to check these out.

Patents

Patents tend to be highly overrated. Since not one patent in two hundred ever shows a net positive cash flow, a patent repository is mostly of, for, and by

losers. Studying patents can (and almost always does) end up as a mind-rotting waste of time.

Nonetheless, there is an intriguing site up at patent.womplex.ibm.com. This one has summaries and full images of most patents back to 1971, along with collections of other IP info.

More on the perils and pitfalls on patents and patenting are found at my www.tinaja.com/patnt01.html. Along with my tested and proven real-world alternatives.

Bee's Favorites

Bee is an unindicted *Guru's Lair* co-conspirator. Her tastes in web sites are wildly different from mine. At any rate, here are some of the sites that Bee uses the most ...

For investments, stock quotes from quote.yahoo.com and the actual trades at www.etrade.com. This one does take a membership and investment. For free medline access, www.healthy.net.

For movies, us.imdb.com.

For timely customer package real time tracking, www.ups.com.

For postal rates www.usps.com. Or their zip code directory over at www.usps.gov/ncsc.

Plus, of course, Dilbert who is over at www.unitedmedia.com/comics/dilbert. Virtual flowers at www.virtualflorist.com. And don't forget the essential hacker nutrients at www.mohotta.com.

Bee is also very much into string bending, so two sites of major interest are a weaving guild at www.weavespindye.org plus the weaving links at www.ghgcorp.com/stilgar/shuttlelinks. Additional craft links of all flavors are found at www.craftsfaironline.com.

There is also the new www.ebay.com auction site. But this one can end up a giant time and dollar sink.

Lots of additional annotated links (similar and otherwise) can be found at www.tinaja.com/beewb01.html.

Plus a Few More of Mine ...

Such as that periodical table of the elements chem info you should find at www2.shelf.ac.uk/~chem/web-elements. Or the extensive job opportunities at www.datamation.com/PlugIn/jobs/jobs.html or at www.monster.com. Or blue book car values at www.kbb.com. Or car sales at www.classifieds2000.com.

Or the good old Thomas Registry at www.thomasregister.com. That web url registration site

TECH FORUM

CONTINUED FROM PAGE 73

up at www.internic.net. Or their Whois site finder service up at www.internic.net/cgi-bin/whois. Or the people finders at www.whois.com. At www.drebes.com. At www.bigfoot.com. Or at www.infospace.com.

More of my favorites are found at www.tinaja.com/dtek-wb01.html or at my www.tinaja.com/dntkwb01.html.

For More Info

Annotated links to many hundreds of other useful web sites are found on various pages of my www.tinaja.com. I also have a service where I can do fee-based research for you. Web centered or otherwise. Many times I can find better and more useful answers a lot quicker than you might by yourself. See www.tinaja.com/info01.html.

We also have a unique consultant's network of individuals which I can personally recommend for just about any technically related task. You will find their links and capabilities up at www.tinaja.com/consul01.html.

There's also my US no-fee helpline service as noted below.

This Month's Contest

As our contest for this month, just tell me about your favorite web site and why you like it.

There'll be a dozen or more of my new *Incredible Secret Money Machine III* books going to the better entries. Plus an all expense paid *tinaja quest* for two (FOB Thatcher, AZ) going to the very best of all.

Send your written and snail-mailed entries on this contest directly to me here at Synergetics. Let's hear from you. **NV**

Microcomputer pioneer and guru Don Lancaster is the author of 35 books and countless tech articles. Don maintains his no-charge US tech helpline found at (520) 428-4073, besides offering all of his own books reprints, and consulting services. Don also offers a free catalog full of his unique products and resource secrets. The best calling times are 8-5 on weekdays, Mountain Standard Time.

Don is the webmaster of his Guru's Lair found at <http://www.tinaja.com>. Full reprints and preprints of all Don's columns and ongoing tech support appear here. You can reach Don at Synergetics, Box 809, Thatcher, AZ 85552. Or send any messages to don@tinaja.com.


Now, when you connect your sensor's signal to pin #3 of the LM 358, a signal 10X as large will appear at pin #1.

Thomas Ng
San Jose, CA

ANSWER TO #129816 - DEC. 1998

You can use an analog voltmeter to retrieve the trouble codes from the on-board computer. The diagnostic connector and voltmeter hook-up varies with the model and year.

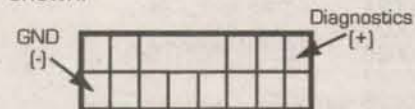On the Galant, Starion, Van, Montero V6 (1987 and 1988) and all models 1989 and on, the diagnostic connector is in or under the glove compartment. To retrieve trouble codes, connect the meter as shown.



On 1983 to 1986 models, the diagnostic connector is located under the battery tray or the right side firewall near the computer.

On the Mirage Turbo (1987/1988), connect the meter to a good ground and the single connector on the firewall near the set timing connector.

Turn the ignition on and watch the voltmeter, count the number of sweeps. The meter will sweep every 2 seconds in a 10 second period. The codes can be determined as follows:

00000 = 0
10000 = 1
01000 = 2
11000 = 3 etc.

This is based on the binary numbering system.

You should consider buying a scanner instead of trying to build one. The two companies most likely to have a scanner to fit your needs are: **OTC Tools**, 655 Eisenhower Dr., Owatonna, MN 55060. Or **Snap On Tools, Inc.**, Kenosha, WI 53141-1410. Phone number is 414-656-5200.

Dennis Gifford
Henagar, AL

ANSWER TO #129810 - DEC. 1998

The FUJITSU M2312K disk drive is [according to the FUJITSU CE manual] an 84MB SMD disk drive. Transfer rate is 1.229 MB/sec. It requires +5, +24, and -12 volts.

Digital Equipment Corp., Prime Computer, Data General, and many other manufacturers used them either as OEM drives, or third-party companies made controllers to use them with the previous computer manufacturers.



I have two of them hooked to a DEC 11/73 computer, and they make quite a bit of noise and heat.

Joe Heck
Wrentham, MA

Digital Storage Oscilloscopes

From \$189?

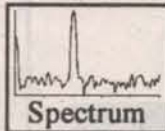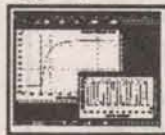ATC modules connect to your PC printer port and transform it into a full-function DSO, spectrum analyzer, logger, & DVM. Units DC to 25MHz



Captured Waveforms
Pico Tech
ADC-200 in
Windows

O-Scope II
in DOS



ATC proudly announces the addition of Pico Technology Ltd. products to our product line. Pico is based in Britain and offers a variety of data logging and virtual instrument modules.

O-Scope Ip (ST 50KHz).....\$189
O-Scope II (DT 500KHz).....\$349
ADC-100 (DT 12bit 50KHz)..... \$449
ADC-200/20 (DT 10MHz)....
ADC-200/50 (DT 25MHz)....
Loggers 1-22 ch. (8-16 bit) from \$99
Shipping UPS \$7.50 grnd, \$11.50 (2 day)

CALL

800-980-9806
Allison Technology Corporation
2006 Finney Valley Rd., Rosenberg, TX 77471
Fax: 281-239-8006 Technical: 281-239-8500
E-Mail: atc@accesscomm.net
<http://www.atcweb.com>

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

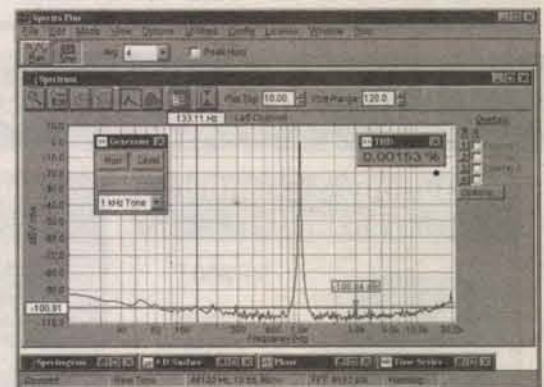- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only - not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

Spectra Plus
FFT Spectral Analysis System

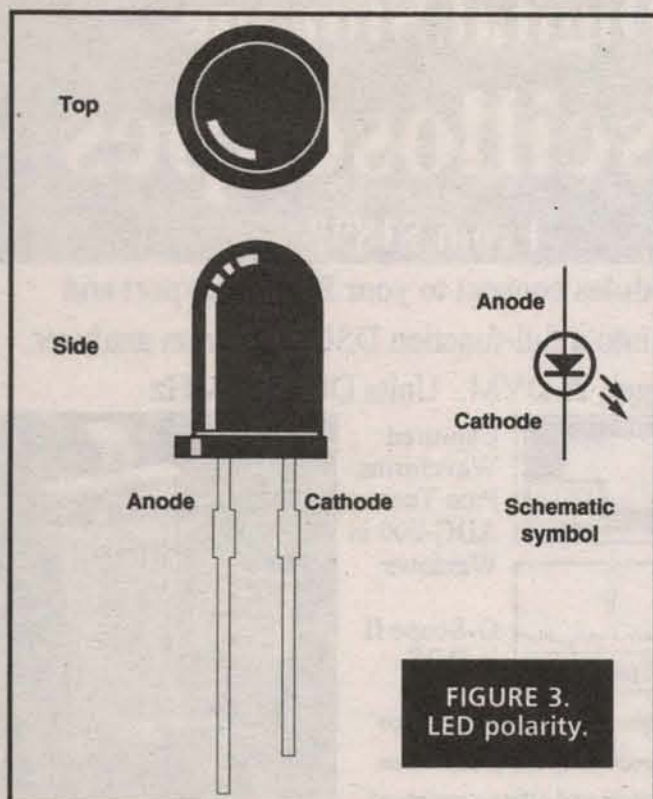


FIGURE 3.
LED polarity.

ing you so the SIMMStick's notch is to the lower left, C1 goes in the upper left corner of the board just above C5; C2 goes to the right of J1.

When you've completed the power supply section of the DT101, apply 9V to SS-Bus pin 4 and ground to pin 9. First, test the voltage at the output of the voltage regulator, then at pin 14 of E1, and finally at pin 7 of the SS-Bus; you should read a nice, clean +5V at all three points.

If any of these tests fail, go back and check your solder joints and check continuity of the board against the schematic. In particular, make sure you have continuity between E1 pin 5 and SS-Bus pin 9 (the ground connections) and then between E1 pin 14 and Vdd

(the +5V supply). Verify power and ground connections for all the options you install. A good way to do this is to use a highlighter and a photocopy of the schematic; highlight each connection as you probe them out on the board until you either find a problem or you run out of circuit board traces.

Reset Circuitry

The minimum reset circuitry consists of two 10K ohm resistors R1 and R2; in the absence of other reset circuitry, they function as a 20K pull up

```

LOC OBJECT CODE  LINE SOURCE TEXT
VALUE

00001 title "test1 - Poll a Bit"
00002 ;
00003 ; Constantly polls input bit for switch closure, indicates result with LED
00004 ;
00005 ;
00006 LIST P=16F84, F=INHX8M, R=DEC
00007 errorlevel 0,-305
00008 INCLUDE "pic\mpasm\16F84.inc"
00009 LIST
00010 ; P16F84.INC Standard Header File, Version 2.00 Microchip Technology, Inc.
00011 LIST
00012 ; Configuration Registers
00013 ;
00014 ;
00015 ;
00016 org 0
00017 ;
00018 bsf STATUS, RP0
00019 bcf TRISB & 0x07F, 0 ; Set RB0 to Output
00020 bcf STATUS, RP0
00021 ;
00022 wait_ON
00023 btfs PORTB,7 ; Wait for switch press
00024 goto wait_ON
00025 ;
00026 bcf PORTB,0 ; Turn LED ON
00027 ;
00028 wait_OFF
00029 btfs PORTB,7 ;
00030 goto wait_OFF ; Wait for switch release
00031 ;
00032 bsf PORTB,0 ; Turn LED OFF
00033 ;
00034 goto wait_ON
00035 ;
00036 end
  
```

on the MCLR or Res, SS-Bus pin 8. In addition to these two resistors, you can install a reset IC. Note 1 in Figure 1 gives a list of optional brownout voltage detector reset ICs that will work for this board. While strictly not required — my DT101 worked fine without one — I find these reset chips to be quite valuable in that they increase reliability and predictability of the reset action, and I plan to install them in all future boards.

When a reset chip is installed, R2

serves to limit current at the OUT pin of the reset IC, especially for CMOS versions with an active pull up, such as the Panasonic MN1381-S; for open collector versions, R1 functions as the pull up resistor.

While you are soldering in the above reset pull up and current limiting resistors, you might as well solder in R3, too. It pulls the MCU's RTCC input high so the pin doesn't float, leading to possible spurious counts at the RTCC input.

To test these components, measure the resistance between SS-Bus pins 7 and 8 (between Vdd and Res) without power applied to the board; it should read about 20K ohms. If you have installed one of the brownout reset ICs, measure the voltage at SS-Bus pin 8 while gradually increasing a variable DC input at SS-Bus pin 4 (Vin) from 0V to 9V. The Res line should stay low until Vin reaches somewhere above 4.5V, at which point it will jump up to about the same level as Vdd. If you temporarily tie the Res line low, pin 4 of E1 should also drop low, regardless of the voltage at Vin.

Oscillator Section

The oscillator section is just two 15pF capacitors, C4 and C5, and a 10-MHz crystal. If you choose to use a three-lead ceramic resonator with built-in load capacitors, you don't need C4 and C5. In any case, make sure that the load caps (built-in or external) are between 15pF and 33pF to ensure reliable oscillator start-up.

Finish up the SIMMStick hardware by plugging in a programmed PIC16F84, and you're all set.

What? You don't have a pre-programmed F84? Check out the December '98 "Amateur Robotics Notebook" for PIC programmer resources. As I said then, I use two dif-

Miniature Transmitters and Receivers

2 Button / 3 Channel Transmitter



RF300T

1...\$22.95
5...\$19.95 ea
10...\$16.95 ea

RF300XT

1...\$25.95
5...\$22.95 ea
10...\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

4 Button / 15 Channel Transmitter



RF304XT

1...\$27.95
5...\$24.95 ea
10...\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

2-4 Data / 3-15 Channel Receivers



RF300RL
RF300RM

1...\$27.95
5...\$24.95 ea
10...\$22.95 ea

RF304RL
RF304RM

1...\$29.95
5...\$26.95 ea
10...\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454 Email: Support@Visitect.Com
P.O. Box 14156, Fremont, CA 94539 Visa / Mastercard, COD

ferent parallel port programmers — the DonTronics DT001 and the Parallax PIC16Cxx-PGM; I use these with Igor, the 386 DOS machine I keep chained up in my basement.

The DT001 can be configured to program individual chips, to program SIMMStick boards in-circuit, or to function as a SIMMStick motherboard, with lots of expansion connectors and an RS-232 communications port. It comes as a bare PC board directly from DonTronics in Australia or from any of the numerous SIMMStick distributors worldwide. It costs about \$75.00 US to build if you install all the many options DonTronics has provided.

The Parallax PIC16Cxx-PGM costs a bit more than the DT001, but it comes already built and can handle a wider range of PIC chips, including the older 12-bit core family, which uses a different programming method than Microchip's newer PICs. It's available in a "Hobbyist Pack" for \$109.00 US from Digi-Key.

If you use the Parallax programmer, you'll be using Parallax's own programming software, which is well described in the manual that you can download from their website. If you've never built a microcontroller system before, you may want to go this route just so you have one less piece of hardware to debug.


To use the DT001 as a programmer, you will need to download an appropriate version of Nigel Goodwin's PIC84PGM software. You can find all his versions for DOS and Windows at: <http://www.lpilsley.demon.co.uk/programs.htm>. You can also find the software at DonTronics at <http://www.dontronics.com/download.html>. The latest version of the DOS software is at <http://www.dontronics.com/zip/picprog2.zip>.

The DOS screen capture shows the various menu options for the PIC84PGM software. Use "M" to toggle between the PIC16C84 and the PIC16F84 (you want the latter), "H" to load your hex file, and "P" to program the chip. Easy. Unless your parallel port doesn't want to talk with PIC84PGM.


This happened to me. For some reason, Igor's parallel printer port wasn't recognized by PIC84PGM. Installing a cheap \$13.00 parallel port card in Igor solved the problem. Be sure to read all of Goodwin's documentation, too, because he has a couple command line switches that invoke debugging modes of PIC84PGM to help troubleshoot parallel port problems. "/D" turns on a debugging mode that shows program initialization details, in particular the PICPROG.CFG setting. Another handy debugging mode is the "/T" test mode option which helps sort out problems with the connection between the parallel port and the programmer.

Igor, Bring in the Hex!

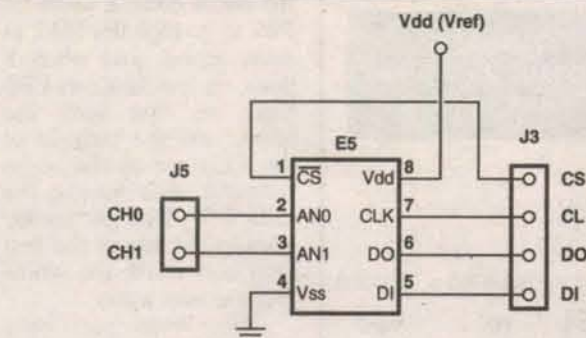
None of the above will do you any good if you don't have a .HEX or .OBJ file to load into the program buffer. TEST1.ASM is a simple test program to exercise the DT101 hardware, and TEST1.LST shows this same file after it's been assembled by MPASM. I've



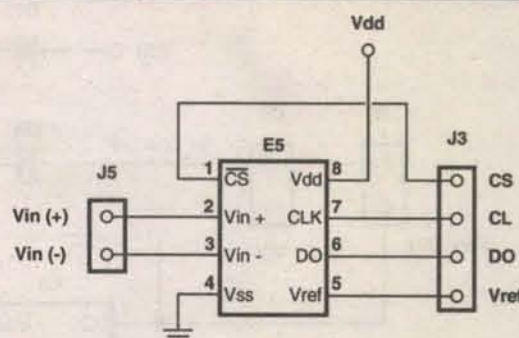a: Serial A/D converter, dual channel option



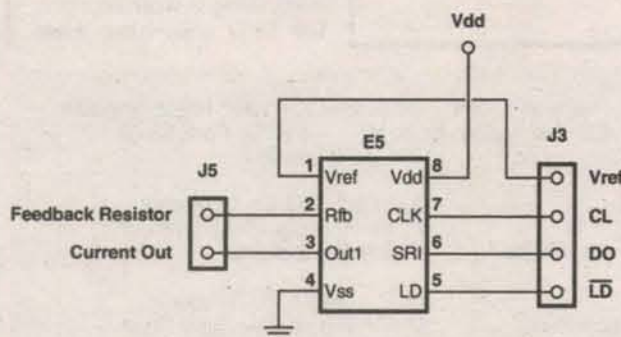b: Serial A/D converter, differential input option



c: Serial D/A converter option

FIGURE 4. DT101 ADC & DAC options.

Serial ADC chips:

National	ADC0832	8-bit, 2-channel
National	ADC0831	8-bit, 1-channel, differential input
Linear Tech	LTC1298	12-bit, 2-channel
Linear Tech	LTC1292	12-bit, 1-channel, differential input
Linear Tech	LTC1297	12-bit, 1-channel, diff. input, w. low power auto-shutdown

Serial DAC chips:

Linear Tech	LTC8043	12-bit, multiplying current output DAC
Linear Tech	LTC1595	16-bit, multiplying current output DAC

been using both the Parallax assembler and Microchip's MPASM for my PIC development work, but here I'll just talk about MPASM.

MPASM is available for free download from the Microchip website ("asm22000.zip" is the file you want). It comes with all the INCLUDE files for every PIC Microchip makes; this means you don't have to retype all of the register names and equates; for working with the PIC16F84 chip, you just include the P16F84.inc file in your source file (see line 8 of TEST1.LST).

While you're visiting the Microchip site, you might also want to download MPSIM, a software PIC simulator. This program has a horrible user interface (more about that next time), but it is free and it runs under DOS so computers like my Igor can handle it. For those of you running Windows (the majority, I suppose), you

might want to try MPLAB, instead. It does everything that MPASM and MPSIM do (and quite a lot more), it's also free, and the MPLAB simulator interface is far superior to MPSIM. The point is, you need to get yourself set up with one or another of these packages.

This is Only a Test ...

The simplest blinky light program uses great gobs of time delay loops to make the LED change state slow enough that the human eye can perceive the blink. Another, only slightly more complicated system, is a program that causes the LED to turn on and off in response to an external input, say, a switch. The software is actually simpler to write for this one, and the extra hardware is just a switch and a pull up resistor, so that's what I've used (Figure 2). The code for this


is easy (see TEST1.ASM).

If you've never worked with assembly language before, TEST1.ASM may seem quite daunting. It's really quite simple, though. I'll use the TEST1.LST file to show, line-by-line, what's going on.

Lines 1 through 5 are just title and comments, all of which the assembler ignores when producing code; they're just there to help you, the programmer, keep track of what you're doing. Line 6 tells the assembler that we want to use the PIC16F84 chip, that we want the output file (the ".HEX" file) to be in the form of an eight-bit Intel Hex format (nevermind, trust me), and that we want to use decimal numbers as the default. Line 7 sets up which types of error messages will be displayed during assembly. Line 8, as I said above, includes the standard equates and goofy register names that Microchip

ADDRESSABLE STEPPER MOTOR CONTROLLER

Part Number: JWP1X-1A
\$199.95

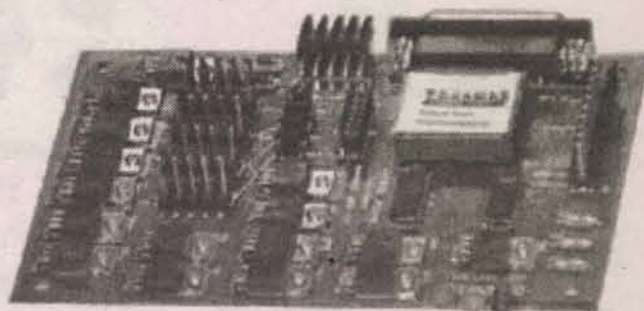

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data throughput rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

Also available at:
FORD ELECTRONICS, INC
(714) 521-8080

PARAMAX INC.
(800) 473-8080

Come and visit us on the internet at:
www.paramax.net

In Volume 1, you build his Charcoal Foundry with which you learn to make aluminum castings in green sand molds. Volume 2 — The Metal Lathe — details how you use those aluminum castings from the foundry to build a precision bench-top metal-cutting lathe with a 7" swing and 12" between centers. You then use the lathe and the foundry to build practically everything else required for a fully-equipped machine shop, including The Metal Shaper in Volume 3; The Drill Press in Volume 4; the Milling Machine in Volume 5; and Dividing Head & Deluxe Accessories in Volume 6. Volume 7 — Sheet Metal Brake — doesn't require the lathe or other tools of the earlier volumes, though it does require some welding and simple drilling.

Can you build a whole metal-working shop from scrap? Well, Dave Gingery has done it, and so have quite a few others. The only precision tool Dave used for building his first lathe was a blade-type feeler gauge, yet that

same lathe holds to within 0.001" taper an eight-inch piece of stock, pretty impressive for a \$50.00 home-made lathe!

Many others have built Gingery machines, too, just by following his directions. I know, I've talked with some of them. Gingery isn't a professional machinist or a foundryman, and you don't need to be either to use his books to build your own machine shop. Gingery's a dedicated amateur who likes to build precision machines, be they lathes or steam engines, and I think robot builders can get a lot of insight from his books. The whole seven-volume set costs about \$60.00, but none of the individual books cost more than \$10.00 US, so you can check them out one at a time, if you want. By all means, though, at least get "The Charcoal Foundry," because that is the foundation from which the rest of the series builds.

That's it. Next month, I'll continue with the DT101 brain transplant, with a few surprises thrown in. NV

Item	Description	Vender	P/N
C1,C2	0.01µF 50WV, 5%, polyester	Digi-Key	P4582-ND
C4*,C5*	15 pF 5% monolith ceramic cap	"	P4839-ND
C5,C6,C7,C8	1µF, 16V tantalum	"	P2105-ND
D1,D2	Schottky diodes (see Figure 5)	"	11DQ03-ND
E1*	10 MHz PIC16F84 MCU	"	PIC16F84-10/P-ND
E2	24LCXX I2C EEPROM	"	
E3	RS-232 level converter	"	MAX232CPE-ND
E4	Real-Time Clock option (see Figure 5)	"	
E5	ADC/DAC option (see Figure 4)	"	
J1,J2,	2-pin single row straight pin header	"	929647-02-36-ND
J5-J7	4-pin single row straight pin header	"	
J3,J4	J1-J7 above are cut from 36-pin pin header	"	
J8*	30-pin single row, RA pin header	"	S1111-30-ND
R1*,R2*,	10K ohm	"	10KQBK-ND
R3*,R4,R5	Reset Voltage Detector, 4.5V, CMOS	"	MN1381-S-ND
RVD	DT101 or DT111 SIMMStick	Wirz Elex	DT101 or DT111
PCB*	+5V positive regulator, 100 mA,	"	
VR1	TO-92	Digi-Key	NJM78L05A-ND
XTAL1*	10 MHz crystal, HC49/US case	"	X422-ND
XTAL2	32.768 KHz (see Figure 5)	"	
Misc:	8-pin DIP IC sockets	Digi-Key	ED3308-ND
	16-pin " " "	"	ED3316-ND
	18-pin " " "	"	ED3318-ND
	Shorting jumper (to isolate +5V from Vdd)	"	SPC02SYAN

* Required components; see text & figures.

RESOURCES MENTIONED IN THIS ARTICLE:

Dallas Semiconductor
4401 South Beltwood Parkway
Dallas, TX 75244-3292
Tel: 1-972-371-4448
Fax: 1-972-371-3715
www.dalsemi.com
(Serial RTCs, temp. sensors, batt. monitors)

DonTronics
P.O. Box 595
Tullamarine 3043
Australia
Tel: 613+9338-6286
Fax: 613+9338-2935
dontronics.com
(SIMMStick PC boards, development systems, & software)

Lindsay Publications
P.O. Box 538
Bradley, IL 60915-0538
Tel: 1-815-935-5353
Fax: 1-815-935-5477
www.lindsaybks.com
(Unusual technical books on metalworking and other subjects)

Linear Technology Corporation
1630 McCarthy Blvd.
Milpitas, CA 95035-7417
Tel: 1-800-454-6327, 1-408-432-1900
Fax: 1-408-434-0507

www.linear-tech.com
(Serial A/D & D/A converters)

Microchip Technology, Inc.
Tel: 1-888-628-6247, 1-602-786-7200
Fax: 1-602-899-9210
www.microchip.com
(PIC chips, PICSTART development systems, MPASM assembler, MPSIM simulator, serial EEPROMs)

National Semiconductor Corp.
2900 Semiconductor Drive
Santa Clara, CA 95052-8090
Tel: 1-800-272-9959
TWX: 1-910-339-9240
www.national.com
(Serial A/D & D/A converters)

Parallax, Inc.
3805 Atherton Road, Ste. #102
Rocklin, CA 95765
Tel: 1-800-512-1024, 1-916-624-8333
www.parallaxinc.com
(PIC16Cxx-PGM programmer, SX-Key debugger/programmer, BASIC Stamps)

Wirz Electronics SIMMSticks
P.O. Box 457
Littleton, MA 01460-0457
Tel: 1-888-289-9479
Fax: 1-978-448-0196
www.wirz.com
(SIMMSticks, SLI serial LCD interface, kits)

Credit Card FINANCING

2 Easy Payments of
\$29!
97 Edition

2 Payments of
\$29!
back issue, Perfect for Service & Experimenter

\$195
Publisher

IC MASTER
97 ICM CD
2 Easy Payments of
\$75!!

\$115
Publisher

\$235
Publisher

2 Easy Payments Any Product

Complete Catalogs of ALL Major Component Manufacturers

2 payments of
\$29
97 EEM CD

2 payments of
\$44
98 EEM CD

2 payments of
\$75
97 ICM CD
for Moderate Design Work

2 payments of
\$65
97 ICM Books

2 payment of
\$52
96 ICM Books
for Service or Lite Design

2 payments of
\$99
98 ICM CD
for Advanced Design Work

Save Time with "REFEREE"

#1 Choice of Service Centers

CROSS
REFERENCE
& SPEC

Quarter Million

Transistors,

ICs & Diodes

A Specialist in "Hard to Cross House Numbers"

Easy, Powerful & Fast.

The Most Comprehensive Software Sold.

A selection yields Device Specifications & 75 to 250 Potential Replacements!

Replacement Numbers are Totally Global including Domestic, Asian, European, House

Branded, as well as ECG, NTE, SK & GE. Displays Case Drawings, Lead

Configuration & Pin-outs for many Devices. Coverage of Replacement Numbers

is Very Impressive. 7 Disk Set (17 Meg decompressed) For DOS, Win3.1 & 95

Latest Version 7.11 Includes Many Helpful Conversion Utilities, Tables & Formulas.

Includes: 4 HUGE Consumer Electronics Industry Directories

1- Consumer Electronics Parts Sources (Service) 2- Consumer Electronics Manufacturers

3- The Entire Computer Industry 4- Semiconductor Manufacturers

Perfect for Service, Engineering and Purchasing.

Shop the way the Pro's do, Use Their Tools!

These are the books that find the "Gold". For many years they've been used by the

Sharpest Purchasing Agents. Look under every rock...they're impossible to find

at ANY price, let alone a great deal like this. Find: Distributors, Manufacturers

and Service providers for Products, Services or ANY Component Parts

imaginable. Sources for Everything from Gears to Semiconductors to Foreign

Assembly Services.

WOW 2 easy payments of
\$282!
0% Financing!
On Credit Cards only

the Perfect Gift
Only a few left:

2 Payments of
\$282 Compaq 486 DX4-100
16m - 710m - 10.4"ds - W95 - PCMCIA

2 Payments of
\$379 Compaq Pentium 90
16m - 810m - 9.4"Active - PCMCIA

may differ slightly from illustration

2 Easy Payments of

49!

Single payment of
\$25

Parts Sources

Library

Best Kept Secrets


Complete Library

Huge

All Cards & COD Int'l orders email: netcomd@aol.com FAX 516-826-7776
Netcom 800-733-3733 ext 6300 516-826-1808 10-9 EST 7Days

A/D CONVERTERS with SERIAL OUTPUT

Tiny (1.75"x1.41") fully assembled and tested printed circuit board includes two 8-bit A/D converters and one digital input. Up to 16 units addressable (DIP switch setting) totalling 32 converters on a single serial port. Output is ASCII encoded bit count (0 to 255) at 2400 BPS via RJ-11 interface. Fully programmed PIC16C71 installed in IC socket. Sample software in BASIC included. Requires 8-28Vdc At 1-2mA. *\$49.95*. Optional DC adapter \$19.95. Add \$5.00 shipping.

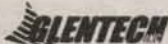

Tele: 847-891-2584
Fax: 847-891-2587
www.glentech-rf.com

SURPLUS SALE

1,000,000 WALL TRANSFORMERS



3VDC/100MA CX099 \$0.75
6VDC/100MA CS039 \$1.45
9VDC/100MA CR314 \$1.45
12VDC/200MA CS033 \$0.99
13.5VAC/400MA.. CR574 \$1.29
24VDC/500MA CR174 \$3.40

Min 1000/type -- Call for other types

SURPLUS TRADERS

PO Box 276,
Albany, VT 05440
Tel: (01) 514-739-9328
Fax: (01) 514-345-8303
http://www.73.com/w

FREE CATALOG!

PROGRAMMERS

ADVANTECH EETOOLS NEEDHAM DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX
629 ICE TECH MICROV 795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUP/R
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUP/R
509 EETOOLS MEGAMAX4 49 EPROM 1G to 512K
369 XELTEK SUPERPRO II 69 EPROM 1G to 1MEG
409 XELTEK SUPERPRO II P 99 EPROM 4G to 1MEG
249 XELTEK SUPERPRO L 199 EPROM 16G to 1MEG
165 XELTEK ROMMASTER II 89 EPROM 1G to 8MEG
479 MOD-MCT-EMUPA 129 EPROM 4G to 8MEG
739 STAG ORBIT-32 250 EPROM 8G to 8MEG



General Device Instruments

Sales 916-393-1655 Fax 916-392-4949
Web www.generaldevice.com E-Mail icdevice@best.com

BATTERY — YUASA



Sealed Lead-Acid/Gel-Cell
12V: 7AH \$19, 2.3/4AH \$16
18AH \$39, 1.2AH \$13
6V: 4AH \$9, 10AH \$13

Quantity Discounts Available
Call for other models

Aventrade

4518 Temple City Blvd., Temple City, CA 91780
Tel. 626-286-0118 Fax 626-287-9618
E-Mail: sales@aventrade.com
www.aventrade.com

Serial Problems???

Use your PC compatible desktop or laptop computer to debug serial communications problems with Serial, our test tool for serial communications.

Serial works with the standard data rates and asynchronous serial formats commonly found in modern office and industrial environments. Suitable for development, service work, and end-user problem diagnosis.

- Easy to Use
- Menu and Windows
- Highly Configurable
- Contextual Help
- Autobaud Detect
- Time Stamping
- Custom font editor for EGA/VGA Screens
- Saves Configurations
- Extensive Manual
- Block transmit ability
- CRC/LRC generation

Serial, with manual \$99.95
Cable for full duplex monitoring \$49.95

For Orders and Inquiries Call: 1-800-980-9806

Allison Technology Corporation

2006 Finney Valley Rd., Rosenberg, TX 77471
281-239-8500 • 281-239-8006 FAX

GET IT UP BEFORE WINTER!

MARCONI ANTENNA 700W 50 Ω
THE BEST "LITTLE" LOW BAND ANTENNA

EASY TO INSTALL.
— 160M —
130' OVERALL
\$63.95 PP
— 80M —
67' OVERALL
\$46.95 PP

THE OCR, AN OPTICALLY COUPLED REGEN. IS AN EXCEPTIONAL REGEN RECEIVER KIT. EASY TO ASSEMBLE (SEE QST JUNE 98) \$91.95 PP

SEND FOR FREE CATALOG:


- SMART BATTERY CONTROLLER KITS
- CODE PRACTICE OSCILLATOR \$23.45 PP
- CURTIS KEYSER KIT \$46.95 PP

1-800 JADE PRO (523-3776)

www.jadepro.com/
email: jadepro@jadepro.com
JADE PRODUCTS INC. E HAMPSHIRE NH 03828-0368

PCB's in Minutes From LaserPrint!*

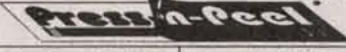8 1/2" x 11" Sheets * Or Photocopier Use household iron to apply.



PnP BLUE or PnP WET

- For High Precision Professional PCB Layouts
- 1. LaserPrint
- 2. Iron-On
- 3. Peel-Off
- 4. Etch

Adds an Extra Layer of Resist for Super Fine Lines on Std Clad Bds

205h\$30/405h\$50/1005h\$100 Blue/Wet (No Mix)
Sample Pack 5 Shets Blue + 5 Shets Wet \$80
VISA/MC/PO/CH/MO \$4 S&H -- 2nd Day Mail

Techniks Inc. P.O. Box 463 Ringoes NJ 08551

(908)788-8249

100% Money Back Guarantee-Dealer Inquiries Invited

Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to 1,000 feet, at up to 1 MEGA-BPS, full or half duplex, up to 32 units on one serial link, with 31 jumper options for flexible configuration, LED indicators.



COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

R.E. SMITH

(513) 874-4796
4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011
www.rs485.com

TV 85 PJ & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE
VOICE 1-800-473-0506
FAX 1-800-488-0525

FOSS
WAREHOUSE
DISTRIBUTORS
285 Schenck St.
N. Tonawanda, NY 14120
www.fossw.com

PCBs
PER SQIN
\$100.00 SETUP
WE SPECIALIZE IN SINGLE SIDED, 1 OZ, PC75

PCB
LAYOUT
PER COMPONENT PIN \$100.00 MINIMUM

ENGINEERING
DIAGRAMS
PER COMPONENT PIN \$100.00 MINIMUM

V&V MACH. & EQUIP., INC. (HOUSTON, TX OFFICE)
PH (281) 397-8101 FAX (281) 397-6220
MARKETING TECH. S.A. (MEXICO/PLANT)
PH 011 (525) 361-3351 FAX 011 (525) 361-5996

Peltier Junction



WITH HEATSINK AND LEADS
\$10 EACH
OR THREE FOR \$25

SHREVE SYSTEMS
318-424-9777
Ask for Jake

RGB Color Composite Displays ON SALE!



*refurbished with 90-day warranty
ONLY \$79!!
Excellent for studio, lab or surveillance applications
640x480 resolution, RCA-style connectors

Returns subject to a 15% restocking fee. Prices are subject to change without notice.
WE ACCEPT VISA, MASTERCARD, AMEX, DISCOVER
HTTP://WWW.SHREVEYSTEMS.COM

Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.

RING-IT! TELCO SIMULATOR
• Single Line (two RJ-11 Jacks)
• LED Display
• DTMF Operation
• Automatic Ring-up Mode
• \$325 (\$149 kit available)

PARTY-LINE TELCO SIMULATOR
• Six Extensions
• Caller-ID (Name/Nbr)
• Distinctive Ringing
• \$425 (\$199.95 kit avail)

Digital Products
COMPANY

134 Windstar Circle
Folsom, CA 95630 USA
Tel: 916-985-7219
Fax: 916-985-8460

http://www.digitalproductsco.com

ADAPT-11 & ADAPT-12 Low-cost modules for HC11 & HC12 plug into solderless breadboards

- Evaluate your idea instantly!
- Breadboard it, for quick hardware changes
- Program it in-circuit, for quick software changes
- Debug your application-- not the basics!

ADAPT-11 Modules feature three 8-bit I/O ports, SPI, SCI, eight 8-bit analog input channels, hardware timers/counters, & interrupts. All Starter Packages include PC serial download cable, documentation, & disk of utilities & examples. Bundle ImageCraft C for Windows (ICC11) with any Starter Package for an additional US\$120 + \$5 S&H.

HC11 Starter Package Configurations:
AD11-SP 2K EE/256 bytes RAM US\$ 74.95 + \$5 S&H
AD11C75-SP 8K EE/512 bytes RAM US\$ 87.00 + \$5 S&H
AD11C750X-SP 8K EE/32K bytes RAM US\$120.00 + \$5 S&H
AD11-SP64K ADAPT-11 w/ 32K EE/32K RAM memory expansion card & dual slot adapter (2 I/O ports lost) US\$123.00 + \$5 S&H

ADAPT-12 features 68HC12A4, 1K EE, 1K RAM, 85 I/O lines, eight high speed 8-bit analog inputs, memory expansion connector, RS232 & RS485, convenient firmware bootloaders, plus support for all BDM pods. All this on a compact 2.25" x 3.25" board. Starter Package (AD12-SP) US\$99 + \$5 S&H. Add US\$125 for ICC12WIN. AVAILABLE SOON! ADAPT-12 features 68HC12B32 (32K Flash, 768 EE, 1K RAM, 56 I/O lines, 8 chan. analog), RS232 and RS485. All this and more on a compact 2.25" x 3.25" board! Starter Package (AD12-SP) US\$99 + \$5 S&H. Add US\$125 for ICC12WIN.

TECHNOLOGICAL ARTS
voice/fax: (416) 963-8996
www.interlog.com/~techart

PIC PROJECTS Book & CD-ROM

Many PIC Projects for Beginners & Experts!
Includes Software, Documentation, and PCB Layout

- LCDs
- X10 -- Home Automation
- Keypads
- Serial Port Interface
- On-Screen Displays
- Robotics
- Data Logging
- Serial-Parallel
- And Many More!

Book & CD Only \$29.95

PIC Programmer
Programs all PIC16C55x/6x/7x/8x/9x, PIC16F8x, and PIC12C devices. Optional ZIF adapters for SOIC & PLCC. Includes all necessary software. Only \$39.95

We accept VISA • MasterCard • American Express
To order, call Worldwide @ 1-800-773-8898
21365 Randall Street • Farmington Hills, MI 48336
Visit us on the web at www.worldwide.com/plc

VIDEO CHARACTER OVERLAY GENERATOR

New BOB-II superimposes up to 308 characters on standard video or generates video. 30-pin SIMM design, RS-232 interface, easy to use for:

- Video Inspection - NDT
- Home Automation Display
- ATV - CCTV Security - CATV
- Remotely Piloted Vehicles
- Gaming - Racing - Sports
- Process/Experiment Monitor
- Robotics - Electronic Signs

Single units only \$79.95

DECADE ENGINEERING

5504 ValView Dr. SE, Turner, OR 97392
Tel: 503.743.3194 ~ Fax: 503.743.2095
mikeh@decadenet.com ~ www.decadenet.com

RESISTORS

SPECIALS FOR ENGINEERS, TECHNICIANS, HOBBYISTS, SCHOOLS, ETC.

5,000 1/4W 1-5% metal & carbon film. 50 each of **100** standard values (our selection of values) \$45.00 (less than 1¢ each).

10,000 1/4W 1-5% metal & carbon film. 50 each of **200** values (our selection of values) \$95.00 (less than 1¢ each).

OR: You select the values and the quantity of each. Minimum of each value 50 pieces. Minimum order \$50.00. 5% - 1¢ each/1-2% - 2¢ each.

Shipping and tax included. Each value clearly marked for ID. Over 500 values available from a stock of millions. Groups put your order together and then split the cost.

HYATT ELECTRONIC SURPLUS

371 N. JOHNSON AVE., EL CAJON, CA 92020

TEL: (619) 444-2434 FAX: (619) 444-1987

ATTENTION DEALERS

WHOLESALE ONLY!

• ANY CABLE MFRG CONVERTERS & ACC

• BEST PRICING & SERVICE

• SHOP US **NOW**

PANASONIC • NOVA, ETC.

800-777-7731

ATOMIC TIME FOR ANY COMPUTER

WWVB based time code receiver and real time clock with RS232 interface

FEATURES

Sensitive receiver
Direct UTC readout in ASCII
Y2K compatible calendar
0.1 second accuracy
RS232 powered
Low cost

APPLICATIONS

Remote data acquisition
Embedded systems
Automatic sequencers
Tamperproof time stamping

ULTRA LINK

702 782 9758 www.ulio.com

EPS EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	87S1
2732A	27C4096	28F020	87S5
27C32	574000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C62
27C512-90	27C010	8744	GAL16V8

STATIC RAM

HM628128
62256
6264
6116

PROCESSOR

8255
8254
80C31

MEMORY
D-RAMS
SIMM

• Many more parts in stock
• All major brands
• All guaranteed
E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822

WE BUY EXCESS INVENTORY

FREE SAMPLE COPY! ANTIQUE RADIO CLASSIFIED

Antique Radio's Leading Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)

6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23
Carlsle, MA 01741
Call: 978-371-0512 • Fax: 978-371-7129
Web: www.antiqueradio.com

TOGGLE SWITCHES — All sizes, all types

LEDs — 1.8mm to 10mm all colors, shapes & intensities

MINIATURE LAMPS — for all applications

HOOK-UP WIRE — 18 to 26 gauge, 10 colors

SMALL ELECTRIC MOTORS — 3 to 12 volt

SOCKETS & PLUGS

DEMAR ELECTRONICS

P.O. Box 7215, Algonquin, IL 60102

Toll Free 877-655-6433

Fax 847-854-4434

Call or Fax for Quotes

Catalogs Available

CUT MANUFACTURING COST!

CUSTOM METAL BOXES
WE ACCEPT SMALL ORDERS TOO

SHEET METAL

20 GAUGE

SILK SCREEN

PRINTED

WITH YOUR CO. NAME

ALSO PCB, SMT, PROTOTYPES, ASSEMBLY, PLASTIC, MOLDS, INJECTION MOLDING.

USA Office: V&V Mach. & Equipment, Inc.

Ph: (281) 397-8101, Fax: (281) 397-6220.

Mexico Plant: Marketing Tech.

Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

CUSTOM PLASTIC PARTS

• MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.
• MOLD DESIGN AND BUILDING.



• PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.
• VERY COMPETITIVE ON HIGH LABOR PARTS.

We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA Office: V&V Mach. And Equip. Inc.
Tel. (218) 397-8101, Fax: (218) 397-6220.
Please send blue prints or samples to:
Marketing Tech. S.A. • Alamo 93, 4 Piso • Sta. Monica,
Tlal • Eco. De Mexico 54040 • Tel. 011 (525) 361-3351.
Fax: 011 (525) 361-5996. ATTN: VICTOR M. MCENDOZA
e-mail: marktech@infonet.net.mx

ASSEMBLY & ENGINEERING

Producible designs since 1970
Contract Engineering

Embedded Microprocessors
PCB Layout and Packaging Design
Analog including RF to 1 GHz
Instrumentation
A/D and D/A

Contract Assembly

High-Speed Fuji Surface Mount
Through hole
Turn-key or Kit
Run sizes one through thousands
Test and burn-in available

Bilocon Corp.
800-736-5927
425-353-2276
www.bilocon.com

ST241A

Stereo microscope

\$240.00

New - 1 year warranty



650/367-8320
Fax - 365-5845

3580 Haven Avenue
Redwood City, CA 94063-4803

Email: jlittle@netwizards.net

CONTROL • MEASURE • INPUT

MODEL 40-\$109

• RS-232 interface
• 28 lines digital I/O
• Eight analog inputs
• PWM output
• Three stepper ports



MODEL 100-\$279

• 12-bit 100KHz A/D • Four analog outputs
• Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.
920 SEVENTEENTH ST., INDUSTRIAL PARK
PRAIRIE DU SAC, WI 53578
TEL: (608) 643-8599 • FAX: (608) 643-6754

BASE2 COMPUTER

Complete Data Acquisition for only
\$99.00

See us on the web
www.loop.com/~base2

Voice: 818-730-8024
Mail: POB 250
Pasadena, CA 91102

10 Hr. Telephone Recorder \$69

FCC Approved



Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!
BEST PRICE AROUND!

FREE CATALOG
www.mscelectronics.com

MSC Electronics


PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925



2.4GHZ Wireless Transmitter & Receiver

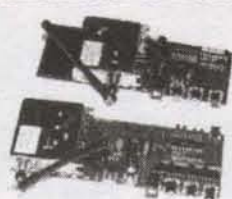


2.4GHz ~ 2.48GHz User Selectable
• Over 700' Range and 4 Chl auto-scan
• Compatible B/W & Color Video, Stereo
• Designed for wireless security system
• \$89/set @ 100pcs. Customization avail.

MATCO INC

www.mat-co.com (800)440-0299

SBC2000-074

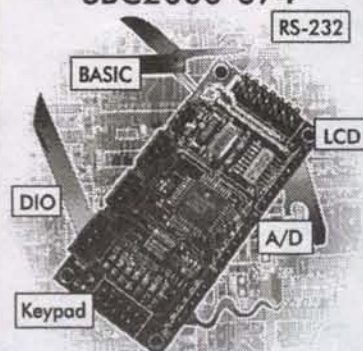

Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800

www.sbc2000.com

Vesta Technology, Inc.

GPS Units

Trimble Placer 400
6 Channel w/ 3" diam. Antenna
\$59.95

Trimble Placer 300
6 Channel w/ Wedge Antenna
\$99.95

GEOTEK Units

Call for a List of Equipment

Communications Surplus

713-526-8000 or 1-877-878-6GPS
ishaef@flash.net Fax to 713-522-6309



DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209
RT Systems
Amateur Radio Supply
8207 Stephanie Dr.
Huntsville 35802

ARIZONA

Elliott Electronic Supply
1251 S. Tyndall Ave.
Tucson 85713
The Electronic Thrift Store
12329 N.W. Grand Ave. #F
El Mirage 85375
Tower Records
3 E. 9th St.
Tempe 85281

AUSTRALIA

DonTronics
P.O. Box 595
29 Ellesmere Cres.
Tullamarine 3043
www.dontronics.com

CALIFORNIA

Abletronics
9155 Archibald Ave. Unit E
Cucamonga 91730
Advanced Computer Products, Inc.
1310 "B" E. Edinger Ave.
Santa Ana 92705
All Electronics
905 S. Vermont Ave.
Los Angeles 90006
14928 Oxnard St.
Van Nuys 91411
Allen's To Go
13461 Hwy. 88
Lockeford 95237
Alltronics
2300-D Zanker Rd.
San Jose 95131
Brand Newsstand
234-1/2 N. Brand Blvd.
Glendale 91203
Centerfold International
716 N. Fairfax Ave.
Los Angeles 90046
Del Amo Books & News
3758 Sepulveda Blvd.
Torrance 90505
Electro Mavin
2985 E. Harcourt St.
Rancho Dominguez 90221
Ford Electronics
8431 Commonwealth Ave.
Buena Park 90621
Harding Way News
113 W. Harding Way
Stockton 95204
Harold's Newsstand
524 Geary St.
San Francisco 94102
HdB Electronics
2860 Spring St.
Redwood City 94063
Hi-Fi Doctor
1814 E. Ball Rd.
Anaheim 92805
HSC Electronic Supply
4837 Amber Ln.
Sacramento 95841
3500 Ryder St.
Santa Clara 95051
5681 Redwood Dr.
Rohnert Park 94928
JK Electronics
6395 Westminster Ave.
Westminster 92683
Laurel Park News
4346 Laurel Canyon Blvd.
Studio City 91604

Lion Electronic Labs

4948 E. Townsend Ave.
Fresno 93727
NetSeller
7207 Arlington Ave. Ste. G
Riverside 92503
Op Amp Technical Books
1033 N. Sycamore Ave.
Los Angeles 90038
Panorama Electronics
8737 Van Nuys Blvd.
Panorama City 91402
Sandy's Electronics Supply, Inc.
20655 Soledad Cyn. Rd. #15
Santa Clarita 91351
Sav-On Electronics
13225 Harbor Blvd.
Garden Grove 92643
SIERRA MADRE NEWSSTAND
55 N. Baldwin Ave.
Sierra Madre 91024
The Red Barn
Hwy. 299
Bieber 96009
Tower Books
211 Main St.
Chico 95928

7840 Macy Plaza Dr.

Citrus Heights 95610

1280 E. Willow Pass Rd.
Concord 94520

630 San Antonio Rd.
Mountain View 94040

1600 Broadway
Sacramento 95818

5950 Florin Rd.
Sacramento 95823

2538 Watt Ave.
Sacramento 95812

2727 El Camino Real
San Mateo 94403

Tower Magazines/News

885 Riverside Pkwy.
West Sacramento 95605

Tower Records/Video

220 N. Beach Blvd.
Anaheim 92801

2520 Durant
Berkeley 94704

212 F St.
Davis 95616

5703 Christie Ave.
Emeryville 94608

2052 Redwood Hwy.
Greenbrae 94904

6310 E. Pacific Coast Hwy.
Long Beach 90803

2280 Market St.
San Francisco 94114

3205 20th Ave.
San Francisco 94132

2525 Jones St.
San Francisco 94133

871 Blossom Hill Rd.
San Jose 95123

1205 W. Covina Pkwy.
West Covina 91790

Video Electronics

3829 University Ave.
San Diego 92105

CANADA

Com-West Radio

Systems Ltd.

48 E. 69th Ave.
Vancouver, BC V5X 4K6

Muir Communications Ltd.

3214 Douglas St.
Victoria, BC V8Z 3K6

COLORADO

TH Electronics

216 Commerce Dr., Unit 2
Ft. Collins 80524
Tower Records/Video
2500 E. 1st Ave.
Denver 80206
Western Test Systems
530 Compton #C
Broomfield 80020

CONNECTICUT

Archway News
64 Bank St.
New Milford 06776
Electronic Service Products
437 Washington Ave.
North Haven 06473

DELAWARE

Newark Newsstand
70 E. Main St.
Newark 19711

DISTRICT OF COLUMBIA

Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Alfa Electronic Supply
1502 S. St. Rd. #7
Hollywood 33023
Al's News
8219 S.W. 124th St.
Miami 33156
Bob's News & Books
1515 S. Andrew Ave.
Fort Lauderdale 33316
Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301
Mike's Electronic Distributing Co.
1001 N.W. 52nd St.
Fort Lauderdale 33309
Skycraft Parts & Surplus, Inc.
2245 W. Fairbanks
Winter Park 32789
Sunny's At Sunset, Inc.
8260 Sunset Strip
Sunrise 33322

GEORGIA

Tower Records
3400 Around Lenox Dr.
Atlanta 30326

HAWAII

SolarWorks!
525 Lotus Blossom Ln.
Ocean View 96737
Tower Records
4211 Wai'alae Ave.
Honolulu 96816
611 Keeaumoku
Honolulu 96814

IDAH0

The Current Source
5159 Glenwood
Boise 83714

ILLINOIS

City Newsstand
4018 N. Cicero
Chicago 60641
Tower Records/Video/Books
383 W. Army Trail Rd.
Bloomington 61008
2301 N. Clark St. #200
Chicago 60614
1209 E. Golf Rd.
Schaumburg 60173

INDIANA

Harbourtown Sales
108 Park 32 W. Dr.
Noblesville 46060

KANSAS

Hollywood At Home

9063 Metcalf Ave.
Overland Park 66212
Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

LOUISIANA

Lakeside News
3323 Severn Ave.
Metairie 70002

MARYLAND

Silicon Valley Electronics
2014-A Industrial Dr.
Annapolis 21401
Tower Records/Video
2566 Solomons Island Rd.
Annapolis 21401
1601 Rockville Pike #210
Rockville 20852

MASSACHUSETTS

Full Spectrum Communications
244 Essex St.
Salem 01970
Newsbreak, Inc.
579 G.A.R. Hwy. Rt. 6
Swansea 02777
Tower Records #172
360 Newbury St.
Boston 02115

MICHIGAN

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124
MW Electronics
229 E. Michigan Ave.
Paw Paw 49079
Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104
Tower Records
1214 S. University Ave.
Ann Arbor 48104

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Accurate Instruments
11201 E. 24 Hwy.
Independence 64054
Electronics Exchange
8644 St. Charles Rock Rd.
St. Louis 63114

NEVADA

Amateur Electronic Supply
1072 N. Rancho Dr.
Las Vegas 89106
Less Butler's Electronics
2930 N. Las Vegas Blvd.
VSTG-22
North Las Vegas 89030
Radio World
1656 Nevada Hwy.
Boulder City 89005
Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102
6450 S. Virginia
Reno 89511

NEW JERSEY

Sys-Cor
707 22nd St.
Union City 07087
JR Tech Systems
1309 Hwy. 71
Belmar 07719

NEW MEXICO

Newsland Bookstore
2112 Central S.E.
Albuquerque 87106

NEW YORK

All Phase Video Security, Inc.
70 Cain Dr.
Brentwood 11717
Goldcrest Electronics
480 St. Paul St.
Rochester 14605
Ham Central
3 Neptune Rd.
Poughkeepsie 12601
Hirsch Sales Corporation
219 California Dr.
Williamsville 14221
Tower Records/Video
105 Old Country Rd.
Carle Place 11514
350-370 Route 110
Huntington 11746
1961 Broadway
New York 10023
383 Lafayette St.
New York 10003

OHIO

Compustuff
241 Great Oaks Trl.
Wadsworth 44281
Digital One
7603 Mentor Ave.
Mentor 44060
Footsteps
4925 Jackman Rd. Store #58
Toledo 43613
Hosfelt Electronics, Inc.
2700 Sunset Blvd.
Steubenville 43952
Keyways, Inc.
204 S. 3rd St.
Miamisburg 45342
Leo's Book Shop
330 N. Superior St.
Toledo 43604
Powermaxx, Inc.
1587 U.S. Route 68 N.
Xenia 45385

OKLAHOMA

Steve's Books & Magazines
2612 S. Harvard
Tulsa 74114

OREGON

News & Smokes
2295 W. Main St.
Medford 97501
News & Smokes #8
259-C Barnett Rd.
Medford 97501
Norvac Electronics
7940 S.W. Nimbus Ave. Bldg. 8
Beaverton 97005
960 Conger
Eugene 97402
1545 N. Commercial N.E.
Salem 97303
Powell's Technical Bookstore
33 N.W. Park
Portland 97209
Taylor News & Books
133 W. Main, Ste. 102
Oklahoma City 73102
Tower Books
1307 N.E. 102nd Ave.
Portland 97220

PENNSYLVANIA

Bedford St. News
308 Bedford St.
Johnstown 15901
Genes Books, Inc.
King of Prussia 19406
Lehman Scientific
2997 F. Cape Horn Rd.
Red Lion 17356
Montco Electronics &

Computers

2555 Industry Ln. Ste. D
Norristown 19403
Surplus Al
RR 1 Box 337
Hunlock Creek 18621
Tower Books
425 South St.
Philadelphia 19147
Tower Records
340 W. Dekalb Pike
King of Prussia 19406

SOUTH CAROLINA

555 Electronics
5646 Farrow Rd.
Columbia 29203

TENNESSEE

Tower Books
204 W. End Ave.
Nashville 37203

TEXAS

BDL News, Inc.
809 Pierce
Houston 77002
Electronic Parts Outlet
3753-B Fondren Rd.
Houston 77063
Mouser Electronics
958 N. Main St.
Mansfield 76063
Tanner Electronics
1301 W. Beltline #105
Carrollton 75006
Tower Records
2403 Guadalupe
Austin 78705

VIRGINIA

Satellite Headquarters
7920 Timberlake Rd.
Lynchburg 24502
Tower Records/Video/Books
4110 W. Ox Rd. #12124
Fairfax 22033
1601 Willow Lawn Dr.
Richmond 23230
8389 E. Leesburg Pike
Vienna 22182

WASHINGTON

A-B-C Communications, Inc.
17541 15th Ave. N.E.
Seattle 98155
Bohica Concepts
214 2nd St.
Morton 98356
Cody Books Ltd.
1125 Fir Ave.
Blaine 98230
Service Request
3304 W. Rowan Ave.
Spokane 99205
Supertronix
18650 68th Ave. S.
Kent 98032
Tower Books
10635 N.E. 8th St.
Bellevue 98004
20 Mercer St.
Seattle 98109
WISCONSIN
Amateur Electronic Supply, Inc.
5710 W. Good Hope Rd.
Milwaukee 53223
Greenfield News & Hobby
6815 W. Layton Ave.
Greenfield 53220
Cudahy News & Hobby Ctr.
4758 Packard Ave.
Cudahy 53110

Doing Electronic Calculations With ELCAD

by Fred Blechman

ELCAD (Electronic Computer-Aided Design) is a simple, \$14.95 software program for the IBM PC with Windows 3.1 or 95. It allows you to do some fairly complex electronic calculations easily and quickly, and print out the results.

There are a number of ways that electronic circuits come into being. Some hobbyists and professionals have the "knack" and the experience to put together solid-state circuits with the proper transistors and integrated circuits, using the correct resistance, capacitance, and inductance values, with little apparent effort.

Some build a circuit using the

already designed to do the job, commonly created by designers using data sheets and books full of electronic formulae.

With the advent of the computer, circuit design has become more available to hobbyists and experimenters using some sophisticated software, most costing hundreds of dollars.

But what if you just need to do some occasional circuit design that doesn't justify the cost and time to learn to use the expensive

many commonly-used electronic calculations. Probably the best way to illustrate this is to describe how the program operates and the kind of calculations it performs. You can then decide for yourself how it might be helpful in your situation.

FEATURES

ELCAD does 23 different types of calculations, as well as presenting the resistor color code in a graphical manner. The calculations include: Ohm's Law for DC and AC circuits; parallel resistors; RC time constants; power supply ripple filter capacitance; single-layer coil windings; transformer

heatsink calculations for size, wattage, and temperature; transistor common-emitter, common-collector, and common-base designs.

In all cases, context-sensitive HELP files are available for every screen, and the entire HELP file can be printed out. Navigation between screens is effortless.

Each calculation screen shows a schematic, and the appropriate boxes to enter data. The results are shown, and can be printed out for future reference.

To give you an idea of how the program works, we'll briefly cruise through many of the functions.

MAIN MENU (Figure 1)

No formal installation is required. Just run ELCAD.EXE from the supplied 3.5-inch diskette while in Windows, and the Main Menu screen pops up.

The menu bar at the top of the screen lets you "Exit," or get "Help" about this screen, or get details "About" ELCAD, or "Print Instructions" (the entire Help file). ALT-H or F1 on any screen will also call up context-sensitive help.

Using the mouse is the easiest way to maneuver through this program. All mouse clicks are with the left mouse button.

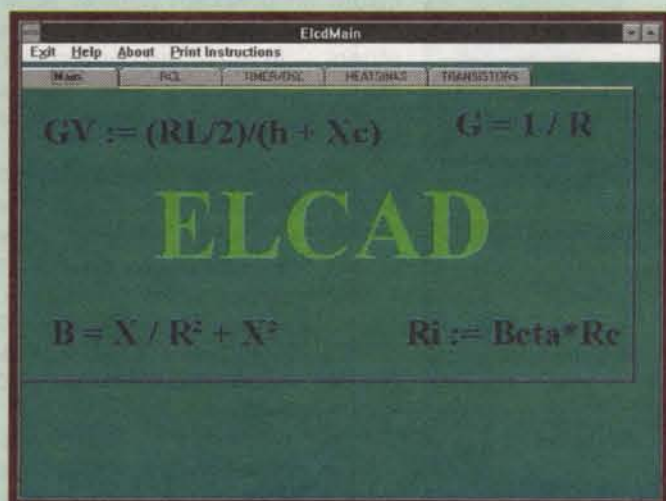


Figure 1. ELCAD Main Menu offers four category "tabs" for calculations.

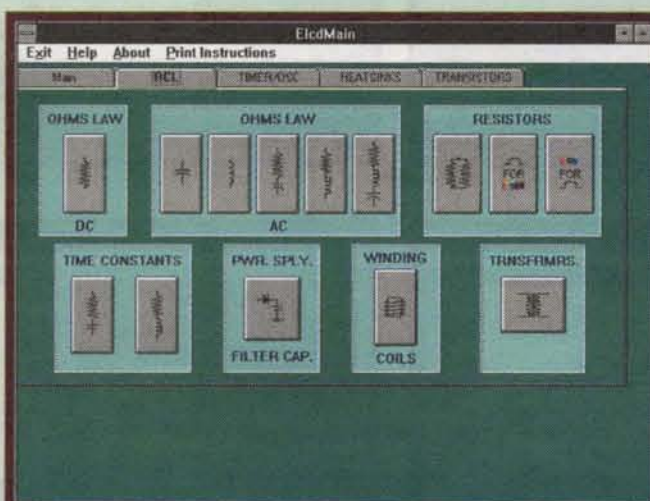


Figure 2. RCL screen offers seven types of calculations.

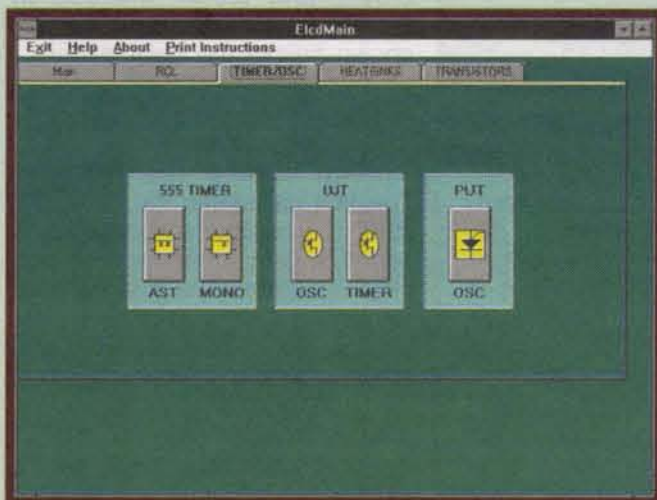


Figure 3. TIMER/OSC screen offers three types of calculations.



Figure 4. HEATSINKS screen offers three types of calculations.

"cut and try" approach, eventually getting to the proper component values.

Others follow schematics

all-encompassing circuit design programs? Enter ELCAD.

For only \$14.95, ELCAD allows you to quickly and easily do

windings; 555 astable and monostable circuits; unijunction oscillator and timer circuits; programmable unijunction transistor oscillator;

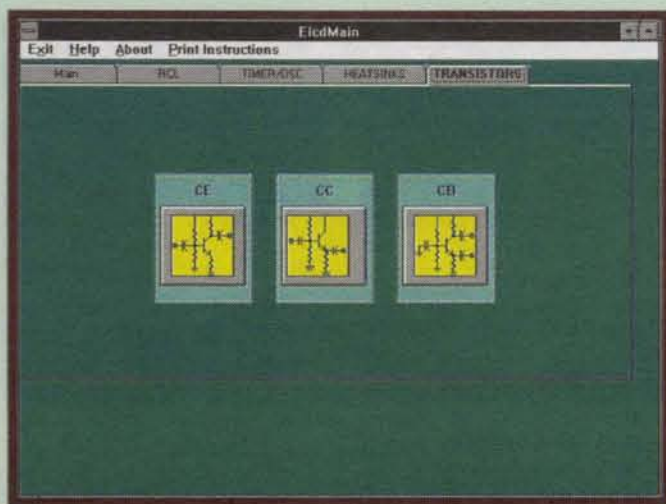


Figure 5. TRANSISTORS screen offers three types of calculations.

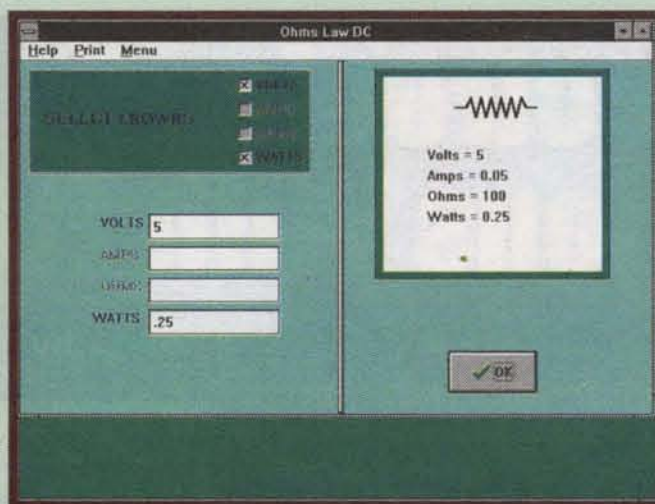


Figure 6. Ohm's Law DC Calculation.



Figure 7. Ohm's Law AC Calculations.

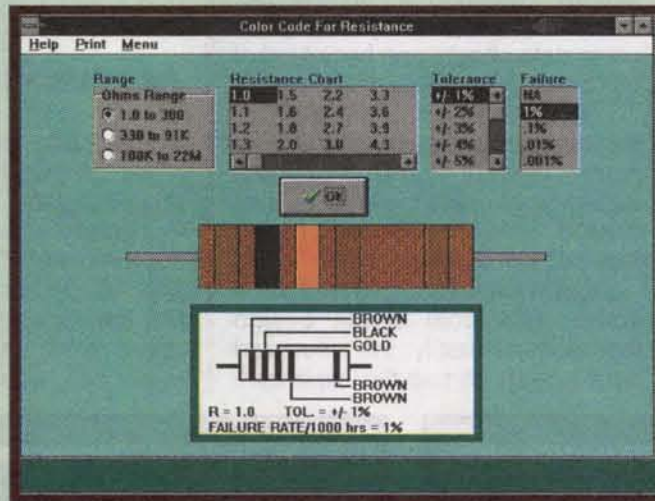


Figure 8. Resistance Color Code.

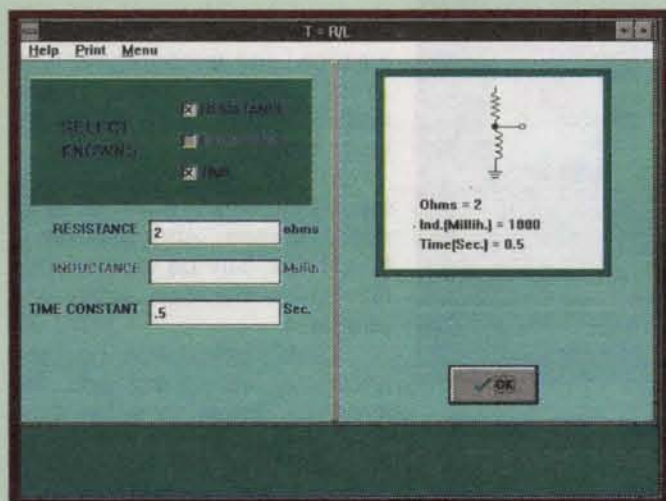


Figure 9. Time Constant Calculation.

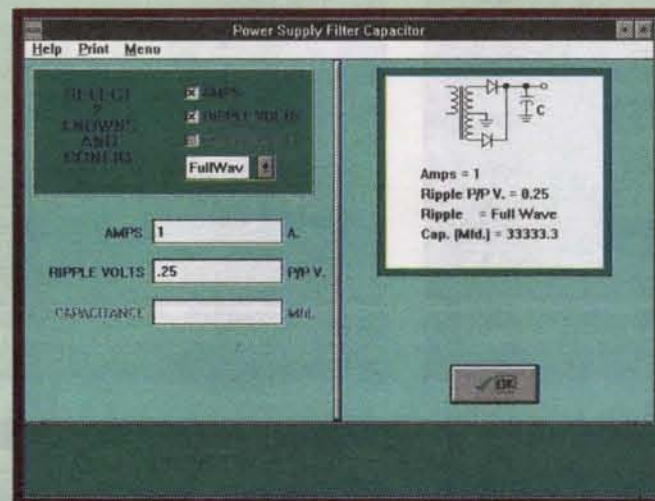


Figure 10. Filter Capacitor Calculation.

Five categories are shown as tabs near the top of the screen. Using the mouse or arrow keys, you select the category you wish to access. Figures 2, 3, 4, and 5 show each of the category screens.

RCL CALCULATIONS

Ohm's Law for DC Circuits

Figure 6 shows typically how most of the ELCAD screens work. You select those items for which you have data, and the rest are calculated. The results are then displayed and can be printed out.

On this screen VOLTS, AMPS,

OHMS, and WATTS are the variables. You simply check the boxes for the items for which you have data. When check box titles go gray, there are enough selections to compute for the grayed items.

For example, suppose you need a resistor to dissipate .25 watts at 5 volts. Put a check in the box by VOLTS and WATTS. The AMPS and OHMS check boxes become gray. The VOLTS and WATTS titles become black, ready for you to enter 5 and .25, respectively.

You use the tab or mouse to select the edit box, and enter the data. When you click on the OK

button, or press Enter, the Amps and Ohms calculations are displayed in the white box to the right. To print out the results, just click on PRINT. To return to the main menu, click on MENU.

Ohm's Law for AC Circuits

Five screens allow you to calculate: capacitive reactance; inductive reactance; resistor and capacitor in series; resistor and inductor in series; or resistor, inductor, and capacitor in series. The latter screen is shown in Figure 7.

As you can see, there are 11 different data entry boxes available

here, but you only need to use some. When you "Select Knowns" by checking boxes at the top left of the screen, the values that can be calculated turn gray.

For example, suppose you want to know what size capacitor and inductor to use at 1000 Hz to get a capacitive reactance of 1000 ohms and an inductive reactance of 500 ohms, and what size resistor is needed to get an impedance of 1000 ohms and what wattage resistor is needed at 100 volts. This is not a simple calculation, since there are so many variables. But it's easy in ELCAD.

You select the knowns: FREQUENCY, CAP.REACT, IND.REACT, IMPEDANCE, and VOLTS, and enter the data in those boxes. Click on "OK" and answers are instantly displayed in the white box to the upper right. The watts shown are for the resistor. Simple!

Resistors

Three screens are available for resistors. The first is for up to six resistors in parallel. The calculation for two is easy, but much more involved for six! The real "plus" here is that you can also calculate an unknown parallel resistance — together with up to five others — to make the combination equal to a desired value. This is real handy when trying to trim a circuit.

The other two screens in this section show resistor codes; one "decodes" known resistor color bands, the other shows the bands to look for when seeking a particular value of resistor. These screens go beyond just the three normal bands, and include tolerance and failure rate band colors.

Figure 8 shows the determination of color codes for a desired resistor value. In this case, 1 ohm with a 1% tolerance and 1% failure rate indicated the bands would be (left to right) brown, black, gold, brown, and brown. Interestingly enough, the actual colors are shown (within the color accuracy of your monitor settings).

Time Constants

Two screens are available. The first calculates the time constant for a resistor and capacitor in series, a fairly common (and simple) calculation. The time constant value is the time it takes for the capacitance to be charged to 63% of its full potential charge level.

The other screen allows the calculation of the time constant for a resistor and inductor in series, much less common. Here the time constant value is the time it takes for the induced current to reach 63% of its full value.

For the example shown in Figure 9, we entered a resistance of 2 ohms and a time constant of .5 seconds to determine that the

inductor would need to be 1000 millihenries. Of course, either of the three variables can be calculated from any two specified values.

Power Supply Filter Capacitor

On this single screen, you can determine the proper size filter capacitor for a desired ripple voltage with either a full-wave or half-wave power supply operating at a designated current. Or, knowing the capacitance used, you can calculate the ripple at a particular current.

As shown in Figure 10, you select two knowns and either full-wave or half-wave. We wanted to know the size filter capacitor to use to have .25 ripple volts with a full-wave supply delivering 1 ampere. We would need a hefty 33,333 microfarad capacitor!

Air Core Coil Inductance

The inductance of a single-layer air-core coil depends on its length, radius, and turns per inch. The wire size determines the turns per inch if close wound. With this screen, as shown in Figure 11, you can either find the total number of turns or the inductance by entering the proper values. Notice that a WIRE GAUGE window pull-down allows you to select wire gauge, and shows turns per inch (TPI) for the selected gauge.

This is no trivial calculation. We wanted to calculate what it would take to make a 10 microhenry air core coil using 8-gauge wire wound on 1-inch radius for a length of .5 inches. The result shows this would take 11.8 turns of wire. Alternately, we could have calculated the inductance using the radius, length, and number of turns.

Transformers

Figure 12 shows the transformer calculations, where you select the data you have, and the program calculates the result. For example, say you have a common collector transistor audio output stage that gives you a 10-volt RMS output. You want to deliver a 0.5 watts of power to an 8-ohm speaker.

To deliver 0.5 watts to an 8-ohm speaker, you would need 2 volts RMS. (This is based on volts = square-root of the product of the watts and resistance. In this case, voltage is the square root of .5 watts times 8 ohms, or the square root of 4, which equals 2. Oddly, this calculation is NOT done by the program!)

Checking PRI.VOLTS, SEC.VOLTS, and SEC.IMPED, and entering 10, 2, and 8, respectively, in those boxes yields a result of 200 ohms for the primary impedance needed.

TIMER/OSCILLATORS

555 Timer

Two different configurations of

Figure 11. Air Core Coil Calculation.

Figure 12. Transformer Calculation.

Figure 13. Monostable 555 Calculation.

Figure 14. UJT Timer Calculation.

Figure 15. PUT Oscillator Calculation.

Figure 16. Heatsink Wattage Calculation.

555 timers are shown, astable (runs by itself — an oscillator) and monostable (stays in one condition until triggered, then resets when it times out).

Figure 13 shows the monostable 555 screen. You select two knowns in the selection box and then enter the data in the edit boxes that are selected. Click on "OK" to display the results. Here it can be seen that a 100 microfarad capacitance with a required time out of 2.5 seconds would require a resistor value of 22,727.3 ohms.

Note that this is calculated based on the presumed value of the typical electrolytic capacitor,

which in actuality is highly variable from the marked value. In this case, it would make sense to use a 50K potentiometer in place of the resistor to set the time. The calculated value merely gives you an idea of the resistance needed.

Unijunction Transistor (UJT)

Two Unijunction Transistor screens are provided. One is an oscillator circuit, the other a timer. The timer circuit is shown in Figure 14.

The 2N2646 is shown as the default UJT type, but a pull-down allows you to select from nine oth-

ers, and enters the appropriate values for that UJT in the fill-in boxes.

If you want to use a UJT other than that shown, either select "NOT LISTED" and fill in your own UJT data, or select one that has data close to what you need and alter only the UJT data that you need to alter.

Fill in the TIME and VBB that you want, click on OK, and the circuit component values are calculated and displayed.

Programmable Unijunction Transistor (PUT) Oscillator

Figure 15 shows the PUT

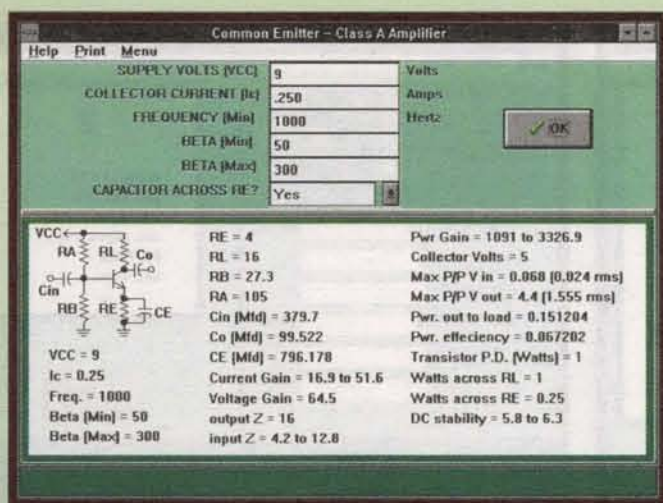


Figure 17. Common Emitter Calculation.

Oscillator screen. Only one PUT, a 2N6068, has pre-entered data. If you want to use some other PUT, either select "OTHER" and fill in your own PUT data, or select 2N6028 and alter only the PUT data that you need to alter. When you type in the VSS and FREQ, clicking on OK computes the results.

HEATSINKS

Three screens allow you to perform some complex calculations. You can determine various parameters concerning heatsink size, heatsink wattage, or heatsink temperature.

Figure 16 shows the screen for calculations involving the maximum wattage for an ambient-cooled heatsink. For those not familiar with heatsink technology, many strange symbols are used. Typical values for some are shown at the upper left part of the screen. Temperatures are in Centigrade.

Use this screen when you want to know how many watts a particular heatsink can safely dissipate. Say that you have a transistor in a TO-220 case and want to use it in a maximum ambient temperature of 50 degrees Centigrade. You intend to use a heatsink that its source catalog has rated with a sink to air thermal impedance of .5 watts per degree Centigrade.

Using the information in the upper boxes, you would enter in the following data:

TmaxJ = 80
Zsa = .5
Zjc = 2.7
Zcs = 1
TmaxA = 50

Click on OK and the result shows maximum watts = 7.1

TRANSISTORS

Three transistor amplifier screens are available: common emitter, common collector, and common base. The common emitter amplifier screen is shown in Figure 17.

The SUPPLY VOLTS must be greater than 1 volt. After entering in the COLLECTOR CURRENT, the minimum FREQUENCY, and the BETA range, you select if you want a CAPACITOR ACROSS RE, the emitter resistor, or not. If you use a capacitor, you get more stage gain, but at the cost of more distortion.

Click OK and the component values and parameter results are displayed. You can change any of the entered values and re-compute to fine-tune the circuit.

SUMMARY

While not intended to do the hundreds (thousands?) of possible types of electronic calculations, ELCAD very easily and elegantly performs the common calculations described. As a hobbyist or experimenter, you may find it handy. **NV**

Source

By the time you read this, ELCAD's author, programmer Brian Ellis (bellis@aol.com) intends to add even more calculations. The program, supplied on a 3.5-inch 1.44MB diskette for the IBM PC using Windows 3.1 or 95 (not available for the Macintosh), can be ordered for \$10.00 postpaid USA from:

F.N.C. Corp.
350 Adam Dr.
South Elgin, IL 60177
(847) 695-1210

MFJ-922 VHF/UHF DUAL BAND ANTENNA TUNER



This compact dual band VHF/UHF antenna tuner from MFJ Enterprises, has a single meter that reads SWR and power. No adjustment is needed.

It covers VHF from 136 to 175 MHz, and UHF from 420 to 460 MHz. You can read power up to 150 watts in two ranges: 60 watts or 160 watts.

The MFJ-922 works for HTs, mobile rigs, or amplifiers up to 150 watts. It has a compact size — 4x2x1-1/4 inches — so it will fit in a shirt pocket. Cost is \$79.95.

COMMUNICATION HEADPHONES



MFJ's new communication headphones work well for amateur radio and short-wave radio listening in all modes — SSB, FM, AM, data, and CW. Each earphone has individual volume/bass controls.

A 40 mm driver unit reproduces enhanced communication sound, and there is near zero loss on signal transmission from the gold-plated plug and cord. The lightweight earphones (eight ounces) come with nine feet of cord.

The MFJ-392 handles 450 mW and has a frequency response of 100-24,000 Hz. Impedance is 16 ohms at 1 KHz; sensitivity is 102 dB/mW. It works in mono or stereo mode and includes a free 1/4-inch phono adapter. Price is \$19.95.

VOX SPEAKER/MICROPHONE



MFJ-2981 features an electronic adjustable VOX control and is handy for use with any kind of handheld VHF, commercial, amateur, or marine radio. It also works for mobile hams and emergency operators on-the-go who need total hands-free operation.

In the VOX position, you just talk and the MFJ-2981 automatically keys your HT. A "TRANSMIT" red LED lights up while your VOX is enabled.

This VOX mic picks up your voice, not background sound. Two condenser microphones are installed for feedback prevention. Sensitivity is adjustable by rotating the trimmer switch which accommodates loud or soft voices. With MFJ's VOX speaker/microphone in the appropriate position (attached to your front pocket or lapel), the sensitive microphone picks up your normal speaking voice.

This mic works well for emergency operators such as fire, police, EMT, and active ham radio operators because it runs off of two "AA" batteries. Transmission is voice-activated in the "on" position. In the "off" position, you can use the MFJ VOX mic as a regular speaker/microphone. Transmission is activated only by pushing the PTT switch. The durable, hard plastic speaker mic fits in the palm of your hand.

A free external earphone is included. The earphone can be connected to the earphone jack for total hands-free operation, or for monitoring the frequency.

The VOX speaker/microphone is compatible with most Icom, Yaesu, Standard, RadioShack, Alinco, and ADI handheld transceivers with two prong plug-ins.

Price is \$39.95. For further specifications and other details on this or any of the other MFJ products listed here, contact:

MFJ ENTERPRISES, INC.
P.O. BOX 494, DEPT. NV
MISSISSIPPI STATE, MS 39762
601-323-5869 FAX: 601-323-6551

Showcase your New Products here! Send all press releases or information/photos to:
Nuts & Volts Magazine
New Product News
430 Princland Court, Corona, CA 91719
or E-Mail to newproducts@nutsvolts.com

New Product News



BASICBOX

Advanced Graphic Systems announces the release of their newest product — a single board computer — the BasicBox.

The BasicBox is an all-inclusive system that comes with everything needed to get up and running in a short amount of time. Within minutes, the system is fully assembled, cabled into the PC, and powered on providing fully functional computing around its 8052 microprocessor with built-in BASIC-52 interpreter.


The computer, whose concept was adopted from Jan Axelsson's *Microcontroller Idea Book*, was designed with education in mind, but built to meet the demands of real-world control applications.

The BasicBox comes with an industrial-quality single board computer, an experimenter's board which allows testing and debugging of Basic programs, power supply, all necessary cables, Jan Axelsson's *Microcontroller Idea Book*, communications software, and lots of programming examples.

It retails currently for \$249.00 in single quantities.

For more information, contact:

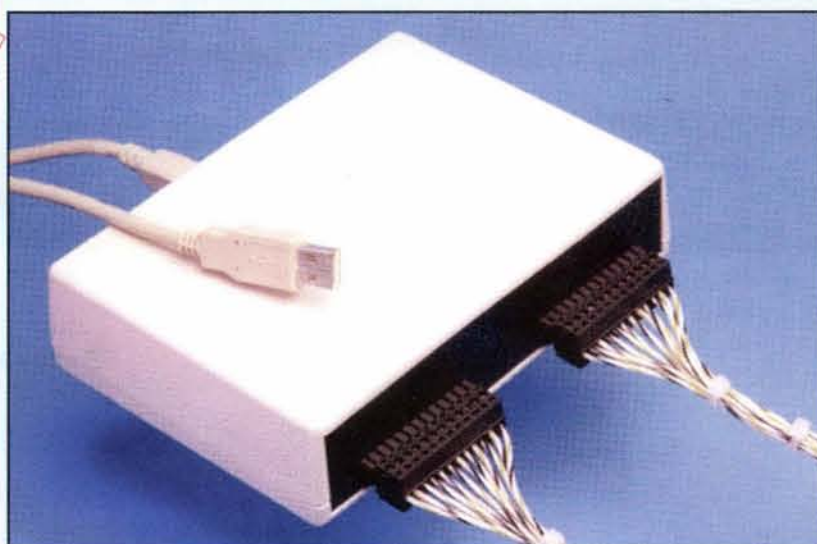ADVANCED GRAPHIC SYSTEMS
4055 GRASS VALLEY HWY., #103
DEPT. NV
AUBURN, CA 95602
530-887-1619 FAX: 530-887-0107
WEB: <http://www.ags-gv.com>



JSB-210 USB RELAY MODULE

amp @ 120VAC.

J-Works, Inc. has begun shipping the Model JSB-210 USB Relay Module.

The Model JSB-210 has 8 or 16 "form C" relays and plugs 'n plays into the standard USB (Universal Serial Bus). The user controls the relays from any programming language that supports USB communications.

Plug-in style terminal block connectors allow quick hook-up to three contacts per relay. Each relay contact is rated at 1 amp @ 30VDC, and 0.5

The module replaces internal PC-based plug-in cards in various test, control, and measurement applications. The single unit price for the Model JSB-210 is \$170.00 to \$205.00.

For more information, contact:

J-WORKS, INC.
12328 GLADSTONE AVE., UNIT 4
DEPT. NV
SYLMAR, CA 91342
818-361-0787 FAX: 818-270-2413
E-MAIL: admin@j-works.com
WEB: <http://www.j-works.com>

E-Mail your New Products to: newproducts@nutsvolts.com



DIGITAL MULTIMETERS/CURRENT CLAMPS

Jensen Tools introduces a full line of high-quality digital multimeters and current clamps. From the full-featured JTM-105 — a true RMS meter — to the JTM-63 — a low-cost, pocket-sized meter — the line provides a good value, costing less than comparable meters.

The entire line has been engineered to exacting tolerance and is manufactured using components of the highest quality, allowing Jensen Tools to offer a three-year "no hassle" warranty.

Jensen Tools can also ship the meters within 24 hours with a certificate of calibration for a small fee.

For more details, contact:

JENSEN TOOLS, INC.
7815 S. 46TH ST., DEPT. NV
PHOENIX, AZ 85044-5399
602-968-6241 FAX: 602-438-1690
WEB: <http://www.jensentools.com>

PCS64I PC OSCILLOSCOPE

Velleman, Inc., announces the PCS64I PC Digital Storage Oscilloscope for use with an IBM-compatible PC. The PCS64I is geared towards both hobbyists and professionals.

It is a factory assembled and tested unit featuring two separate channels and a maximum sample rate of 64MHz. All standard scope functions are available, including features only found on digital equipment.


Apart from Y-position and input coupling, all settings are software-controlled.

The supplied WinDSO software (Windows™ 3.11/95/98) includes oscilloscope, spectrum analyzer, and recorder modules. A DOS oscilloscope module is also provided.

Some features included are:

Oscilloscope — Timebase 0.1µs to 100ms/div sensitivity; 10mV to 5V/div selectable trigger source, edge and level with pre-triggering; on-screen markers; true RMS readout; and X/Y mode.

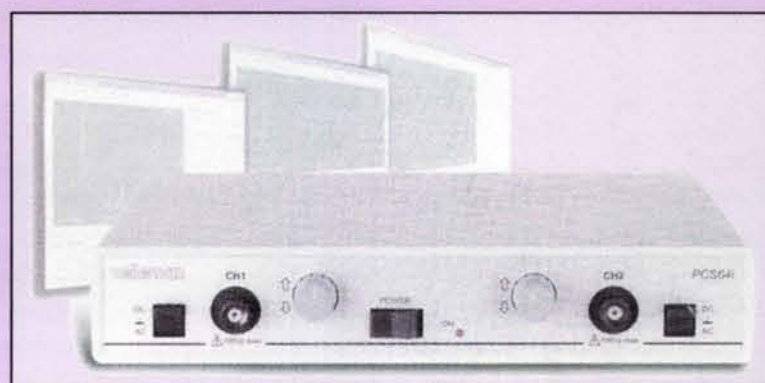Spectrum analyzer — Frequency range 0 to 16 MHz; linear or logarithmic readout; zoom



function; and on-screen markers.

Recorder — Timebase 20ms to 2000s/div; automatic storage (up to one year); on-screen markers; and zoom function.

WinDSO allows saving of the sampled data as a graphic or ASCII format.

The oscilloscope is FCC-approved, fully optically isolated from the PC, and is equipped with a charging circuit for an optional battery pack.

For more information, contact:

VELLEMAN, INC.
7415 WHITEHALL ST., STE. 119, DEPT. NV
FORT WORTH, TX 76118
817-284-7785 FAX: 817-284-7712
E-MAIL: velleman@earthlink.net
WEB: www.velleman.be

VECTRONICS NEW KIT LINE

Vectronics announces the arrival of the highest quality in electronic hobby kits.

Over 30 different kits are included in VECTRONICS new kit line, which provide a professional product at a hobby price. From short-wave converters to aircraft receivers, and ham radio kits to an old fashioned crystal

radio kit.

The kits are created by engineers who are hobbyists-at-heart. Each kit features a professional quality epoxy glass PC board with solder mask and screen printed components legend, and the highest quality components.

Our kits also feature an extensive "owner's manual," which has been written specifically for each kit. This detailed, yet still easy-to-follow manual features illustrations, specific instructions, and even a schematic

diagram. Not only are step-by-step instructions and helpful tips provided, our comprehensive manual also guides you into the next step — the fun of using your equipment!

For more information, contact:

VECTRONICS
1007 HWY. 25 S., DEPT. NV
STARKVILLE, MS 39759
601-323-5800 FAX: 601-323-6551
WEB: <http://www.vectronics.com>

The LITTLE Black Box with BIG Performance!

OPTOCOM SETS THE STANDARD.....

Combining a high speed, high performance receiver,
Motorola®/LTR Trunking, and full featured decoding.

**NOW TRACKS
EDACS WITH THIRD
PARTY SOFTWARE**



Computer
Not Included

**INTRODUCTORY
PRICE**

\$459

FREE Trakkstar Software
Suggested list price \$549

**Order Now!
Save \$90**

CHECK OUT THESE FEATURES

- High speed triple conversion GRE receiver board (50 channels per second)
- Track Motorola 400MHz, 500MHz, 800MHz, and 900MHz systems, as well as conventional frequencies, simultaneously
- Decode CTCSS, DCS, LTR, DTMF, and Motorola talk group ID
- Reaction Tune with the Scout Frequency Recorder
- Built-in Data Slicer Circuit for decoding of FSK programs
- Software and hardware controlled volume and squelch
- Download up to 100 different frequencies for scanning away from computer
- Supplied with the all NEW TRAKKSTAR software from ScanStar
- Backwards compatible with third party software that supports Optoscan 456/535
- Trunk Track LTR systems
- Scans conventional frequencies from 25-520, 760-823.995, 849.005-868.995, 894.005-1300MHz (Cellular frequencies are blocked except for FCC approved users)

FACTORY DIRECT ORDER LINE 800-327-5912

OPTOELECTRONICS®

5821 NE 14th Avenue • Ft. Lauderdale, FL • 33334

Telephone: 954-771-2050 Fax: 954-771-2052 Email: sales@optoelectronics.com

Prices including Promotions and Specifications are subject to change without notice or obligation

www.optoelectronics.com OPTOCOM supplied with Software, Antenna & Cables. Operates under Windows 3.1, 3.11, 95, and 98

Flexibility



Built-in data slicer circuit for
decoding of popular FSK pro-
grams.

Portability



For use without the computer,
download up to 100 different
frequencies for scanning away
from computer.

CC50 Carry Case
Holds OptoCom & Laptop
Computer.....\$25



CLONE, TEST OR REPAIR ANY HARD DRIVE

"THE MOST COMPLETE HARD DRIVE WORKSTATION WE'VE SEEN!" BOB ROSENBLOOM, DIGITAL VIDEO, INC.

DRIVE SERVICE STATION

Copy entire hard drives with ease. Drive duplicators are essential tools for dealers and system builders. Don't spend hours installing and formatting drives. Do it instantly with the Pro. Set up any SCSI or IDE drive with your original software. Connect blank drives to the Pro and press start. You'll copy entire drives faster and more accurately than is possible on any PC. With our combination IDE and SCSI model, you can even copy data between different interfaces. All models include both 2.5" and 3.5" interface adapters. The Pro also supports SCA and Wide SCSI drives.

Choose the Pro, and you'll also have an entire factory drive test and repair system for under \$1000. The Pro gives

BUY MANUFACTURER DIRECT: \$995
408 330-5525

you the ability to copy, reformat, repair, translate, and test any hard drive. Use the Pro to put any hard drive through its paces. A full factory final test and performance analysis is performed. Complete test and repair reports are sent to any standard printer.

The Pro will also reassign and eliminate drive defects. Here's how it works: First, a precise media analysis system scans the disk for errors. Defects are mapped out, and effectively "erased." The error correcting system then "trains" the drive to permanently avoid defective areas. Data is stored only on the safe

areas of the disk. Capacity is reduced by an insignificant amount, and the drive works flawlessly once again. Get the technology used by major repair shops and data recovery centers. The Pro repairs all disk defects caused by normal wear. Drives with mechanical damage may not be repairable.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DRIVEDUPLICATORS.COM

Call today for high volume multi-drive copiers and CD Duplicators
Sold and intended for backup purposes only. Copyright laws must be observed.

#28190

BASIC ToolBox

Microcontroller Kit for the Electronics Apprentice!

ONLY \$149 + S&H
(\$180 value)

Offer expires March 31, 1999

Minimal Hardware Required!

It really doesn't take many tools to get started with BASIC Stamps -- just an ordinary PC running DOS or Windows 95/98/NT. Loading your first program into a BASIC Stamp is a matter of connecting the Board of Education to your PC and running our software. We're providing a couple of LEDs and resistors for your first project.

Learn BASIC Stamps using the Board of Education

During the month of February and March we're offering the BASIC ToolBox -- which is similar to the BASIC Stamp II Starter Kit except we've replaced the carrier board with the new Board of Education. BASIC Stamp I/O pins, power, and ground connections are accessible adjacent to the breadboard.


For beginners the Board of Education temporarily eliminates the need for a soldering iron, and for advanced engineers it's a quick BASIC Stamp project area.

BASIC Tool Box #28190 (\$149 + S&H)

- BASIC Stamp II module
- Board of Education
- (10) jumper wires
- BASIC Stamp Manual Version 1.9
- (2) each LEDs and resistors
- DOS & Win95/98/NT software
- power supply and serial cable

What's a microcontroller?

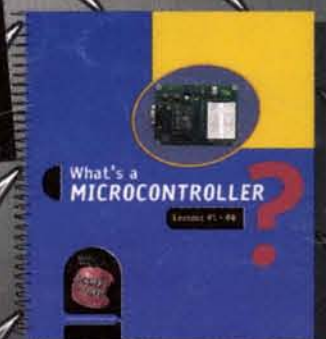For the real beginner take a look at our educational web site <http://www.stampsinclass.com> and download the "What's a Microcontroller?" Experiment Set, or purchase a copy for yourself! Download for free or printed version sold separately (#28123) for \$19.



PARALLAX

To order: 916.624.8333 More info: <http://www.parallaxinc.com>

BASIC Stamp and the Parallax, Inc. logo are registered trademarks of Parallax, Inc.

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
 430 PRINCELAND COURT
 CORONA, CA 91719

CHANGE SERVICE REQUESTED

BULK RATE
 U.S. POSTAGE
PAID
 PERMIT No. 49
 LONG BEACH CA

